

NETWORKS (Repeat)

Page

Ports represent a window through which we provide energy or information or access energy or information.

Each port associated with a physical system having two type of variable. Kinetic variable & potential variable.

Physical system 3 domains

	Electrical Domain	Mechanical	Magnetic
KV	Voltage	Torque, force	$MMF = NI$
P.V	Current	Angular vel., velocity	Flux

In any domain product of pot. variable & kinetic variable is power variable.

State Variable - Variable associated with dynamic element which is responsible for stored energy or information.

I/P and P.V known. To find O/P. This is N/W analysis.

I/P and O/P known. This is N/W synthesis.
To find PU

- Synthesis - 1) whether system is realizable or not.
2) If the system is realizable, one solⁿ to the given prob exists, then ∞ no. of solⁿ's are possible.

3) To find which solⁿ or design is the best.
means:- optimal solⁿ. cost ↓ performance ↑

CLASSIFICATION OF SYSTEM / NW.

1) static / Dynamic

Static - It is the one whose response is totally dependent on present excitation.
eg:- resistor.

Dynamic - Response dependent on present I/P as well as past O/P.
eg:- capacitor or inductor.

2) Continuous/ Discrete


Continuous - system whose response is defined w.r.t to independent variable on continuous basis. eg: - R, RC ckt

Discrete - Response is defined whose O/P is discrete w.r.t to independent variable.

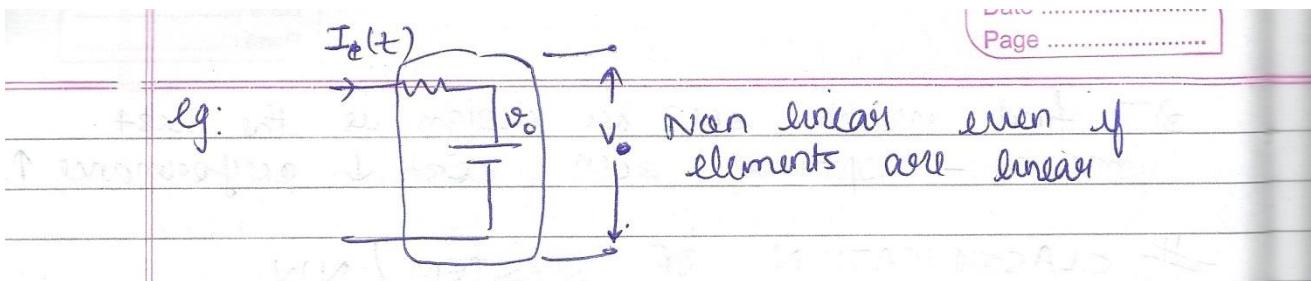
3) Linear / Non linear

Homogeneity $x_1(t) \rightarrow y_1(t)$ $a_1 x_1(t) \rightarrow a_1 y_1(t)$
 $x_2(t) \rightarrow y_2(t)$ $a_2 x_2(t) \rightarrow a_2 y_2(t)$

Additivity $a_1 x_1(t) + a_2 x_2(t) \rightarrow a_1 y_1(t) + a_2 y_2(t)$



Q

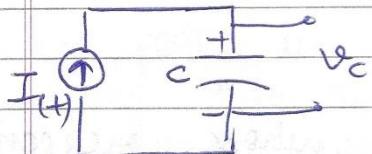

$$\text{Initial voltage } v_c(0^-) = v_0$$

$$I(A) \Leftrightarrow \frac{d}{dt} \quad v_{c1}(t) = \frac{1}{C} \int I_{c1}(t) dt + v_0$$

$$v_{c2}(t) = \frac{1}{C} \int I_{c2}(t) dt + v_0$$

$$v_{c1}(t) + v_{c2}(t) = \frac{1}{C} \int (I_{c1}(t) + I_{c2}(t)) dt + v_0$$

so non linear

net $2v_0$

→ If mathematical description of a static system is given by linear algebraic eqⁿ then the system is linear.

If mathematical description of a dynamic system is given by linear differential eqⁿ or linear difference eqⁿ then system is stable.

To check linearity If coeff of differential operators are independent of dependent variable then, diff eqⁿ is linear diff eqⁿ.

$$1) 4 \frac{d^2y}{dt^2} + 3 \frac{dy}{dt} + 5y = 2x + 5 \frac{dx}{dt} \quad \text{linear (T.I)}$$

$$2) y(n+2) + 3y(n+1) + 3y(n) = 6x(n) \quad \text{linear (T.I)}$$

$$3) 4t \frac{dy}{dt} + 2t^2y = 6x + 5 \frac{dx}{dt} \quad \text{linear (T.V)}$$

$\left(\frac{dy}{dx}\right) = 0$ Non linear eqn
 but system linear
 because $\left[\frac{dy}{dx} \neq 0\right]$

- 4) $4\frac{dy}{dt} + 6y + 3\frac{dx}{dt} = \sin t$ Linear
- 5) $4y \frac{dy}{dt} + 6y = 2x$ Non linear
- 6) $y^{(n+2)} + y_{(n+1)} = 3y_{(n)} + 6x_{(n)}$ Non linear
- $\underbrace{y_{(n+2)} + y_{(n+1)}}_{\text{dependent}} = 3y_{(n)} + 6x_{(n)}$

4) Time variant / Time invariant


$$x(t) \rightarrow y(t)$$

$$x(t-T_0) \rightarrow y(t-T_0)$$

differential operator

If coeff. of dependent variable is independent of independent variable then it is time invariant.

5) Causal / Non causal.

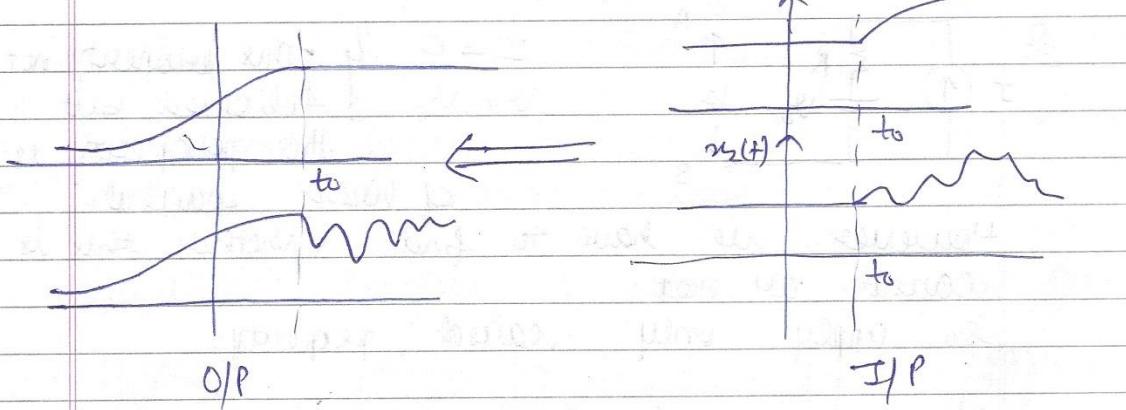

$$m_1(t) \rightarrow y_1(t)$$

$$m_2(t) \rightarrow y_2(t)$$

for causal system if

$$x_1(t) = x_2(t) \text{ for } t \leq t_0 \\ \text{then } y_1(t) = y_2(t) \quad t \leq t_0$$

Causal system also known as Anticipatory sys.
It cannot anticipate what shall be applied
to I/P port in future.


→ Causal signals - These are one which are zero till $t = 0$

→ linear causal system -

$$x(t) = x_1(t) - x_2(t) \Rightarrow y(t) = y_1(t) - y_2(t)$$

$$\begin{cases} 0 & t \leq t_0 \\ x_1(t) - x_2(t) & t > t_0 \end{cases} \quad \begin{cases} y(t) = 0 & t \leq t_0 \\ y_1(t) - y_2(t) & t > t_0 \end{cases}$$

i.e. if $x(t) = 0$ then $y(t) = 0$

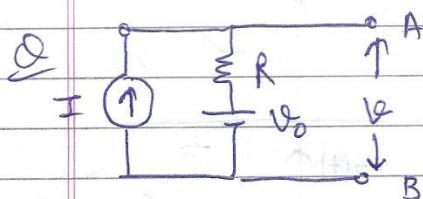

$I = 0$ $V = V_0$ This property not
followed but
this property is
of linear causal.

However, we have to find whether this is causal or not.

so apply only causal property.

$$\text{If } I = I_1(t) \text{ for } t \leq t_0 \quad V_1(t) = V_2(t) \\ I = I_2(t)$$

This is causal system.

causal system, causal signal has response zero till $t=0$.

6) Lumped / Distributed

Distributed - When physical dimension of the system is comparable to wavelength of excitation, then system is said to be of distributed type.

Lumped - When physical dimensions are negligible as compared to wavelength of excitation.

calculate wavelength of ac supply system in Andhra

$$v = 2\pi \lambda$$


$$\lambda = \frac{v}{2\pi} = \frac{3 \times 10^8 \text{ m/s}}{2\pi \times 50 \text{ Hz}}$$

$$= 0.6 \times 10^7$$
$$= 6 \times 10^6$$

$$\lambda = 6000 \text{ km}$$

- Distributed - Power tx lines
- Lumped - m/w used in labs.

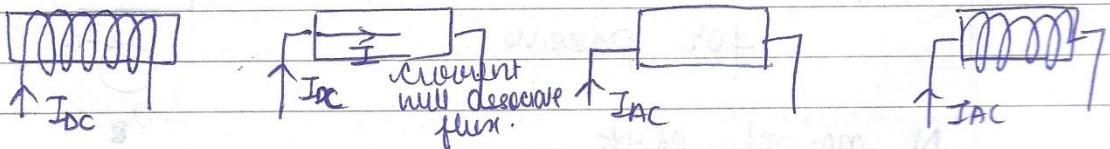
Inductance - property to associate magnetic flux.



Inductance is all. because inductance is property of material.

Page
that a medium can withstand

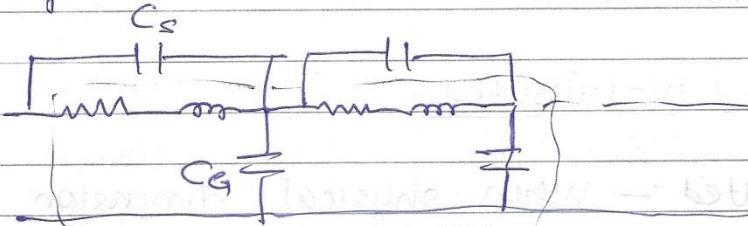
dielectric - max. electric field, without polarization
strength



This is distributed.

To convert to lumped - Neglect C_s

Then convert T to TI or TI to T.

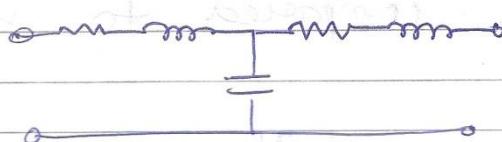

7) finite / infinite N/W


8) One dimensional / multi-dimensional

No. of independent variable 1 - 1 dimensional
n n n n n 2 - 2 "

9) Active / Passive

Total energy supplied by excitations to the system is greater than or equal to zero then system is passive

$$\sum_{k=1}^N \int v_k I_k dt \geq 0$$

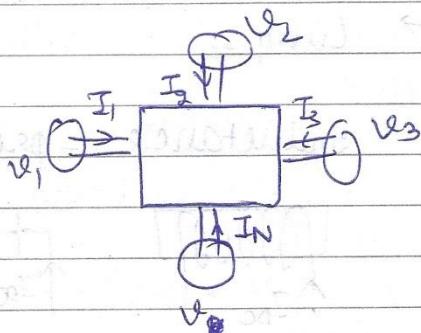



for passive

N no. of ports

\Rightarrow shows internal loss is zero.
Jtna I/P diya exactly utna O/P.

Active - when internal any energy source.

10) Unilateral / Bilateral

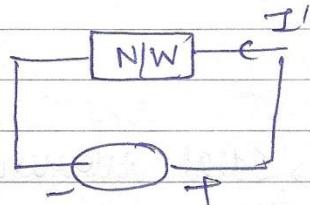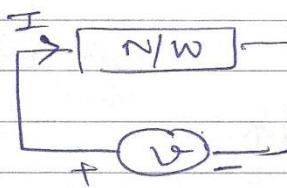

$$I' = I \quad (\text{Bilateral})$$


Unilateral

eg:- resistor


eg:- diode.

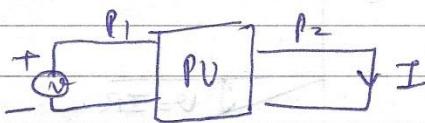11) Reciprocal / Non Reciprocal N/W

A n/w is reciprocal if interchange of excitation & response doesn't change relationship of excitation & response.




If $I' = I$ then
reciprocal n/w.

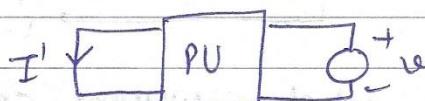

If the n/w consists of only bilateral elements then the n/w must be reciprocal.

If n/w contains some unilateral elements, then it may be possible that n/w is reciprocal.


Non reciprocal

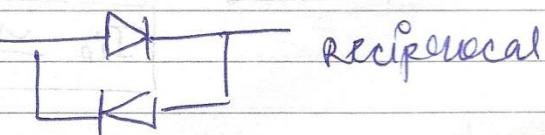


Network Elements

1) voltage source



\Rightarrow Ideal voltage source

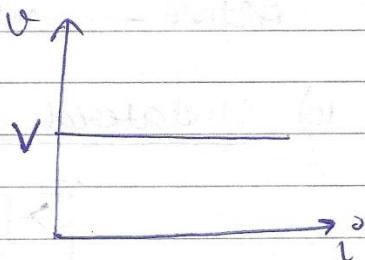


\Rightarrow Ideal current source

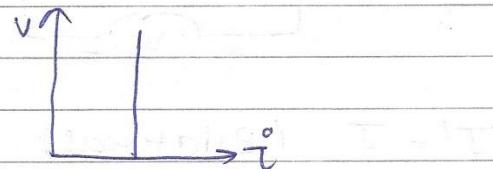

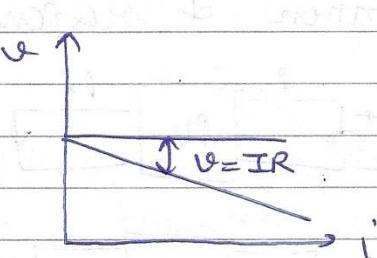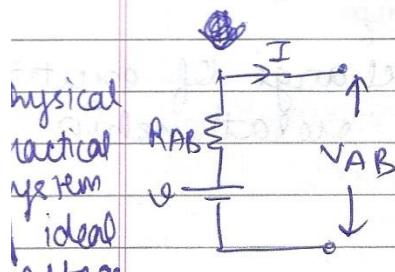ideal current source \uparrow $V \neq 0$ (IMP).




Practical system of ideal current source

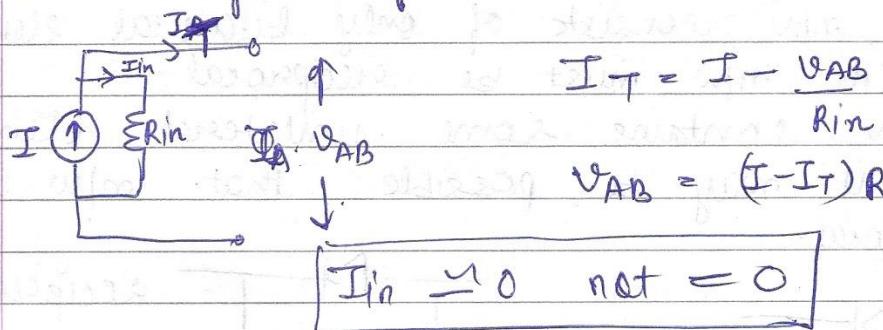

If in ideal case $R_{in} = \infty$ then I is short circuit i.e. O/P voltage $v_{AB} = 0$.
 so, ~~volt~~ ~~to~~ Thus, value of I diminishes as this shows that no energy is supplied.
 Thus we can't assume voltage across current source as zero.


$$I_T = I - \frac{v_{AB}}{R_{in}}$$

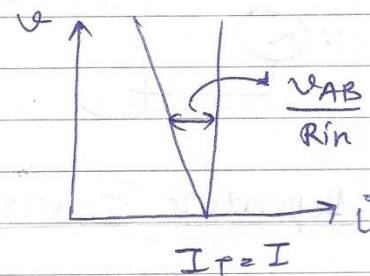


$$I_T = I$$

- It is impossible to achieve short circuit cond. of ideal voltage source. is not a valid representation
- Open circuit cond. of ideal current source is not valid representation

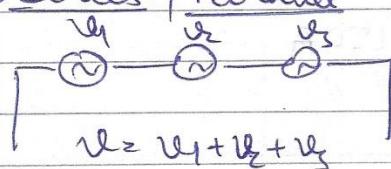
Series / Parallel combination of ideal sources




$$V = V_1 + V_2 + V_3$$

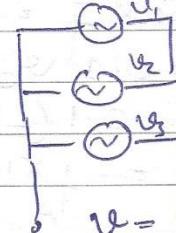

$$V = 0 \text{ not defined}$$

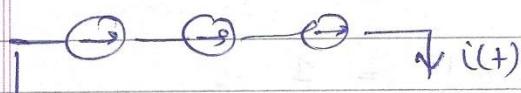

$$i(+) = \text{Not defined}$$

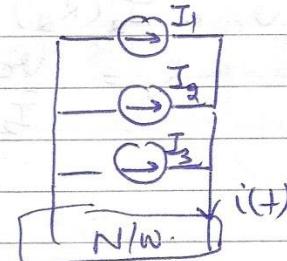


$$i(+) = I_1 + I_2 + I_3$$

I = some current going to V
some to N/W (i)

MBDWRITEWELL


Date
Page

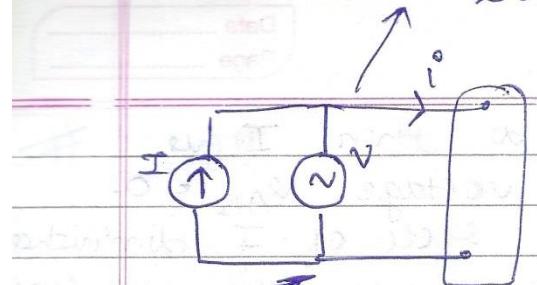

voltage is affecting
N/W. However I

is无关 to N/W


Here thus I source is
redundant.

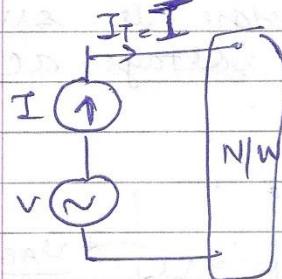

Here V source is redundant
as I is constant.

Dependent Sources

1/2/2014

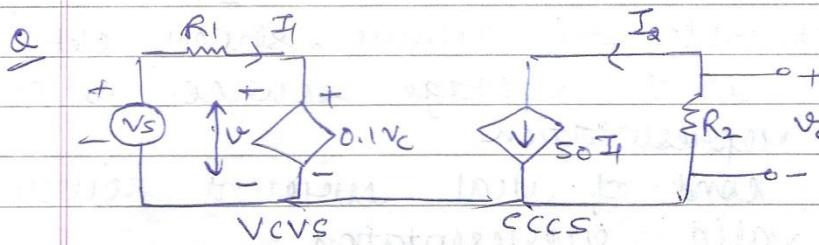

$$V_c = -10 \text{ V}$$

$$I_1 = 3 \text{ A}$$

$$I_2 = ? \quad V_c = ?$$

$$I_2 = 50 \times I_1 = 50 \times 3 = 150 \text{ A}$$

$$V = 0.1 V_c$$

$$= 0.1 (-10)$$

$$= -\frac{1}{10} \times 10 = -1 \text{ V}$$






$$V_c = I_2 (R_2)$$

$$R_2 = \frac{V_c}{I_2} = \frac{-10}{-150} = \frac{1}{15} \Omega$$


Alexander → 1, 2, 3, 6 Read

MBD WRITEWELL

Date
Page

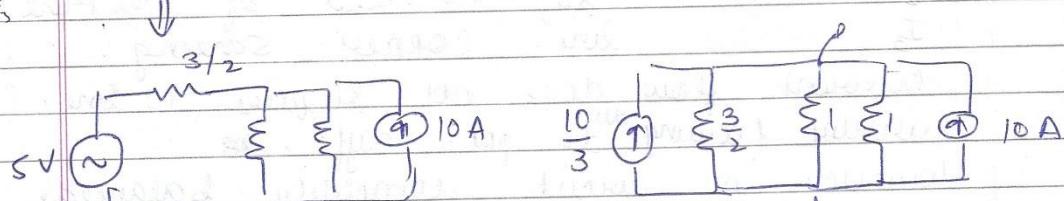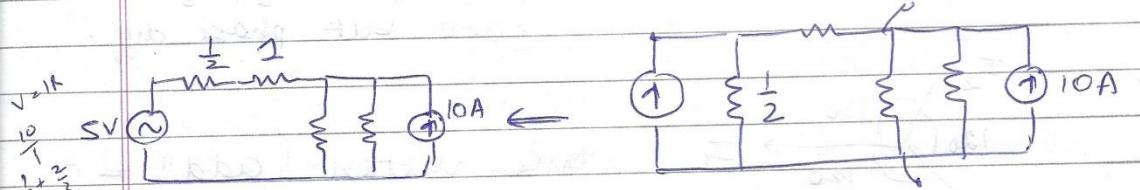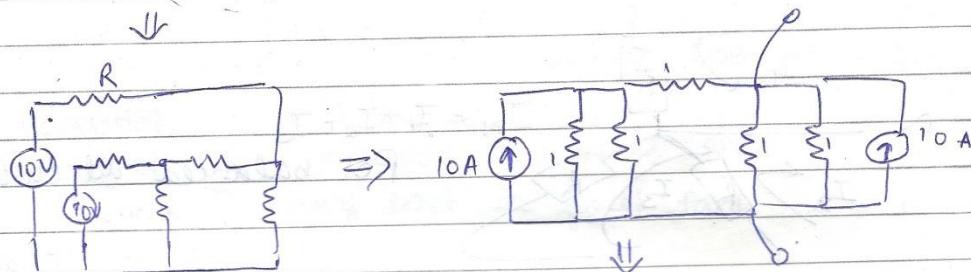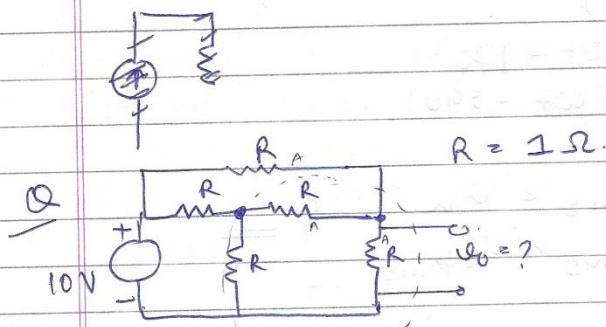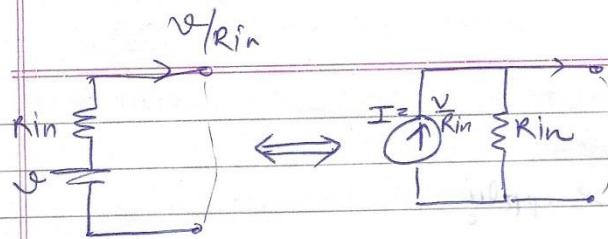
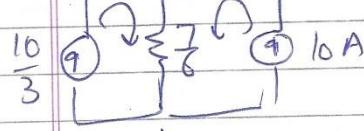
$$\frac{2}{3} + \frac{1}{2} = \frac{4+3}{6} = \frac{7}{6}$$



$$\text{dry} = 11$$

AC Source


Balanced 3 ϕ supply

$$v_R = v_{MR} \sin(\omega t)$$

$$v_Y = v_{MY} \sin(\omega t + 120^\circ)$$

$$v_B = v_{MB} \sin(\omega t + 240^\circ)$$

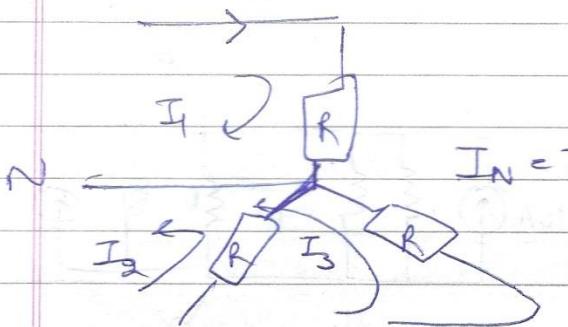
$$\begin{aligned} v_{MR} &= v_{MY} = v_{MB} = v_m \\ (v_R)_{RMS} &= (v_Y)_{RMS} = (v_B)_{RMS} \end{aligned} \quad] =$$



$$I_N = I_1 + I_2 + I_3$$

For balanced all current same.

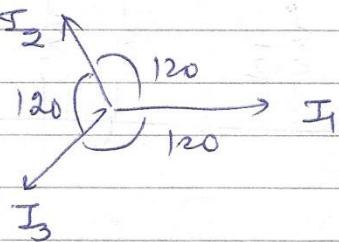mag. of I_1 , I_2 , I_3 all same but phase diff.



True vector addⁿ = 0

so, no need of neutral line. copper saving.

Current flow does not require N line.

Current flowing due to pot. diff. .

However, no circuit completely balanced.

Analogous Mechanical System

W.R.C. calculator

Date
Page

or volume of tank

H = total capacity of tank to store water

C = " " " capacitor " " charge

H or Volume analogous to C

Charge q represents volume of water stored inside the tank.

I/P in form of K.E storage " " " P.E

In cap. also energy stored in form of P.E

Q

$$K_{out} = K_{in} - P_1 - P_{1L} - P_2 - P_{2L}$$

Potential
energy of
tank 1

energy lost in first tank

↓ ↓ → energy lost in second tank

Potential
energy of
second tank

Q

$$\text{Area} = A$$

$$\frac{d}{d} \quad \epsilon_0 \quad \frac{d}{d}$$

$$\epsilon_0 A/d$$

All in series

$$d \quad \frac{d}{\epsilon_0 k} \quad d$$

$$\epsilon_0 k A/d$$


$$d \quad \epsilon_0 \quad \frac{d}{d}$$


$$\epsilon_0 A/d$$

$$B$$


means
gauge plate

Q done

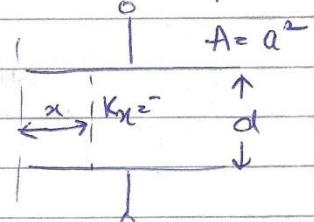


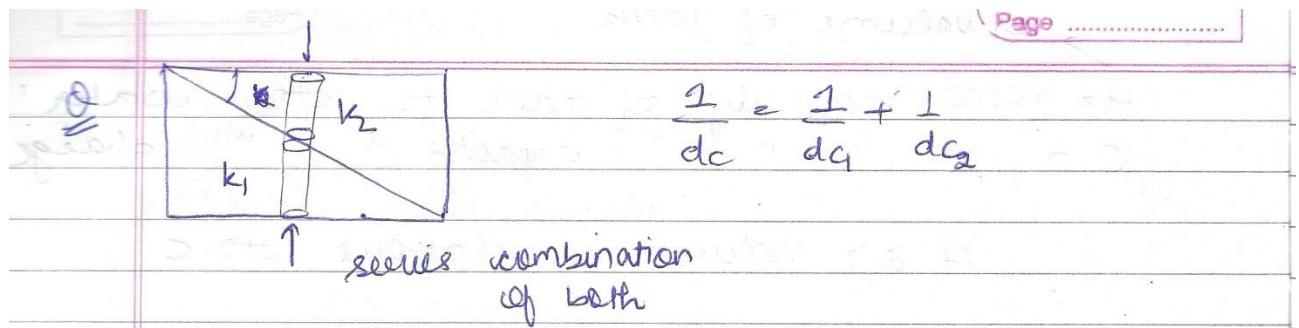

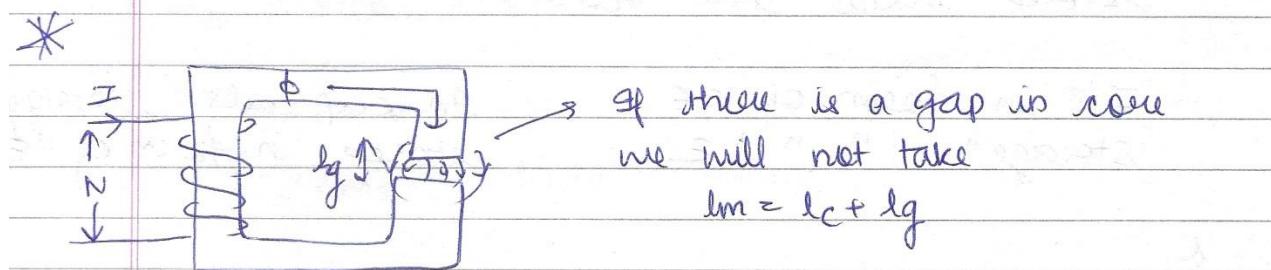Now after calculating dc , now parallel combination -



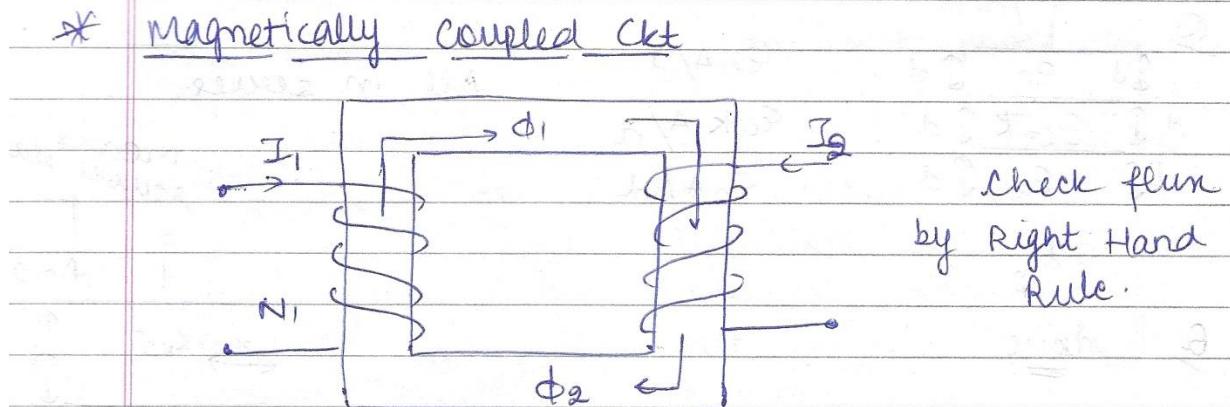If mean path length = l_c
 then take $l_m = l_c + 2l_g$ practically by experiment
 R, ϕ all changing.



flux same direction = +ve coupling
 flux opp " = -ve "

3) L = Ability to generate flux due to MMF applied at coil with coil


M same for both as they both are associated with same core.

* DOT CONVENTION

amount to


- If both the coils are entering to the dotted terminal or leaving from dotted terminal then coupling is +ve.
- If current through one of coil is entering to the dot and other leaving from dot then coupling -ve.
- Potential of dotted terminals ^{to both the coils} is always in phase.

Q

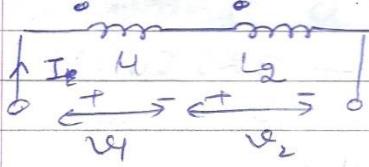


$$\begin{aligned} V &= V_1 + V_2 \\ &= L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} + 2M \frac{dI}{dt} \end{aligned}$$

①

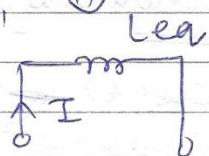

$$I = L_1 + L_2 + 2M$$

Q

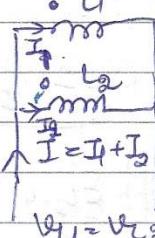

$$V = V_1 = L_1 \frac{dI}{dt} + \cancel{L_2 \frac{dI}{dt}} + \cancel{2M \frac{dI}{dt}}$$


$$V = V_2 = L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt}$$

$$V_1 = V_2 = V$$

$$V = \text{Leq } I'$$


$$V = \text{Leq } I'_1 + \text{Leq } I'_2$$

But values of I' and I'_2 from above

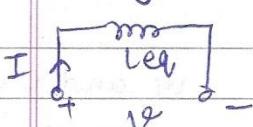

NIBBLE WRITE WELL
Date _____
Page _____

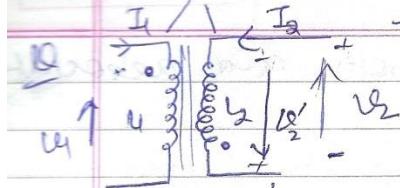head of arrow means the head of arrow considered acc to dotted terminal. Where dotted i.e. +ve.



$$I = I_1, I'_1 - M I_2$$

$$I'_2 = I_2, I'_2 - M I_1$$

$$V_1 = L_1 \frac{dI_1}{dt} - M \frac{dI_2}{dt}$$

$$V_2 = -L_2 \frac{dI_2}{dt} - M \frac{dI_1}{dt}$$

$$\begin{aligned} V_1 &= 2 \frac{dI_1}{dt} - M \frac{dI_2}{dt} \\ &= 2 \frac{d}{dt} (325 \sin(2\pi 50t) + 4e^{-2t}) - \frac{d}{dt} (325 \cos(2\pi 50t)) \\ &= 2 (325 \cos(2\pi 50t) (\omega) + 4(-2)e^{-2t}) \\ &\quad + 325 \sin(2\pi 50t) (\omega) \end{aligned}$$

$$\text{Let } \omega = 1.$$



$$= 2 (325 \cos t - 8e^{-2t}) + 325 \sin t$$

$$= 650 \cos t - 16e^{-2t} + 325 \sin t$$

Mistake

$$\begin{aligned} V_2 &= L_2 \frac{dI_2}{dt} - M \frac{dI_1}{dt} \quad \text{(Here there will be } -V_2) \\ &= 3(-325 \sin t) - 1(325 \cos t + 8e^{-2t}) \end{aligned}$$
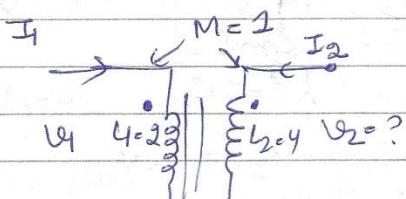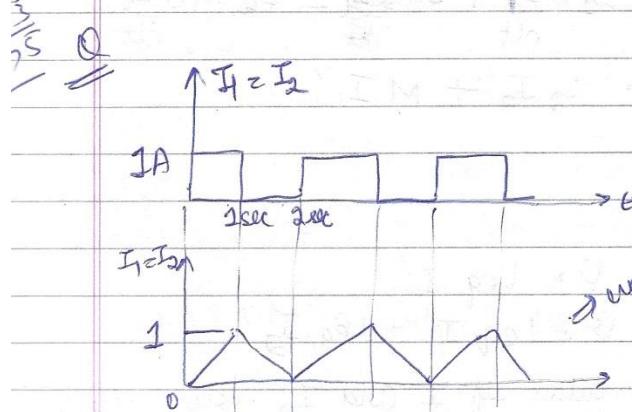
$$V_2 = -975 \sin t - 325 \cos t + 8e^{-2t}.$$




find v_1 and v_2 waveform

$$v_1 = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$$

$$= 2 \frac{dI_1}{dt} + \frac{dI_2}{dt}$$
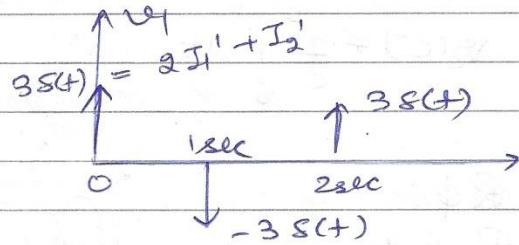
$$v_2 = L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt} = 4 \frac{dI_2}{dt} + \frac{dI_1}{dt}$$



This does not mean that at $t = 0$ amplitude 3. Amplitude is ∞ . This represents that there is change of 3.

$$\rightarrow Y = \frac{1}{R} = \text{conductance}$$


$$\rightarrow \text{Reactance } X_L = j\omega L \quad (\text{dynamic elements})$$

$$X_C = \frac{1}{j\omega C}$$

Impedance $Z =$ (Used for sinusoidal signals)

$$\text{Admittance } \frac{1}{Z}$$

\rightarrow

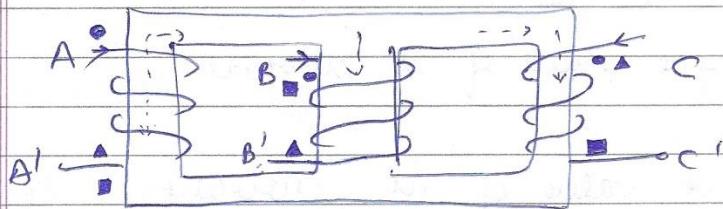

CAPACITOR

Data
Page

Say initial charge on cap. is q_0 .
Then charge at any time t

$$q(t) = q_0 + \int i_c dt$$

$$v_c(t) = \frac{q(t)}{C} = \frac{q_0}{C} + \frac{1}{C} \int i_c dt$$

$$v_c(t) = v_c(0) + \frac{1}{C} \int_0^t i_c dt$$


INDUCTOR

$$NI = R\phi$$

$$NI = R \cdot B \cdot A_c$$

$$= R \cdot M_{0}M_{r}H A_c$$

$$H \propto I$$

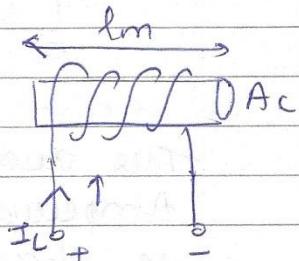

i.e. flux associated
with coil even


if $I = 0$.

Residual
flux density

$$\vec{B}$$

$$B_{sat}$$

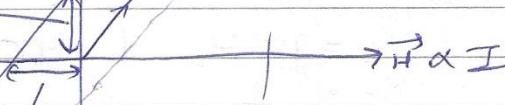Region - $I \uparrow$ but mag
field does not \uparrow



\rightarrow negative saturation

(flux changes direction) Cohesive force - excessive force req.
to make flux zero inside core


$\nearrow \rightarrow$ for +ve value of ac moment

$\searrow \rightarrow$ for -ve value of ac moment.

Area under curve = hysteresis loss.

freq. of ac loop = freq. of traversal of hysteresis loss.

More freq. of ac current = More loss.

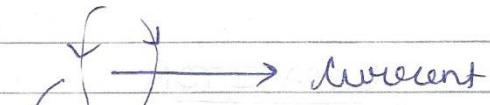
→ Eddy current loss = 

Reversal of Ampere's law

Moment will be induced

in core i.e. eddy current

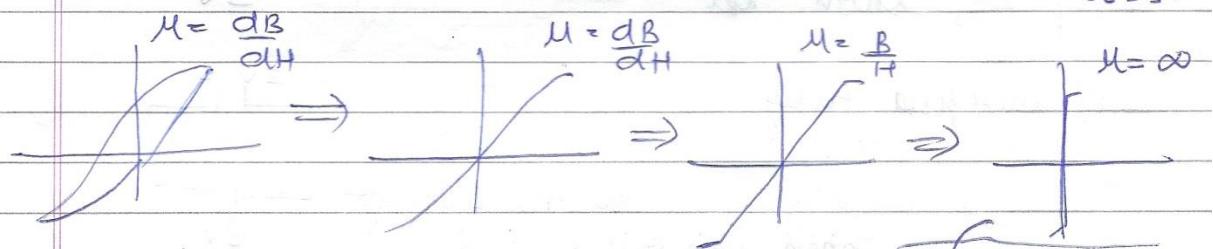Intra jada ϕ , utra jada I . \uparrow eddy current loss.



Practical core

Hysteresis loss is that the electrical energy we give does not totally get

Change in I connected in magnetic domain
⇒ Flux is always & smooth.

even $I=0$ current sufficient to generate flux.

$(I=0)$

) Inductor under unexcited state. (dc case)

Initially $\frac{d\phi}{dt}$ very large. Offers ∞ resistance

to current.

$$V = L \frac{d\phi}{dt}$$

V = nearly equal to source

so current zero.

2) Fully energised — $\frac{d\phi}{dt} = 0$. (dc case)


$V = 0$ (i.e. short circuit)

\Rightarrow If ac supply, $\frac{d\phi}{dt}$ will not be zero at any pt.

CAPACITOR

1) uncharged ($q_1 = 0$)

Initially
or or

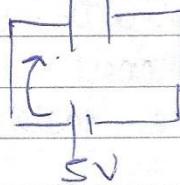

so flow of

current due to Pot. difference


so, short ckt.

2) energised fully

no P.D

so no current

open circuit

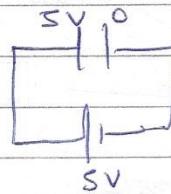

formulae

1) Lorentz force

A diagram showing a charged particle with charge q and velocity \vec{v} moving perpendicular to a uniform magnetic field \vec{B} . The particle follows a circular path with radius r .

$$\text{III} \rightarrow F_L = q\vec{v} + q(\vec{v} \times \vec{B})$$


②

A diagram showing a rectangular loop carrying a clockwise current I . A uniform magnetic field \vec{B} is applied perpendicular to the plane of the loop. The forces on the top and bottom sides are shown as \vec{F} , with the top force pointing right and the bottom force pointing left.

$$\text{III} \rightarrow \vec{F} = i\vec{l} \times \vec{B}$$

(3) BIOT-SAVART LAW:


$$\vec{dB} = \frac{\mu_0}{4\pi} \frac{i \vec{dl} \times \vec{r}}{|\vec{r}|^3}$$

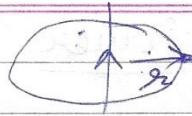

$\vec{I} \times \vec{II} = \vec{III}$ } all three
 ↓ Right Hand
 finger palm Thumbs

OHM'S LAW
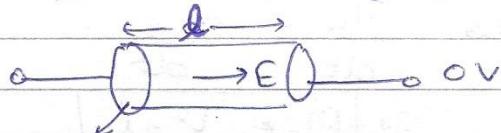
$$J \propto E \quad (\text{at constant temp.})$$



$$AC \quad J = \frac{I}{A_c}$$

$$J = \sigma E$$

$$J = \frac{1}{\rho} E = \frac{1}{\rho} \frac{V}{l}$$

$$\frac{I}{A} = \frac{V}{\rho l}$$


$$V = \left(\frac{\rho l}{A} \right) I$$

↓ Resistance = R

$$R = \frac{dV}{dI} \quad (\text{non linear})$$

- Voltage division rule
- Current " rule

\Rightarrow Power

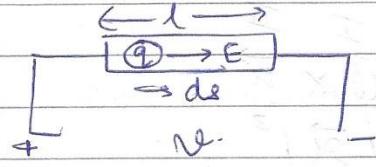

Mechanical power

$$P = \frac{dE}{dt}$$

$$P = \frac{dW}{dt}$$

$$F = q, E$$

$$W = F \cdot ds$$

$$= qE \cdot ds = q, E, l \cos(\theta)$$

$$W = q, E, l$$

$$W = q, V$$

Work done by electrical force q, E

$$\frac{dw}{dt} = v \frac{da}{dt}$$

$$P_e = V \cdot i$$


CRAMER'S RULE

KCL / KVL

Loop - Closed path.

Mesh - fundamental loops = one mesh.

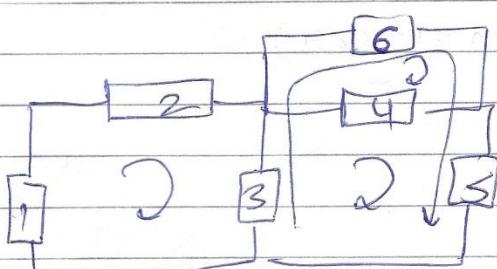
i.e. smallest closed path present in a n/w which does not include any other closed path.



$e_6, e_4 \rightarrow M$


$e_3, e_5, e_6 \rightarrow M$

$e_3, e_6, e_5 \rightarrow$ also
mesh

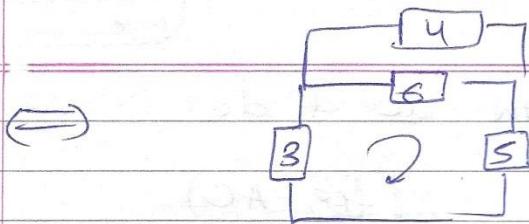


Now $e_3 e_6 e_5$
also mesh

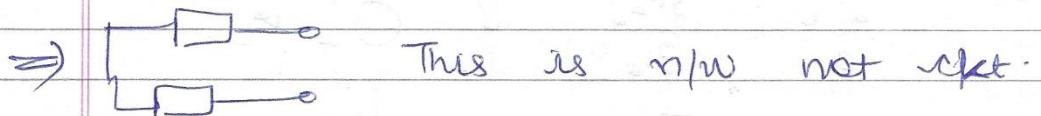If asked to count no. of meshes = 4
If no. of mesh eqns = 3 because in that
→ Circuit - closed path A single ckt
has to be chosen
in which no. of meshes = 3




Power Flow

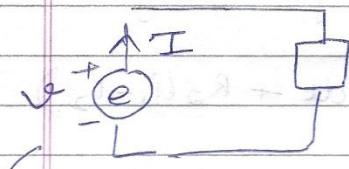

Source delivering power to load as +ve terminal se aavant bahan ga raha.

Power delivered by element e to rest of n/w is $+vI$.

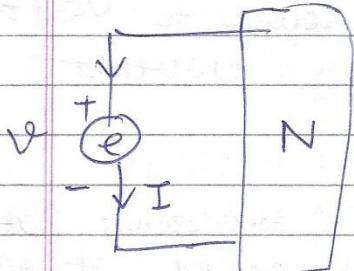Power received by n/w element from N/W $-vI$



Power delivered by e to rest of N/W = $-vI$
Power received by e from rest of N/W = vI


KVL applied for both ac & dc.

$$\sum E_k = 0 \quad (\text{for AC})$$

$\forall k$

RMS value with phase

$$i_1 = i_2 + x$$

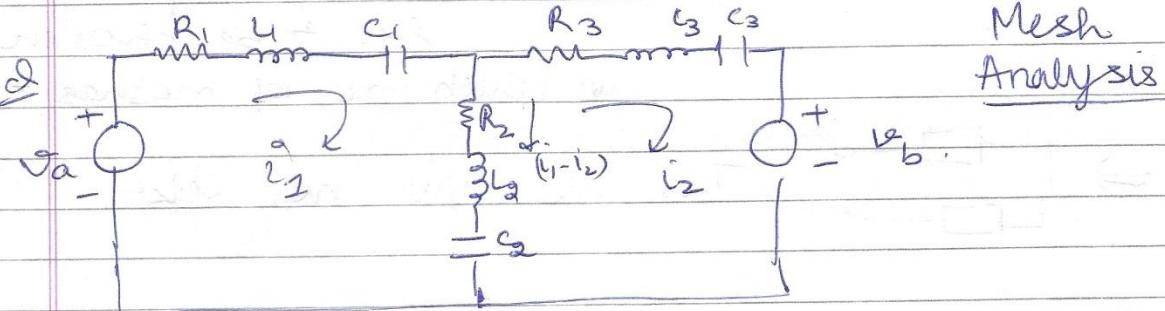

All cap & inductors initially unegised.


$$V_a = R_1 i_2 + L_1 \frac{di_1}{dt} + \frac{1}{C_1} \int i_1 dt + R_3 (i_1 - i_2)$$

$$+ L_2 \frac{d(i_1 - i_2)}{dt} + \frac{1}{C_2} \int (i_1 - i_2) dt$$

$$V_b = R_3 i_2 + L_3 \frac{di_2}{dt} + V_b = R_2 (i_1 - i_2) + L_2 \frac{d(i_1 - i_2)}{dt}$$

$$+ \frac{1}{C_3} \int i_2 dt + \frac{1}{C_2} \int (i_1 - i_2) dt$$

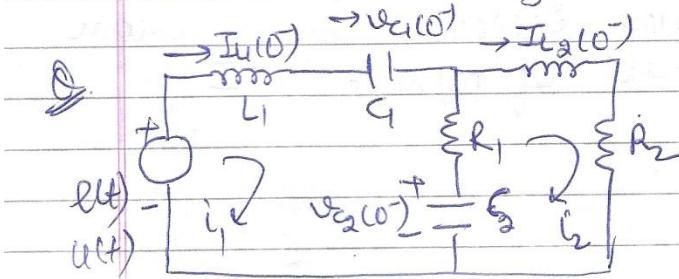In mesh connect, convert source to voltage source because voltage across current source is not zero.



$u(t)$ represents that
 $e(t)$ applied at $t=0$

X this already includes
initial condition

WIRE WELL
Date _____
Page _____

$$e(t) u(t) = L_1 I_{L1}(0^-) + L_1 \frac{di_1}{dt} + v_{C1}(0^-) + \frac{1}{C_1} \int_{t=0}^t i_1 dt \\ + (i_1 - i_2) R_1 + v_{C2}(0^-) + \frac{1}{C_2} \int_{t=0}^t (i_1 - i_2) dt$$

$$\cancel{L_2 I_{L2}(0^-)} + R_2 i_2 = \frac{1}{C_2} \int_{t=0}^t (i_1 - i_2) dt + v_{C2}(0^+) \\ + L_2 \frac{di_2}{dt} + R_1 (i_1 - i_2)$$


as $v_L(t) = L \frac{dI_L(t)}{dt}$ \rightarrow at time ($t = t$) which already includes $t = 0$.

~~Imp~~ However in capacitor

$$v_C(t) = v_C(0^-) + \frac{1}{C} \int_0^t i dt$$


$\brace{ }$ change in voltage.

Nodal Analysis

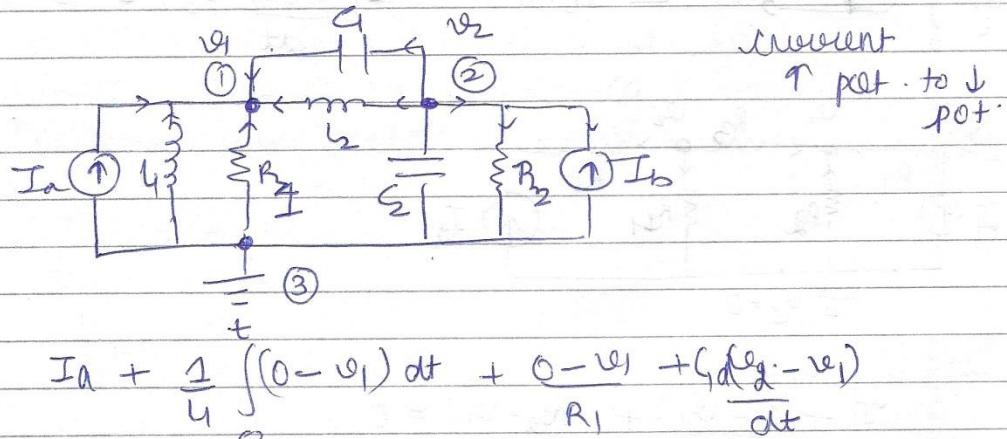

$$I_a + \frac{1}{R_1} \int_0^t (0 - v_1) dt + \frac{0 - v_1}{R_1} + G_1 \frac{d(v_2 - v_1)}{dt}$$

$$G_2 \frac{d(v_2 + v_1)}{dt} + \frac{v_2 - v_1}{R_2} - I_b + \frac{1}{L_2} \int_0^t (v_2 - v_1) dt + \frac{G_1 d(v_2 - v_1)}{dt} < 0. \\ + \frac{1}{L_2} \int_0^t (v_2 - v_1) dt = C$$

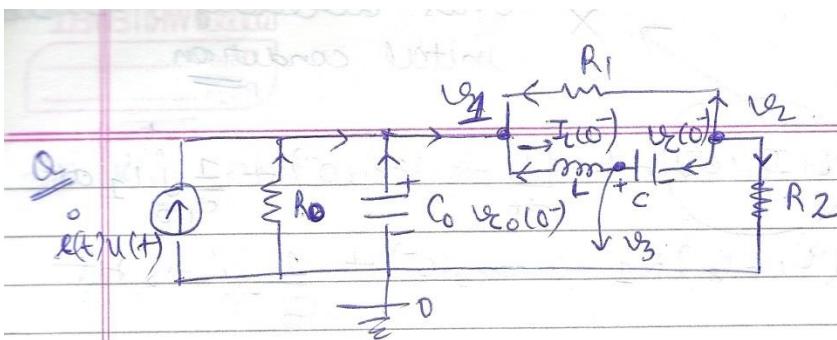
Soln

Whenever this situation occurs we have to introduce another node v_3 because we need voltage across inductor & capacitor.

$$i(+v(t)) + \frac{(0-v_1)}{R_B} + C_0 \frac{d(0-v_1)}{dt} + \frac{(v_2-v_1)}{R_1} + \frac{1}{L} \int_{0}^{t} (v_3 - v_1) dt - I_L(0^-) = 0.$$

$$\frac{v_2}{R_2} + \frac{v_2 - v_1}{R_1} + C \frac{d(v_2 - v_3)}{dt} = 0.$$

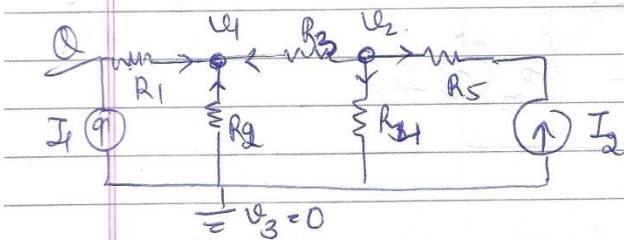
$$\frac{1}{L} \int_{0}^{t} (v_2 - v_3) dt + I_L(0^-) + I_1 \frac{d(v_2 - v_3)}{dt} = 0$$



$$I_1 + \frac{(0-v_1)}{R_2} + \frac{(v_2-v_1)}{R_2} = 0.$$


$$\frac{v_2 - v_1}{R_3} + \frac{v_2}{R_4} = I_2$$

Ideal Source

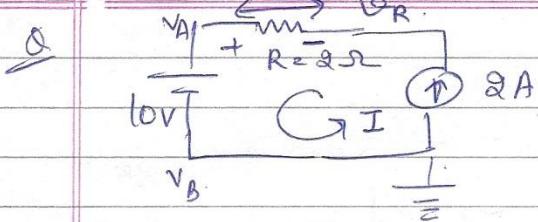

find V_R and I .

Soln

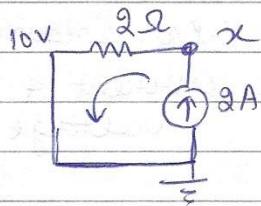

Current source delivers constant current = 2A.

$$V_R = 2 \times 2 = 4 \text{ V}$$

$$\boxed{V_R = -4 \text{ V}} \quad \underline{\text{Ans}}$$

alt

$$(10 - 2x) = 4$$


$$10 - 2x = 6$$

~~Opposite~~

$$x - 10 = -4$$

$$x = -4 + 10$$

$$= 6$$

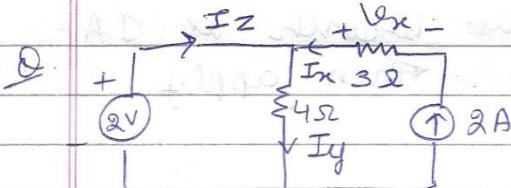

1) find, I_Z , V_x , I_y , I_x

2) Power delivered by current source

3) Power received by voltage source

4) Power dissipated in m/w

Soln

$$I_x = 2 \text{ A}$$

$$V_x = -6 \text{ V}$$

$$I_y = \frac{1}{2} \text{ A}$$

$$I_Z + I_x = I_y$$

$$I_Z = \frac{1}{2} - 2 = -\frac{3}{2} \text{ A}$$

$$3) I_x \cdot V$$

$$8 \times 2 = 16 \text{ W}$$

Power delivered



Power receive
↑

$$3) 8 \times 3 = 3 \text{ V}$$

$$4) 16 - 3$$

$$= 13 \text{ W}$$

8/2/2013

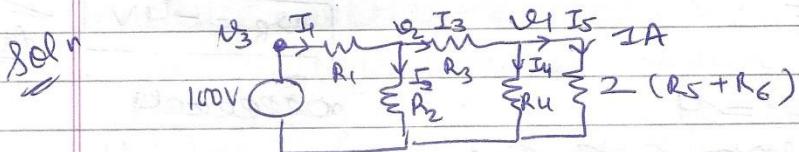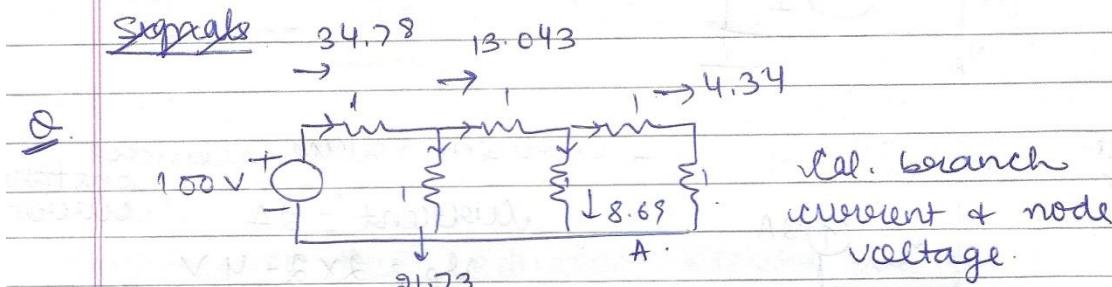Network Analysis

$$\text{eq. voltage } R = 2 \quad (\text{last branch})$$

other
method
Assume current in last branch is 1A.
find voltage for that. Then apply
unitary method.

$$V_1 = (R_5 + R_6)$$


$$I_4 = \frac{R_5 + R_6}{R_4} \quad I_3 = I_4 + I_5 \\ I_3 = I_4 + 1$$

$$V_2 = V_1 + I_3 R_3$$

$$I_2 = \frac{V_2}{R_2} = \frac{V_1 + I_3 R_3}{R_2}$$

$$I = I_2 + I_3$$

$$V_2 = I_1 R_1 + V_2$$

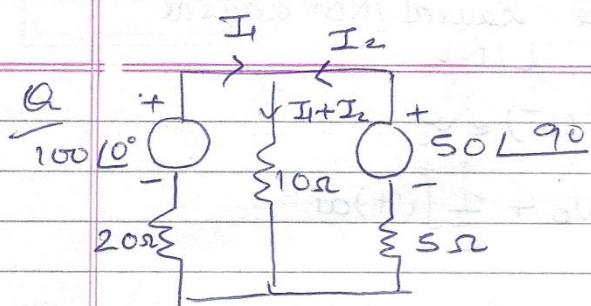

find I_1, I_2

$$100 \angle 0^\circ = 10(I_1 + I_2) + 20I_1$$

$$100 \angle 0^\circ = 30I_1 + 10I_2$$

Q always in
+ve x axis

$$50 \angle 90^\circ = 10(I_1 + I_2) + 5I_2$$

$$10 \angle 90^\circ = 10^2 I_1 + 10^2 I_2$$

$$10 \angle 90^\circ = 2I_1 + 3I_2$$

$$-30 \angle 0^\circ = -9I_1 - 3I_2$$

$$10 \angle 90^\circ - 30 \angle 0^\circ = -7I_1$$


$$7I_1 = 30 \angle 0^\circ - 10 \angle 90^\circ$$

$$I_1 = \frac{30 \angle 0^\circ}{7} - \frac{10 \angle 90^\circ}{7}$$

$$\text{Mag} = \sqrt{\left(\frac{30}{7}\right)^2 + \left(-\frac{10}{7}\right)^2}$$

$$\theta = \tan^{-1}\left(\frac{-10}{7} / \frac{30}{7}\right)$$

\tan is -ve.

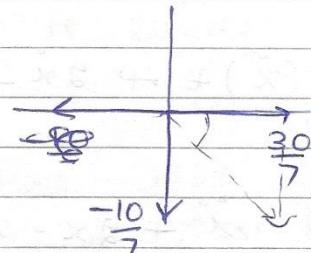

Q UNL / c/nc / TN/TI

$$1) y_n = 6x_{(n-2)}$$

$$y_n = 6x_{(n-2)} x_{(n-2)} \text{ NL}$$




T

$$2) n^3 y_n = 6x_{(n-2)} \quad L, TIV, C$$

$$3) y_n = 3x_{(n)} - 2x_{(n-1)} \quad L, TIV, C$$

$$4) 3x_{(n-1)} + x_{(n+1)} = y_n \quad L, TIV, NC$$

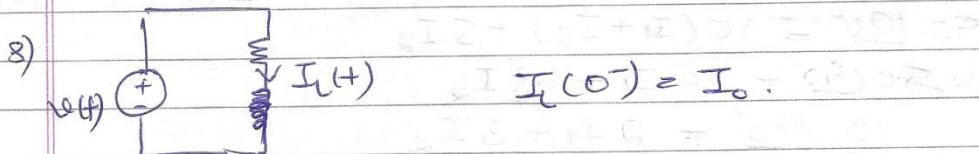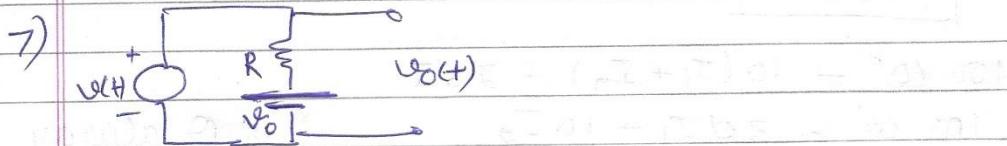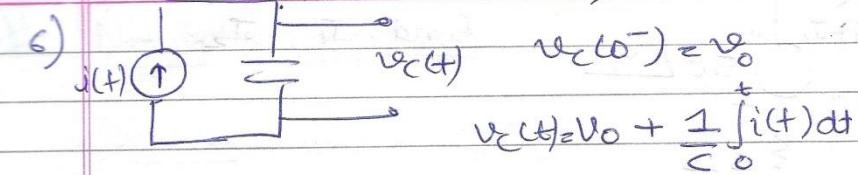find if these ckt's are causal / Non causal
 TV / TI , L / NL




9) $\ddot{x} + 2\dot{x} - 3x = \sin 4t$ L, TI, C

10) $(\ddot{x})^2 + 2\dot{x} - 3x = \sqrt{\sin 4t}$ NL, TI, C


11) $(\ddot{x})t + 2\dot{x} - 3x = \sin 4t$ L, TV, C

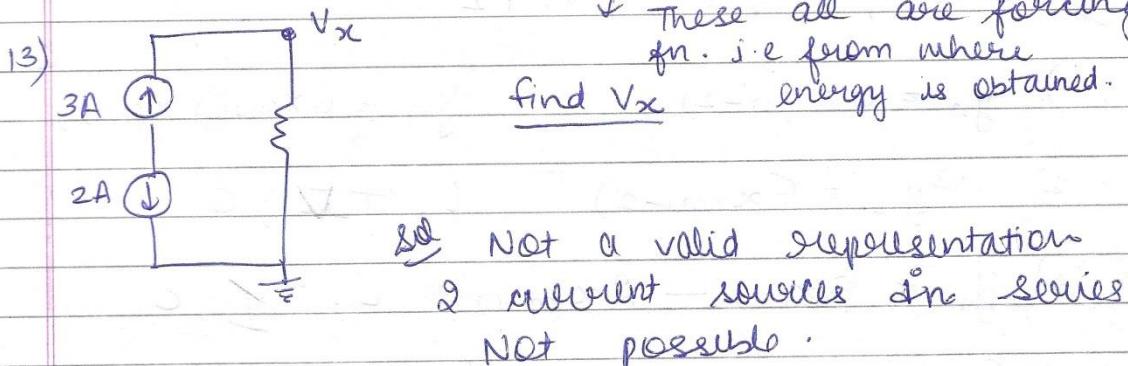12) $\ddot{x} + 2x \cdot x - 3x = 4t$ NL, TI, C


These all are forcing fn. i.e from where find V_x energy is obtained.



Unrealistic ckt.

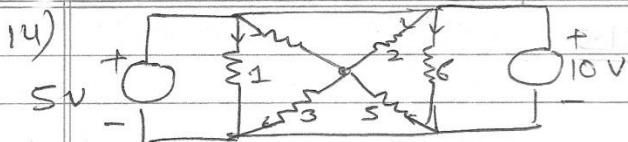

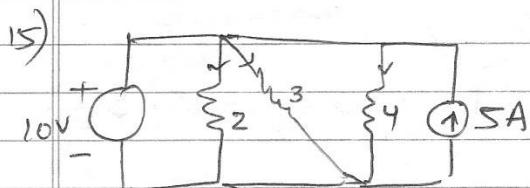Not valid as
2 voltage sources
in parallel.



In this I source
redundant.

$$V \text{ across } 2, 3, 4 = 10V$$

$$I_{(2)} = \frac{10}{2} = 5A$$

$$I_{(3)} = \frac{10}{3}$$

$$I_{(4)} = \frac{10}{4} = 2.5$$

6) Non linear. even though eqⁿ is linear.

7) Linear

first, for homogeneity check that for zero IP, zero OP, then further to check if linear.

8) Non linear.


If zero IP, no zero OP = Non linear.

$$I_{(n)} = I_0 + \frac{1}{L} \int_0^t [v(t) - I_n(t) \cdot R] dt$$

\Rightarrow for linear - diff. eqⁿ should be linear +
for 0 IP, 0 OP.

NETWORK ANALYSIS

→ Signals

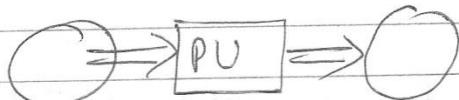

I/P = Energy / Material / Info
 ↓
 i.e. Signals

O/P = Energy / Mat. / Info.
 ↓
 eg:- coal given in furnaces.


→ Information carriers are called signals

$$v(t) = \sin t$$

$$v(t) = \sin t + V$$

$v(t)$ not voltage

$v(t) = v$ voltage

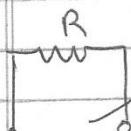

$$v(t) = \sin t + V \Rightarrow \text{not strictly signal.}$$

$$v(t) \rightarrow$$

Above all 3, not signals.


$$\begin{aligned} \text{Signal} &\rightarrow \text{Static} = v(t) = \sin t \\ &\rightarrow \text{Dynamic} = v(t) = s v \end{aligned}$$

Strict signals carry info which is variable.
def.

Loosely, DC signal also signal.

→ signal Representation

i) dc signal.

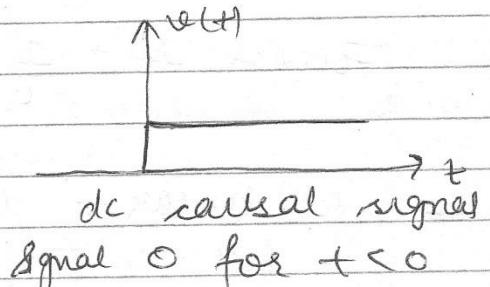

2) Sinusoidal signal.

$$v(t) = \sqrt{2} A \sin(\omega t + \phi)$$

A = RMS value of $v(t)$

3) Exponential signal

$$v(t) = A e^{st}$$

A, s = complex quantities

Any signal can be represented in this four continuous time

$$\Rightarrow s = (\sigma + j\omega)$$

complex \downarrow Radian 2
Naper 2

$$v(t) = (a+jb) e^{\sigma t} + (a-jb) e^{\sigma t}$$

$$= 2a e^{\sigma t}$$

for any physical system A = real.

$$\begin{aligned} v(t) &= A e^{(\sigma+j\omega)t} + A e^{(\sigma-j\omega)t} \\ &= A \left[e^{\sigma t} [e^{j\omega t} + e^{-j\omega t}] \right] \\ &= A e^{\sigma t} \left[e^{j\omega t} + e^{-j\omega t} \right] \\ &\quad \left[(j\omega - j\omega) \cancel{A} \right] \\ &= 2A e^{\sigma t} \cos \omega t \end{aligned}$$

$$\boxed{v(t) = 2A e^{\sigma t} \cos \omega t}$$

$$1) \cos(2t + 30^\circ)$$

$$\sigma = 0$$

$$\omega = 2$$

$$s = \pm 2j$$

$$2) 2\cos 3t + 4\sin 3t$$

$$s = \pm 3j$$

$$s = \pm 3j$$

$$\sigma = 0$$

static signal

$$3) e^{-2t} + e^{-3t} \cos(4t + \phi)$$

$$\sigma = -2$$

$$s = -2 \pm j0$$

$$s = -3 \pm 4j$$

$$4) e^{j2t} + e^{-3t} \cos(4t + \phi)$$

$$s = \pm 2j$$

$$s = -3 \pm 4j$$

\cos or \sin must contain $e^{j\omega t}$ and $e^{-j\omega t}$. That is why \pm

$$5) u + s e^{2t} \cos(5t + \phi)$$

$$s = 0$$

$$s = 2 \pm 5j$$


Singularity functions

→ used to represent a discontinuous fn or a fn having discontinuous derivative.



1) Unit step

$$a) 2u(t-2)$$

$$b) 2u(2-t)$$

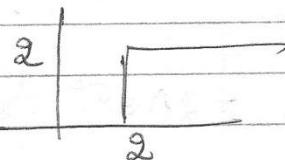


b) $2u(-t+2)$

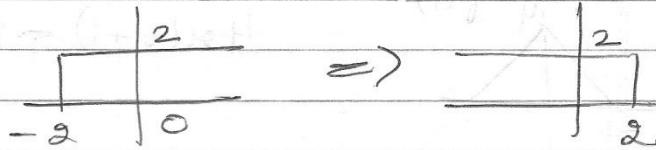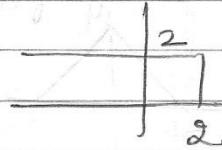
 \Rightarrow 

c) $-4u(2-t)$

$-4u(-t+2)$

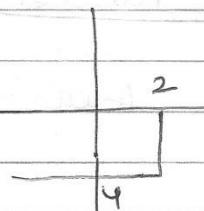 $=$ 


d)

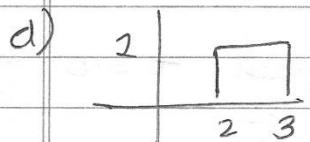

$u(t-2) - u(t-3)$

e) $f(t)$

$f(t) = u(t-1) + 2u(t-2) - 3u(t-3)$

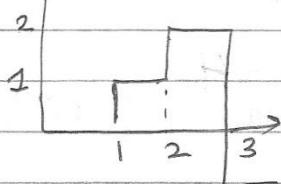


$f(2) = 1 + 1 = 2$

$f(3) = -1$

2) Ramp signal

a) $g_1(t-1)$

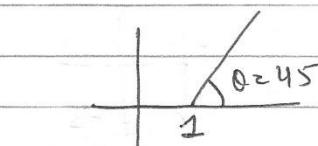


b) $-g_1(t-1)$




c)

$3g_1(3-t)$

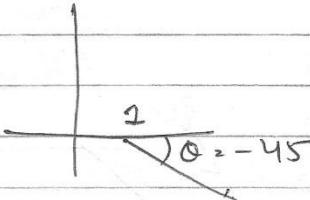

$\frac{0}{3}, 0$



$\frac{g_1}{3} = 3$

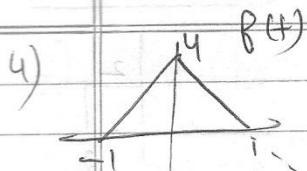

$$4u(t+1) \leftarrow 8u(t) + 4u(t-1)$$

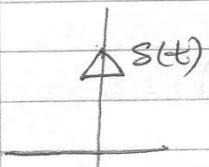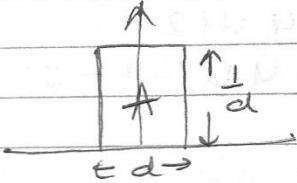3) Impulse function

$$\lim_{d \rightarrow 0} \text{Area} = A$$



$$s(t) = \begin{cases} 0 & t \neq 0 \\ \text{not defined} & t = 0 \\ \infty & \text{or } \infty \end{cases}$$

$$\boxed{\int_{0^-}^{0^+} s(t) dt = 1}$$


1) 4 represents area under curve = $\oint f(t) dt$

$\oint_0^0 f(t) dt$ not magnitude


$$\int_{-0}^{0^+} f(t) dt = 4$$

$$4s(t)$$

2) $-3s(t+4)$

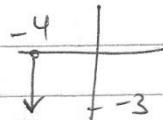


3)

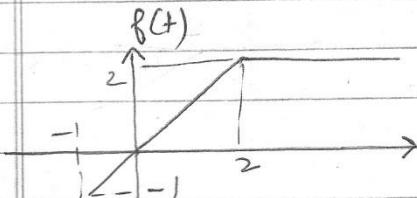


Want $f(t)u(t)$, $f(t-1)u(t)$, $f(t) \cdot u(t-1)$

i) $f(t) u(t)$

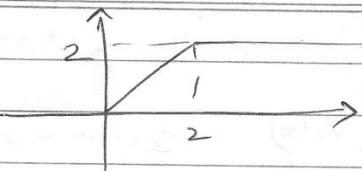


ii) $f(t-1) \Rightarrow$

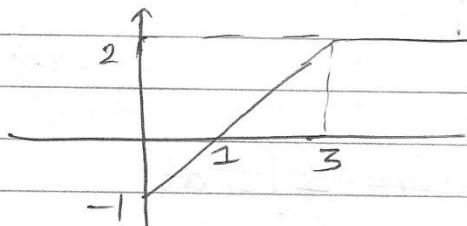


$f(t-1) u(t) = \text{same}$

iii)

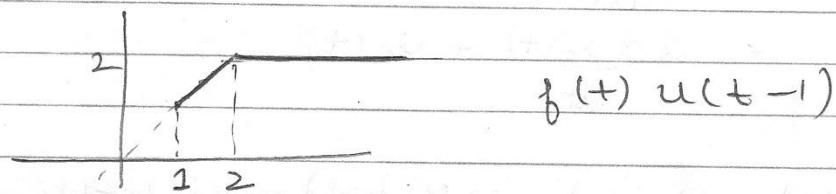

Q

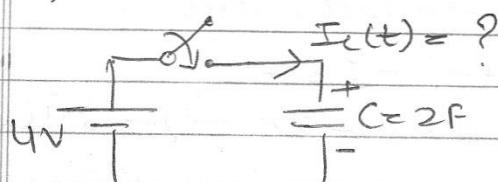

$$v_C(0^-) = 0$$

Find $I_C(t)$

Solⁿ



$$4u(t) = I/P \quad \text{Now close switch}$$

$$I_C = C \frac{dv_C}{dt} = 2 \frac{d(4u(t))}{dt}$$

$$I_C = 8 \delta(t)$$

i.e. in zero time ∞ current flows and max. charge is attained by capacitor.

Q

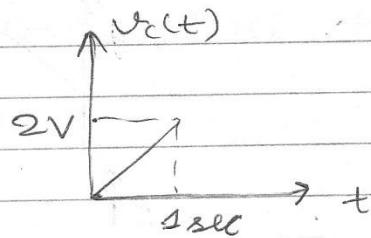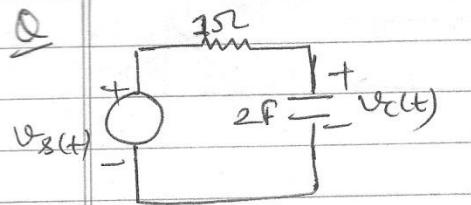

find

$$v_s(t)$$

$$v_s(t) =$$

$$v_c(t) = \frac{1}{C} \int I_C dt$$

(1, 2)


$$(0, 0) \frac{2}{\frac{1}{2}} = 2$$

$$\begin{aligned} v_s(t) &= I_C(t) + v_c(t) \\ &= C \frac{d v_c(t)}{dt} + v_c(t) \\ &\approx 2 \frac{d v_c(t)}{dt} + v_c(t) \end{aligned}$$


$$v_c(t) = 2u(t) - 2u(t-1) - 2u(t-1)$$

$$v_s(t) = 2[2u(t) - 2u(t-1) - 2s(t-1) + 2u(t) - 2u(t-1) - 2u(t-1)]$$

Q

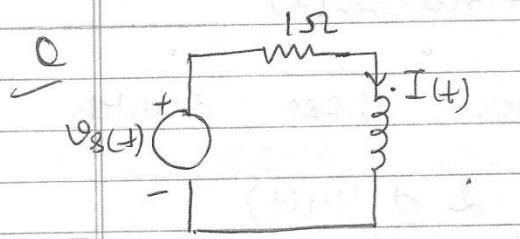

$$I(t)$$

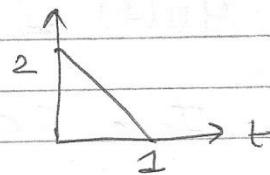

$\downarrow -ve$
 $\uparrow +ve$

$$v_s(t) = 1 \cdot I(t) + L \frac{d I(t)}{dt}$$

(0, 2)

$$v_s(t) = I(t) + L \frac{d I(t)}{dt}$$

(0)

$\frac{2}{1}$

$$2i(t) = -2i(t-1) \quad 2i(-t+1)$$

$$\text{Signal} = 2u(t) - 2u(t) + 2u(t-1)$$


Computer Organisation / EMMI.] for ES
MBDWRITEWELL

Date
Page

Q.

$$(2, 10) \quad (1, 0)$$
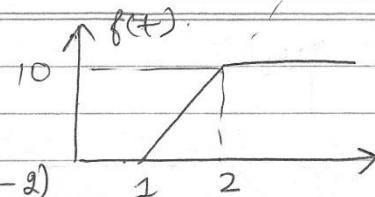
$$\frac{10}{2-1} = \underline{\underline{10}}$$



$$\text{find } f(t) \quad 10 u(t-1) - 10 u(t-2)$$

$$\cancel{10 u(t-1)} - \cancel{10 u(t-2)}$$


$$\cancel{10 u(t-1)} + \cancel{10 u(t-1)} - \cancel{10 u(t-2)}$$

Q

$$(0, -4) \quad (1, 0)$$

$$-4 = \underline{\underline{4}}$$

$$-1$$

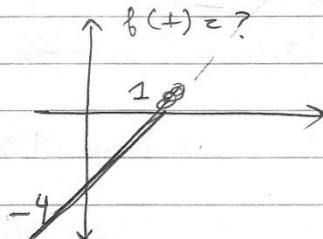

$$4 u(t-1)$$


$$4 u(1-t)$$

$$\boxed{-4 u(1-t)}$$

Q

$$-3u(t-1) - u(t-1) \quad (1, -3) \quad (2, -4)$$

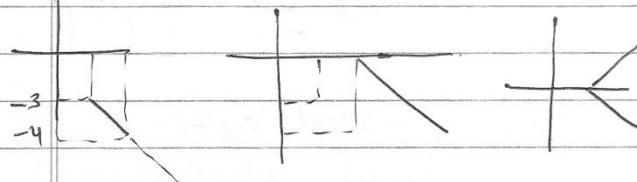
$$+ 4u(t-2) + u(t-2) \quad \frac{-3+4}{1-2} = \underline{\underline{-1}}$$



Q

$$2u(t-1) - 5u(t-2)$$



$$- 2u(t-3.5)$$

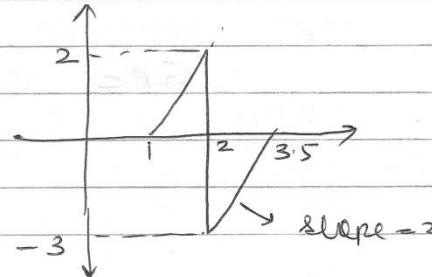

$$(2, 2) \quad (1, 0)$$

$$\frac{2-0}{2-1} = \underline{\underline{2}}$$

$$(0, -3) \quad 0.35$$

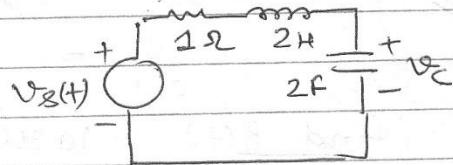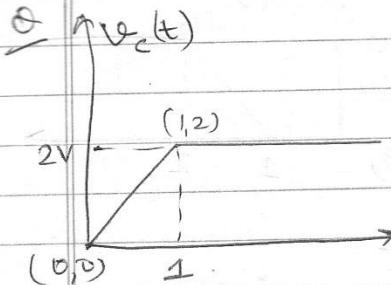

$$v_c(t) = 2u(t) - 2u(t-1)$$



I through circuit

$$I_c = C \frac{dv_c}{dt}$$

$$v_s(t) = 1 \times I_c + L \frac{dI_c}{dt} + v_c(t)$$

$$= C \frac{dv_c}{dt} + L \frac{d}{dt} \left(C \frac{dv_c}{dt} \right) + v_c(t)$$
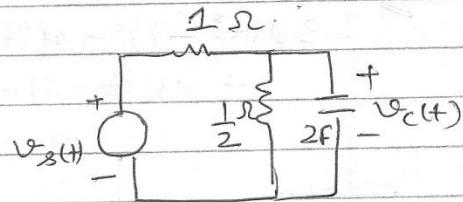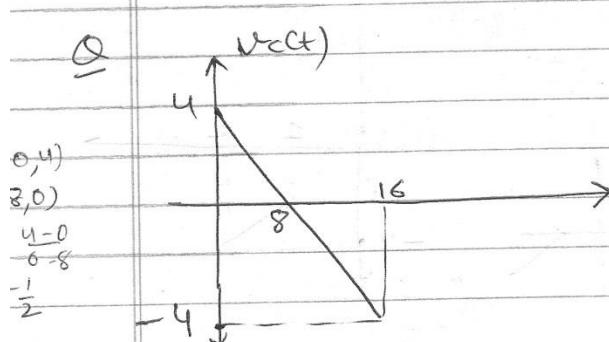
$$= C \frac{dv_c}{dt} + LC \frac{d^2 v_c}{dt^2} + v_c(t).$$



Find $v_s(t)$.

$$v_s(t) = 1i_o(t) + v_c(t)$$

~~$$v_s(t) = v_c(t) + C \frac{dv_c(t)}{dt} + \frac{v_c(t)}{L}$$~~

$$= v_c(t) + 2v_c(t) + C \frac{dv_c(t)}{dt}$$

$$= 3v_c(t) + 2 \frac{dv_c(t)}{dt}$$

$$\text{Signal.} = 4u(t) - \frac{1}{2}u(t) + 4u(t-16) + \frac{1}{2}u(t-16)$$

$$\begin{aligned}
 & 12u(t) - \frac{3}{2} s_1(t) + 12u(t-16) + \frac{3}{2} s_1(t-16) \\
 & + 2 \left(4s(t) - \frac{1}{2} u(t) + 4s(t-16) + \frac{1}{2} u(t-16) \right) \\
 & 12u(t) - \frac{3}{2} s_1(t) + 12u(t-16) + \frac{3}{2} s_1(t-16) + 8s(t) \\
 & - u(t) + 16s(t-16) + u(t-16) \\
 \Rightarrow & 11u(t) - \frac{3}{2} s_1(t) + 13u(t-16) + \frac{3}{2} s_1(t-16) \\
 & + 8s(t) + 16s(t-16)
 \end{aligned}$$

State of system

A system is said to be in steady state when its behaviour across all the elements of the system are either a constant or a regular type of periodic fn.

Variation of any state variable during the transition from one steady state to another steady state is smooth until unless there is some impulsive type of action happens inside the system. In presence of impulsive type of action, it may be possible that state variable changes sharply from one state to another.

if $\frac{d(x)}{dt}$ dt cannot be zero. i.e no impulse.

α response means Impulse.

MBDWRITEWELL

Date

Page

Different ways of characterizing LTI system-

- 1) Differential eqn approach
- 2) Impulse Response
- 3) Step Response
- 4) Black BOX Description.

→ In general, total no. of independent dynamic variables =

dynamic elements present in a system = No.

of state variables =


Order of system = No. of poles =

No. of zeroes = No. of natural v

⇒ No. of poles always equal to No. of zeroes.

⇒ Natural v or poles location represents freq. of the system under zero excitation.

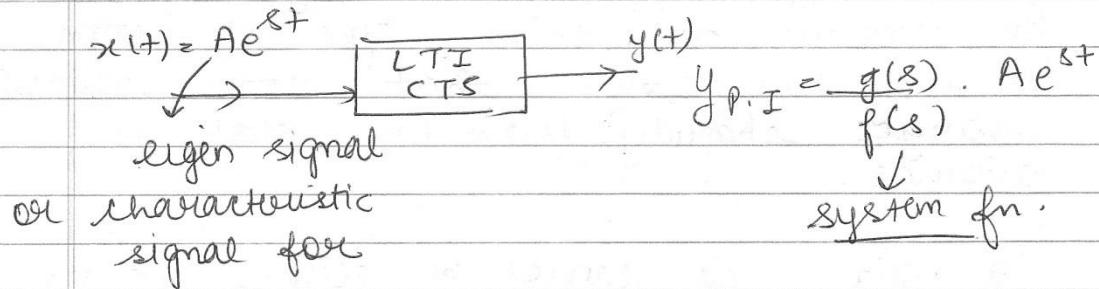i.e. freq. of system when it is switching from one transi. steady state to another.



$\Rightarrow 2)$ If $\sigma = 0$

$$s = \pm j\omega$$

$$x(t) = Ae^{\pm j\omega t} \rightarrow \boxed{\text{LTI CTS}} \rightarrow y_{PI} = \frac{g(j\omega)}{f(j\omega)} A e^{\pm j\omega t}$$

fourier

3) If excitation available at discrete intervals.

$$x(t) = \underbrace{Ae^{\frac{sTm}{z}}} \quad t = nT$$

$$\rightarrow \boxed{\text{LTI (DTS)}} \rightarrow y(z) = \frac{g(z)}{f(z)} x(n)$$

$$x(t) = Az^n \quad n = \text{variable}$$

$z = \text{complex } \nu \text{ of discrete time system.}$

$y(z)$ in form of difference equation.

$$a_2 y(n+2) + a_1 y(n+1) + a_0 y(n) = b_2 x(n+2)$$

$$+ b_1 x(n+1) + b_0 x(n)$$

$$(a_2 E^2 + a_1 E + a_0) y(n) = [b_2 E^2 + b_1 E + b_0] x(n)$$

$$y(n) = \left(\frac{b_2 E^2 + b_1 E + b_0}{a_2 E^2 + a_1 E + a_0} \right) x(n)$$

$$= \frac{g(E)}{f(E)} | x(n) .$$


$$y_{PI} = \frac{g(E)}{f(E)} | x(n)$$

$E = \text{complex } \nu \text{ i.e. } z$

steady state Analysis of Dynamic N/W
with DC excitation

1) closed at $t=0$


find $i_L(t)$, $v_C(t)$, $i_R(t)$

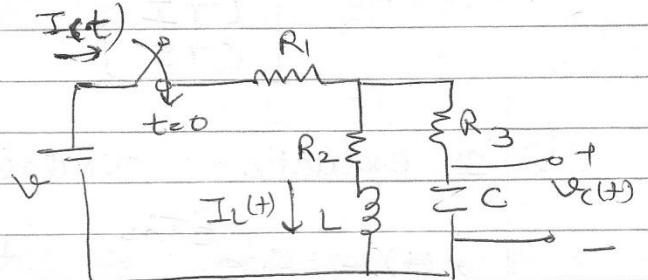



$$\text{Solu} \quad \text{as } I_{ss} = \frac{V}{R_1 + R_2}$$

$$I_{ss} = I_{ss}$$

$$v_{ss} = \frac{R_2}{R_1 + R_2} V$$

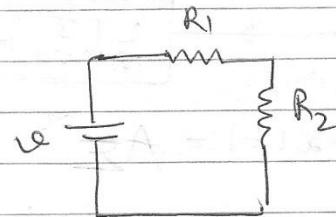

2)

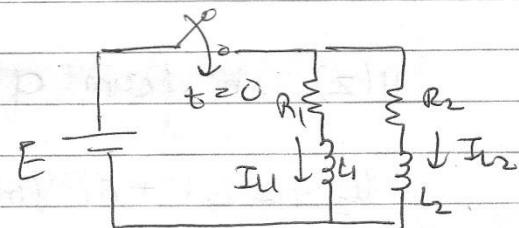
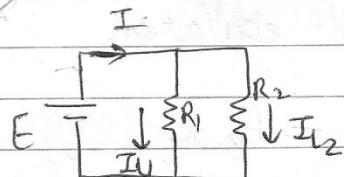


$$Req = \frac{R_1 R_2}{R_1 + R_2}$$

$$I = \frac{E(R_1 + R_2)}{R_1 R_2}$$


$$I_{L1} = \frac{R_2}{(R_1 + R_2)} \frac{E(R_1 + R_2)}{R_1 R_2} = \frac{R_2 E}{R_1 + R_2} = \frac{E}{R_1}$$
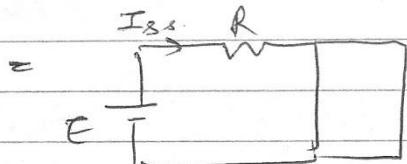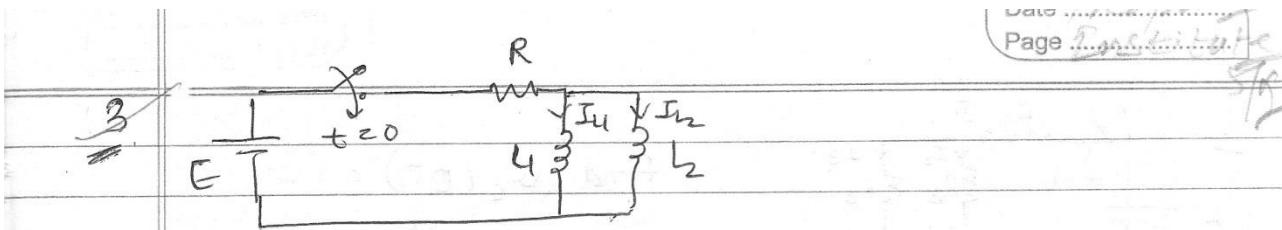
$$I_{L2} = \frac{R_1 E}{R_1 R_2} = \frac{E}{R_2}$$



$$I_{ss} = \frac{E}{R}$$


$$I_{1,ss} = I_{2,ss} = \frac{E}{2R}$$

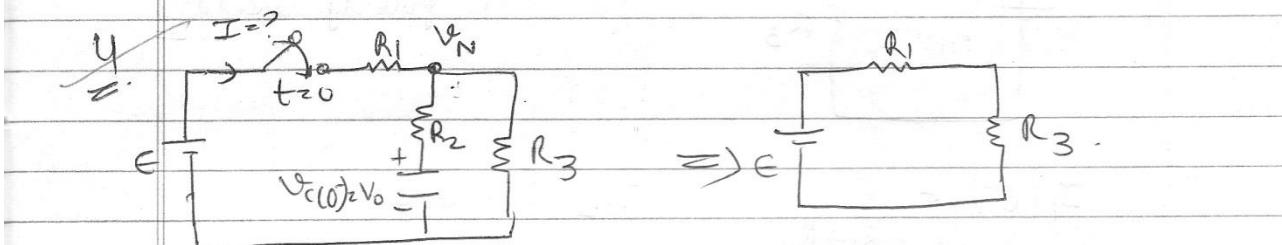


$$I_{ss} = \frac{E}{R_1 + R_3}$$

$$V_N = \frac{E}{R_1 + R_3} = V_{0(ss)}$$

V_N ..

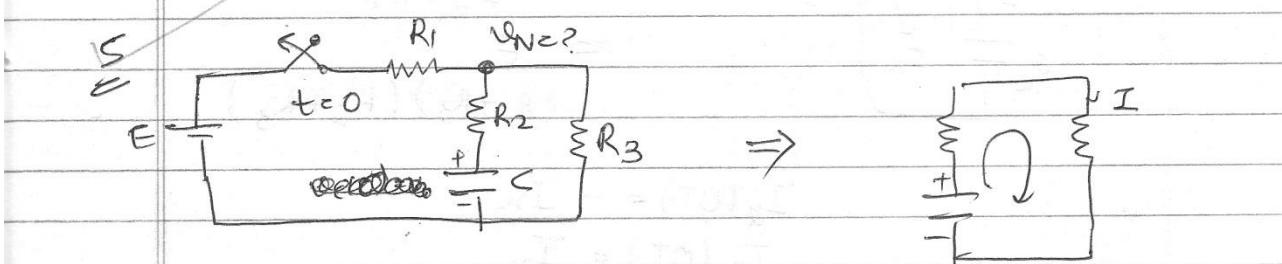


After ∞ time $I = 0$.

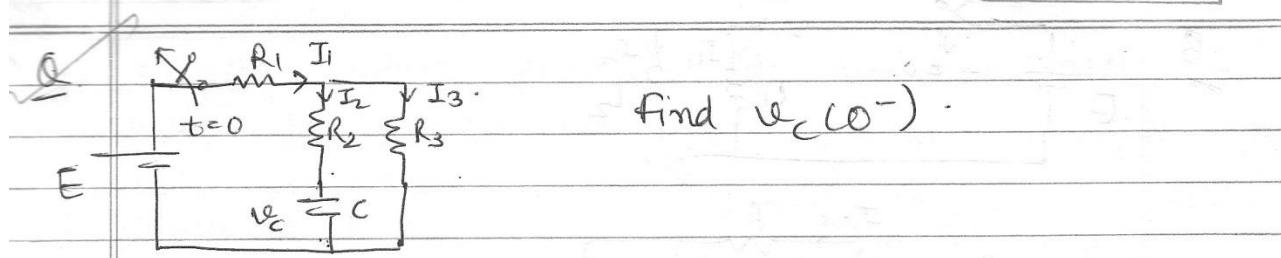

$$I = \frac{E}{R_1 + R_3}$$
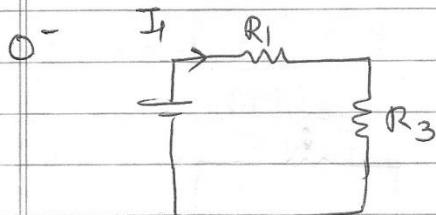
$$V = \frac{E}{R_1 + R_3} R_3 = V_c(0^-) = V_c(0^+).$$




C fully charged

$$I_1(0^-) = \frac{E}{R_1 + R_3} \quad I_2(0^-) = 0$$

$$I_3(0^-) = I_1(0^-).$$

0^+

$$I_1(0^+) = 0.$$

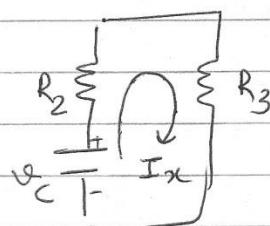

$$\begin{aligned} I_x &= \frac{V_c(0^+)}{R_2 + R_3} \\ &= \frac{E}{(R_1 + R_3)(R_2 + R_3)} \end{aligned}$$

$$I_2(0^+) = -I_x$$




$$I_B(0^+) = I_x$$

$$I_1(\infty) = 0$$

$$I_2(\infty) = 0$$

$$I_3(\infty) = 0$$



$$V_C(\infty) = 0$$

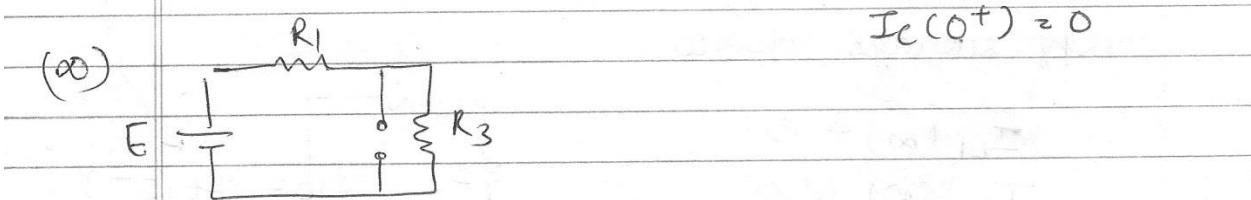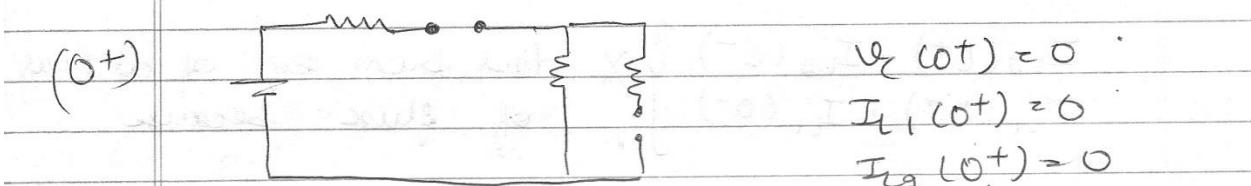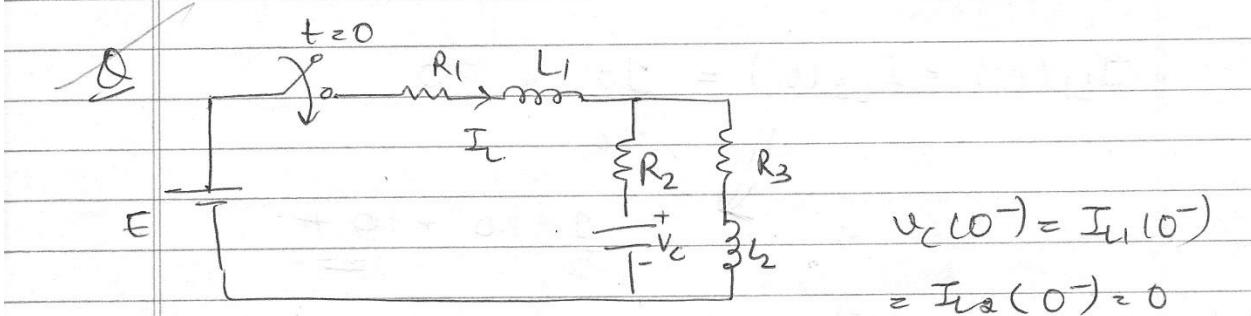

$$V_C(\infty) = \frac{ER_3}{R_1 + R_3}$$

$$I_C(\infty) = 0$$

$$\frac{1 \times 1}{1+1} = \frac{1}{2}$$

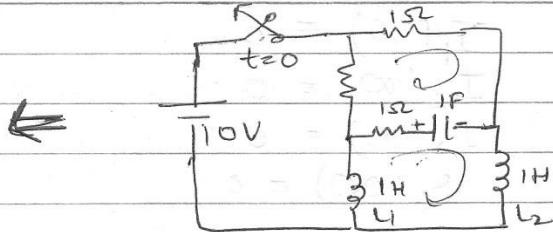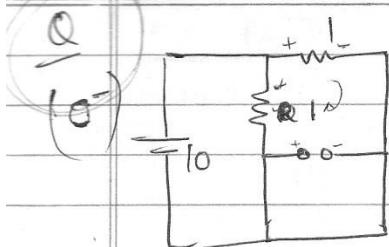

$$I_{L1}(0^-) = I_{L2}(0^-) = \frac{10}{\frac{1}{2}} = 20$$

$$= \frac{1}{2} \times 20 = 10 \text{ A.}$$

$$V_C(0^-) = 0 \text{ V}$$


$$\begin{aligned} I_{L2}(0^+) &= I_{L2}(0^-) \\ I_{L1}(0^+) &= I_{L1}(0^-) \end{aligned} \quad \left. \begin{array}{l} \text{find from eq'n of continuity} \\ \text{of flux because} \end{array} \right)$$

current flow in both loops as there are 3 energy storage devices.

$$I_{L1}(\infty) = 0$$




$$I_{L2}(\infty) = 0$$

$$V_C(\infty) = 0$$

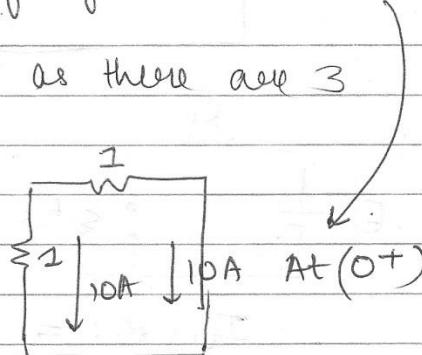


15/2/2014

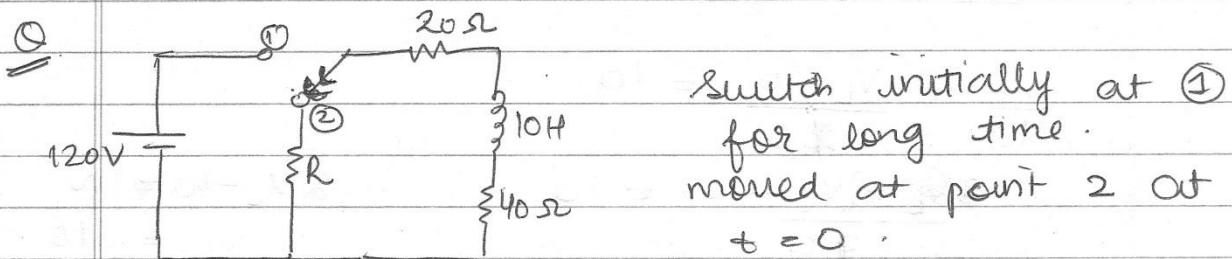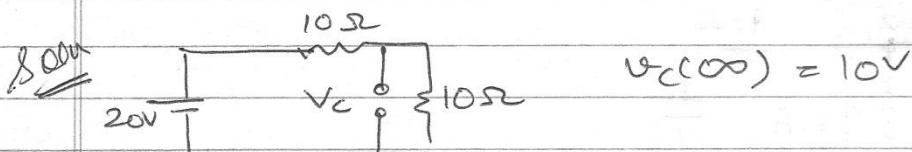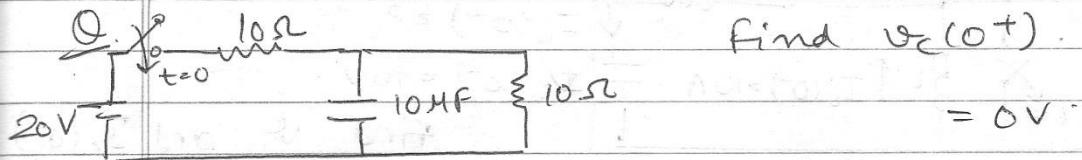
same current now has to flow through the loop.
i.e. impulsive type of action,
current through Inductor is forcibly changed.



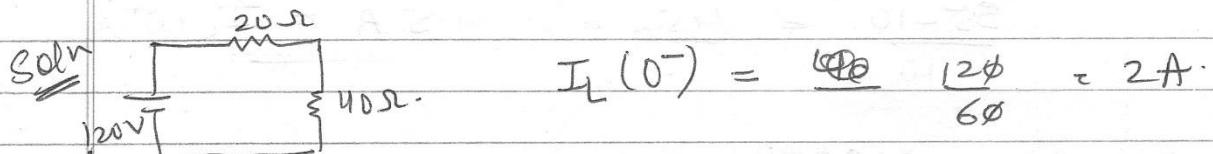At $t = 0^+$, the voltage across the coil i.e. (L with R) is 120 V. The value of resistance R ?





$$\text{i.e } I_L(0^+) = 2A$$

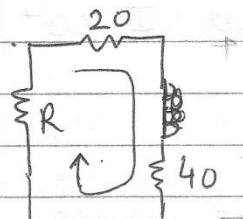

$$20 \times 2 + 120 + R(2) = 0$$

$$\frac{120}{20+R} = 40 \Omega$$

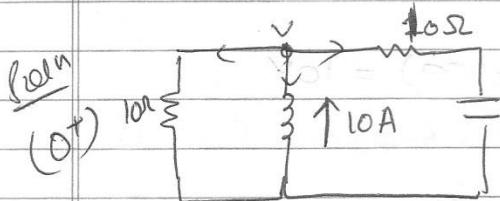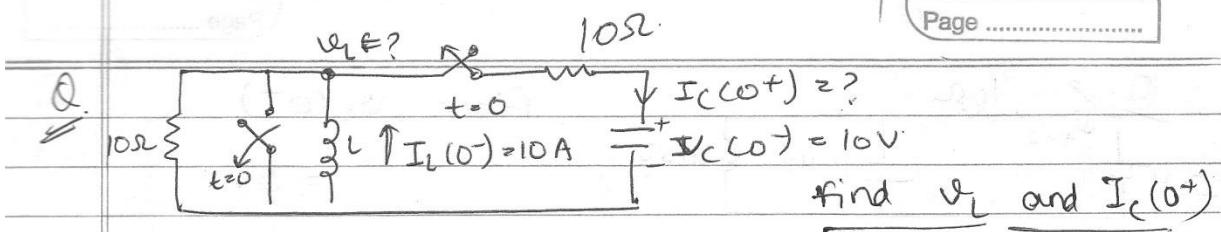

$$\frac{V_L}{10} + \frac{V_L - 10}{10} = 10$$

$$\frac{2V_L - 10}{10} = 10$$

$$2V_L - 10 = 100$$

$$2V_L = 110$$


$$V_L = 55$$

$$2V_L - 10 = 100$$

$$V_L = \frac{110}{2}$$

$$V_L = 55$$

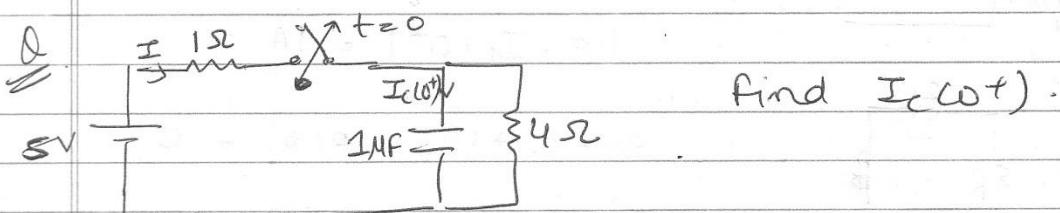
$$\frac{55 - 10}{10} = \frac{45}{10} = 4.5\text{A} = I_C(0^+)$$



solve



$$I(0) = \frac{5}{5} = 1\text{A}$$

$$V_C(0^-) = 4 \times 1 = 4\text{V}$$

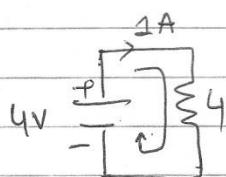

Result

$$I_C(0^+) = -1\text{A}$$

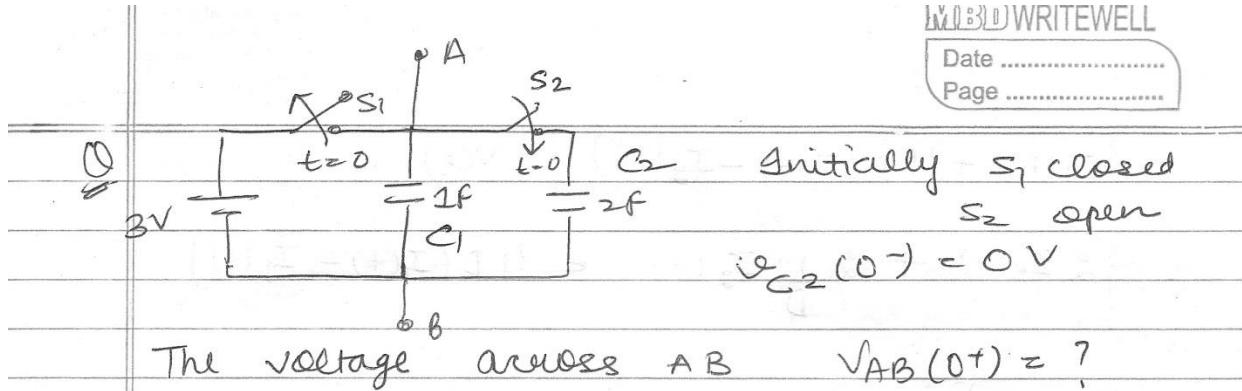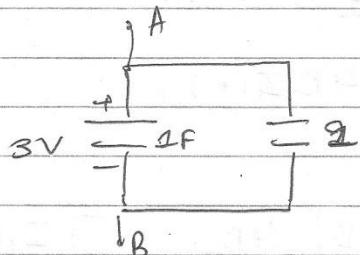~~Solve~~ 0^+ 

Impulsive type of action

In parallel

$$C_{eq} = C_1 + C_2 = 3F$$

$$q = q_1 + q_2$$

$$q = 3 \times 1 = 3C$$

$$\frac{q_1}{1} = \frac{q_2}{2} = \frac{3}{3} = 1$$

$$\begin{matrix} q_1 = 1 \\ q_2 = 2 \end{matrix}$$


$$V_{AB} = \frac{q_1}{C_1} = \frac{1}{1} = 1V$$

TIME DOMAIN ANALYSIS OF Electrical N/W

~~(Q)~~ $I_1(0^-) = 0$

$V_C(0^-) = 0$

$\text{cal. } I_1(t)$

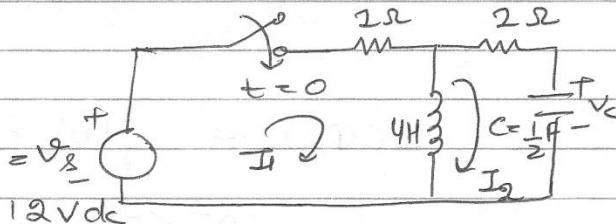

$$I_1(+) + 4 \cdot \frac{d}{dt} (I_1(+) - I_2(+)) = V_S$$

$$2 I_2(+) + 2 \int I_2(t) dt = 4 \frac{d}{dt} (I_1(+) - I_2(+))$$

$$I_1(t) + 4D(I_1(t) - I_2(t)) = V(s)$$

$$2I_2(t) + 2 \frac{1}{D} I_2(t) = 4D(I_1(t) - I_2(t))$$

$$I_1(t)[1+4D] - 4DI_2(t) = V(s)$$

$$\left(2 + \frac{2}{D} + 4D\right) I_2(t) = 4D I_1(t)$$

$$I_1(t)[1+4D] - 4D \left[\frac{4D}{2 + \frac{2}{D} + 4D} \right] I_1(t) = V(s)$$

$$\left[1 + 4D - 4D \left(\frac{4D}{2 + \frac{2}{D} + 4D} \right) \right] I_1(t) = V(s)$$

$$\left[1 + 4D - \frac{16D^2(D)}{2D + 2 + 4D^2} \right] I_1(t) = V(s)$$

$$\frac{2D + 2 + 4D^2 + 8D^2 + 8D + 16D^3 - 16D^5}{2D + 2 + 4D^2}$$

$$\left[\frac{12D^2 + 10D + 2}{4D^2 + 2D + 2} \right] I_1(t) = V(s)$$

$$I_1(t) = \left(\frac{2D^2 + D + 1}{6D^2 + 5D + 2} \right) V(s)$$

$$I_{C(PS)} = f(D) = 0$$

$$6D^2 + 5D + 1 = 0$$

$$(D^2 - 4 \times 6 \times 1) \\ 25 - 24$$

$$= 1$$

$$\frac{-5+1}{2 \times 6} = -\frac{6}{2 \times 6} \\ = -\frac{1}{2}, -\frac{1}{3}$$

$$D = -\frac{1}{2}, -\frac{1}{3}$$

$k_1 e^{-\frac{1}{2}t} + k_2 e^{-\frac{1}{3}t}$ Complex 2) present in PI soln or of steady state response is same as 2) of excitation

$$I_1(\text{PI}) = \left. \frac{g(D)}{f(D)} \right|_{D=\text{complex 2}} \cdot v(s)$$

$$= 1 \cdot 12$$

$$= \underline{\underline{12}}$$

$$\therefore I_1(t) = 12 + k_1 e^{-\frac{1}{2}t} + k_2 e^{-\frac{1}{3}t}$$

At ∞ mag. of this fn = 0
but this signal is present

$$I_1(0^+) = I_2(0^-) = 0$$

$$v_c(0^+) = v_c(0^-) = 0$$

$$I_1(0^+) - I_2(0^+) = I_L(0^+) = 0$$

$$I_1(0^+) = I_2(0^+).$$

$$\boxed{I_L'(0^+) = 2A/s}$$

$$I_1(0^+) = 4A = I_2(0^+).$$

$$v_L(0^+) = 8V$$

$$4 = C \frac{dv_c(0^+)}{dt}$$

$$v_c'(0^+) = 8V/\text{sec}$$

$$I_1'(0^+), I_2'(0^+).$$

$$V(s) = I_1 R_1 + I_2 R_2 + \underbrace{2 \int I_2 dt}_{v_c \text{ or }} \quad \text{or}$$

$$0 = I_1'(R_1) + I_2' R_2 + 2 \int I_2 dt \cdot v_c'$$

$$I_1'(0^+) + I_2'(0^+) 2 + 8 = 0$$

$$I_2 R_2 + V_C = L \frac{d}{dt} (I_1 - I_2)$$

$$2I_2(0^+) + V_C(0^+) = 4 [I_1'(0^+) - I_2'(0^+)]$$

$$2 \times 4 + 0 = 4 [I_1'(0^+) = I_2'(0^+)]$$

$$4I_1'(0^+) - 4I_2'(0^+) = 8$$

$$I_1'(0^+) + 2I_2'(0^+) = 8$$

$$\cancel{8I_1'(0^+)} - \cancel{2I_2'(0^+)} = \cancel{-16}$$

$$9I_1'(0^+) = 8$$

$$I_1'(0^+) = -\frac{4}{3} \quad I_2'(0^+) = -\frac{10}{3}$$

$$I_1(0^+) = 12 + k_1 + k_2$$

$$I_1'(0^+) = 0 + k_1 \left(-\frac{1}{2}\right) e^{-\frac{1}{2}t} + k_2 \left(-\frac{1}{3}\right) e^{-\frac{1}{3}t}$$

$$I_1(0^+) = 0 - \frac{1}{2}k_1 - \frac{1}{3}k_2$$

$I_1(t) = \frac{2D^2 + D + 1}{6D^2 + 5D + 1} V(s)$

Upper eqⁿ roots

$$(1) = 4 \times 2 \times 1$$


$$1 - 8 = -7$$

roots.

$$\frac{-1 \pm \sqrt{7}}{4}$$

\Rightarrow If zeroes = complex \Rightarrow of excitation then response zero at steady state.

Special case of discontinuity for C and L

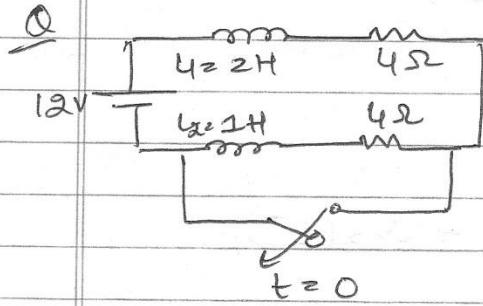

Case I




$$I_{L1}(0^-) = 3A \quad I_{L2}(0^-) = 0$$


Equation of continuity of Flux.

$$L_1 I_{L1}(0^-) + L_2 I_{L2}(0^-) = L_1 I_{L1}(0^+) + L_2 I_{L2}(0^+)$$

tells only magnitude of current.

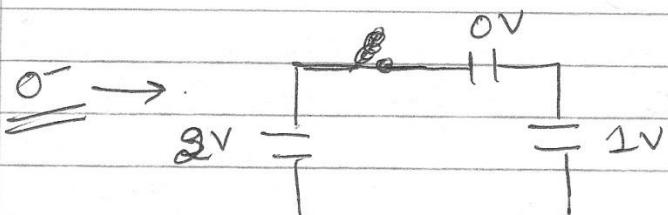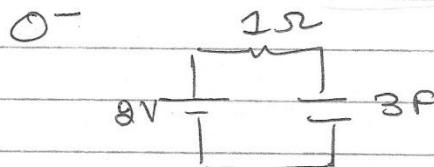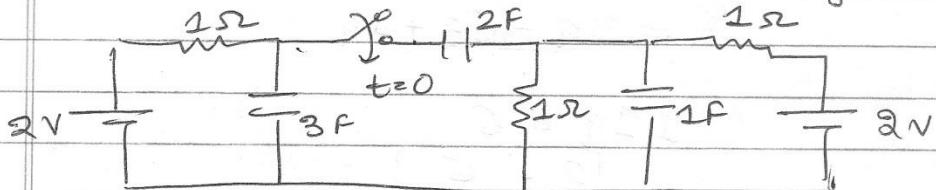Case II - discontinuous voltage of capacitor



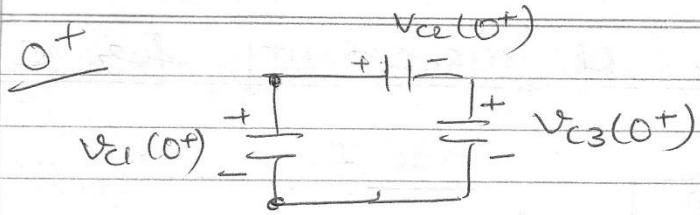

Impulsive type of action.

$$v_{c1}(0^+) = v_{c2}(0^+) + v_{c3}(0^+)$$

Let q amount of charge flow through the loop in the interval of $t = 0^-$ to 0^+ .

series - q same

$$v_{c1}(0^-) - \frac{q}{C_1} = v_{c2}(0^-) + \frac{q}{C_2} + v_{c3}(0^-) + \frac{q}{C_3}$$

$$\frac{2}{3} - \frac{q}{3} = 0 + \frac{q}{2} + 1 + \frac{q}{1}$$

$$2 = \frac{q}{2} + q + \frac{q}{3}$$

$$6 = 3q + 6q + 2q$$


$$11q = 6$$

$$q = \frac{6}{11}$$

$$j = \frac{dq}{dt} u(t)$$

$$i = \frac{6}{11} s(t)$$

Impulse Response

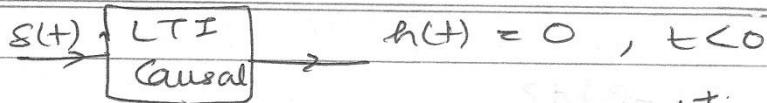


$$x(t) \downarrow \text{causal} \rightarrow \begin{array}{|c|} \hline \text{LTI} \\ \hline \text{causal} \\ \hline \end{array} \rightarrow y(t) = \int_{0^-}^{t^+} x(\tau) h(t-\tau) d\tau$$

Impulse may occur at 0^- to 0^+

If $c > t$ $h(t-\tau) = 0$

If impulse occurs at t , so integration to be taken till t^+ as it has to be included.

\Rightarrow If convolution integral $= \infty$, i.e. system unstable.

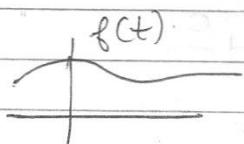Q 1) $f(t) * s(t)$ 

2) $u(t) * u(t)$

3) $s(t) \rightarrow$ LTI
I.C. = 0 $\rightarrow h(t) = (2e^{-2t} - e^{-t})u(t)$

Find response if excitation

a) $x(t) = u(t)$

b) $x(t) = e^{-3t} u(t)$


4) Impulse response of initially relaxed LTI N/W is $4e^{-2t}u(t)$. find response of same N/W to an IP

a) $u(t)$

b) $e^{-t} u(t)$

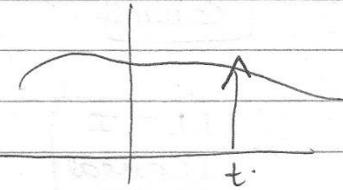1) $f(t) * s(t)$

$$\int_{-\infty}^{\infty} f(\tau) \cdot s(t-\tau) d\tau$$




- 5) for a SISO LTI system having system
fn $H(s) = \frac{2s+1}{s^2+s+1}$. find the complex

freq. in the natural response of system.
find the forced response to an excitation

a) e^{-2t}

b) $e^{-\frac{1}{2}t} \cos(\sqrt{3}t + 70^\circ)$


6)

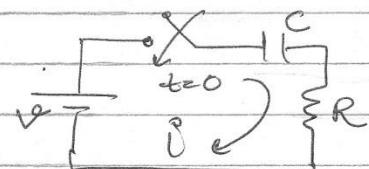

$$v_C(0^-) = 0$$

cal $i(0^+)$, $i'(0^+)$


7)

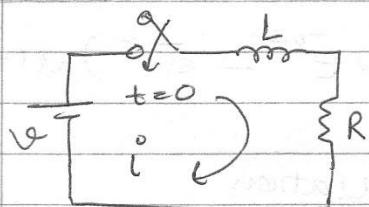

$$i_L(0^-) = 0$$

find $j(0^+)$ and $j'(0^+)$





8)

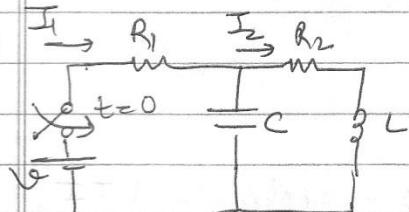

$$v_C(0^-) = 0$$

$$I_L(0^-) = 0$$

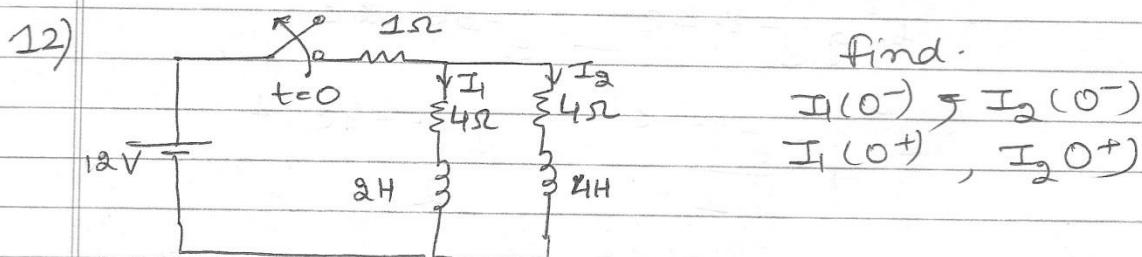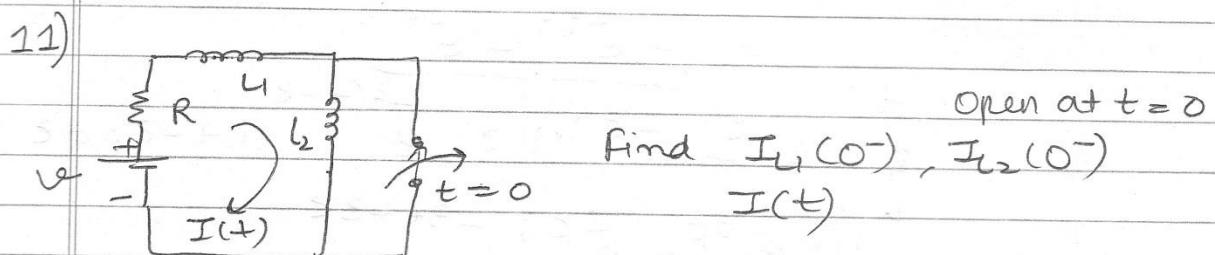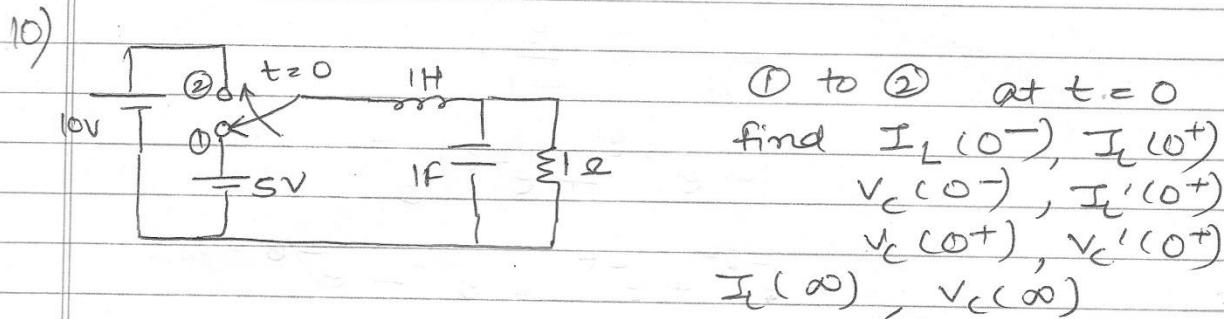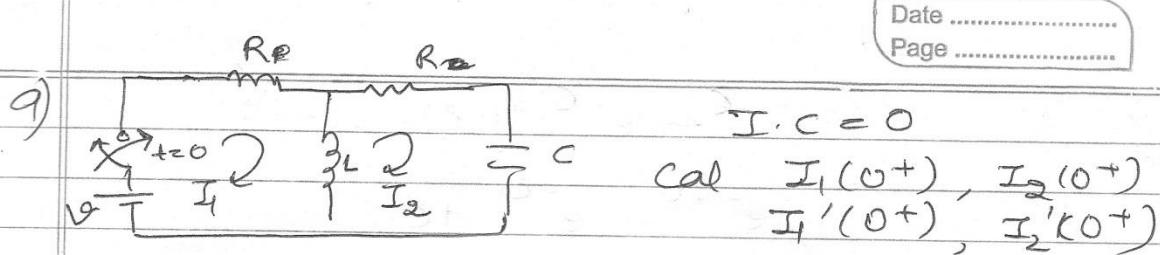find $I_1(0^+)$, $I_2(0^+)$
 $I_1(\infty)$, $I_2(\infty)$.



$\hat{u}(t) \otimes u(t)$

$$\int_0^t u(z) u(t-z) dz$$

$$= t = \underline{\underline{u(t)}}$$

3. a)
$$\int_0^t (2e^{-2z} - e^{-z}) u(z) u(t-z) dz$$

$$= \int_0^t (2e^{-2z} - e^{-z}) dz$$

$$= \left[\frac{2e^{-2z}}{-2} + \frac{e^{-z}}{-1} \right]_0^t$$

$$= (-e^{-2t} + e^{-z}) \Big|_0^t$$

$$= -e^{-2t} + e^{-t} + e^0 - e^0$$

$$= \boxed{-e^{-2t} + e^{-t}}$$

b)
$$\int_0^t (2e^{-2z} - e^{-z}) u(z) e^{-3(t-z)} u(t-z) dz$$

$$= \int_0^t (2e^{-2z} - e^{-z}) e^{-3t+3z} dz$$

$$= \int_0^t 2e^{-3t+2z} - e^{-3t+2z} dz$$

$$= \left[\frac{2e^{-3t+2z}}{2} - \frac{e^{-3t+2z}}{2} \right]_0^t$$

$$= \left[2e^{-3t+t} - \frac{e^{-3t+2t}}{2} - 2e^{-3t} + \frac{e^{-3t}}{2} \right]$$

$$= 2e^{-2t} - \frac{e^{-t}}{2} - 2e^{-3t} + \frac{e^{-3t}}{2}$$

$$= \boxed{2e^{-2t} - \frac{e^{-t}}{2} - \frac{3}{2} e^{-3t}}$$

a) $\int_0^t 4e^{-2z} u(z) u(t-z) dz$

$$\int_0^t 4e^{-2z}$$

$$\left[\frac{4e^{-2z}}{-2} \right]_0^t = -2e^{-2t} + 2e^0 \\ = \boxed{-2e^{-2t} + 2}$$

b) $\int_0^t 4e^{-2z} u(z) e^{-(t-z)} u(t-z) dz$

$$\int_0^t 4e^{-2z} e^{-(t-z)} dz \\ = 4 e^{-2z-t+z} dz \\ = \int_0^t 4 e^{-(t+z)} dz \\ = \frac{4e^{-t-z}}{-1} \\ = -4e^{-t-t} + 4e^{-t-0} \\ = \boxed{-4e^{-2t} + 4e^{-t}}$$

5 $H(s) = \frac{2s+1}{s^2+s+1}$

$$s^2 + s + 1 = 0$$

$$(1)^2 - 4 \times 1 \times 1$$

$$1 - 4 = -3$$

$$= \frac{-1 \pm \sqrt{3}}{2}$$

forced response for

$$\begin{aligned}
 a) \quad & e^{-at} \\
 & = \frac{2(-2)+1}{(-2)^2+(-2)+1} \underbrace{e^{-2t}}_{\frac{-4+1}{4-2+1}} = \frac{-4+1}{4-2+1} \\
 & = \frac{-3}{3} e^{-2t} \\
 & = -\underline{\underline{e^{-2t}}}
 \end{aligned}$$

$$\begin{aligned}
 \text{complex freq} &= -\frac{1}{2} + \sqrt{3}j \\
 &= 2 \left(-\frac{1}{2} + \sqrt{3}j \right) + 1 \quad \text{I/P}
 \end{aligned}$$

$$\begin{aligned}
 \text{natural } v \text{ i.e. } & \overline{(-\frac{1}{2} + \sqrt{3}j)^2 + (-\frac{1}{2} + \sqrt{3}j) + 1} \\
 \text{pole} &= \text{complex } v
 \end{aligned}$$

$$\begin{aligned}
 \frac{2s+4}{(s-P_1)(s-P_2)} &= \frac{-\frac{1}{2} + \sqrt{3}j + 1}{\frac{1}{4} - 3 - \sqrt{3}j - \frac{1}{2} + \sqrt{3}j + 1} = \frac{\frac{\sqrt{3}j}{2}}{\frac{1}{4} - 2} \\
 (s-P_1) &= 0 \quad X = \frac{\sqrt{3}j}{\frac{1}{2}} = -\frac{2\sqrt{3}j}{7} \quad \text{I/P}
 \end{aligned}$$

∵ $\therefore \infty$. I/P
 α_R = undefined fn
 But steady state response will be defined.

$$\begin{aligned}
 \frac{6}{s} & \xrightarrow[s=0]{X} 1 \quad v(0^+) = 0 \\
 \times \frac{1}{s} & \boxed{i \geq R} \quad \text{find } i(0^+), j(0^+)
 \end{aligned}$$

$$v \boxed{\frac{1}{s} \geq R}$$

$$j(0^+) = \frac{v}{R}$$


$$v = \frac{1}{C} \int i dt + i \times R$$

$$0 = \frac{1}{C} i + R i'$$

$$= \frac{1}{C} i(0^+) + R i'(0^+)$$

$$= i'(0^+) = -\frac{1}{CR} i(0^+)$$
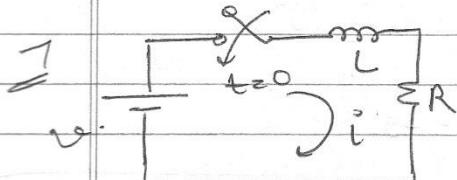
$$= -\frac{1}{CR} \frac{v}{R} = \boxed{-\frac{v}{CR^2}}$$



$$I_L(0^+) = 0$$

find $i(0^+)$ & $i'(0^+)$.


$$\boxed{i(0^+) = 0}$$

$$v = L \frac{di}{dt} + iR$$

$$v = L i'(0^+) + i(0^+) R$$

$$v = L i'(0^+) + 0$$


$$\boxed{i'(0^+) = \frac{v}{L}}$$

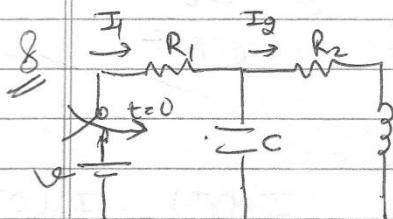

$$v_C(0^+) = 0$$

$$I_L(0^+) = 0$$

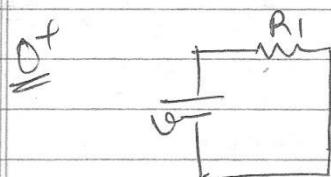
find $I_1(0^+)$, $I_1(\infty)$, $I_2(0^+)$, $I_2(\infty)$



$$\text{i.e. } I_2(0^+) = 0$$

$$I_1(0^+) = \frac{v}{R_1}$$

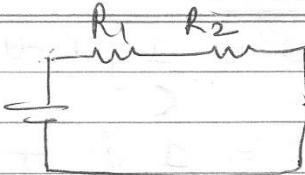~~at ∞~~ $I_1(\infty) = I_2(\infty)$
~~at ∞~~ $= \frac{V}{R_1 + R_2}$



Also find $i_1'(0^+)$, $i_2'(0^+)$, $v_c'(0^+)$, $v_c(0^+)$

$\Rightarrow v_c(0^+) = 0$

$$V = I_1 R_1 + I_2 R_2 + L \frac{dI_2}{dt}$$

$$V = I_1(0^+) R_1 + I_2(0^+) R_2 + L I_2'(0^+)$$

$$V = \cancel{V} \times R_1 + 0 + L I_2'(0^+)$$

$$0 = L I_2'(0^+)$$


$$\boxed{I_2'(0^+) = 0}$$

$$V = I_1 R_1 + \frac{1}{C} \int (I_1 - I_2) dt$$

$$0 = I_1'(0^+) R_1 + \frac{1}{C} [I_1(0^+) - I_2(0^+)]$$


$$0 = I_1'(0^+) R_1 + \frac{1}{C} \left(\frac{V}{R_1} - 0 \right)$$
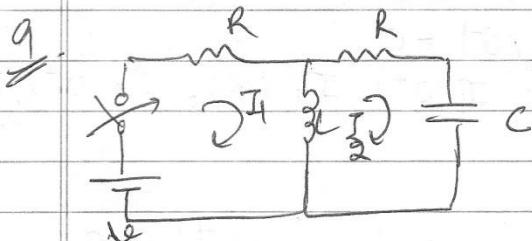
$$I_1'(0^+) = -\frac{1}{C} \frac{V}{R_1 \times R_1} = \frac{-V}{CR_1^2}$$



$$I \cdot C = 0$$

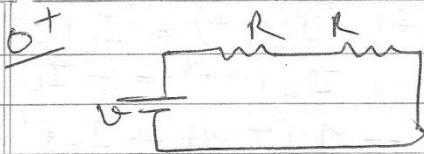find $I_1(0^+)$, $I_2(0^+)$
 $I_1'(0^+)$, $I_2'(0^+)$



$$I_1(0^+) = I_2(0^+) = \frac{V}{2R}$$

$$v = I_1 R + L \frac{d}{dt} (I_1 - I_2)$$

$$v = I_1(0^+) R + L (I_1'(0^+) - I_2'(0^+))$$

$$v = \frac{V}{2R} R + L (I_1'(0^+) - I_2'(0^+))$$

$$\frac{V}{2L} = I_1'(0^+) - I_2'(0^+). \quad \text{--- (1)}$$

$$v = I_1 R + I_2 R + \frac{1}{C} \int I_2 dt$$

$$v = I_1'(0^+) R + I_2'(0^+) R + \frac{1}{C} I_2(0^+)$$

$$v = R [I_1'(0^+) + I_2'(0^+)] + \frac{1}{C} \frac{v}{2R}$$


$$\frac{V}{R} \left[1 - \frac{1}{2CR} \right] = I_1'(0^+) + I_2'(0^+) \quad \text{--- (2)}$$

$$2I_1'(0^+) = \frac{V}{2L} + \frac{V}{R} \left[1 - \frac{1}{2CR} \right]$$

$$I_1'(0^+) = \frac{V}{4L} + \frac{V}{2R} \left[1 - \frac{1}{2CR} \right]$$

Similarly $\underline{I_2'(0^+)}$

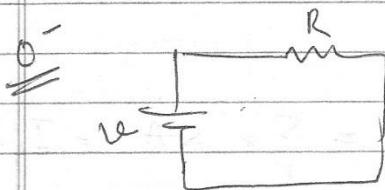\Rightarrow Another ones if switch is open.




$$I_2(0^-) = 0$$

$$I_1(0^-) = \frac{V}{R}$$

$$I_1(0^-) = \frac{V}{R} = I_1(0^+)$$

$$V_C(0^-) = 0 = V_C(0^+)$$

Also

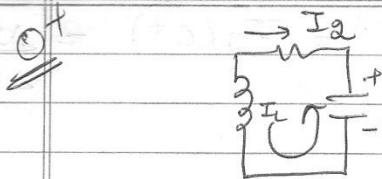

$$I_1(0^+) - I_2(0^+) = I_L(0^+)$$

$$I_2(0^+) = -I_L(0^+) = -V$$

$$L \frac{dI_L}{dt} - \frac{1}{C} \int I_2 dt - I_2 R = 0 \quad R$$

~~Kazee~~

$$I_L = I_1 - I_2$$

$$L [I'_1 - I'_2] - \underbrace{\frac{1}{C} \int I_2 dt - I_2 R}_{R} = 0$$



$$\text{At } 0^+ \quad V_C(0^+) = 0$$

$$L (I'_1(0^+) - I'_2(0^+) - I_2^{(0^+)}) = 0$$

$$L (I'_1(0^+) - I'_2(0^+)) + \underbrace{V_{CR}}_R = 0$$


$$I'_1(0^+) - I'_2(0^+) = -\frac{V}{L}$$
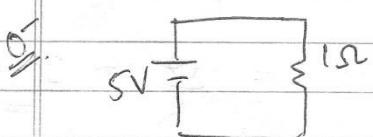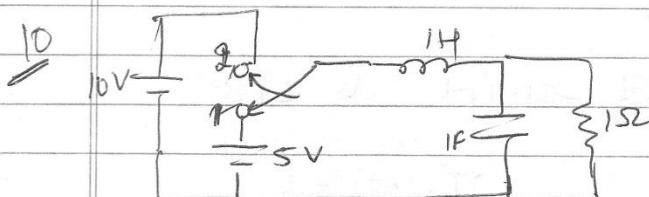
$$V_L(0^+) = L \frac{dI_L}{dt} = L I'_L(0^+)$$



$$I_L(0^-) = \frac{5}{1} = 5A = I_L(0^+)$$

$$V_C(0^-) = 5V = V_C(0^+)$$

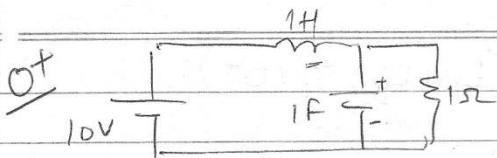

$$10 = L \frac{dI_L}{dt} + V$$

$$\frac{10 - V}{L} = I_L'(0^+) = \frac{V}{1} = 5A$$

Voltage across $1\Omega = 5$


$$\text{Current} = \frac{5}{1} = 5A$$

$$\frac{dV_{DC}}{dt} = i_C(0^+)$$


$V_C(0^+) = 0$ because current through cap = 0 at 0^+ .

$$i_L(\infty) = 10A$$

$$V_C(\infty) = 10V$$

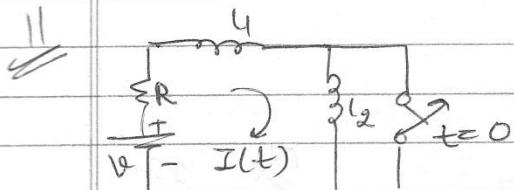


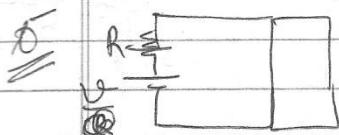find $I_{L1}(0^-)$, $I_{L2}(0^-)$
 $I(0^+)$



$$I_{L1}(0^-) = \frac{V}{R}$$

$$I_{L2}(0^-) = \frac{V}{2R}$$

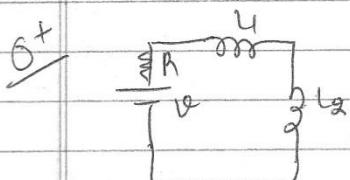

$$L_1 I_{L1}(0^-) + L_2 I_{L2}(0^-) = L_1 I_L(0^+) + L_2 I_L(0^+)$$

because current same

$$L_1 \frac{V}{R} + L_2 \frac{V}{2R} = (L_1 + L_2) I_L(0^+)$$

$$\frac{V}{R} \left(L_1 + \frac{L_2}{2} \right) = (L_1 + L_2) I_L(0^+)$$

$$I_L(0^+) = \frac{V}{R(L_1 + L_2)} \left(L_1 + \frac{L_2}{2} \right)$$

$$V = L_1 \frac{dI_L}{dt} + L_2 \frac{dI_L}{dt} + R I_L$$

$$V = (L_1 D + L_2 D) I_L + R I_L$$

$$\frac{V}{D(L_1 + L_2) + R} = I_L$$

$$D = -\frac{R}{(L_1 + L_2)}$$



$$I_L(t) = e^{-\frac{Rt}{L_1 + L_2}} + \left(\frac{V}{R} \right) \text{ forced response}$$

↓
natural
response

12.

$$I_1(0^-), I_2(0^-)$$

$$I_1(0^+), I_2(0^+)$$

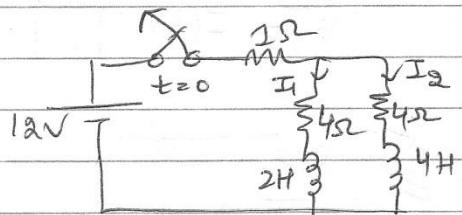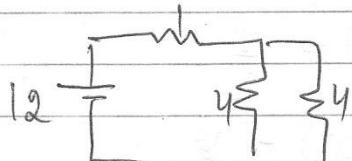

$$\frac{12}{3} = 4 - A$$

$$I_1(0^-) = 2A = I_2(0^-)$$

flux eqⁿ only gives magnitude

$$2x(2) + 4(2) = (2+4)x$$

$$\frac{4+8}{6} = x$$

$$\frac{12}{6} = x$$



$$\underline{x = 2A}$$

$$I_1(0^+) = 2A$$

$$I_2(0^+) = \underline{-2A}$$

~~x - y - x -~~

* Freq. of Impulse Response = CFS freq.
Remaining = PI freq.
i.e excitation freq.

(CF)

Suppose Impulse response $h(t) = (2t^{-2t} - e^{-t})u(t)$

excitation


$$a) x(t) = u(t)$$

$$b) e^{-3t} u(t) \stackrel{PI}{=} \underline{\underline{}}$$

$$i) PI = 0, CFS = -1, -2$$

$$PI = 3, CFS = -2, -1$$


23/2/2014

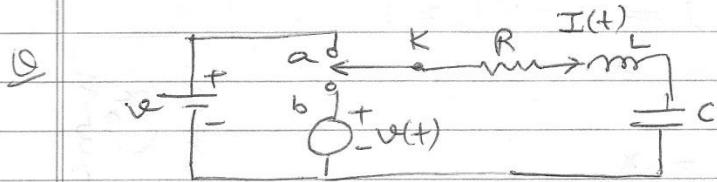

K is held at position a till the time at which current I_0 flows through inductor and cap. charged to voltage V_0 . At that instant switch is thrown to position b. find $I(s)$

$$V_C(0^-) = V_0$$


$$I_L(0^-) = I_0$$

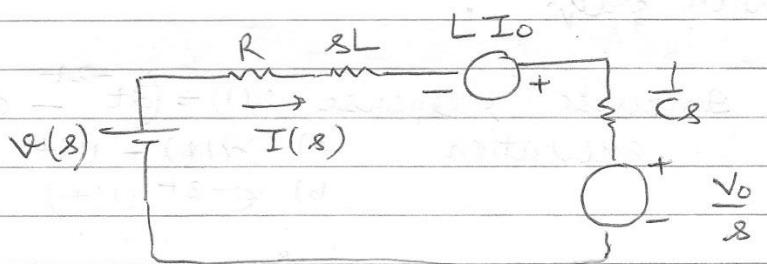


$$V(s) + L I_0 - \frac{V_0}{s} = (R + sL + \frac{1}{Cs}) I(s)$$

$$V(s) + L I_0 - \frac{V_0}{s}$$

$$\frac{R + sL + \frac{1}{Cs}}{s}$$

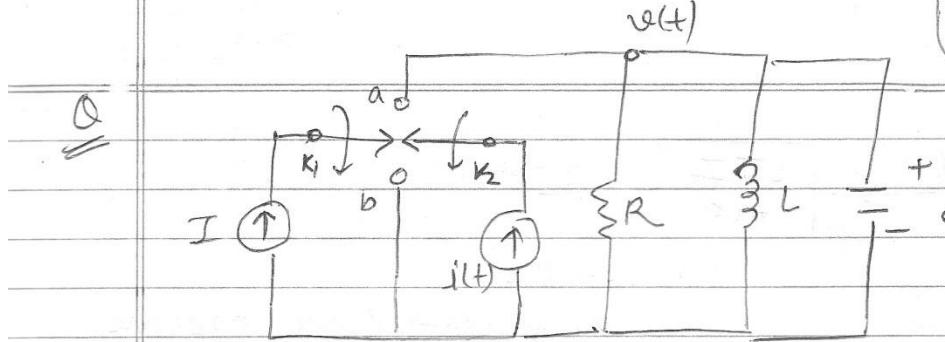

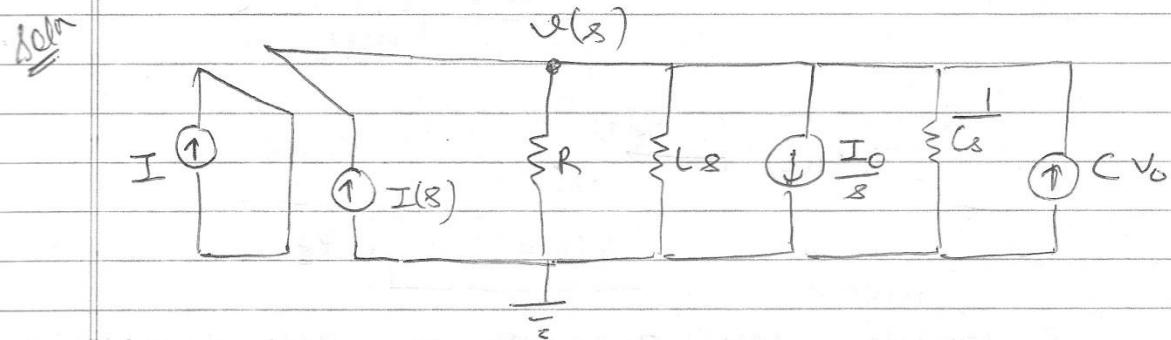Initially switch K_1 held at pos. a. ~~at t=0~~
and K_2 at b. At an instant when
inductor current is I_0 and capacitor
is charged to V_0 , pos. of K_1 and K_2
interchanged. Find node voltage $v(s)$.




$$(Cv_0 + I(s)) = \frac{V(s)}{R} + \frac{V(s)}{Ls} + \frac{I_0}{s} + \frac{V(s)}{Cs}$$

$$Cv_0 + I(s) - \frac{I_0}{s} = V(s) \left[\frac{1}{R} + \frac{1}{Ls} + \frac{1}{Cs} \right]$$

$$V(s) = \frac{Cv_0 + I(s) - I_0/s}{\left(\frac{1}{R} + \frac{1}{Ls} + \frac{1}{Cs} \right)}$$


or Voltage = Current = same
Admittance

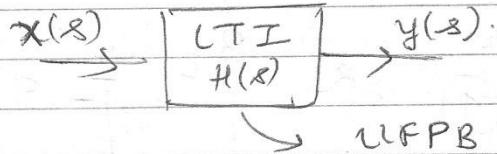



UFPB

Linear Lumped finite passive bilateral


Then $H(s) = \frac{g(s)}{f(s)}$
 $I.C = 0$

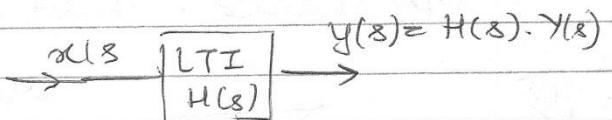Properties of system function

1)

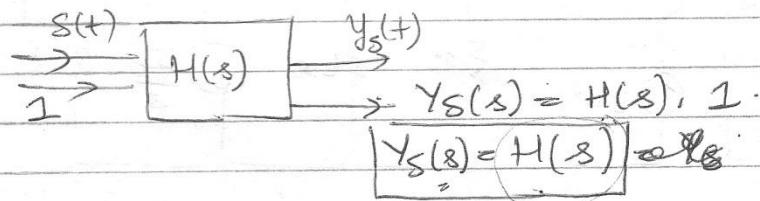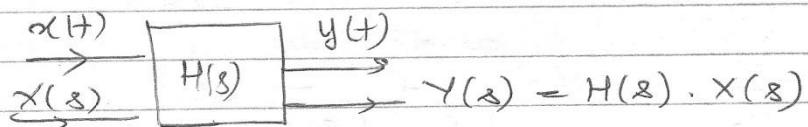2) Response corresponding to any excitation $x(t)$ in terms of impulse response.

3) Step response

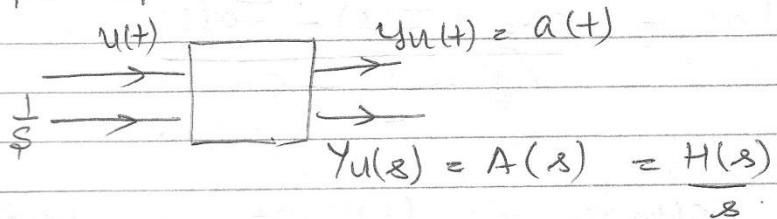

$$\boxed{H(s) = sA(s)}$$

Impulse response

- 4) \Rightarrow Response corresponding to any excitation $x(t)$ in terms of step response.

$$\begin{array}{c}
 \xrightarrow{x(t)} \boxed{H(s)} \xrightarrow{Y(t)} \\
 \xrightarrow{x(s)} \quad Y(s) = H(s) \cdot X(s) \\
 = s A(s) \cdot X(s) \\
 \text{or} \quad = [s X(s)] \cdot A(s)
 \end{array}$$

Multiplication in freq. domain = convolution in time

$$\begin{aligned}
 y(t) &= x'(t) \Big|_{t>0^-} * a(t) \\
 &= \left[f(x(0^+) - x(0^-)) s(t) + x'(t) \right] \Big|_{t>0^-} * a(t)
 \end{aligned}$$

i.e convolution integral we have to calculate from 0^- to ∞ .

whenever there is step response, there are chances that impulse will occur at zero.

- 5) Concept of poles & zeros of system fn.

$$H(s) = \frac{g(s)}{f(s)} \quad \begin{matrix} g(s) \rightarrow m \\ f(s) \rightarrow n \end{matrix} \quad \text{degree}$$

$$\begin{aligned}
 g(s) &= 0 \quad \text{known as zeros} \\
 f(s) &= 0 \quad \text{poles}
 \end{aligned}$$

No. of finite zeros not ^{only} $= m$
 " " " " poles $= n$

* strictly No. of poles = No. of zeros
 always

① If $m > n$	② $m = n$	③ $m < n$
a) non Improper system function		proper rational fn.
b) $m - n = \text{No. of poles}$ will be available at infinity.	No. of poles at $\infty = \text{No. of zeroes}$ at $\infty = 0$.	$(n - m) = \text{No. of zeros}$ at infinity.
c) physically unrealizable		Physically realizable

$$H(s) = \frac{(s+1)}{(s+2)(s+3)}$$

zeros mean $H(s) = 0$

Now if $\lim_{s \rightarrow a} H(s) = 0$ then it means

$s = a$ is a zero

NOW

$\lim_{s \rightarrow \infty} H(s) = 0$: one location of zero may be ∞ .

Poles represent $H(s) = \infty$

$$\text{If } H(s) = \frac{(s+1)(s+2)}{(s+3)}$$

then $\lim_{s \rightarrow \infty} H(s) = \infty$ Thus one location of pole may be ∞ .

$$\textcircled{1} \quad \frac{4s^3 + 3s^2 + s + 1}{2s + 1}$$

Partial frac $K_1 s^2 + K_2 s + (\text{proper rational fn})$

$$K_1 \xrightarrow{\text{L.I}} s(t)$$

$$K_2 s \rightarrow s'(t)$$

$$K_1 s^2 \rightarrow s''(t)$$

$s(t)$ ka derivative at ∞ . \therefore definitely system will burn out. i.e. mag. ∞

$$(2) \frac{as+b}{cs+a}$$

Partial frac. $K_1 + K_2$ (Proper sat. fn)
 \checkmark
 One impulse present.

X * If location of poles = complex λ of excitation

$$\text{eg.: } H(s) = \frac{(s+1)(s+2)}{(s+3)}$$

$$x(t) = 2e^{-\alpha t} \rightarrow \text{means } 2e^{-\frac{t}{\tau}}$$

$$X(s) = \frac{2}{(s+\infty)}$$

in zero time
it decays to $\frac{A}{e}$
i.e. impulse

$$Y(s) = \frac{(s+1)(s+2)}{(s+3)(s+\infty)}$$

$$Y^{-1}(s) = \frac{A}{(s+3)} + \frac{B}{(s+\infty)}$$

=

There will be impulse present in impulse response.

$$Y(s) = H(s) \cdot X(s)$$

Partial fraction expansions of $H(s)$ will contain 2 parts

terms containing
location of poles
same as poles of
system function.

terms containing
poles same as complex
2) present in excitation.

Inverse laplace of this

as represents natural 2

If $H(s)$ has same pole location as
 $X(s)$ i.e. $s_0(t)$

then both side k will come.

$$(s - s_0)$$

In Inverse laplace there will be $k e^{-s_0 t}$

$$\begin{matrix} \nearrow \\ k_1 \end{matrix} \quad \begin{matrix} \searrow \\ k_2 \end{matrix}$$

Thus $k = k_1 + k_2$

$$k_1 e^{-s_0 t} \text{ for } H(s)$$

$$k_2 e^{-s_0 t} \text{ for } X(s)$$

* forced Response characteristics or
steady state Response

$$x(t) \Big|_{S.S.R/F.R} = H(s) \Big|_{s \rightarrow s_0} \cdot x(t)$$

$$= H(s_0) A e^{-s_0 t}$$

(3) * Freq. Response characteristics i.e. excitation purely sinusoidal.


$$x(t) = e^{\pm j\omega t}$$

$$\underset{\text{SSR}}{|y(t)|} = H(+j\omega) \cos(\omega t).$$

* Free Response or stability

$$\zeta = \frac{1}{\alpha}$$

time where amplitude reduces to $1/e$.

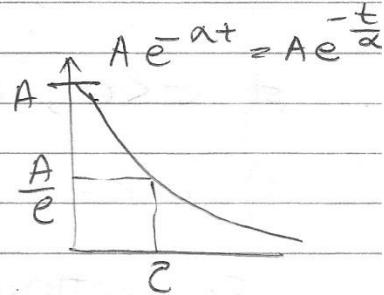

It's large ζ , ultra fast decay

→ Equilibrium point of the system is defined as the point where the system dynamic becomes zero. i.e. $\frac{dx}{dt}, \frac{d^2x}{dt^2}, \dots = 0$.

Instead all dynamics i.e. v_c'', i_c'', v_c''' and higher derivatives be zero.

If after disturbance, system going away from operating pt then unstable.

marginal stability i.e. deviated from operating point but is maintained there

Asymptotic stability - If system going back to $\cong m$ point

Exponential stability - If system going back to $\cong m$ point at a very fast rate

$$s_n = \sigma \pm j\omega \quad (\text{natural freq})$$

- 1) $\sigma < 0, \omega = 0$ Asymptotically stable
- 2) $\sigma > 0, \omega = 0$ Unstable
- 3) $\sigma = 0, \omega = 0$ dc (marginal stability)
- 4) $\sigma = 0, \omega = \pm j\omega$ Marginally stable
- 5) $\sigma < 0, \omega = \pm j\omega$ Asymptotically stable
- 6) $\sigma > 0, \omega = \pm j\omega$ Unstable

Exponentially stable depends on value of σ .
All Asymptotically " system are exponentially stable but vice versa not true.

\Rightarrow Initial value theorem

$$f(t) \xrightarrow{\text{LT}} F(s)$$

$$\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} sF(s).$$

$F(s)$ = system should be proper rational fn for this theorem to be implemented.

\Rightarrow Final value theorem


$$f(t) \xrightarrow{\text{LT}} F(s)$$

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$$

Theorem applicable only when $f(t)$ is non growing signal i.e if $f(t)$ is bounded.

i.e if poles on R.H.S, then this not applicable

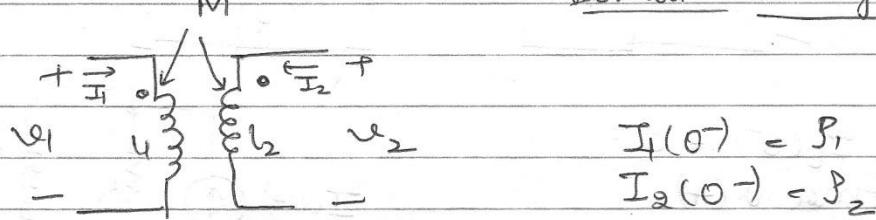
* Mutually Coupled INDUCTORS (Transform Domain Analysis)



$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_1(s) = L_1 [s I_1(s) - P_1] + M [s I_2(s) - P_2]$$

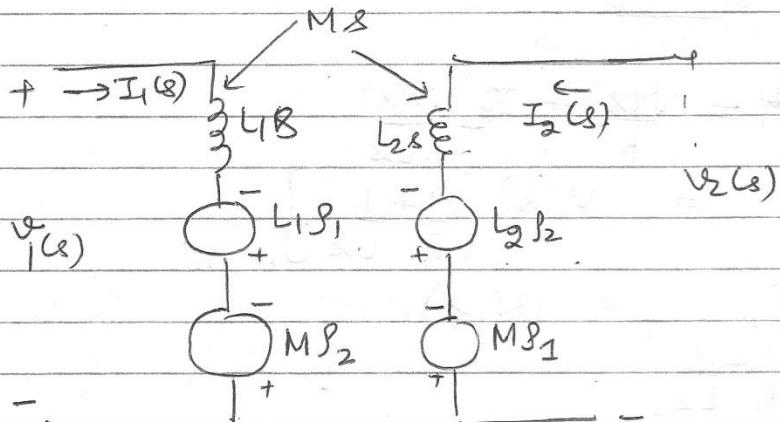
$$v_2(s) = L_2 [s I_2(s) - P_2] + M [s I_1(s) - P_1]$$



In terms of current source

$$v_1(s) = L_1 s \left[I_1(s) - \frac{\beta_1}{s} \right] + M s \left[I_2(s) - \frac{\beta_2}{s} \right]$$

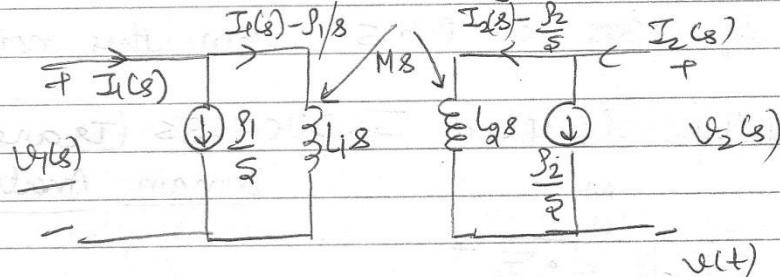
$$v_2(s) = L_2 s \left[I_2(s) - \frac{\beta_2}{s} \right] + M s \left[I_1(s) - \frac{\beta_1}{s} \right]$$




Q $I_L(0^-) = 0$

Find $v(+)$

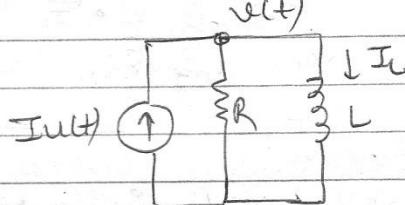Define defn nature
of $v(t)$ as $g \rightarrow 0$
i.e. conductance



Defn

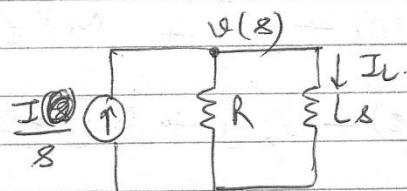

$$\frac{I(0)}{s} = \frac{v(s)}{R} + \frac{v(s)}{Ls}$$

$$\frac{I}{s} = v(s) \left[\frac{1}{R} + \frac{1}{Ls} \right]$$


$$\frac{I}{s \left[\frac{1}{R} + \frac{1}{Ls} \right]} = v(s).$$

$$\frac{\frac{I}{s} RLs}{s(Ls + R)} = \frac{I s R}{s \left[\frac{1}{R} + \frac{1}{Ls} \right]} = \frac{RK}{s^2 + \frac{R}{L}s}$$

$$v(t) = R I R e^{-\frac{R}{L} t}$$

$$C = \frac{L}{R}$$
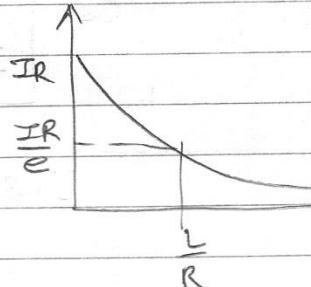
$$R \uparrow \frac{L}{R} \downarrow j.e C \uparrow$$



$$G \rightarrow 0$$

means $R \rightarrow \infty$

Magn. goes to ∞ . decays in zero time. i.e impulsive type of action.

$$H(s) = \frac{R}{s + \frac{R}{L}} \quad \text{as } R \rightarrow \infty \quad (s + \infty)$$

$$e^{-\infty t}$$

$$j.e v(t) \approx k s(t)$$

find value of K

$$\int_0^\infty I R e^{-\frac{R}{L} t} dt = K$$

$$\left[\frac{IR e^{-\frac{R}{L} t}}{-\frac{R}{L}} \right]_0^\infty$$


$$IL \left[-e^{\frac{R}{L} \infty} + e^{\frac{R}{L} 0} \right] = K$$


$$K = I \cdot L$$

Q $t = 0$ position of switch changed find $i(t)$.

soln. $I(0^-) = \frac{V}{R}$

$$v(0^-) = 0$$

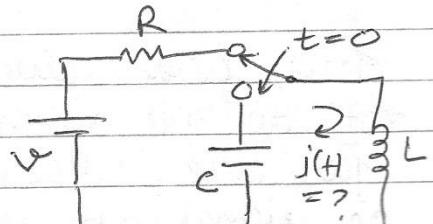

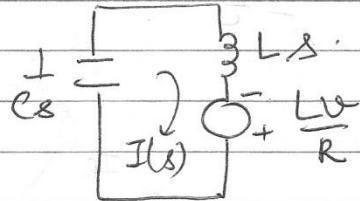

$$I(s) = \frac{V}{R} = \frac{V}{\frac{1}{s+C\omega}} = \frac{V s}{1 + sC\omega}$$

$$\frac{s}{s^2 + \omega^2} = L [\cos \omega t] = \frac{V L \cos \omega t}{R (1 + sC\omega^2)}$$

$$= \frac{V \omega}{R \left(\omega^2 + \frac{1}{LC} \right)}$$

From here

$$i(t) = \frac{V}{R} \left(\cos \sqrt{\frac{1}{LC}} t \right) \rightarrow i(0) = \text{not defined.}$$

\Leftrightarrow From cut

$$\text{No. of poles} = \text{No. of zeroes} = \text{Degree} = 2$$

From final value theorem


$$j(\infty) = \lim_{s \rightarrow 0} s F(s) = \frac{V \omega^2}{R \left(\omega^2 + \frac{1}{LC} \right)}$$

True, final value theorem
not to use when poles on
jw axis. However, for
dc signal it is to be used.

$$< \frac{V}{R(1+\infty)} = \frac{1}{\infty} = 0$$


$$\frac{10 - 3I}{6} = I - 2 \quad \Rightarrow \quad I = \frac{22}{9} \quad \boxed{I_{6\Omega} = \frac{4}{9}}$$

Q find $I(s)$

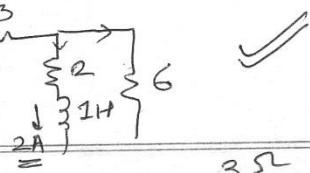

MBD WRITEWELL
Date
Page


$$I(0^+) = \frac{10}{5} = 2A$$

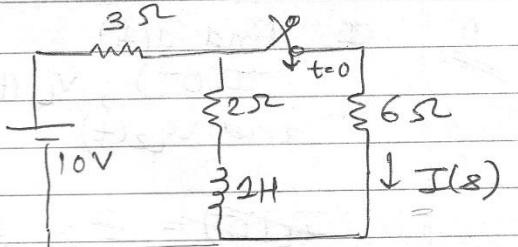

~~$\frac{10 + 2s}{s} =$~~

$$\frac{10}{s} - \frac{10}{s+2} = \frac{V(s)}{6}$$

3

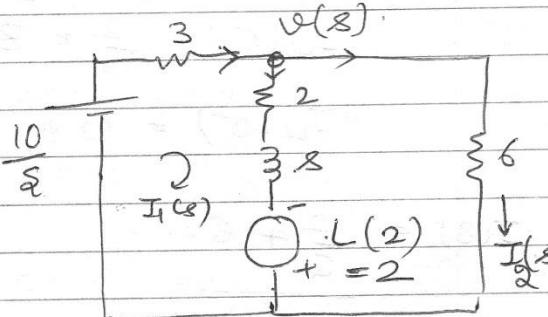

$$\frac{10}{s} = 3I_1(s) + (2+s)(I_1(s) - I_2(s)) - 2.$$

$$6I_2(s) + 2 = (2+s)(I_1(s) - I_2(s))$$

$$\frac{10}{s} + 2 = (3+2+s)I_1(s) + (2+s)I_2(s)$$

$$2 = (2+s)I_1(s) - (2+s+6)I_2(s)$$

Ans correct

$$I_2(s) = \frac{4s + 20}{9s(s+4)}$$

Ans not correct

find $I_2(0^+)$, $I_2(\infty)$

$$\lim_{s \rightarrow \infty} \frac{4s + 20}{9(s+4)} = \frac{s(4 + \frac{20}{s})}{9s(1 + \frac{4}{s})}$$


$$I(0^+) = \frac{5}{9}$$

Cross check Ans by finding $I(0^+)$ and $I(\infty)$ = $\frac{4}{9}$

From final value theorem $I_2(\infty) = \frac{5}{9}$

Q. find $i(t)$

$I(0^+)$, $v_{L1}(t)$
and $v_{L2}(t)$

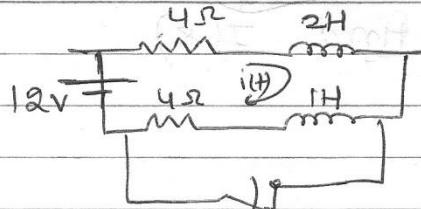


$$I_L(0) = \frac{12}{8} = \frac{3}{2}$$

$$I_U(0) = \frac{12}{4} = 3 \text{ A}$$

$$I_{L2}(0^-) = 0 \text{ A}$$

$$I(s) = \frac{12 + 6}{\frac{8}{s}}$$

$$4 + 3s + 4$$

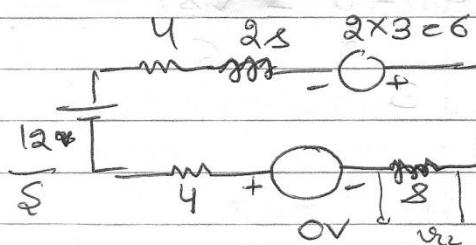

Voltage across Inductor

$$v_{L1}(s) = 2s I(s) - 6$$

$$v_{L2}(s) = s I(s)$$

$$I(s) = \frac{3/2}{s} + \frac{1/2}{s + 8/3}$$

$$i(t) = \frac{3}{2} + \frac{1}{2} e^{-\frac{8t}{3}}$$

$$\boxed{I(0^+) = 2}$$

$$v_{L1}(s) = 2s \left(\frac{12 + 6}{s} \right) = \frac{2s(12 + 6s)}{s(4 + 3s + 4)} = \frac{2(12 + 6s)}{4 + 3s + 4} - 6$$

$$v_{L1}(s) = 2s \left[\frac{k_1}{s} + \frac{k_2}{s + 8/3} \right]$$

$$\check{v}_{L1}(s) = -\frac{2(s+4)}{(s + \frac{8}{3})}$$

MBD WRITEWELL

Date
Page

$2k_1$ = Constant Inverse Impulse.

$$\check{v}_{L1}(s) = -2 - \frac{8}{\frac{3}{s+8}}$$

$$v_{L1}(t) = -2s(t) - \frac{8}{3} e^{-\frac{8}{3}t}$$

$$t \rightarrow 0^+ \quad s(t) \rightarrow 0$$



$$\begin{aligned} \text{Initial value} \quad v_{L1}(s) &= -2s - \frac{8}{\frac{3}{s+8}} = -2s - \frac{8}{3} \frac{1+\frac{8}{3}s}{(1+\frac{8}{3}s)} \\ \text{Thm} \end{aligned}$$

$$= -2(\infty) - \frac{8}{3}$$

True, if there is no proper rational fn, we can't use Initial value theorem

$$v_{L2}(t) = 2s(t) - \frac{4}{3} e^{-\frac{8}{3}t}$$

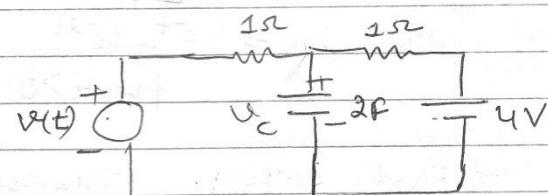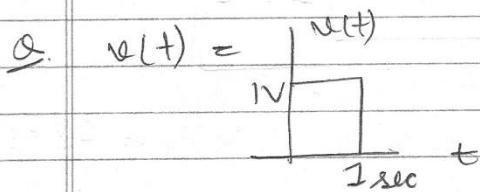Natural freq. present in every response through the system ^{resonance}. Mag. may change till nature of system remains same.



find $v_c(t)$


Soln. $v(t) = 2u(t) - u(t-1)$

$$\frac{1}{s} - \frac{8}{s} e^{-s} = LT \text{ of } u(t) - u(t-1)$$

For $t < 0 \quad \underline{v(t)} = 0$

At 0^-


$$v_c(0^-) = 2V$$

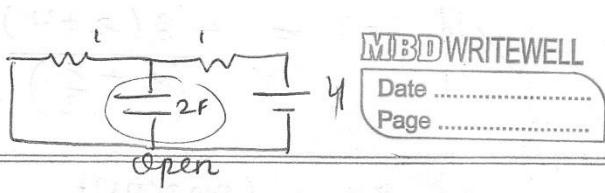

$$\frac{v_c(s) - v(0)}{1} + v_c(s) - \frac{2}{s}$$

$$\frac{1}{2s}$$

$$+ v_c(s) - \frac{4}{s} = 0$$

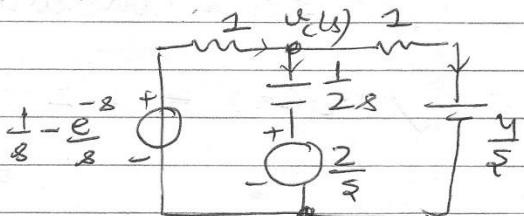

$$v_c(s) \left[1 + 2s + \frac{1}{s} \right] - \frac{2}{s} \times 2s - \frac{4}{s} = 0$$

$$-4 - \frac{4}{s} - \frac{1}{s} + \frac{e^{-s}}{s} = 0$$

$$v_c(t) = 2u(t) + \frac{1}{2}[u(t)]$$

$$-e^{-t}u(t) - \frac{1}{2}[u(t-1) - e^{t-1}u(t-1)]$$

$$v_c(s) = \frac{\frac{5}{s} - \frac{e^{-s}}{s} + 4}{2 + 2s}$$

Or find response for $u(t)$, then delay by 1 $u(t-1)$, then add, superposition.

Q.


$i(t)$ = Response

$v(t)$ = excitation

When $v(t) = 2V$

Then $i(t) = 4e^{-t} - 3e^{-2t}$

for $t > 0$

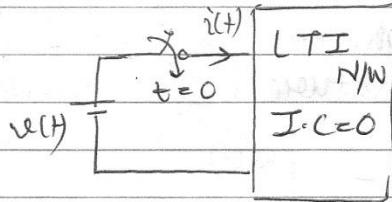

$$v(t) = 2V = u(t)$$

- 1) Find impulse response
- 2) Find system fn
- 3) Response corresponding to excitation $v(t) = e^{-4t}u(t)$
- 4) Find forced response of system corresponding to excitation $v(t) = \cos 2t$.

Soln

$$(i) A(s) = \frac{4}{1+s} - \frac{3}{s+2}$$

$$\checkmark H(s) = s \frac{(s+5)}{(s+1)(s+2)}$$

$$H(s) = s A(s)$$

$$= s \left(\frac{4}{1+s} - \frac{3}{s+2} \right)$$

$$A(s) = \frac{s+5}{(s+1)(s+2)}$$

$$(ii) L^{-1} H(s) = \text{System fn.} \quad \checkmark h(t) = s(t) - 4e^{-t} + 6e^{-2t}$$

$$(iii) h(t) * x(t)$$

$$x(s) = \frac{1}{(s+4)}$$

$$y(t) = -\frac{2}{3}e^{-4t} - \frac{4}{3}e^{-t} + 3e^t$$

$$\text{Response} = x(s) \cdot H(s)$$

$$(iv) H(s) \Big|_{s=j2} \cos 2t$$

$$\checkmark \text{Ans} \quad 1.7(\cos 2t + 3.4)$$

$$\frac{s(s+5)}{(s+1)(s+2)} \Big|_{s=j2} \cos 2t$$

$$\frac{j\omega(j\omega+5)}{(j\omega+1)(j\omega+2)} \cos 2t$$

$$\frac{j\omega(j\omega+5)}{(1-\omega^2)(4-\omega^2)} (2-j\omega)(1-j\omega)$$

$$\frac{17+j}{10} = 1.7 + j$$

$$\frac{(-\omega^2 + 5j\omega)(2-3j\omega - \omega^2)}{(1+\omega^2)(4+\omega^2)}$$


$$\text{Mag} = 1.7$$

$$\text{Angle} = \tan^{-1} \frac{1}{1.7}$$


$$= 3.3^\circ$$

$$\frac{(-4+10j)(2-6j-4)}{(1+4)(4+4)} = \frac{(-4+10j)(-6j-2)}{5(8)}$$

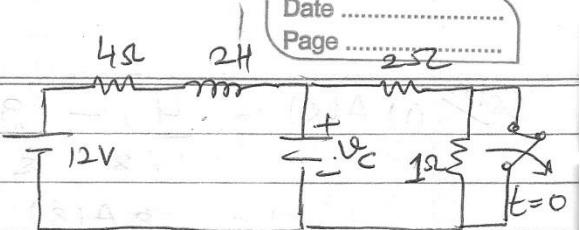Q1 Find v_c' , v_c'' , v_c''' at $t = 0^+$





Q2 Find $I_2(t)$

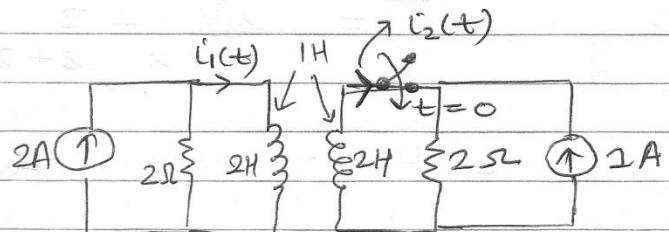

$$I_2(0^-) = 0$$

$$I_1(0^-) = 2A$$

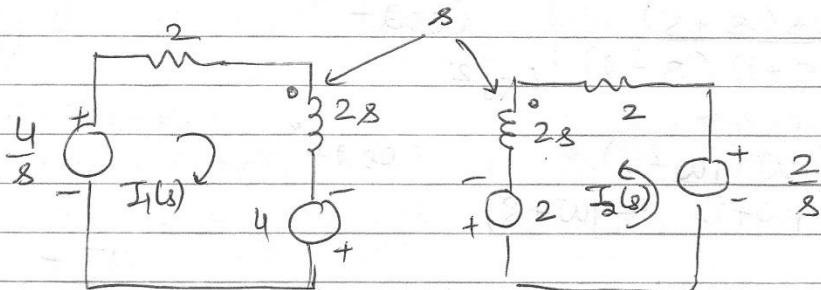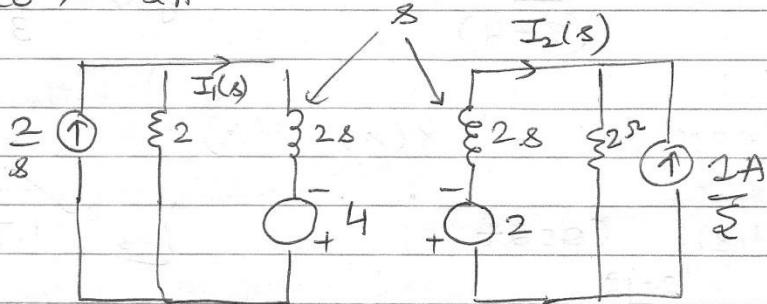


$$\frac{4}{8} = 2I_1(s) + 2sI_1(s) - 4 + 2sI_2(s)$$


$$\frac{2}{8} = 2I_2(s) + 2sI_2(s) - 2 + 2sI_1(s)$$

$I_1(s)$ ko negative karlo at last.

Also do ques for current source.

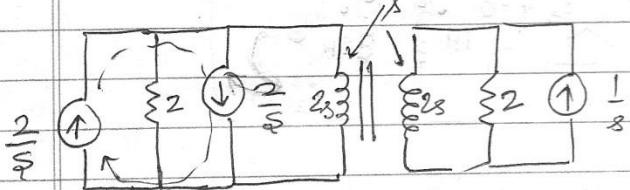


↓ This path independent of whole net.

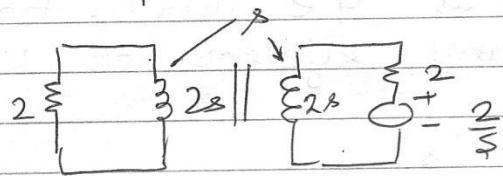

$$\begin{bmatrix} 2s+2 & -s \\ -s & 2s+2 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} 0 \\ -\frac{2}{s} \end{bmatrix}$$

$$I_2 = \left[-1 + \frac{1}{2} e^{-\frac{2}{3}s} t + \frac{1}{2} e^{-2s} t \right] u(t)$$


Q3 find $i_1(t)$ and $i_2(t)$

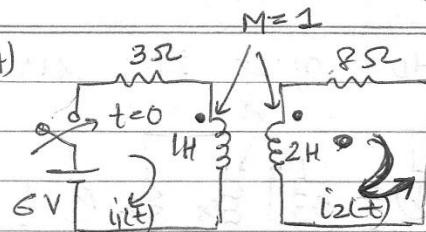

Q4 Response of initially relaxed LTI system to unit impulse is $4e^{-t}u(t)$. Find

- response of same system to unit step IP.
- find system fn $H(s)$
- find response of system to excitation $e^+u(t)$
- find the steady state response to an excitation $\sin st$.

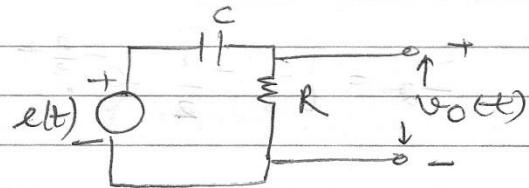
Q5 find condition on RC such that the given n/w will act as differentiator.



$$\text{i.e } v_o(t) = k \frac{d e(t)}{dt}$$

Try in both time and laplace domain

- Q6
- $s = I_s(t)$
 - $s = V_s(t)$

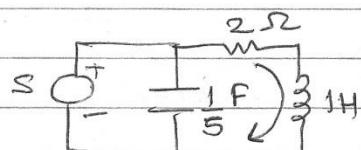

find the form of ^{free response} $i(t)$ for both cases.

Q4

$$H(s) = \frac{4}{(s+1)}$$

a) $\frac{1}{s} \times H(s) = Y(s)$

$$\frac{1}{s} \times \frac{4}{(s+1)} = Y(s)$$

$$\frac{A}{s} + \frac{B}{s+1} = \frac{4}{s} + \frac{4}{(s+1)}$$

$$Y(t) = 4 - 4e^{-t}$$

Impulse response
= Step resp

b) $H(s) = \frac{4}{(s+1)}$

c) $y(s) = \frac{4}{(s+1)} \frac{1}{(s+1)} = \frac{4}{(s+1)^2} = \underline{\underline{-4te^{-t}}}$

d) $H(s) = \frac{4}{(s+1)} \left| \begin{matrix} \sin 2t \\ 2j \end{matrix} \right. = \frac{4}{(2j+1)} \sin 2t$
 $= \frac{4}{\sqrt{4+1}} \sin (2t - \underline{\underline{26.55^\circ}})$

5 I across C $C \frac{dV_C}{dt} = C \frac{d}{dt}(e(t) - v_o(t))$

$$v_o(t) = RC \frac{d}{dt}(e(t) - v_o(t))$$

To act as differentiator $v_o(t) \equiv 0$
i.e. $R \approx 0$

In laplace

$$v_o(s) = \frac{R}{R + \frac{1}{Cs}} e(s) = \frac{R Cs}{Rs + 1} e(s)$$

In laplace

$v_o(s)$ should be $k s e(s)$


i.e $R Cs \lll 1$

$$\boxed{s \lll \frac{1}{RC}}$$

b) $s = I_s(t)$

$$I(s) = \frac{1}{Cs} I_s(s)$$

$$\frac{1}{Cs} + 2 + Ls$$

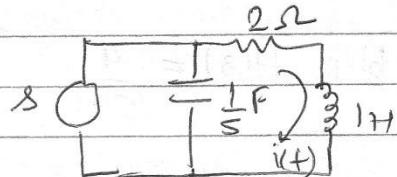

$$s = -1 \pm 2j \quad = \frac{5}{s} = \frac{5}{s + 2s + s^2} = \frac{5}{s^2 + 2s + 5}$$

represent
natural freq.
of free response

$$iH = k \bar{e}^{-t+2j} + k_2 \bar{e}^{-t-2j} = \frac{5}{(s+1-2j)(s+1+2j)}$$

b) When $s = V_s(t)$.

$$2I(s) + Ls I(s) = V_s(s)$$


$$(2 + s) I(s) = V_s(s)$$

$$I(s) = \frac{V_s(s)}{(s+2)}$$

$$k e^{-2t}$$

3
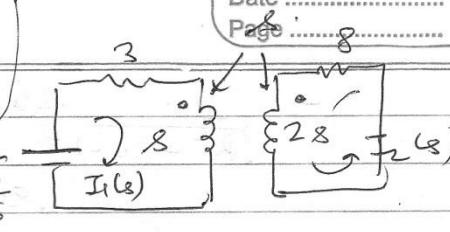
$$\begin{aligned} 6 &= (3+8) I_1(s) + 8 I_2(s) \\ \underline{(8)} &\quad \underline{(8)} \\ (8+2s) I_2(s) + 8 I_1(s) &= 0 \end{aligned}$$



$$I_1(t) = k_1 e^{-2t} + k_2 e^{-12t} + 2$$


$$I_2(t) = k_3 e^{-2t} + k_2 e^{-12t} + 0$$

Q.

$$e(t) = \sin(\omega t + \theta)$$

then find $i(t)$

$$E(s) = (R + Ls) I(s)$$

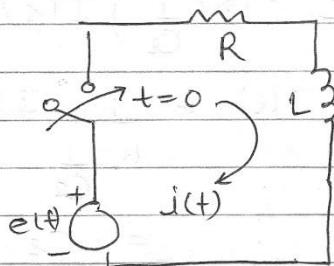

$$i(t) = k_1 e^{-\frac{R}{L}t} + k_2 \sin(\omega t + \theta)$$

$$= k_1 e^{-\frac{R}{L}t} + \frac{1}{R+j\omega L} \sin(\omega t + \theta)$$

$$i(t) = k_1 e^{-\frac{R}{L}t} + \frac{1}{\sqrt{R^2 + (\omega L)^2}} \sin(\omega t + \theta - \tan^{-1} \frac{\omega L}{R})$$

$$j(0) = k_1 + \frac{1}{\sqrt{R^2 + (\omega L)^2}} \sin(\theta - \tan^{-1} \frac{\omega L}{R})$$

$$k_1 = -\frac{1}{\sqrt{R^2 + (\omega L)^2}} \sin(\theta - \tan^{-1} \frac{\omega L}{R})$$

find θ in terms of R , L and ω if transient response of soln is zero.

means $(k_1 e^{-\frac{R}{L}t} = 0)$. i.e $k_1 = 0$.

\downarrow cf soln.

$$-\frac{1}{\sqrt{R^2 + (\omega L)^2}} \sin(\theta - \tan^{-1} \frac{\omega L}{R}) = 0$$

$$\sin(\theta - \tan^{-1} \frac{\omega L}{R}) = 0$$

$$\theta - \tan^{-1} \frac{\omega L}{R} = n\pi$$

$$\theta = n\pi + \tan^{-1} \frac{\omega L}{R}$$

Q. $I = \left(R + \frac{1}{Cs} \right) I(s)$

$$I(s) = \frac{1}{R + \frac{1}{Cs}}$$

$$= \frac{Cs}{RCs + 1}$$


$$= \frac{s}{R(s + \frac{1}{RC})} = \frac{s}{R(s + \frac{1}{RC})}$$

$$= \frac{(RCs + 1 - 1)}{R(RCs + 1)}$$



$$= \frac{1}{R} \left(1 - \frac{1}{RCs + 1} \right)$$

$$= \frac{1}{R} \left(1 - \frac{1}{R(RCs + 1)} \right) = \frac{1}{R} - \frac{1}{R(RCs + 1)}$$
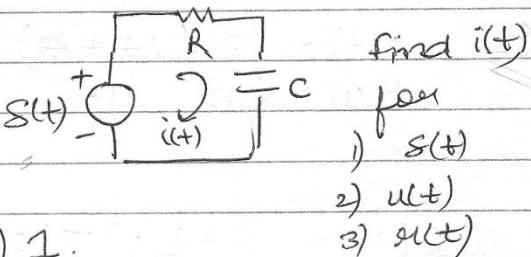
$$= \boxed{\frac{1}{R} s(t) - \frac{1}{R^2 C} e^{-\frac{t}{RC}}}$$



Q. $v_c(0^-) = 0$.

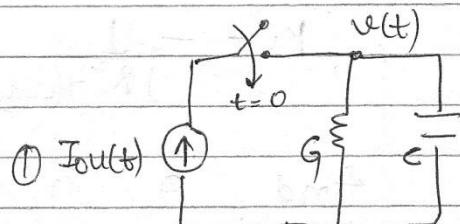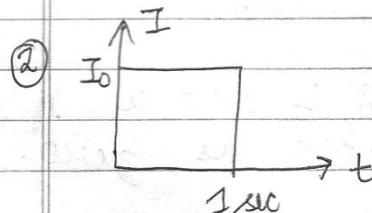

$$③ I = I_0 \sin \omega_0 t$$

SOLN

$$\underline{I_0(s)} = \underline{V(s)G + \frac{V(s)}{Cs}}$$

$$\underline{I_0(s)} = \underline{V(s)G} + \underline{Cs V(s)}$$

$$\frac{\underline{I_0(s)}}{G + Cs} = \underline{V(s)}$$

$$1) \quad I_0(s) = \frac{I_0}{s}$$

$$3) \quad I_0 \frac{\omega_0}{s^2 + \omega_0^2}$$

$$2) \quad I_0(s) = \frac{I_0}{s} - \frac{I_0}{s} e^{-s}$$

$$ke^{-\frac{Gt}{C}} + \frac{1}{(G + j\omega_0)}$$


$$ke^{-\frac{Gt}{C}} + \frac{I_0 \sin \omega_0 t - \tan^{-1} \frac{C}{G}}{\sqrt{G^2 + (j\omega_0)^2}}$$

Network function

N/W fn.

$$H(s) = \frac{R(s)}{E(s)} = \frac{L \{ R(t) \}}{L \{ E(t) \}}$$

$I, C = 0$

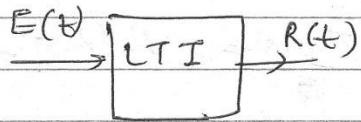

$$\left. \frac{R(s)}{E(s)} \right|_{I, C = 0} = \frac{N(s)}{D(s)}$$

either Impedance
or Admittance

N/W fn

when Excitation & Response variable
both are associated with same port

when excitation
at response both
are associated with
two different ports.

$$V_1 \rightarrow V_2$$

$$H(s) = \frac{V_2}{V_1} \text{ Ratio fn}$$

$$I_1 \rightarrow I_2$$

Ratio fn

$$V_1 \rightarrow I_2$$

$$H(s) = \frac{I_2}{V_1} \text{ Admittance fn}$$

$$I_1 \rightarrow V_2$$

Impedance fn

Q) find D.P. Impedance


D.P. Admittance

Transfer Impedance

Admittance


Voltage ratio

voltage ratio

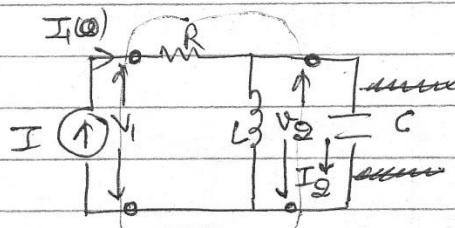

$$= \frac{1 + Ls}{Cs} + R$$

~~$\frac{1}{Cs} \times Ls$~~

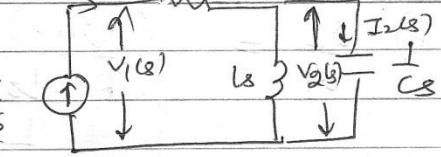

$$= \cancel{\frac{1 + Ls^2}{L}} + R$$

$$= \cancel{\frac{C(1 + Ls^2)}{L}} + R = \cancel{C(1 + Ls^2)} + RL$$

$$\begin{aligned} I_1(s) &= \cancel{\frac{I}{s}} \\ &\quad \cancel{C(1 + Ls^2) + RL} \\ &\quad \cancel{L} \end{aligned} \quad i) \quad \frac{V_1(s)}{I_1(s)} = \frac{Ls \cdot \frac{1}{Cs} + R}{Ls + \frac{1}{Cs}}$$

$$2) \quad \frac{I_1(s)}{V_1(s)} = \frac{Ls + \frac{1}{Cs}}{Ls \cdot \frac{1}{Cs} + R(Ls + \frac{1}{Cs})}$$

* Driving point Admittance $fn = \frac{1}{D.P. \text{ Impedance } fn}$

Not applicable with transfer fn.

$$3) \quad \frac{V_2(s)}{I_1(s)} = Z_{21} = \left(\frac{Ls}{Ls + \frac{1}{Cs}} \right) \frac{I_1(s) \cdot \frac{1}{Cs}}{R}$$

$$4) \quad \frac{I_2(s)}{V_1(s)} = \frac{V_1(s)}{R + Ls \cdot \frac{1}{Cs}} \left(\frac{Ls - \frac{1}{Cs}}{Ls + \frac{1}{Cs}} \right) \quad \begin{matrix} I_1(s) \\ \cancel{R + Ls \cdot \frac{1}{Cs}} \\ \cancel{Ls + \frac{1}{Cs}} \end{matrix} \quad \begin{matrix} V_1(s) \\ \cancel{Ls - \frac{1}{Cs}} \\ \cancel{Ls + \frac{1}{Cs}} \end{matrix}$$

$$s) \frac{V_2}{V_1} = \left(\frac{\frac{V_1(s)}{R + Ls + \frac{1}{Cs}}}{\frac{Ls + 1}{Cs}} \right) \left(\frac{\frac{Ls}{Ls + 1}}{\frac{Ls + 1}{Cs}} \right) \cdot \frac{1}{Cs}$$

$V_1(s)$

$$d) \frac{I_2}{I_1} = \frac{\frac{Ls}{Ls + 1}}{\frac{Cs}{I_1}}$$

Soldering type of entry - Then ① source maintains architecture of original ckt
 ② source doesn't

Cutting type of entry - ① source maintains architecture of original ckt. ② source doesn't

\Rightarrow 2 port m/w may be 4 terminal or 3 terminal m/w

2 port means first 2 terminals represent excitation, left " " " response.

However, if m/w 4 terminal, then any 2 terminals as excitation & any 2 as response.


22/3/2014

Date 22/3/14
Page


One port n/w

All fns will be deriving point fns.
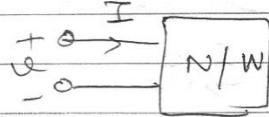
$$Z = \frac{V}{I}, \quad \frac{I}{V} = Y$$



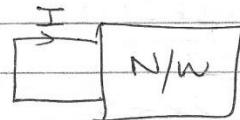$Y = \frac{I}{V}$ represents natural ν of system when excitation zero
i.e.



$$Z = \frac{V}{I} \Big|_{I=0}$$


open - circuit impedance parameter
excitation response in this is I

$Z(s) = g(s)$ $f(s) = 0$
 $f(s)$ roots of this eqn are
 poles of $Z(s)$ represent
 natural ν of n/w under the
 conditions that both terminals are
 open.


Poles of $Z(s)$ are zeroes of $Y(s)$. Only in case of one port.

$I = Z$
Y

Q Define $v(s)$ and $z(s)$

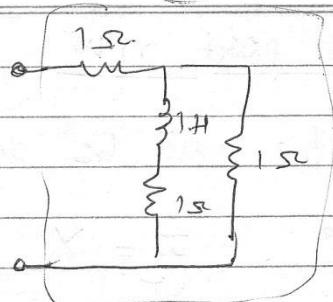

Soln in Laplace

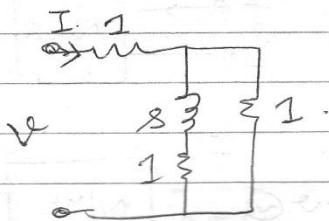

$$\frac{1(s+1) + 1}{1+s+1} = \frac{s+1+1}{s+2}$$


$$Z(s) = \frac{V}{I} = \frac{\frac{1(2s+3)}{(s+2)}}{\frac{1}{2}} = \frac{2s+3}{s+2}$$

Cross check - (i) Put $s=0$ i.e dc
i.e inductor as short ckt.
then eq. resistance = $\frac{3}{2}$

(ii) When s goes to ∞ i.e $X_L = \infty$.
i.e branch of L open ckt.

$$\lim_{s \rightarrow 0} \frac{2s+3}{s+2} = \frac{s\left(\frac{2+3}{s}\right) = 2}{s(1+\frac{2}{s})}$$

Same from ckt.

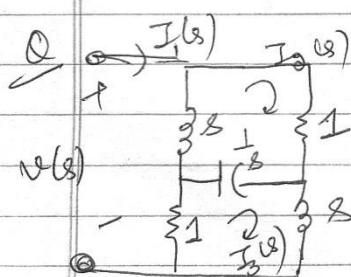

Find $Y(s)$

Sol'n $\gamma(s) = \frac{I(s)}{V(s)}$ self Impedance for loop
Mutual Impedance b/w loops

$$\begin{bmatrix} (s+1) & -s & -1 \\ -s & (s+1+s) & s \\ -1 & s & \left(\frac{1+s+1}{s}\right) \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \end{bmatrix} = \begin{bmatrix} V_E(s) \\ 0 \\ 0 \end{bmatrix}$$

$$I_1(s) = \frac{\Delta_{11}}{\Delta} (V_E(s))$$


$$\frac{I_1(s)}{V(s)} = \frac{\Delta_{11}}{\Delta}$$

$$\text{Ans} = \frac{s^2 + s + 2}{2s^2 + s + 1}$$

This method is more suitable for finding Admittance parameters.

If we have to find impedance parameter w/ mode eqn.
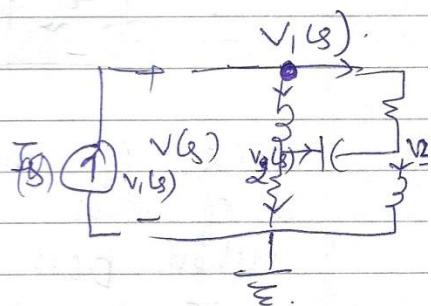
$$\begin{bmatrix} \frac{1+s}{s} & -\frac{1}{s} & -1 \\ -\frac{1}{s} & \left(\frac{1+s+1}{s}\right) & -s \\ -1 & -s & \left(\frac{1+s+1}{s}\right) \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \\ V_3(s) \end{bmatrix} = \begin{bmatrix} I(s) \\ 0 \\ 0 \end{bmatrix}$$



for outgoing

source should be merging towards node.

2 Port N/W

ExcitationResponseDes. fn (Describing) fn.

$$I_1, I_2$$

$$V_1, V_2$$

$$Z$$

$$V_1, V_2$$

$$I_1, I_2$$

$$Y$$

$$I_1, V_2$$

$$V_1, I_2$$

$$h$$

~~$$I_1, V_1, I_2$$~~

$$I_1, V_2$$

$$g$$

$$V_1, I_1$$

$$V_2, -I_2$$

$$ABCD \text{ OR } Tx \text{ line}$$


$$V_2, I_2$$

$$V_1, -I_1$$

$$A'B'C'D' \text{ OR } Inv.$$


Tx line# Z parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

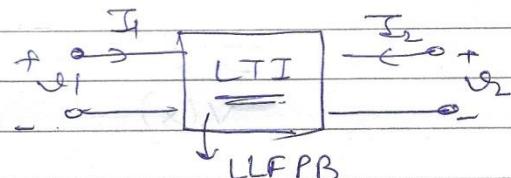

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

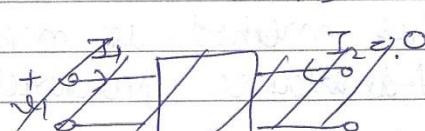

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

Poles of this n/w fn gives the natural ω of this system under the condition when both ports open.

I_1 is already open. To find natural ω excitation I_1 also zero i.e. Open ckt.

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

Also both port open
then natural ω .

Z_{11} = Driving point Impedance for
 Z_{12} = Transfer Admittance
 $Z_{21} = " D.P \text{ Impedance fn. } "$
 $Z_{22} = " D.P \text{ Impedance fn. } "$

WRITE WELL


Date
Page

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$


$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

i.e. in same state, the natural V of
m/w is defined. So poles must be
same in all. So, lower polynomial
in all Z must be same

chain

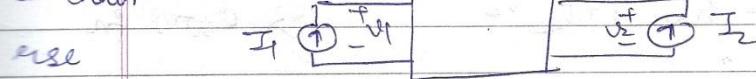

Apply superposition

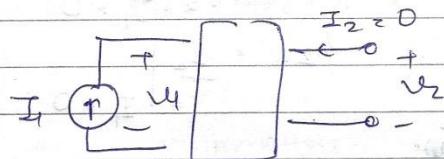

$$V_1 \Rightarrow | I_2 = 0$$

$$V_2 \Rightarrow | I_2 = 0$$

$$V_1 \Rightarrow | I_1 = 0$$

$$V_2 \Rightarrow | I_1 = 0$$

$$Z_{11} I_1, Z_{21} I_1$$

$$Z_{12} I_2, Z_{22} I_2$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$


$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

[Open Shunt parameter]

Y parameters

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

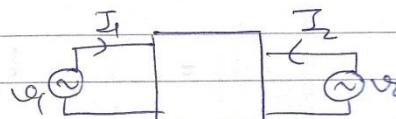

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

Poles of this fn represent natural V when
both ports are short ckt.

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

Y also called short net parameters.

h parameters

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

voltage
backward gain

Gain fr
Ratio fr

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

↓ forward current gain

poles of this fr

represent natural V

when second port short
and first open


↓

second short


first open

for

All —


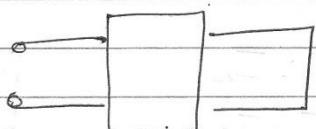


natural V in
this state

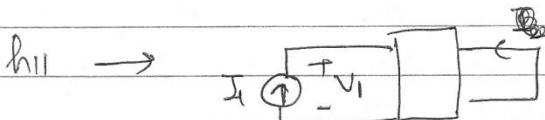


$$h_{11} =$$

$$h_{12} =$$

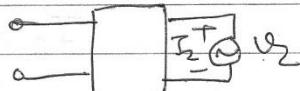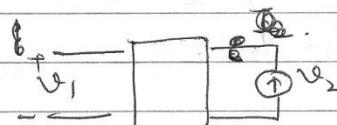

$$h_{21} =$$

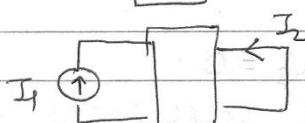

Deriving fn - associated with same port
 Transfer fn - " " different port

WORD WRITTEN BY _____
 Date
 Page

g parameters

$$I_1 = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$


$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0}$$

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0}$$

$$g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0}$$


$$g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

Natural freq \rightarrow

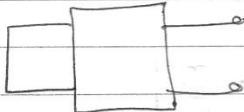

ABCD parameters
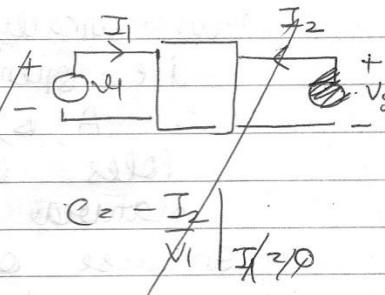
$$\begin{cases} V_2 = A V_1 + B I_1 \\ -I_2 = C V_1 + D I_1 \end{cases}$$




$$A = \frac{V_2}{V_1} \Big|_{I_1=0}$$

$$B = \frac{V_2}{I_1} \Big|_{V_1=0}$$

$$C = -\frac{I_1}{V_1} \Big|_{I_2=0}$$

$$D = -\frac{I_2}{V_1} \Big|_{I_1=0}$$

Natural freq

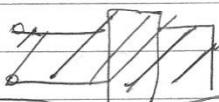


Power delivered by source $V_1 I_1$

Power received by load $= V_1 (-I_2)$

Used to calculate power

A' B' C' D' parameters

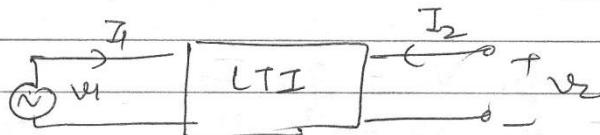

In this case excitation is written in terms of response

$$V_1 = A V_2 + B (-I_2)$$

$$I_1 = C V_2 + D (-I_2)$$

$$\text{Poles: } A = \frac{V_1}{V_2} \Big|_{I_2=0} \quad B = -\frac{V_1}{I_2} \Big|_{V_2=0}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0}$$

$$D = -\frac{I_1}{I_2} \Big|_{V_2=0}$$


Mathematically if $V_2 = 0$ i.e S.C and $I_2 = 0$ i.e open ckt. ~~contradictory~~

$\therefore A, B, C, D$ are not n/w fn.


\therefore Poles of this fn do not represent natural ω of system.

Inverse of these parameters is n/w fn to define behaviour of n/w because actually v_1 is the excitation


$$\frac{1}{A} = \frac{V_2}{V_1} \Big|_{I_2=0}$$

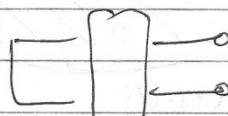


$$\frac{1}{B} = -\frac{I_2}{V_1} \Big|_{V_2=0}$$

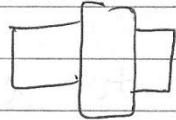

$$\frac{1}{C} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

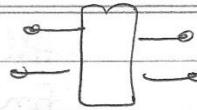

$$\frac{1}{D} = -\frac{I_2}{I_1} \Big|_{V_2=0}$$

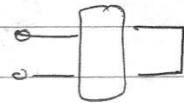

A' B' C' D'

$$V_2 = A'V_1 + B' - I_1 \quad \begin{array}{c} I_1 \\ \rightarrow \\ N/W \\ \leftarrow \\ I_2 \end{array}$$

$$I_2 = C'V_1 + D' - I_1 \quad V_2$$

$$A' = \frac{V_2}{V_1} \Big|_{I_1=0}$$


$$B' = \frac{V_2}{-I_1} \Big|_{V_1=0}$$

$$C' = \frac{I_2}{V_1} \Big|_{I_1=0}$$


$$D' = -\frac{I_2}{I_1} \Big|_{V_1=0}$$

Again contradictory

$$\frac{1}{A'} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

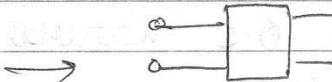

$$\frac{1}{B'} = -\frac{I_1}{V_2} \Big|_{V_1=0}$$

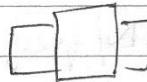


$$\frac{1}{C'} = \frac{V_1}{I_2} \Big|_{I_1=0}$$



$$\frac{1}{D'} = -\frac{I_1}{I_2} \Big|_{V_1=0}$$



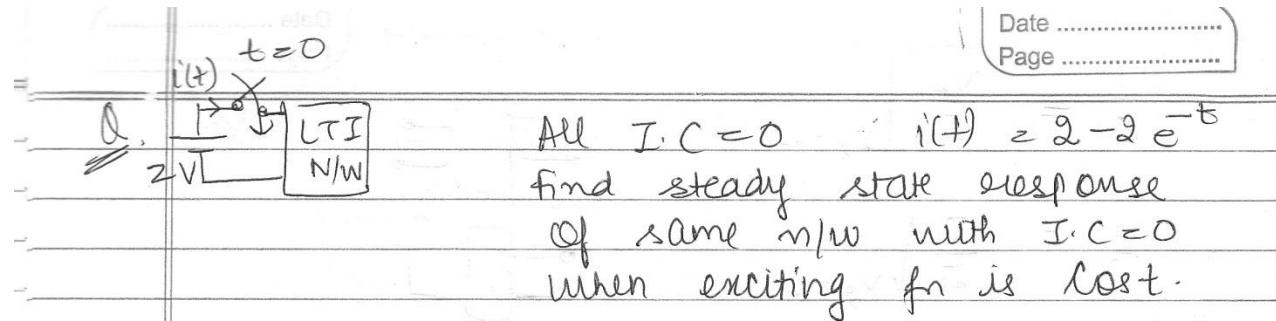i.e poles of these four represent natural modes of system in the following stage.



$$Z(s) = \frac{2}{s} = \frac{2}{s}$$

$$\text{excitation response } Z(s) = \frac{s+2}{s(1+s)} = \frac{s+2}{s(s+1)}$$

$$I(s) = Y(s) \cdot V(s) = \frac{2}{s} = \frac{2(s+1)}{s^2 + 2s + 2}$$

$$= \frac{1}{s+1} V(s) \quad Z(s) = (s+1)$$

$$= \frac{1}{j+1} V(s) \quad = -jw + 1 \quad Y(s) = \frac{1}{(s+1)}$$


Also find O.C natural freq and short ckt natural freq.

S.C N/freq = -1. (poles of $Y(s)$)

O.C N freq = ∞

steady state value = $\frac{1}{j+1}$ Cost

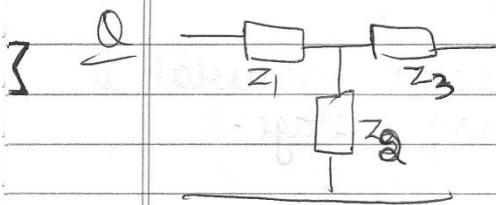
$$= \frac{1}{\sqrt{2}} \cos(t - 45^\circ)$$



Find Z parameter
Y, T and h.

$$\begin{aligned} Z \\ \equiv \\ V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned}$$


$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

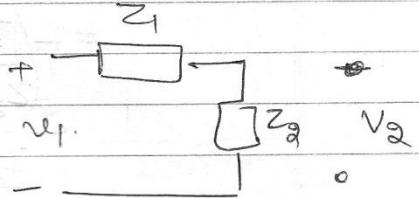

$$\frac{(Z_1 + Z_2) I_1}{I_1}$$

$$Z_{11} = Z_1 + Z_2.$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

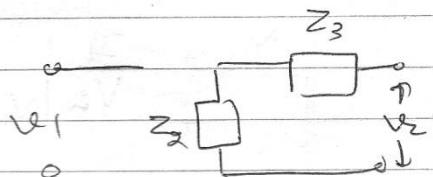

$$= Z_2 I_2 = Z_2.$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \\ = Z_2$$


$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} \\ = I_2 \frac{(Z_3 + Z_2)}{I_2} \\ = Z_3 + Z_2.$$

y parameters

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

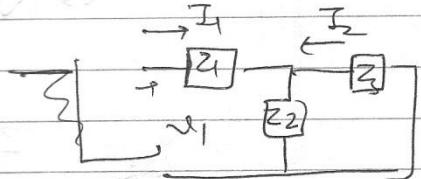


$$= \frac{1}{\frac{Z_2 Z_3}{Z_2 + Z_3} + Z_1} I_1$$

$$Y_{11} = \frac{1}{\frac{Z_2 Z_3}{Z_2 + Z_3} + Z_1} = \frac{Z_2 + Z_3}{Z_2 Z_3 + 4Z_2 + Z_1 Z_3}$$

$$\begin{aligned}
 Y_{21} &= \frac{I_2}{V_1} \\
 &= -\frac{Z_2}{(Z_2 + Z_3)} \cdot \frac{(Z_2 + Z_3)}{(Z_2 + Z_3 + Z_1) I_1} \\
 &= -\frac{Z_2}{Z_2 + Z_3} \cdot \frac{(Z_2 + Z_3)}{(Z_2 + Z_3 + Z_1) I_1} \\
 &= \boxed{-\frac{Z_2}{Z_2 Z_3 + Z_1 Z_3 + Z_1 Z_2}}
 \end{aligned}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

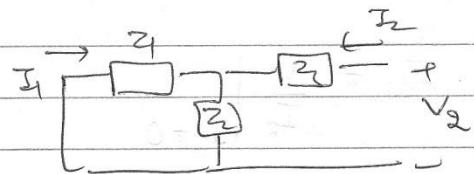


$$\begin{aligned}
 Y_{12} &= -\left[\frac{Z_2}{Z_1 + Z_2} \cdot \frac{(I_2)}{(Z_1 Z_2 + Z_3) I_1} \right] \\
 &= -\frac{Z_2}{Z_1 Z_2 + Z_3 Z_1 + Z_3 Z_2}
 \end{aligned}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{I_2}{Z_1 Z_2 + Z_3 (I_2)}$$


$$Y_{22} = \frac{Z_1 + Z_2}{Z_1 Z_2 + Z_3 Z_1 + Z_3 Z_2} = \frac{Z_1 Z_3 + Z_2 Z_3}{Z_1 Z_2 + Z_2}$$

Q5 find $Z + Y$.


Parallel connection

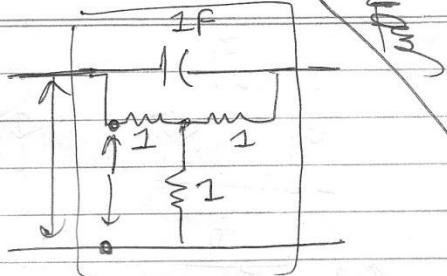

Q6 find Z, Y, h, T

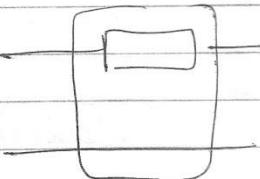


Q7 find Z, Y, h, T

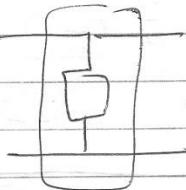

$$\Pi \Leftrightarrow \Delta$$

$$\star \Leftrightarrow Y \Leftrightarrow T$$
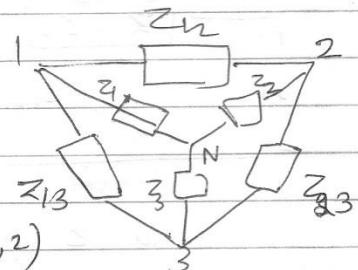
$$Z_{12} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3} \cdot (\text{different from } 1, 2)$$



$$Z_{13} = \frac{\Delta}{Z_2}$$

$$Y \rightarrow \Delta$$

$$Z_{23} = \frac{\Delta}{Z_1}$$

$$Z_1 = \frac{Z_{12} \cdot Z_{13}}{\Sigma Z}$$


$$\Delta \rightarrow Y$$

$$Z_2 = \frac{Z_{21} Z_{23}}{\Sigma Z} \xrightarrow{\text{those connected to node 2}} \Sigma Z = Z_{12} + Z_{13} + Z_{23}$$

$$Z_3 = \frac{Z_{13} \cdot Z_{23}}{\Sigma Z}$$

Unknown


Q8

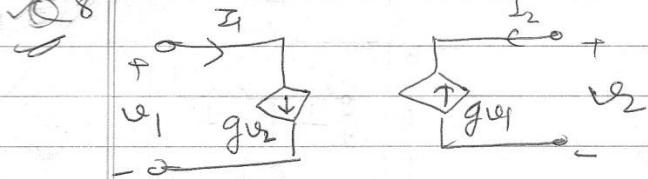

calculate Y


parameter.

Q9

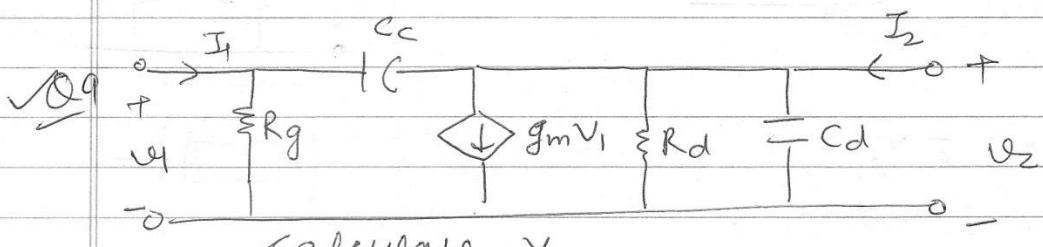


calculate Y.

Q10

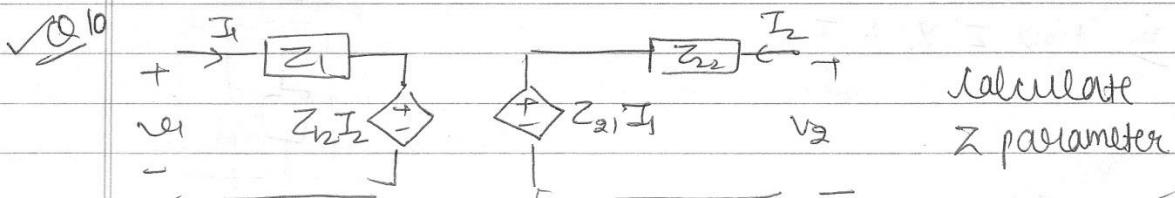


calculate
Z parameter

Q11

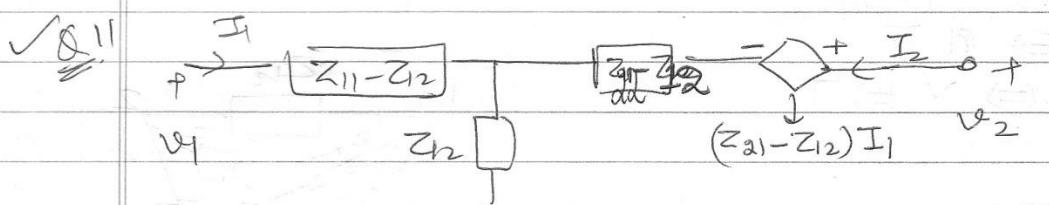


find Z parameters.


Q12

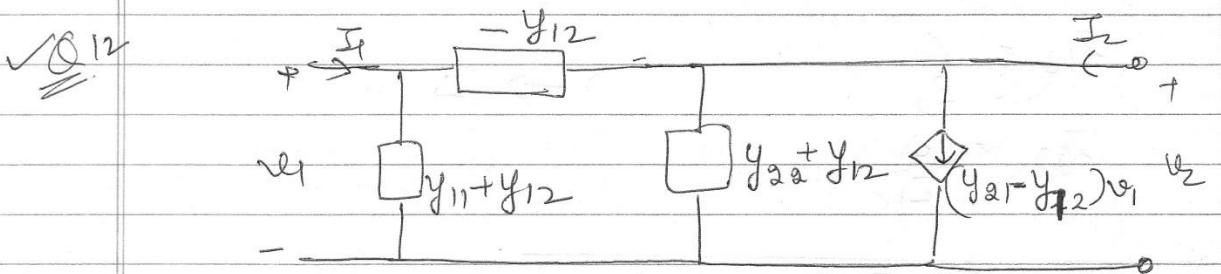


find Y parameter

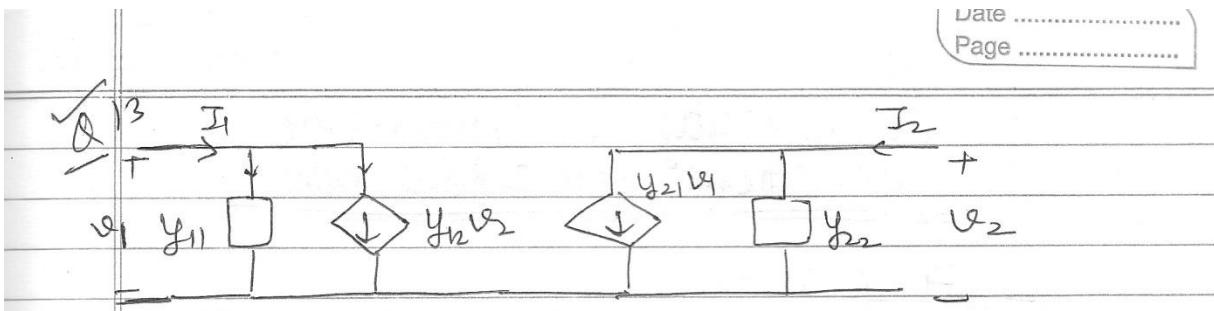

Calculate Y parameter.

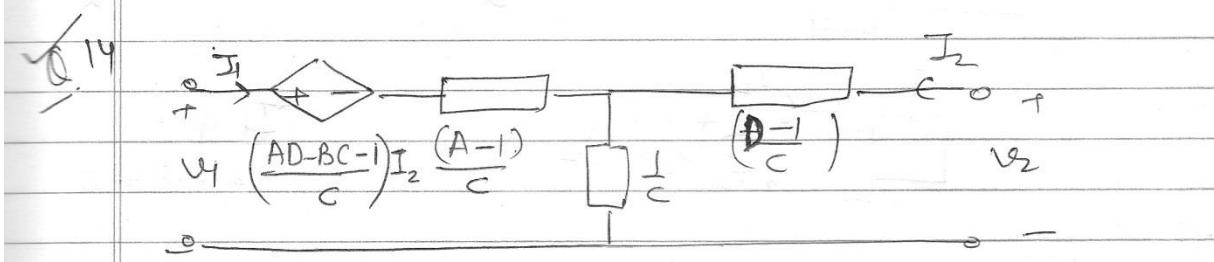


Calculate ABCD parameters.

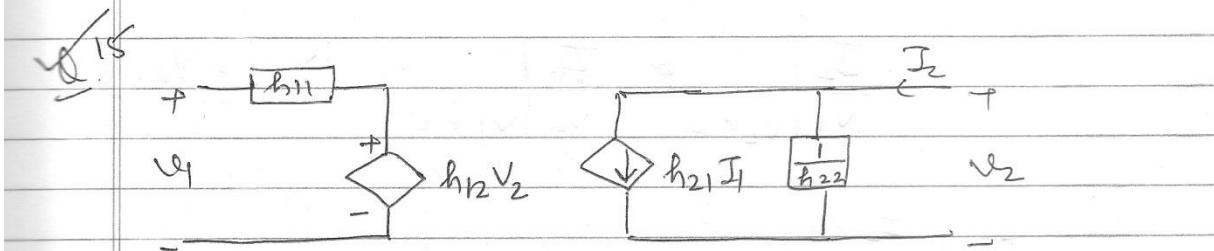

Calculate h parameter

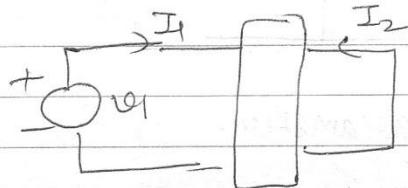
Reciprocity & Symmetric conditions for 2 port N/W



$$v_1 = E$$

$$I_2 = R \cdot$$


$$\left. \frac{I_2}{v_1} \right|_{v_2=0}$$

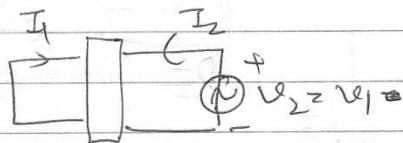


$$\left. \frac{I_1}{v_2} \right|_{v_1=0}$$

Now if these two are equal then
N/W reciprocal.

$$\left. \frac{I_2}{v_1} \right|_{v_2=0} = \left. \frac{I_1}{v_2} \right|_{v_1=0} \quad [Y_{12} = Y_{21}]$$

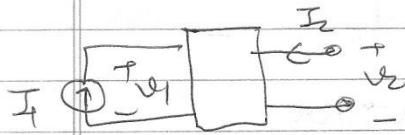

$$\left. \frac{v_2}{I_1} \right|_{I_2=0} = \left. \frac{v_1}{I_2} \right|_{I_1=0}$$

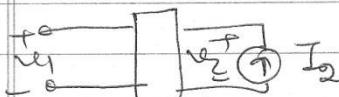

for reciprocal N/W.

∴ for Reciprocal N/W

$$[Z_{12} = Z_{21}]$$


In reciprocity, E and R at diff. ports.

In symmetry, E & R at same port

MBDWRITEWELL


Date

Page

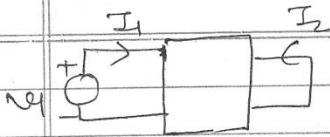

$$\frac{V_1}{I_1} \mid I_2 = 0$$

$$\frac{I_2}{V_1} \mid V_2 = 0$$

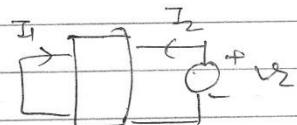


$$\frac{V_2}{I_2} \mid V_1 = 0$$

$$\frac{I_2}{V_2} \mid V_1 = 0$$


$$Y_{11} = Y_{22}$$

$$\text{voltmeter}$$


for symmetric N/W

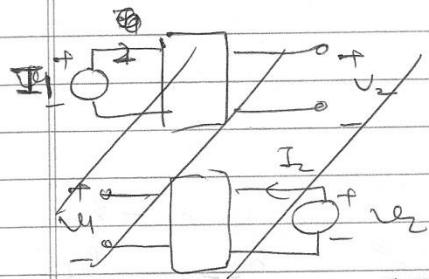
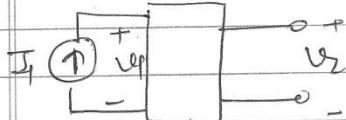
$$\begin{aligned} \frac{V_1}{I_1} \mid I_2 &\neq 0 \\ \frac{V_2}{I_2} \mid I_1 &= 0 \end{aligned}$$



$$\frac{V_1}{I_1} \mid I_2 = 0$$

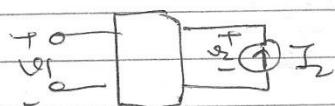

$$\frac{V_2}{I_2} \mid I_1 = 0$$

$$Z_{11} = Z_{22}$$

h parameter

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

Condition of reciprocity is

$$\frac{V_1}{I_2} \mid I_1 = 0 = \frac{V_2}{I_1} \mid I_2 = 0$$

$$Z_{12} = Z_{21}$$

$$0 = I_1 h_{21} + V_2 h_{22}$$

$$\left. \frac{V_2}{I_1} \right|_{I_2=0} = - \frac{h_{21}}{h_{22}} = Z_{21}$$

$$I_2 = V_2 h_{22}$$

$$I_2 = \frac{V_1}{h_{12}} h_{22}$$

$$\boxed{\left. \frac{V_1}{I_2} \right|_{I_2=0} = \frac{h_{12}}{h_{22}} = Z_{12}}$$

$$\frac{h_{12}}{h_{22}} = \frac{h_{21}}{h_{22}}$$

$$\frac{h_{12}}{h_{22}} = - \frac{h_{21}}{h_{22}}$$

$$h_{12}h_{22} + h_{21}h_{22} = 0$$

for ABCD Reciprocity

$$\frac{V_1}{I_1} = A V_2 - B (I_2)$$

$$\frac{V_2}{I_1} = C V_2 - D I_2$$

$$\left. \frac{V_1}{I_2} \right|_{I_2=0} = \text{---} \quad \left. \frac{V_2}{I_1} \right|_{I_2=0} = \text{---}$$

$$\Rightarrow C V_2 = D I_2$$

$$\Rightarrow V_1 = A V_2, \quad I_1 = C V_2$$

$$\frac{V_2}{I_1} = \text{---} \quad \frac{V_2}{C}$$

$$\left(\frac{V_1 + B I_2}{A} \right) C = D I_2$$

$$C(V_1 + B I_2) = AD I_2$$

$$CV_1 = (AD - BC) I_2$$

$$\left. \frac{V_1}{I_2} \right|_{I_2=0} = \frac{AD - BC}{C}$$

$$\frac{AD - BC}{g} = \frac{1}{d} \quad [AD - BC \neq 1]$$

h parameter symmetry

$$\frac{v_1}{I_1} \Big|_{I_2=0} = \frac{v_2}{I_2} \Big|_{I_1=0}$$

$$0 = h_{21} I_1 + \underline{h_{22} v_2}$$

$$0 = h_{21} I_1 + h_{22} \left(v_1 - \frac{h_{11}}{h_{12}} I_1 \right)$$

$$0 = \left(h_{21} - \frac{h_{11} h_{22}}{h_{12}} \right) I_1 - \frac{h_{22} v_1}{h_{12}}$$

$$\frac{v_2}{I_2} \Big|_{I_1=0}$$

$$I_2 = h_{22} v_2$$

$$\frac{v_2}{I_2} = h_{22}$$

$$\frac{v_1}{I_1} = \frac{h_{21} - h_{11} h_{22}}{\underline{h_{22}}} = \frac{h_{21} h_{12} - h_{11} h_{22}}{h_{22}}$$

$$\frac{h_{21} h_{12} - h_{11} h_{22}}{h_{22}} = 1$$

$$[h_{21} h_{12} - h_{11} h_{22} = 1]$$

g parameter.

$$\frac{I_1}{V_2} = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$

$$\left. \frac{V_1}{I_2} \right|_{I_1=0} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$g_{11}V_1 + g_{12}I_2 = 0$$

$$\frac{V_1}{I_2} = -\frac{g_{12}}{g_{11}}$$

$$\frac{V_2}{I_1} = \frac{g_{21}}{g_{11}}$$

$$-\frac{g_{12}}{g_{11}} = \frac{g_{21}}{g_{11}}$$

$$g_{21} + g_{12} = 0$$

Symmetry

$$\frac{V_1}{I_1} = \frac{1}{g_{11}}$$

$$g_{11}V_1 + g_{12}I_2 = 0$$

$$g_{11} \left(\frac{V_2 - g_{22}I_2}{g_{21}} \right) + g_{12}I_2 = 0$$

$$V_2 \left(\frac{g_{11}}{g_{21}} \right) - \left(\frac{g_{22}g_{11} + g_{12}}{g_{21}} \right) I_2 = 0$$

$$= \frac{g_{22}g_{11} + g_{12}g_{21}}{g_{21}}$$

$$\frac{g_{11}}{g_{21}}$$

$$\frac{g_{22}g_{11} + g_{12}g_{21}}{g_{11}} = \frac{1}{g_{11}}$$

$$g_{22}g_{11} + g_{12}g_{21} = 1$$

ABCD (Symmetry)

$$\begin{aligned} \frac{V_1}{I_1} &= A V_2 \\ I_1 &= C V_2 \\ \frac{V_1}{I_1} &= \frac{A}{C} \end{aligned}$$

$$\begin{aligned} C V_2 &= D I_2 \\ \frac{V_2}{I_2} &= \frac{D}{C} \\ \frac{D}{C} &= \frac{A}{C} \end{aligned}$$

$$[A = D]$$

Inverse Tx line (Reciprocity)

$$\begin{aligned} V_2 &= A' V_1 - B' I_1 \\ I_2 &= C' V_1 - D' I_1 \end{aligned}$$

$$V_2 = A V_1$$

$$I_2 = C V_1$$

$$\frac{V_1}{I_2} = \frac{1}{C}$$

$$C V_1 = D I_1$$

$$C \left[\frac{V_2 + B I_1}{A} \right] = D I_1$$

$$[D'A - B'C' = 1]$$

$$\frac{C V_2}{A} = \left(D - \frac{B C}{A} \right) I_1$$

$$\frac{V_2}{I_1} = \frac{D A - B C}{C}$$

Symmetry

$$\frac{N_1}{I_1} = \frac{D}{C}$$

$$V_2 = AV_1$$

$$I_2 = CV_1$$

$$\begin{matrix} A \\ C \end{matrix}$$

$$\frac{D}{C} = \frac{A'}{C}$$

$$[A' = D']$$

* Inter Relationship b/w different types of parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$\checkmark V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$V = [Z][I]$$

$$I = [Y][V]$$

$$V = [Z][Y][V]$$

$$[Z][Y] = I$$

$$[Z] = [Y]^{-1}$$

This doesn't mean

$$Y_{11} = \frac{1}{Z_{11}}$$

h & T

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$V_1 = A V_2 - B I_2$$

$$I_2 = C V_2 - D I_2$$

$$V_1 = \frac{h_{11}}{h_{21}} \left(I_2 - \frac{h_{22} V_2}{h_{21}} \right) + h_{12} V_2$$

$$V_1 = \frac{h_{11}}{h_{21}} I_2 - \left(\frac{h_{22} + h_{12}}{h_{21}} \right) V_2$$

$$A = - \left(\frac{h_{22} + h_{12}}{h_{21}} \right)$$

$$-B = \frac{h_{11}}{h_{21}}$$


$$I_1 = \frac{I_2}{h_{21}} - \frac{h_{22} V_2}{h_{21}}$$

$$C = - \frac{h_{22}}{h_{21}}$$

$$D = - \frac{1}{h_{21}}$$

2 port N/W terminated at a load

$$V_2 = V_L = -Z_L I_2$$




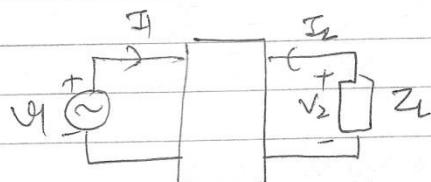


~~$$Z_{11} = V_1 - Z_{12} I_2$$~~

~~$$= V_1 - Z_{12}$$~~

Interconnection of Multiple 2 port N/W

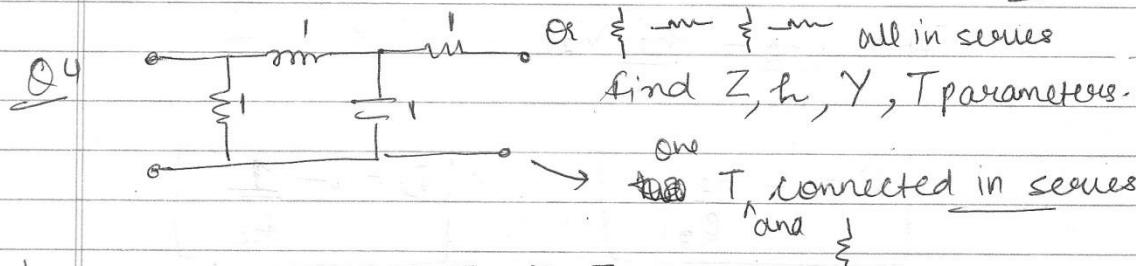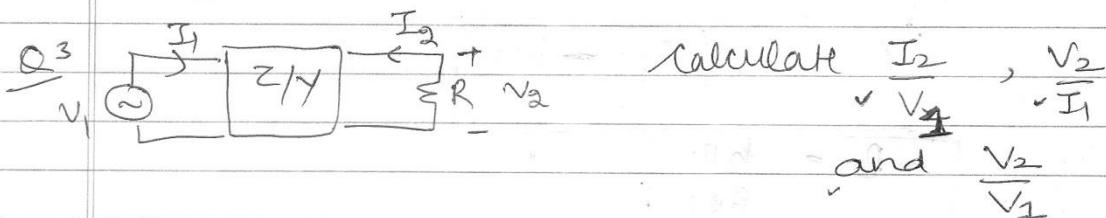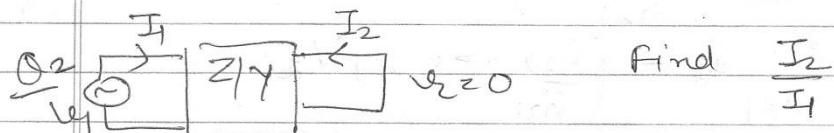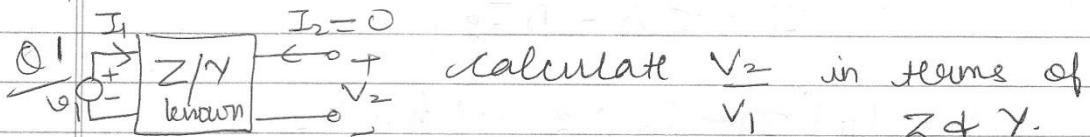- 1) Parallel Interconnection (already done).
- 2) Series
- 3) Cascade.



$$\begin{aligned} V_1 &= Z_{11}I_1 + Z_{12}I_2 \\ V_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned}$$

$$V_1 = Z_{11}I_1$$

$$V_2 = Z_{21}I_1$$

$$\boxed{\frac{V_2}{V_1} = \frac{Z_{21}}{Z_{11}}}$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{21}V_1 = -Y_{22}V_2$$

$$\boxed{\frac{V_2}{V_1} = \frac{-Y_{21}}{Y_{22}}}$$

$$\begin{array}{l} \frac{2}{=} V_1 = Z_{11} I_1 + Z_{12} I_2 \\ 0 = Z_{21} I_1 + Z_{22} I_2 \end{array}$$

$$\begin{array}{l} I_1 = Y_{11} V_1 \\ I_2 = Y_{21} V_1 \end{array}$$

$$\boxed{\frac{I_2}{I_1} = -\frac{Z_{21}}{Z_{22}}}$$

$$\boxed{\frac{I_2}{I_1} = \frac{Y_{21}}{Y_{11}}}$$

$$\begin{array}{l} \frac{3}{=} V_1 = Z_{11} I_1 + Z_{12} I_2 \\ V_2 = Z_{21} I_1 + Z_{22} I_2 \\ V_2 = -R I_2 \end{array}$$

$$\begin{array}{l} -R I_2 = Z_{21} I_1 + Z_{22} I_2 \\ -(R + Z_{22}) I_2 = Z_{21} I_1 \end{array}$$

$$V_1 = Z_{11} \left(-\frac{(R + Z_{22})}{Z_{21}} I_2 \right) + Z_{12} I_2$$

$$V_1 = \left[-\frac{Z_{11}(R + Z_{22}) + Z_{12}}{Z_{21}} \right] I_2$$

$$\frac{I_2}{V_1} = \frac{1}{-\frac{Z_{11}(R + Z_{22}) + Z_{12}}{Z_{21}}} = \frac{Z_{21}}{-Z_{11}R - Z_{11}Z_{22} + Z_{12}Z_{21}}$$

$$V_2 = -R \left(-\frac{Z_{21}}{R + Z_{22}} \right) I_1$$

$$\boxed{\frac{V_2}{I_1} = \frac{RZ_{21}}{R + Z_{22}}}$$

$$V_2 = -R \left(-\frac{V_1 - Z_{11} I_1}{Z_{22}} \right) \Rightarrow V_2 = -R \left(\frac{V_1}{Z_{22}} \right)$$

$$-h \left(V_1 + Z_{11}(R + Z_{22}) I_2 \right)$$

$$\frac{V_2}{V_1} = \frac{Z_{11}I_1 + Z_{12}I_2}{Z_{21}I_1 + Z_{22}I_2}$$

$$= -\frac{Z_{11}(R + Z_{22}) I_2 + Z_{12}I_2}{Z_{21}}$$

$$-\frac{Z_{21}(R + Z_{22}) I_2 + Z_{22}I_2}{Z_{21}}$$

$$= -\frac{Z_{11}(R + Z_{22})}{Z_{21}} + Z_{12}$$

$$-\frac{Z_{21}(R + Z_{22})}{Z_{21}} + Z_{22}$$

$$= -\frac{Z_{11}(R + Z_{22}) + Z_{12}Z_{21}}{Z_{21}(R + Z_{22}) + Z_{22}}$$

8.

$$I_1 = g V_2$$

$$I_2 = -g V_1$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$\frac{I_1}{V_2} = g$$


$$\frac{I_2}{V_1} = -g$$

$$Y_{12} = g$$

$$Y_{21} = -g$$

$$Y_{11} = 0$$

$$Y_{22} = 0$$

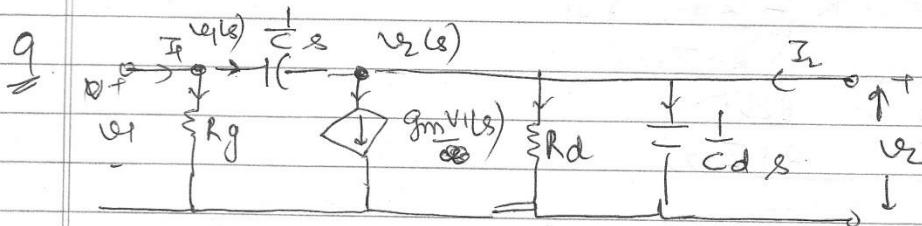

$$v_1(s) + v_2(s) \leftarrow x_2(s) = 0$$

Rg $\frac{1}{Cs}$

$$I_1(s) = \frac{v_1(s)}{Rg} + \frac{v_1(s) - v_2(s)}{\frac{1}{Cs}}$$

$$I_1(s) = v_1(s) \left[\frac{1}{Rg} + Cs \right] - v_2(s) (Cs)$$

$$I_2(s) = v_2(s) \left[C_d s + \frac{1}{R_d} \right] + g_m v(s) + \frac{v_2(s) - v_1(s)}{\frac{1}{Cs}}$$

$$I_2(s) = v_2(s) \left[C_d s + \frac{1}{R_d} + Cs \right] + (g_m - Cs) v_1(s)$$

$$Y_{11} = \frac{1}{Rg} + Cs \quad Y_{12} = -Cs$$


$$Y_{21} = g_m - Cs \quad Y_{22} = C_d s + Cs + \frac{1}{R_d}$$

$$\begin{array}{ll} 10 & v_1 = I_1 Z_{11} + Z_{12} I_2 \\ \hline 11 & v_1 = I_1 Z_{11} + Z_{12} I_2 \\ & v_2 = I_2 Z_{21} + Z_{22} I_1 \\ & v_2 = Z_{21} I_1 + Z_{22} I_2 \end{array}$$

Thus, this is eq. of Z parameters.

$$\begin{array}{ll} 11 & v_1 = I_1 (Z_{11} - Z_{12}) + Z_{12} (I_1 + I_2) \\ \hline & v_2 = I_2 (Z_{21} - Z_{22}) + (Z_{21} - Z_{12}) I_1 + Z_{12} (I_1 + I_2) \\ & v_1 = I_1 (Z_{11} + Z_{22}) - (Z_{11} - Z_{12} + Z_{12}) I_1 + Z_{12} I_2 \\ & v_1 = Z_{11} I_1 + Z_{12} I_2 \\ & v_2 = I_2 (Z_{21} - Z_{12} + Z_{12}) + (Z_{21} - Z_{12} + Z_{12}) I_1 \end{array}$$
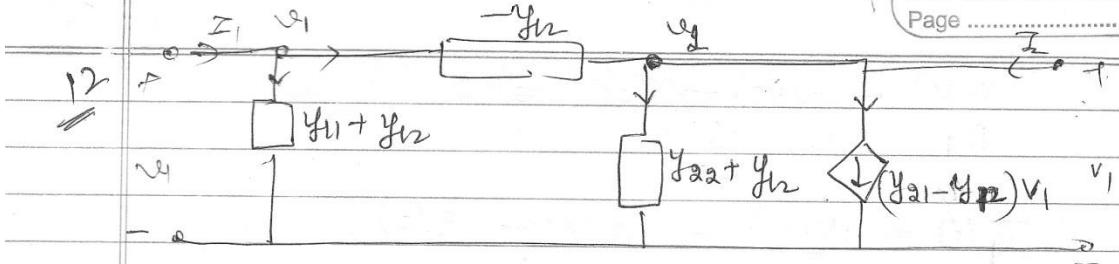
$$\begin{array}{ll} v_2 = I_2 Z_{21} + Z_{21} I_1 \\ v_1 = Z_{11} I_1 + Z_{12} I_2 \end{array} \quad \text{eq. to } Z \text{ n/w.}$$



$$I_1 = V_1 (y_{11} + y_{12}) + (V_1 - V_2) (-y_{12})$$

$$I_1 = V_1 (y_{11} - y_{12}) + V_2 y_{12}$$

$$I_2 = (y_{21} - y_{22}) V_1 + V_2 (y_{22} + y_{12}) + V_2 - V_1 (-y_{12})$$

$$I_2 = V_2 (y_{21} - y_{22} + y_{12})$$

$$I_2 = (y_{21} - y_{22} + y_{12}) V_1 + (y_{22} + y_{12} - y_{12}) V_2$$

$$Y_{11} = y_{11} - y_{12} + y_{12} \quad Y_{12} = y_{12}$$

$$Y_{21} = y_{21} - y_{22} + y_{12} \quad Y_{22} = y_{22} \quad \underline{\text{Y n/w}}$$

$$I_1 = V_1 (y_{11}) + y_{12} V_2$$

$$I_2 = V_2 y_{22} + y_{21} V_1$$

$$Y_{11} = y_{11}$$

$$Y_{12} = y_{12}$$

$$Y_{22} = y_{22}$$

$$Y_{21} = y_{21}$$

eq. n of Y parameters.

$$\text{B} \quad v_1 = \left(\frac{AD-BC-1}{C} \right) I_2 + I_1 \left(\frac{A-1}{C} \right) + \frac{1}{C} (I_1 + I_2)$$

$$v_2 = \left(\frac{D-1}{C} \right) I_2 + \frac{1}{C} (I_1 + I_2)$$

$$v_1 = \left(\frac{AD-BC-1}{C} + \frac{1}{C} \right) I_2 + \left(\frac{A-1}{C} + \frac{1}{C} \right) I_1$$

$$v_1 = \left(\frac{AD-BC-1+1}{C} \right) I_2 + \left(\frac{A-1+1}{C} \right) I_1$$

$$\rightarrow v_1 = \left(\frac{AD-BC}{C} \right) I_2 + \left(\frac{A}{C} \right) I_1$$

$$v_2 = \left(\frac{D-1}{C} + \frac{1}{C} \right) I_2 + \frac{1}{C} I_1$$

$$\rightarrow v_2 = \frac{D}{C} I_2 + \frac{1}{C} I_1$$

$$v_1 = \left(\frac{AD-BC}{C} \right) I_2 + \left(\frac{A}{C} \right) [(v_2 - \frac{D}{C} I_2) C]$$

$$v_1 = \left(\frac{AD-BC}{C} \right) I_2 + A v_2 - \left(\frac{AD}{C} \right) I_2$$

$$v_1 = \left(\frac{AD-BC}{C} - \frac{AD}{C} \right) I_2 + A v_2$$

$$v_1 = A v_2 - \left(\frac{A^2 - AD-BC}{C} \right) I_2 - BI_2$$

$$I_1 = C(v_2 - \frac{D}{C} I_2)$$

$$I_1 = C v_2 - \frac{D}{C} I_2$$

$$A = A$$

$$C = C$$

Eq. 1st of ABCD
parameters

$$B = B \quad D = D$$

IS
Z

$$v_1 = h_{11} I_1 + h_{12} v_2$$


$$I_2 = v_2 h_{22} + h_{21} I_1$$

Eq. 1st of h parameter

of h parameter

~~10~~

$$Z_{12} = \frac{1+1+1}{1}$$

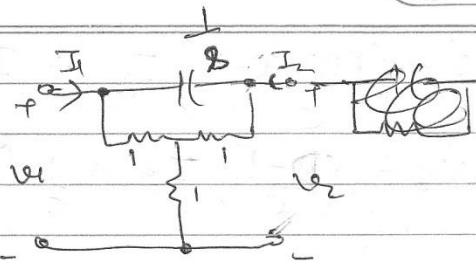



$$Z_{12} = 3$$

$$Z_{21} = \frac{3}{1} = 3$$

$$Z_{13} = 3$$

$$\begin{aligned} & \frac{1 \times 3 - 3}{8} \\ & \frac{1+3}{8} = \frac{3}{8} \end{aligned}$$

$$= \frac{3}{38+1}$$

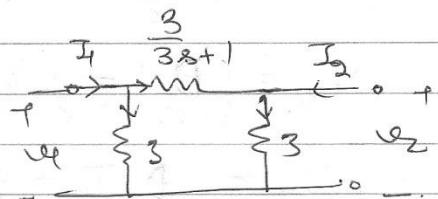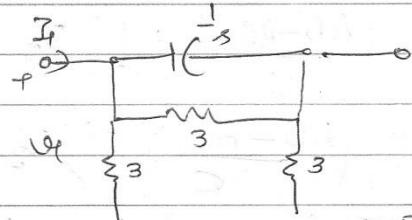

$$I_1 = \frac{v_1(s)}{3} + \frac{v_1(s) - v_2(s)}{\frac{3}{38+1}}$$

$$= \frac{3}{38+1}$$

$$I_1(s) = \frac{v_1(s)}{3} \left[\frac{1}{3} + \frac{38+1}{3} \right] - \frac{38+1}{3} v_2(s)$$

$$I_2(s) = \frac{v_2(s)}{3} - \left(\frac{v_1(s) - v_2(s)}{\frac{3}{38+1}} \right)$$

$$I_2(s) = \frac{v_2(s)}{3} \left[\frac{1}{3} + \frac{38+1}{3} \right] - \frac{38+1}{3} v_1(s)$$

$$Y_{11} = \frac{2+38}{3}$$

~~$$V_1 = Z_{11} I_1 + Z_{12} I_2$$~~

$$Y_{12} = -\frac{38+1}{3}$$

~~$$V_2 = Z_{21} I_1 + Z_{22} I_2$$~~

$$Y_{21} = -\frac{38+1}{3}$$

~~$$I_1 = \frac{V_1}{Z_{11}} + \frac{Z_{12}}{Z_{11}} I_2$$~~

$$Y_{22} = \frac{2+38}{3}$$

~~$$I_1 = \frac{V_1}{Z_{11}} - \frac{Z_{12}}{Z_{11}} \left[\frac{V_2 - Z_{21} I_1}{Z_{22}} \right]$$~~

~~Q~~ ~~else~~

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$V_1 = \frac{I_1 - Y_{12}V_2}{Y_{11} - Y_{11}}$$

$$V_1 = \frac{I_1}{Y_{11}} - \frac{Y_{12}}{Y_{11}} \left(\frac{I_2 - Y_{21}V_1}{Y_{22}} \right)$$

$$V_1 = \frac{I_1}{Y_{11}} - \frac{Y_{12}}{Y_{11}} \frac{I_2}{Y_{22}} + \frac{Y_{12}Y_{21}}{Y_{11}Y_{22}} V_1$$

$$V_1 \left(1 - \frac{Y_{12}Y_{21}}{Y_{11}Y_{22}} \right) = \frac{I_1}{Y_{11}} - \frac{Y_{12}I_2}{Y_{11}Y_{22}}$$

~~$$V_1 \left(\frac{Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_{11}Y_{22}} \right) = \frac{I_1}{Y_{11}} - \frac{Y_{12}}{Y_{11}Y_{22}} I_2$$~~

$$V_1 = \frac{\frac{Y_{22}I_1}{Y_{11}Y_{22} - Y_{12}Y_{21}} - \frac{Y_{12}}{Y_{11}Y_{22} - Y_{12}Y_{21}} I_2}{\frac{Y_{22}}{Y_{11}Y_{22} - Y_{12}Y_{21}}}$$

$$Z_{11} = \frac{Y_{22}}{|Y|}$$

$$= \frac{2+3s}{3}$$

$$\left(\frac{2+3s}{3} \right)^2 - \left(\frac{3s+1}{3} \right)^2 = \frac{1}{9} [4 + 9s^2 + 12s - 9s^2 - 1] - 4s$$

$$= \frac{2s+3}{3}$$

$$= \frac{2s+3}{3}$$

$$= \frac{2s+3}{3}$$

$$Z_{12} = \frac{3s+1}{3} = \frac{3s+1}{9[6s+3]}$$

$$\boxed{\frac{3s+1}{2s+1}}$$

$$= \frac{1}{9} [6s+3]$$

$$= \frac{2s+3 \times 9}{3(2s+1)}$$

$$Z_{21} = \frac{3s+1}{2s+1}$$

$$= \boxed{\frac{2s+3}{2s+1}}$$

$$Z_{22} = \frac{2s+3}{2s+1}$$

~~Solve~~

~~Op. & Soln~~
~~Op. & Soln~~

$$I_1 = -I_2$$

$$V_1 = I_1 R + V_2$$

$$I_1 R = V_1 - V_2$$

$$I_1 = \frac{1}{R} V_1 - \frac{1}{R} V_2 \quad Y_{11} = \frac{1}{R} \quad Y_{12} = -\frac{1}{R}$$

$$I_2 = -\frac{1}{R} V_1 + \frac{1}{R} V_2 \quad Y_{21} = -\frac{1}{R} \quad Y_{22} = \frac{1}{R}$$

$$\begin{aligned} Z_{11} &= Y_{22} = \frac{1}{R} = \infty & h_{11} &= R \\ \frac{\partial Y}{\partial V} &= \frac{1}{R^2} = \frac{1}{R^2} & h_{12} &= \frac{+1}{R} = 1 \\ Z_{12} = Z_{21} = Z_{22} &= 0 & \frac{1}{R} & \\ & & h_{22} &= 0 \end{aligned}$$

$$A = \frac{-1}{R} = 1 \quad B = R \quad C = 0 \quad D = 1$$


~~Solve~~
~~≡~~

$$V_1 = V_2$$

$$V_1 = (I_1 + I_2) R$$

$$V_2 = I_1 R + I_2 R$$

$$V_2 = I_1 R + I_2 R$$

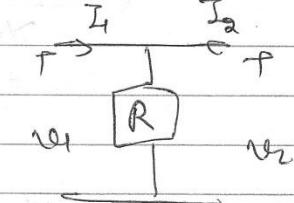

$$Z_{11} = R$$

$$Z_{12} = R$$

$$Z_{21} = R$$

$$Z_{22} = R$$

$$Y_{11} = \frac{Z_{22}}{|Z|} = \frac{R}{R^2 - R^2} = \infty$$

$$Y_{12} = -\frac{Z_{11}}{\Delta Z} = \infty$$

$$Y_{21} = -\frac{Z_{21}}{\Delta Z} = 0 \quad Y_{22} = \frac{Z_{11}}{\Delta Z} = \infty$$

$$h_{11} = \frac{\Delta Z}{Z_{22}} = 0$$

$$h_{21} = -\frac{Z_{21}}{Z_{22}} = -1$$

$$h_{12} = \frac{Z_{12}}{Z_{22}} = 1$$

$$h_{22} = \frac{1}{Z_{22}} = \frac{1}{R}$$

$$T = A = \frac{Z_{22}}{Z_{12}} = 1.$$


$$B = \frac{\Delta Z}{Z_{12}} = 0$$

$$C = \frac{1}{Z_{12}} = \frac{1}{R}$$

$$D = \frac{Z_{11}}{Z_{12}} = 1.$$

 $T = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$

γ, γ, h, g not defined

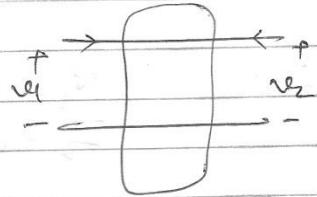

$$v_1 = v_2$$

$$I_1 = -I_2$$

$$A = 1$$

$$D = 1$$

$$B = 0$$

$$C = 0$$

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0}$$

$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0}$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0}$$

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

a) $g_{11} = 0$

b)



c) $g_{21} = 1$

not a valid representation

d) $g_{22} = \text{undefined (same as } g_{12})$


as both arms of v_2 are short circuit.

This is no
valid circuit




Q

all in cascade

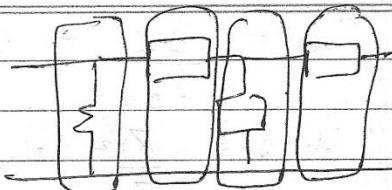

$$\left(\frac{V_1}{I_1}\right) \left[\frac{V_2}{I_2}\right] \left[\frac{V_3}{I_3}\right] \left[\frac{V_4}{I_4}\right]$$

Q

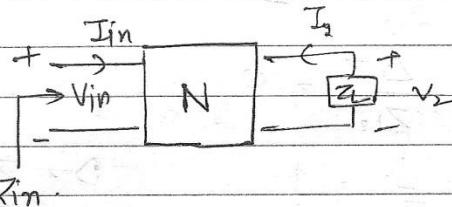

$$Z_{in} = \frac{V_1}{I_1} = -Z_L \quad \text{find h parameters}$$

$$\text{if } \frac{V_1}{I_1} = k$$

Soln.

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$-Z_L I_2 = V_2$$

$$\frac{V_2}{I_2} = -Z_L$$

$$\frac{V_2}{I_2} = \frac{V_1}{I_1}$$

$$\boxed{\frac{V_2}{V_1} = \frac{I_2}{I_1} = \frac{k}{k}}.$$

$$h_{11} = \frac{V_1}{I_1} \\ h_{12} = 0$$

$$\frac{V_1}{I_1} = \frac{V_2}{I_2} = k$$

$$\boxed{\frac{V_1}{I_1} = \frac{V_2}{I_2} = k}$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} = 0$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = k$$

$$h_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{1}{k}$$

$$\begin{bmatrix} 0 & k \\ \frac{1}{k} & 0 \end{bmatrix}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = 0$$

⇒ Check whether n/w is active or passive

$$V_1 = I_2 k$$

$$V_2 = V_2 k$$

$$V_1 \times I_1 + V_2 I_2$$

$$\cancel{kV_2} \cdot kV_2 \cdot kI_2 + V_2 I_2$$

$$V_2 I_2 (k^2 + 1)$$


$$= (1+k^2) (-Z_L) I_2^2$$

$$= -(1+k^2) (Z_L) I_2^2$$

Result ≤ 0 so passive n/w.
i.e O/P


N/W Theorems

Q

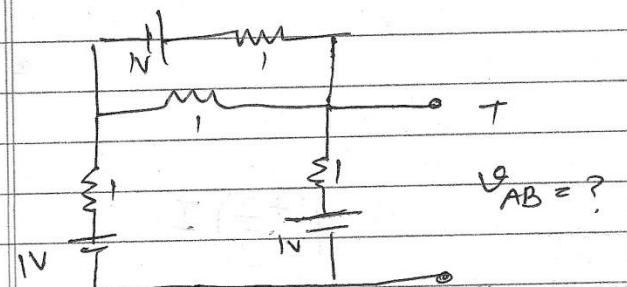

This is non linear
N/W

$$V_{AB} = ?$$

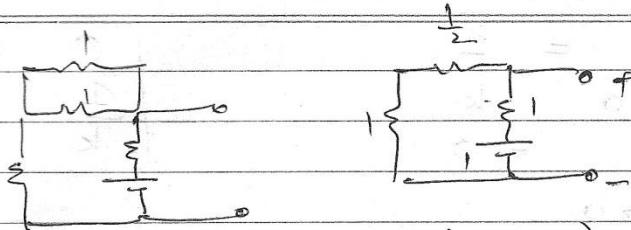


$$I = \left(1 + \frac{1}{2} + 1\right) I$$

$$I = \left(\frac{3}{2} + 1 + 2\right) I$$

$$2 = 5I \quad I = \frac{2}{5}$$

$$\underline{\underline{V_{AB}}} = -1 + 1 \times 2 = \frac{1}{5} V_{AB} = 0$$


$$V_{AB} = +1 - \frac{2}{5}$$

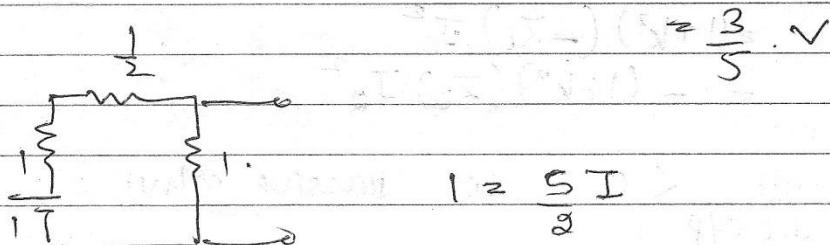


$$I = \frac{5}{2} I$$

$$I = \frac{2}{5}$$

$$V_{AB} = 1 \times 2 = \frac{2}{5} V$$

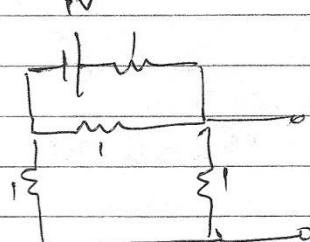
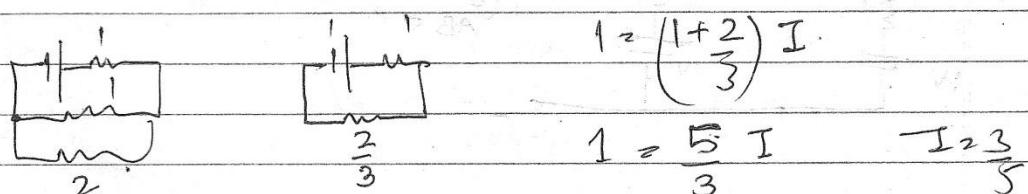
$$I = \left(1 + 2 \cdot \frac{1}{3}\right) I$$





$$I = \frac{5}{3} I \quad I = \frac{3}{5}$$

$$\frac{1}{3} \times 3$$

$$I = \frac{1}{5}$$

$$V = \frac{1}{5}$$
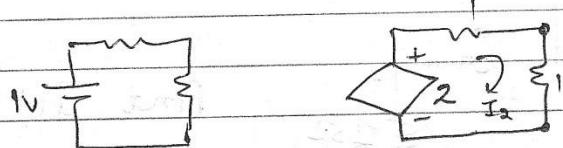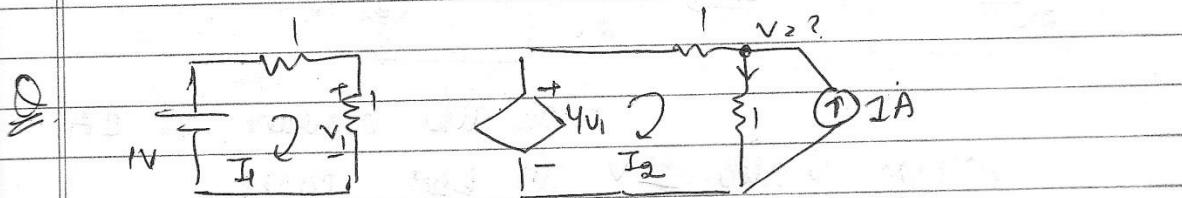
$$\text{Total } V_{AB} = \frac{3}{5} + \frac{2}{5} + \frac{1}{5} = \frac{6}{5} \text{ V}$$



$$I = I_1 + I_2$$

$$1 = 2I$$

$$I_1 = \frac{1}{2}$$


$$2I_2 - 2 = 0$$

$$2I_2 = 2$$

$$I_2 = 1$$

$$V_1 = \frac{1}{2} \times 1 = \frac{1}{2}$$

$$\frac{1 \times I_2}{V = 1}$$

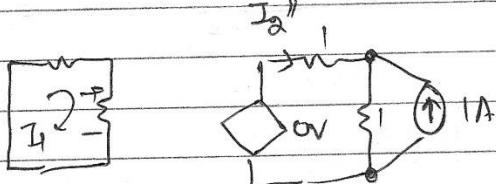

$$I = \frac{1}{2} \times 1$$

$$V = \frac{1}{2} V$$

$$I_2'' = -\frac{1}{2} A$$

$$V = 1 + \frac{1}{2} = \frac{3}{2} V$$

Substitution


MBOWRITEWELL

Date


Page

$$I_1 = 2$$

$$I''_1$$

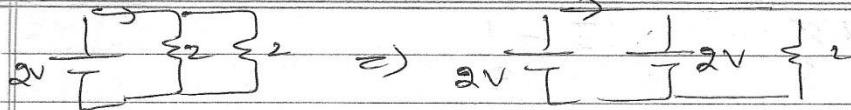


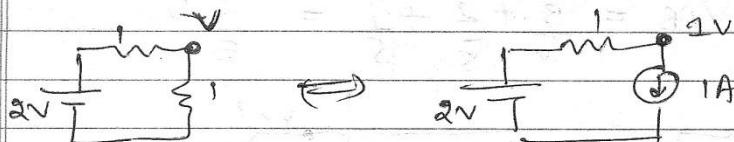Can't be used as initially I_1 was defined to be 2. However I''_1 is not defined




Now also current is 1A

Voltage V also 1V in both cases.

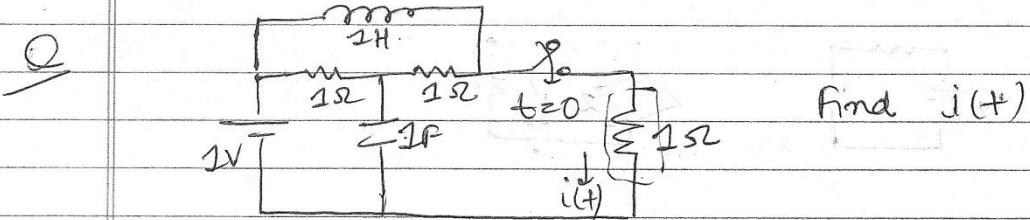

Find $i(+)$

SOLN

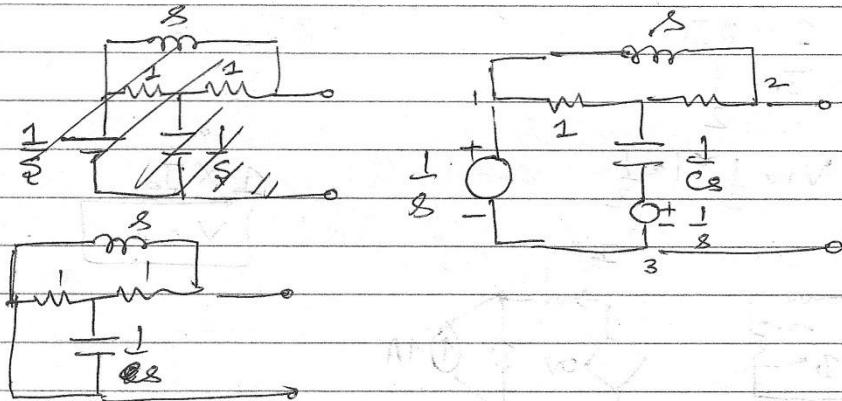

$$1 + \frac{1}{8} + \frac{1}{8} = 1 + \frac{2}{8} = \frac{8+2}{8}$$

$$Z_{12} = \frac{8+2}{\frac{1}{8}} = 8+2$$

$$Z_{13} = \frac{s+2}{s} = \frac{s+2}{s}$$

$$Z_{23} = \frac{s+2}{s} = \frac{s+2}{s}$$

$$\frac{s(s+2)}{s+2+2} = \frac{s(s+2) + s+2}{s+2} \quad \text{circled}$$

$$= s^2(s+2) + (s+2)2(s+1)$$

$$\begin{aligned} & \cancel{s^2(s+2)} \parallel \cancel{s+2} \quad \cancel{2(s+1)s} \\ & \cancel{2s+2} \quad \cancel{s} = s^2(s+2) + 2(s+2)(s+1) \\ & = \cancel{(s+2)} \left[s^2 + 2(s+1) \right] \cancel{\left(s+2 \right)} \\ & \quad \cancel{2(s+1)s} \\ & \quad \frac{(s+2)[s^2 + 2(s+1)]}{2(s+1)s} + \cancel{\frac{s+2}{s}} \end{aligned}$$

Correct
Ans

$$Z_0(s) = \frac{s(s+2)}{s^2 + 2s + 2}$$

$$\frac{(s+2)(s^2 + 2s + 1)}{2(s+1)s} \frac{(s+2)}{s}$$

$$\frac{(s+2)(s^2 + 2(s+1)) + 2(s+1)(s+2)}{2(s+1)s}$$

$$= (s+2) \frac{(s^2 + 2(s+1))(s+2)}{s}$$



$$= \frac{s^2 + 2s + 2 + 2s + 2}{s(s+2)^2}$$

$$\checkmark V_{OC} = \frac{1}{8}$$

$$I(t) = 1 - \frac{1}{2} e^{-t} + t e^{-t}$$

Q Here Norton current = 5

It is already in
Norton eq. circuit

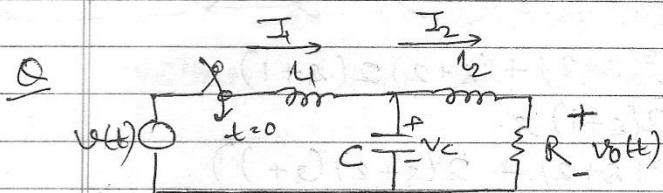
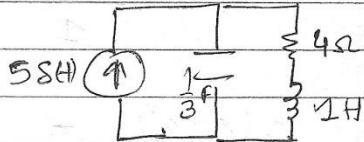


$$I(0^+) \text{ are all non-zero} = I_{10}$$

$$I_{20} \text{ zero values} = I_{20}$$


$$V_{CO} = V_{CO}$$

Calculate $V_0(s)$

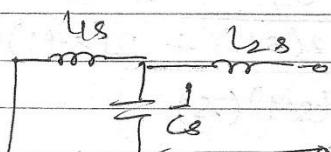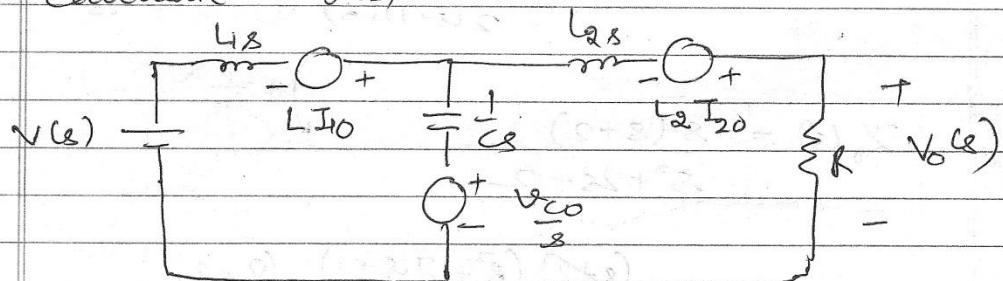

$$\frac{4s \times 1}{Cs} = \frac{4}{Cs} = \frac{L_{10}}{4Cs^2 + 1} + \frac{L_{20}}{Cs}$$
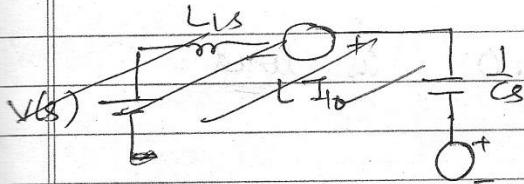
$$R_{eq} = \frac{L_1 s + L_2 s L_1 C s^2 + L_2 s}{4 C s^2 + 1}$$



$$V(s) = \left[V(s) + L_1 I_{10} - \frac{V_{co}}{s} \right] \frac{1}{L_1 s + \frac{1}{C s}}$$


$$I(s) = \left[V(s) - \frac{V_{co} + L_1 I_{10}}{s} \right] \frac{1}{4 C s^2 + 1}$$

$$V_{co}(s) = V(s) - I(s)L_1(s) + L_1 I_{10} + L_2 I_{20}$$


because of presence of $L_2 I_{20}$

$$I_2 = 0$$

$$L_2 s = 0$$

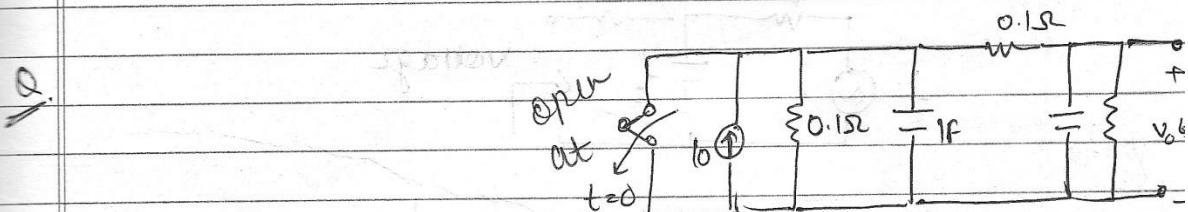

We found all $I_C = 0$


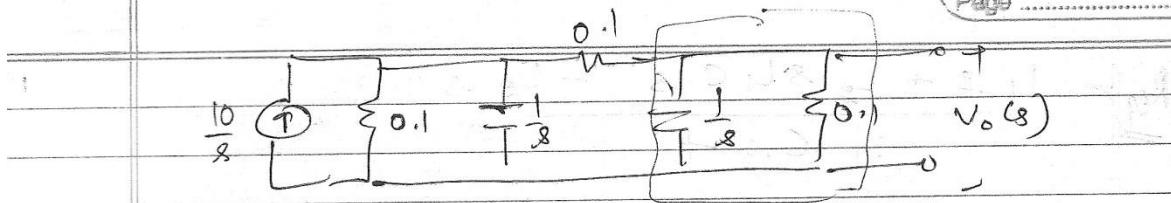


Assume both $\frac{1}{s}$ and 0.1 as load

$$\frac{0.1 \times \frac{1}{s} + 0.1}{0.1 + \frac{1}{s}}$$

$$\frac{0.1 + 0.1}{0.18 + 1} = \frac{\frac{0.1}{s}}{\frac{0.18 + 1}{s}}$$
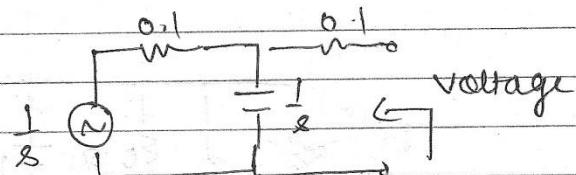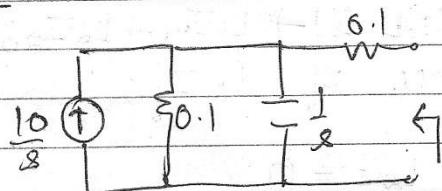
$$Z_{eq} = \frac{0.018 + 0.2}{0.18 + 1}$$




$$V_{th} = \frac{1 \times \frac{1}{s}}{\frac{1 + 0.1}{s}} = \frac{\frac{1}{s}}{\frac{1 + 0.18}{s}}$$

$$V_{th} = \left(\frac{1}{0.18 + 1} \right) \frac{1}{s}$$

$$V_o(s) = \frac{0.1}{1+0.1s} \left(\frac{1}{s(0.1s+1)} \right) \frac{\frac{0.1}{1+0.1s}}{\frac{0.1}{1+0.1s} + \frac{0.01s+0.2}{0.1s+1}} = \frac{0.1}{0.1+0.01s+0.2} \left(\frac{1}{s(0.1s+1)} \right)$$
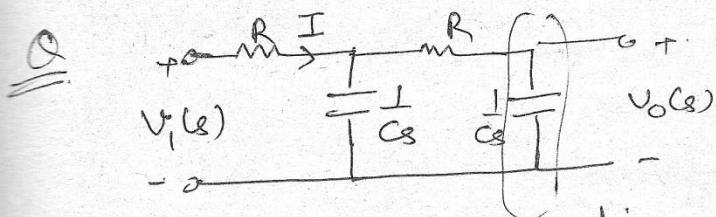
$$V_o(s) = \left(\frac{0.1}{0.01s+0.3} \right) \left(\frac{1}{s(0.1s+1)} \right)$$



All cap.
Initially
uncharged.

find $\frac{V_o(s)}{V_i(s)}$
Angle of $\frac{V_o(s)}{V_i(s)}$
 $= \pi$
at which $V_o(s) = 0$

Let $V_o(s) = 1$
 $I \times \frac{1}{C_s} = 1$
 $I = C_s$


$\frac{1}{C_s} + R + \frac{1}{L} = \infty$



Find mag. of $F(s)$ at this freq.

$$\frac{R \times \frac{1}{C_s}}{R + \frac{1}{C_s}} = \frac{R}{RC_s + 1}$$
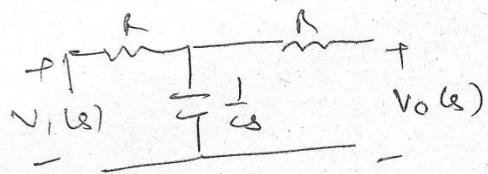
$$\frac{\frac{R}{RC_s + 1} + R}{R + R^2 C_s + R} = \frac{R}{RC_s + 1}$$



$$V_{TH} = \frac{\frac{1}{Cs} V_i(s)}{\frac{1}{Cs} + R} = \underline{\underline{\frac{\frac{1}{Cs} V_i(s)}{1 + R C_s}}}$$

$$V_o(s) = \frac{\frac{1}{Cs} \cdot V_o(c)}{\frac{1}{Cs} + R_{TH}}$$

$$V_o(s) = \frac{\frac{1}{Cs} \cdot \cancel{V_o(s)} \cdot \frac{1}{1 + R s} V_i(s)}{\frac{1}{Cs} + \frac{2R + R^2 C_s}{R C_s + 1}}$$

$$\begin{aligned} \frac{V_o(s)}{V_i(s)} &= \frac{\frac{1}{Cs}}{R C_s + 1 + C_s (2R + R^2 C_s)} \\ &= \frac{1}{R C_s + 1 + C_s (2R + R^2 C_s)} \left[\frac{1}{1 + R s} \right] \end{aligned}$$


Now put $s = j\omega$

$$\text{then } \frac{V_o(s)}{V_i(s)} = a + jb$$

$$\tan^{-1} \frac{b}{a} = \pi$$

$$\omega = ?$$

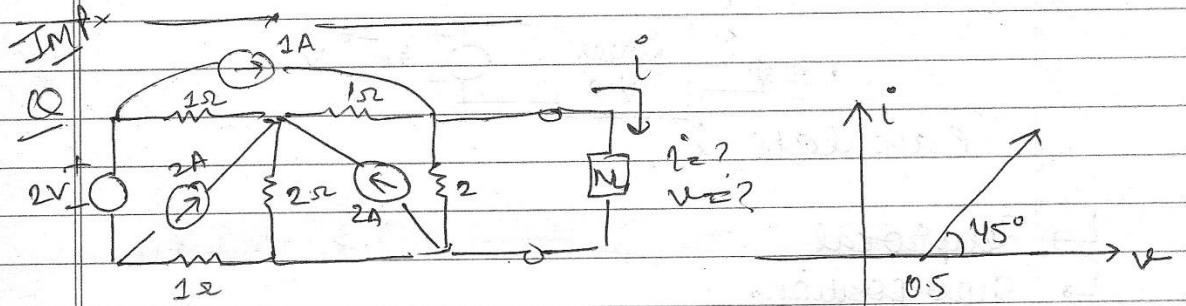
* Dont use theorems in Time domain
especially in Transient Analysis.



find i and v

$$i = \begin{cases} 0 & v \leq 0.5 \\ v - 0.5 & v > 0.5 \end{cases}$$

$$v_{TH} = i R_o = v$$

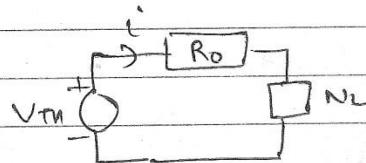


for $v \leq 0.5$

$$v_{TH} = v$$

If $v > 0.5$

then no soln in this reg.

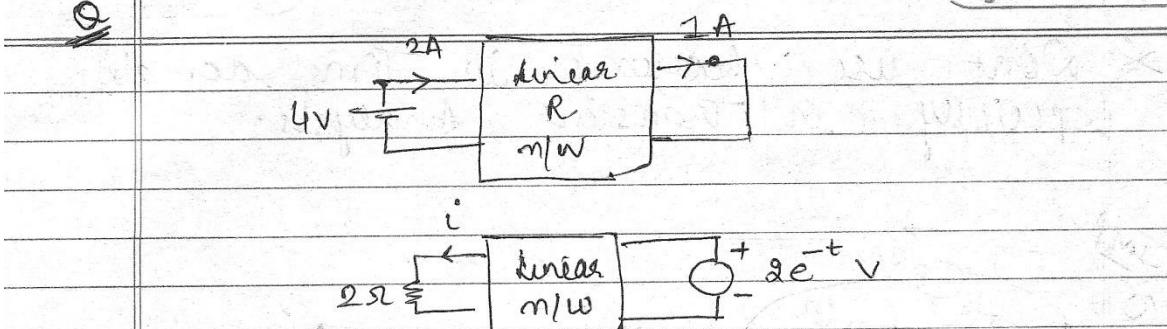


calculate i


- ↳ Reciprocal
- ↳ Superposition
- ↳ Substitution

5/4/2014

UNIVERSITY OF MUMBAI
Date
Page

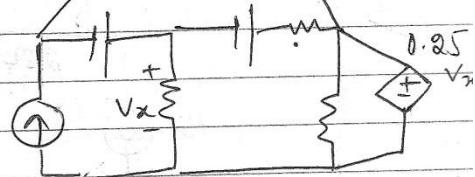

Maximum Power Transfer Theorem

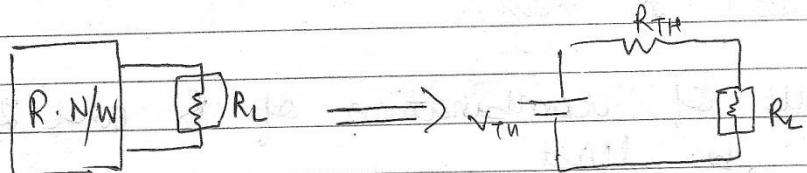

$$P_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L \quad \gamma = \frac{V_{TH}^2}{(R_{TH} + R_L)^2} R_L$$

$$\frac{dP}{dR_{TH}} = 0$$

$$(R_{TH} + R_L)^2 V_{TH}^2 = V_{TH}^2 R_L$$

$$2(R_{TH} + R_L)$$

$$R_{TH} = R_L$$


Internal parameters of n/w delivering power to fixed load R_L is maximum.

$$R_{TH} = R_L \quad \text{for } \frac{dP}{dR_L}$$

↓ condition on well known fixed N/W to variable load.

When $R_{TH} = 0$ P_L maximum if R_{TH} value is ∞ P_L minimum.

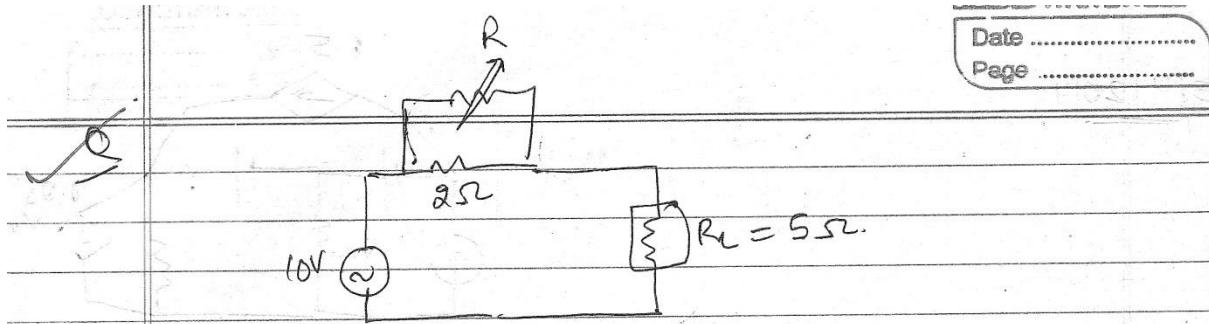$R_L = R_{TH}$ P_L max. if R_L varies.
 $R_L = 0, \infty$ P_L min.



find value of R so that power delivered to load to max.


Sol: Value of combination of R and 2 must be least.

$$R_{eq} = \frac{2R}{R+2} \therefore | R=0 |$$

$$R_{eq} = 0$$

then power transfer max.

of Reactive N/W

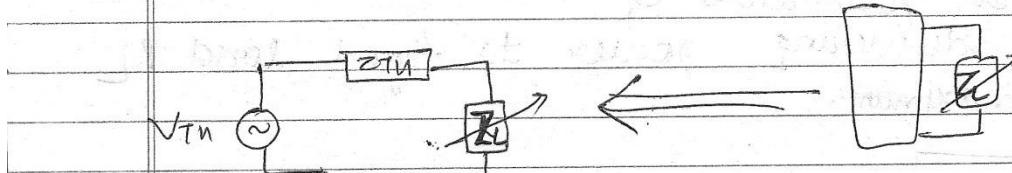

$$Z_L = R_L + jX_L$$

$jI_L^2 X_L$ → Reactive power represents stored energy in reactive element

$$I_L^2 R_L \rightarrow \text{Apparent power}$$

$$\text{Active} = V_L I_L \cos \phi$$

We have to maximise active power.

$$I_L^2 R \cos \phi$$

$$P_L = V_L I_L \cos \phi$$

$$= \left(\frac{V_{TH}}{Z_{TH} + Z_L} \right)^2 Z_L \cos \phi$$

$$\frac{dP_L}{dZ_L} = 0$$


we get

$$Z_L = Z_{TH}^*$$


practically

Three Phase Circuit


\uparrow available

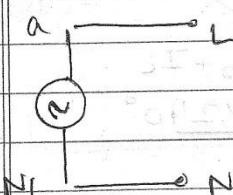

Single ϕ generator

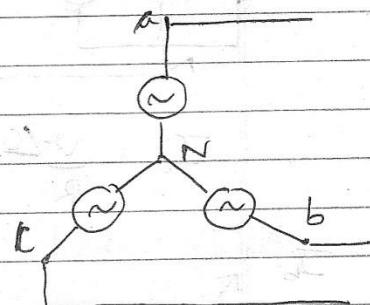

3 ϕ generator

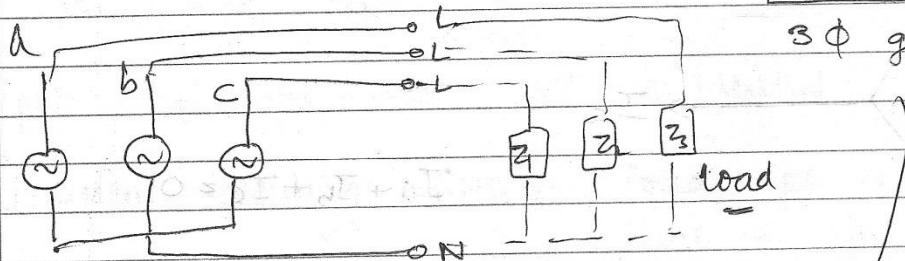

3 ϕ four wire system

→ Balanced 3 ϕ Supply

voltage generated by generator 1

$$V_{RMS}(a) = V_{RMS}(b) = V_{RMS}(c)$$


phase diff b/w voltage signal generated by each phase is 120° .

$$V_a 10^\circ, V_b 120^\circ, V_c 240^\circ$$

Balanced load


$$\text{when } Z_1 = Z_2 = Z_3$$

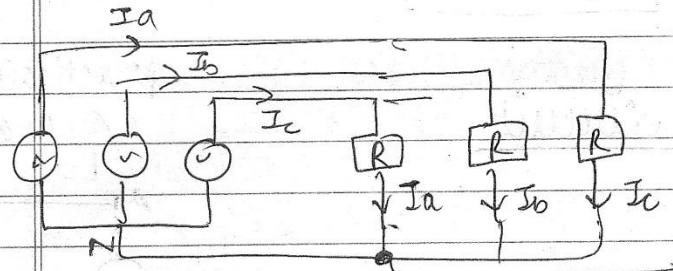means $Z_1 = R + jX_1$, $Z_2 = R - jX_1$ are
not equal because
there is no modulus.



$$I_a = \frac{\sqrt{3}V}{R}, \quad I_b = \frac{\sqrt{3}V}{R}, \quad I_c = \frac{\sqrt{3}V}{R}$$

Mag. of all same

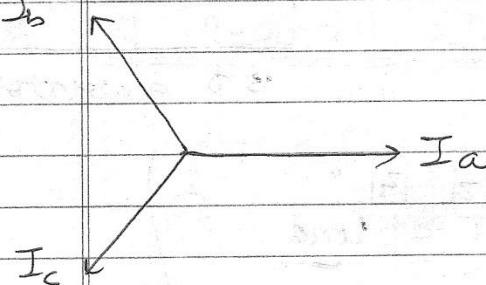


$$I_a + I_b + I_c = 0$$


If exactly balanced type of supply & load are present, then fourth wire N can be removed.

Thus balanced 3ϕ , 3 wire supply.

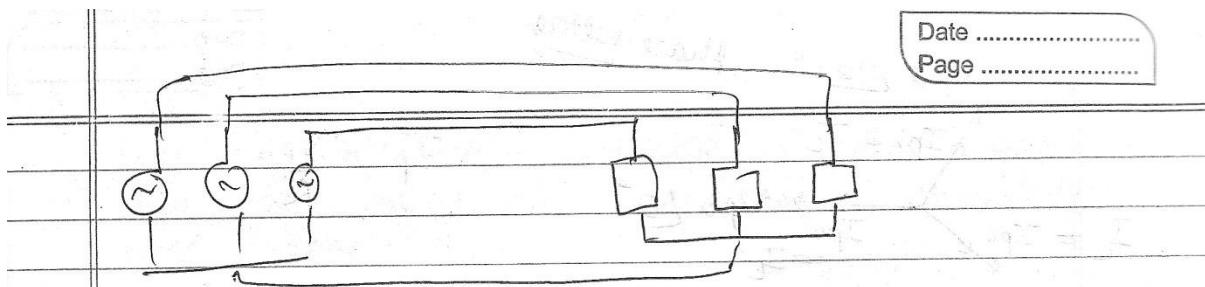If load not equal, then current will flow back, distorting whole N/W making even source unbalanced.



Star connection (either 3 or 4 wire).

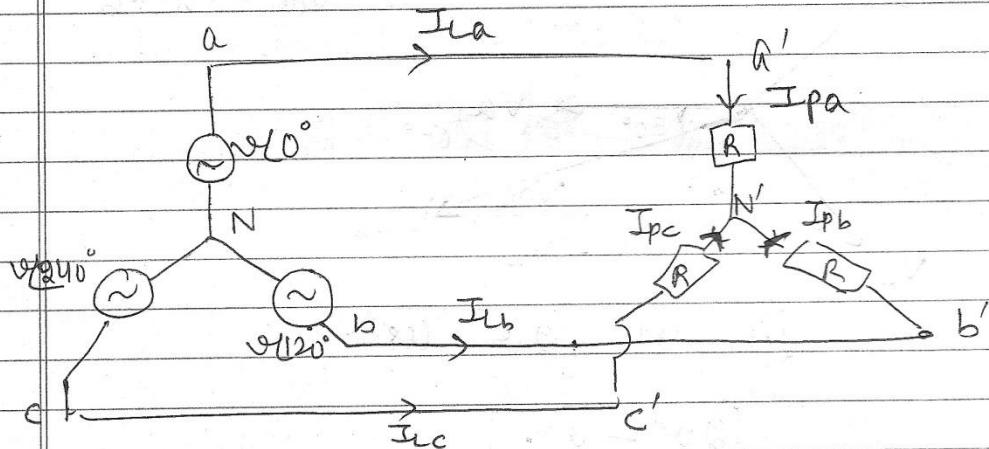

pot. diff b/w two lines — line voltage
 V_{ab} , V_{ac} , V_{bc}

pot. diff b/w two line to Neutral — phase voltage

current flowing through load — phase current
 " " " " " " " "

In this case

$$I_L = I_p.$$

If balanced load, even if it is reactive
 phase b/w currents remain same.

$$\text{if } I_{pa} 0^\circ, I_{pb} 1120^\circ, I_{pc} 240^\circ$$

$V_{pb} \angle 120^\circ$ phase voltage

$$I_{pb} = I_L$$


$$I_p = \frac{V_p}{R}$$

$$I_L = I_{pc} \quad I_{pa} = I_L$$

$$V_{pc} \angle 240^\circ$$

$$V_b$$

$$V_{ab} = V_a - V_b$$

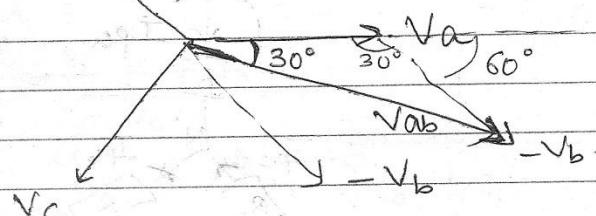


$$\sqrt{V_a^2 + V_b^2 + 2V_a V_b \cos 30^\circ}$$

$$\sqrt{2V_a^2 + V_b^2}$$

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

* Delta N/W

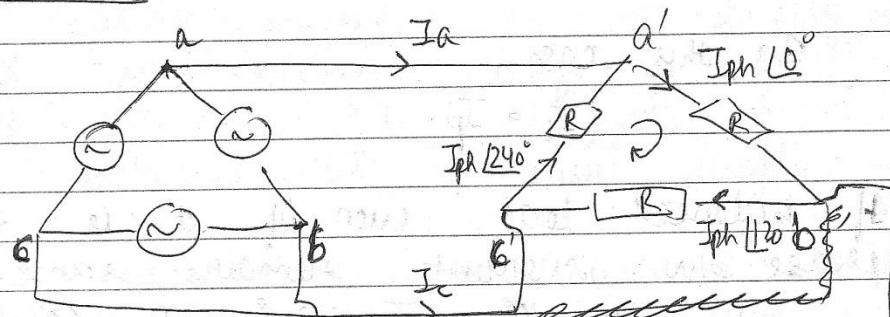

$$\text{In this } V_{ph} = V_L$$


$$I_b$$

Even if distortion created in this loop. ckt, then the remaining current circulates in load loop.

$$V_L = V_{ph}$$

$$I_a + I_{ph} \angle 240^\circ = I_{ph} \angle 0^\circ$$
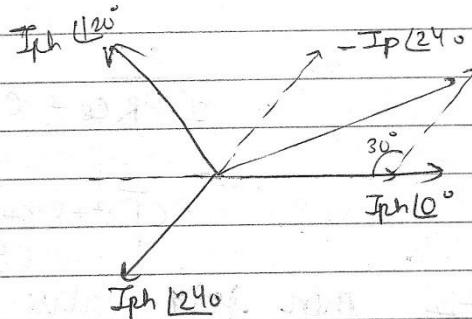
$$I_a = I_{ph} \angle 0^\circ - I_{ph} \angle 240^\circ$$



$$I_L = \sqrt{3} I_{ph}$$

Stage Ckt

$$\text{Power/phase} = V_{ph} I_{ph}$$

$$\text{Total power} = 3 V_{ph} I_{ph}$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L$$

$$= \sqrt{3} V_L I_L$$

Delta Ckt

$$V_{ph} I_{ph}$$

$$3 V_{ph} I_{ph}$$


$$\frac{3 V_L}{\sqrt{3}} I_L$$

$$\sqrt{3} V_L I_L$$

$$\text{Total active power} = \sqrt{3} I_L V_L \cos \phi$$

6/4/2014

Network function

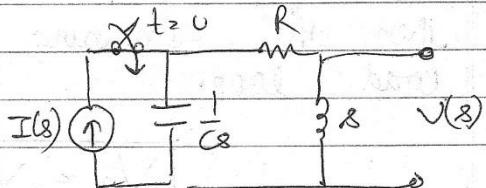Q find $\frac{V(s)}{I(s)}$ 

$$V(s) = \left[\frac{\frac{1}{Cs}}{\frac{1}{Cs} + R + s} \right] I(s) \cdot s$$

$$\frac{V(s)}{I(s)} = \frac{\frac{1}{Cs} \times s}{\frac{1}{Cs} + R + s^2} = \frac{s}{1 + RCs + Cs^2}$$

$$= \frac{s}{Cs^2 + Rs + 1}$$

Q If poles are -2, -1, then find value of R, C

$$(s+2)(s+1) = 1 + RCs + Cs^2$$

$$s^2 + 3s + 2 = 1 + RCs + Cs^2$$

$$C = 1 \quad s^2 + 3s + 2 = s^2 + Rs + 1$$

$$R = 3$$

$$R = 3$$

$$\frac{1}{C} = 2$$

$$C = \frac{1}{2}$$

Q If $i(t) = 2$ (square wave, 1 sec period) then find $v(t)$

$$j(t) = u(t) - u(t-1)$$

$$= \frac{1}{s} - \frac{e^{-s}}{s}$$

$$Z(s) = \frac{2s}{s^2 + 3s + 2}$$

$$N(s) = \frac{2s}{s^2 + 3s + 2} \left[\frac{1}{s} - \frac{e^{-s}}{s} \right].$$

Result $v(t) = 10 \left[e^{-t} - e^{-2t} \right] u(t) - 10 \left[e^{-(t-1)} - e^{-2(t-1)} \right] u(t)$

<u>Q</u>	<u>v(t)</u>	<u>j(t)</u>	<u>I(t)</u>	<u>Linear 1 port N/W</u>	<u>Here system was assumed to be initially relaxed</u>
	$6v(d)$	0	$v(t)$		
	$\sin(t)$	$0.6 \sin t + 0.8 \cos t$			
	$\sin 2t$?			

$$\frac{I(s)}{V(s)} = 0.6 \frac{\sin t + 0.8 \cos t}{\sin(t)}$$

$$= 0.6 \frac{1}{s^2 + 1} + 0.8 \frac{s}{s^2 + 1}$$

$$H(s) = 0.6 + 0.8s$$

$$I(s) = H(s) \cdot V(s)$$

$$= (0.6 + 0.8s) \left[\frac{9}{s^2 + 4} \right]$$

$$= \frac{1.2}{s^2 + 4} + \frac{1.6s}{s^2 + 4}$$

$$= 0.6 \sin 2t + 0.8 \cos 2t$$

e If poles of $\gamma(s) = s - 1 \pm j1$ and 2 zeroes are present. find response corresponding to $\sin 2t$.

$$\frac{I(s)}{V(s)} = \frac{(s-z_1)(s-z_2)}{(s+1+j1)(s+1-j1)}$$

i) $S_0 = 0$ [steady state]. for first case

$$0 = \frac{z_1 z_2}{P_1 P_2} | .6 V$$

$$\boxed{z_1 z_2 = 0}$$

for this ques -

<u>v(t)</u>	<u>i(t) (steady state)</u>
6 V	0
$\sin t$	$0.6 \sin t + 0.8 \cos t$
$\sin 2t$?

iii) Complex $V = ? j1$

$$\sin(t+\phi) = \frac{(j-z_1)(j-z_2)}{(j+1+j)(j+1-j)} | \sin t$$

$$\frac{(j-z_1)(j-z_2)}{(2j+1)}$$

$$\begin{cases} a+jb \\ a-jb \end{cases} \begin{cases} \text{only when zeroes are complex} \end{cases} \begin{cases} \frac{(j-(a+jb))(j-(a-jb))}{(2j+1)} \end{cases}$$

$$\frac{(j(1-b) - a)}{(2j+1)} \left(\sqrt{j(1+b) - a} \right) \tan^{-1}$$

$$\frac{\sqrt{(1-b)^2 + a^2}}{\sqrt{4+1}} \quad \sqrt{(1+b)^2 + a^2}$$

$$\frac{\sqrt{1+b^2 - 2b + a^2}}{\sqrt{5}} \quad \sqrt{1+b^2 + 2b + a^2}$$

$$Z_1 Z_2 = 0$$

$$a^2 + b^2 = 0$$

$$j \cdot e \quad a = b = 0$$

$$\text{so } Z_1 = Z_2 = 0$$

$$Y(s) = \frac{s^f}{(s-p_1)(s-p_2)}$$

$$\frac{-1 - jZ_1 - jZ_2 + Z_1 Z_2}{2j+1}$$

$$Z_1 Z_2 = 0$$

$$\frac{-1 - j(Z_1 + Z_2)}{2j+1} \mid \text{Sum t}$$

Now let $Z_1 = a_1 + jb_1$
 $Z_2 = a_2 + jb_2$

$$\frac{-1 - j(a_1 + jb_1 + a_2 + jb_2)}{2j+1}$$

$$\frac{-1 - j(a_1 + a_2) + b_1 + b_2}{(2j+1)} = \frac{\sqrt{(b_1 + b_2 - 1)^2 + (a_1 + a_2)^2}}{\sqrt{5}}$$

One zeroes are 0 & -2

MBD WRITEWELL

Date

Page

$$\tan^{-1} - \frac{(a_1 + a_2)}{(b_1 + b_2 - 1)} = \tan^{-1} 2$$

$$z_1 z_2 = 0 \rightarrow \text{means } z_1 = 0 \\ (a_1 + j b_1)(a_2 + j b_2) = 0$$

$$a_1 a_2 + j a_1 b_2 + j b_1 a_2 - b_1 b_2 = 0$$

$$(a_1 a_2 - b_1 b_2) + j(a_1 b_2 + a_2 b_1) = 0$$


~~$$j(j - z_2) = -\frac{1 - j z_2}{1 + 2j}$$~~

$$= -\frac{(1 + j z_2)}{1 + 2j} = 0.6 \sin t + 0.8 \cos t$$

$$z_2 = a + jb$$

convert in complex

then compare.

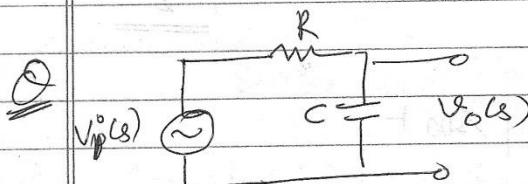


$$\frac{V_{op}(s)}{V_i(s)} = \frac{\frac{1}{Cs}}{\frac{1}{sR} + \frac{1}{L}} = \frac{1}{1 + sCR}$$


$$H(j\omega) = \frac{1}{1 + j\omega CR}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega CR)^2}}$$

$$|H(j\omega)| = -\tan^{-1} \omega CR$$

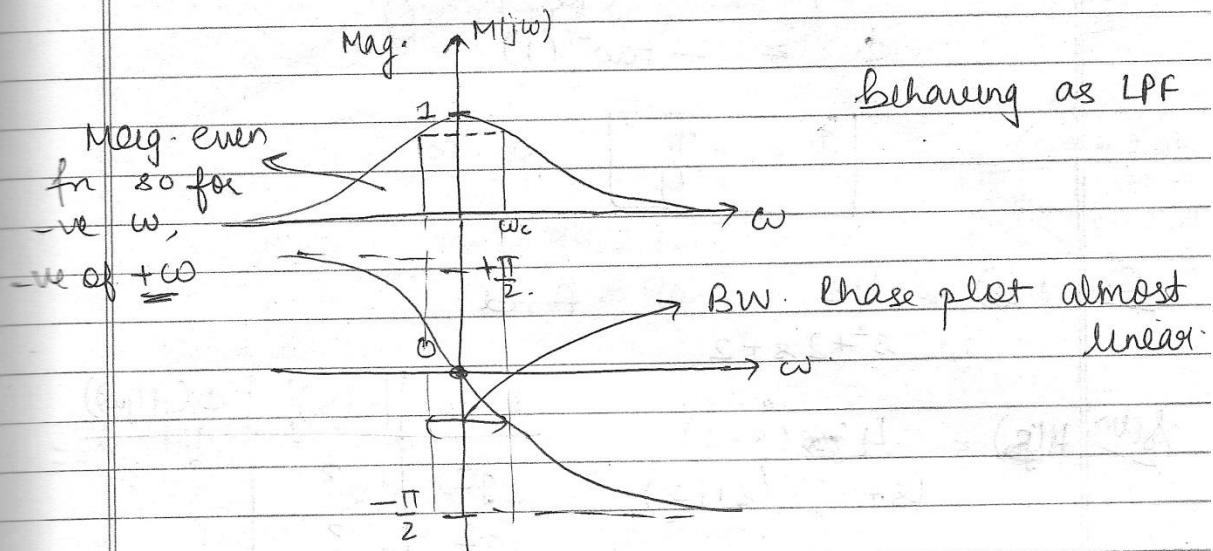

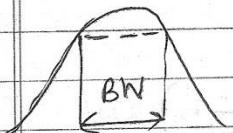Cutoff ω_c - ω at which mag. reduces by $\frac{1}{\sqrt{2}}$



- * If IP contains ω from $-\omega_c$ to ω_c approx. Then shape of waveform will be unaltered.
- If it goes beyond the linear reg. of phase curve, then the shape will be distorted by significant amount.

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1+(\omega CR)^2}} \quad \text{Phase at } \omega_c$$

$$1 + \omega_c^2 C^2 R^2 = 2$$

$$\frac{1}{2} = \frac{1}{1 + \omega_c^2 C^2 R^2}$$

$$\omega_c = \frac{1}{RC}$$

$$= -\tan^{-1} \left(\frac{1}{R} \times R \right)$$

$$\phi = -\tan^{-1}(1)$$

$$\boxed{\phi = -\frac{\pi}{4}}$$

Q) $H(s) = \frac{4s}{s^2 + 2s + 2}$ find

Solve

$$H(s) = \frac{4(j0)(s-0)}{(s+1+j)(s+1-j)}$$

$$H(s) = \frac{4(j0-0)}{(j0+1+j)(j0+1-j)}$$

$s(jw)$	$ H(jw) $	$\phi(H(jw))$
$j0$?	?
$j2$?	?
$j0$?	?

$$\text{Mag} = 0$$

$$\tan^{-1} \frac{0}{0} - \tan^{-1} \frac{1}{1} - \tan^{-1} \left(\frac{-1}{1} \right)$$

$$90 - 45 + 45$$

$$90^\circ$$

(ii)

$$\frac{4(j2-0)}{(j2+1+j)(j2+1-j)}$$

$$\text{Mag}$$

$$\frac{2 \times 4}{\sqrt{10} \sqrt{2}}$$

$$90 - \tan^{-1} 3 - 45$$

$$45 - \tan^{-1} 3$$

$$= 1 - 26.8$$

$$\frac{8}{\sqrt{20}}$$

$$= 1.78$$


(iii) $j(\infty)$

$$\frac{4(j\infty - 0)}{(j\infty + 1 + j)(j\infty + 1 - j)}$$

$$\lim_{\infty} \frac{\infty}{\infty^2} =$$

$$\lim_{\infty} \frac{4 \cdot \infty}{\infty \cdot \infty} = 0$$
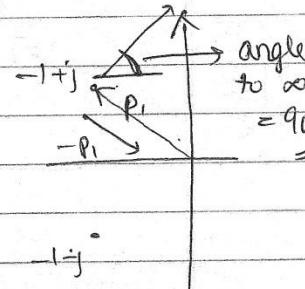
$$\text{Phase } 90^\circ - 90^\circ - 90^\circ = 90^\circ$$



$$\Rightarrow H(s) = \frac{4s}{s^2 + 2s + 2}$$

$$\frac{4j(0)}{0 + j0 + 2} = \frac{4j0}{2} = 2j(0)$$

neglected bcoz it has real part

Mag = 0
Phase 90°

$$H(s) = \frac{4j(\infty)}{-\infty + 2j\infty} \quad \tan^{-1} \frac{\infty}{\infty} \quad \text{undeterminate form}$$

\therefore Do it graphically


Q. $H(s) = \frac{4s}{s^2 + 2s + 2}$

$$H(j\omega) = \frac{4j\omega}{(j\omega)^2 + 2(j\omega) + 2} = \frac{4j\omega}{-\omega^2 + 2j\omega + 2}$$

$$M(j\omega) = \frac{4\omega}{\sqrt{(2-\omega^2)^2 + (2\omega)^2}} = \frac{4}{\sqrt{4 + \left(\frac{2}{\omega} - \omega\right)^2}}$$

$$\phi(j\omega) = \frac{\pi}{2} - \tan^{-1} \left(\frac{2\omega}{2-\omega^2} \right)$$
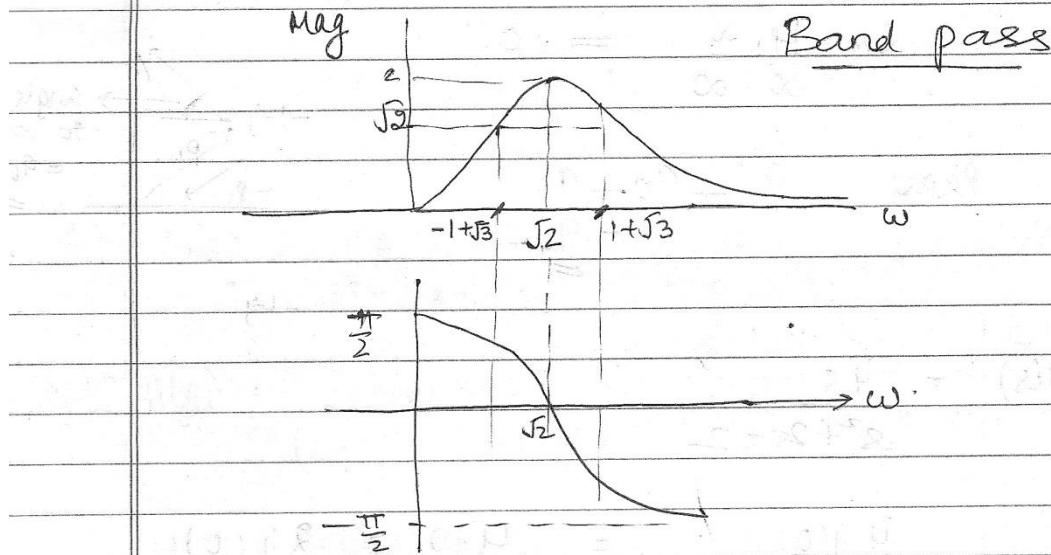
$$\phi(j\omega) = -\tan^{-1} \left(\frac{\omega-2}{2\omega} \right)$$



$$M_{\max} = 2$$

$$\frac{2}{\sqrt{2}} = \sqrt{2}$$

At which ω mag = $\sqrt{2}$

$$\sqrt{2} = \sqrt{4}$$

$$\sqrt{4 + \left(\frac{2}{\omega} - \omega\right)^2}$$

$$4 = \frac{16}{4 + \left(\frac{2}{\omega} - \omega\right)^2} \quad \text{if } \Rightarrow \frac{4}{\sqrt{4 + \left(\frac{2}{\omega} - \omega\right)^2}}$$

$$4 + \left(\frac{2}{\omega} - \omega\right)^2 = 8$$

$$\left(\frac{2}{\omega} - \omega\right)^2 = 4$$

$$\frac{2}{\omega} - \omega^2 = 2$$

other roots we
on side
 $\pm i\sqrt{3}$

$$2 - \omega^2 = 2\omega$$

$$2\omega + \omega - 2 = 0$$

$$\omega + 2\omega - 2 = 0$$

$$(2)^2 - 4 \times 1 \times (-2)$$

$$4 + 8 = 12 = 2\sqrt{3}$$

$$\begin{array}{r} 2 \\ \times 2 \\ \hline 2 \\ 2 \\ \hline 3 \\ 3 \\ \hline 1 \end{array}$$

$$\frac{-2 \pm 2\sqrt{3}}{2}$$

$$\boxed{-1 \pm \sqrt{3}}$$

find phase at cut off freq.

$$\tan^{-1} \left(\frac{(1+\sqrt{3})^2 - 2}{2(1+\sqrt{3})} \right)$$

$$= \tan^{-1} \frac{1+3+2\sqrt{3}-2}{2+2\sqrt{3}}$$

$$= \tan^{-1} \left(\frac{2+2\sqrt{3}}{2+2\sqrt{3}} \right)$$

$$= \tan^{-1}(1) = -\frac{\pi}{4}$$

$$\text{for } -1 + \sqrt{3} = \frac{\pi}{4}$$

$$H(s) = (s^2 + \omega_0^2) F_1(s)$$

$$H(s) = \underbrace{(s+j\omega_0)(s-j\omega_0)}_{\text{Addn of zeroes.}} F_1(s) \nearrow k(\theta)$$

$$(j\omega + j\omega_0)(j\omega - j\omega_0)$$

$$k(\theta) (\omega + \omega_0)/90^\circ (\omega - \omega_0)/-90^\circ$$

Total mag & phase $\frac{k(\omega + \omega_0)(\omega - \omega_0)}{[k(\omega^2 - \omega_0^2)]} \angle \theta$


This is applicable only when $0 < \omega < \omega_0$.
When $\omega > \omega_0$.

$$F(s) = (s - j\omega_0)(s + j\omega_0)$$

$$= k \omega (s - \omega_0)^{-1} (s + \omega_0)^{-1} \quad (9.0)$$

$$= k (\omega^2 - \omega_0^2)^{-1} e^{j180^\circ} \quad (9.0+180)$$


$M(j\omega)$

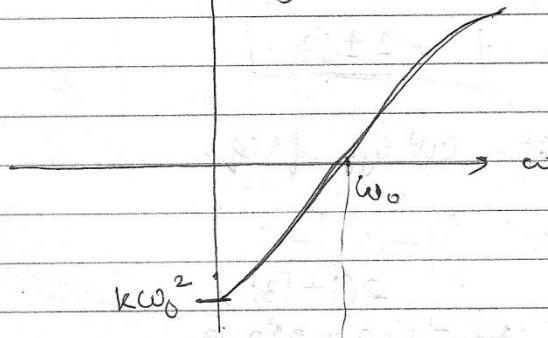

$+180^\circ$ phase shift


Thus there is change from (-) to (+) in mag.

$\Phi(j\omega)$

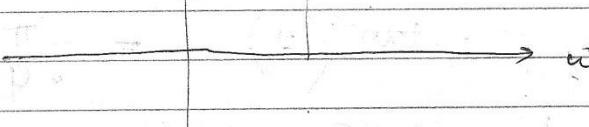

At $\omega = \omega_0$ indeterminate phase otherwise upper value.

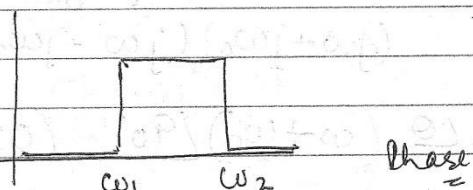C $\frac{s^2 + \omega_1^2}{s^2 + \omega_2^2} = H(s)$ Mag. & phase plot
 $\omega_1 < \omega_2$




$$M(j\omega) = \frac{\omega_1^2 - \omega^2}{\omega_2^2 - \omega^2}$$

$\frac{(j\omega)^2 + \omega_1^2}{(j\omega)^2 + \omega_2^2} \quad \frac{\omega_1^2 - \omega^2}{\omega_2^2 - \omega^2} \quad \left. \begin{array}{l} \text{This is now real} \\ \text{fn i.e angle 0} \end{array} \right.$
but this is wrong.


$$H(j\omega) = \frac{(j\omega - j\omega_1)}{(j\omega - j\omega_2)} \frac{(j\omega - (-j\omega_1))}{(j\omega - (-j\omega_2))}$$
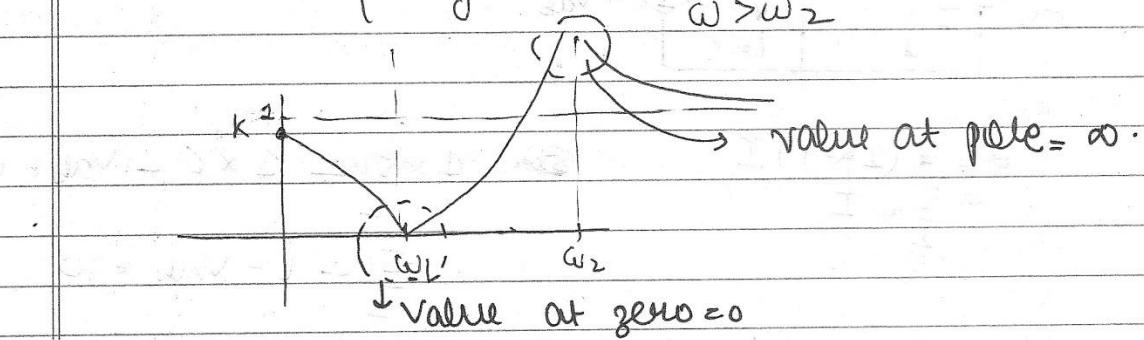
$$\angle H(j\omega) = \begin{cases} 0^\circ & 0 \leq \omega < \omega_1 \\ 0^\circ + 180^\circ & \omega_1 < \omega < \omega_2 \\ 0^\circ & \omega > \omega_2 \end{cases}$$



When plot mag., consider prod.

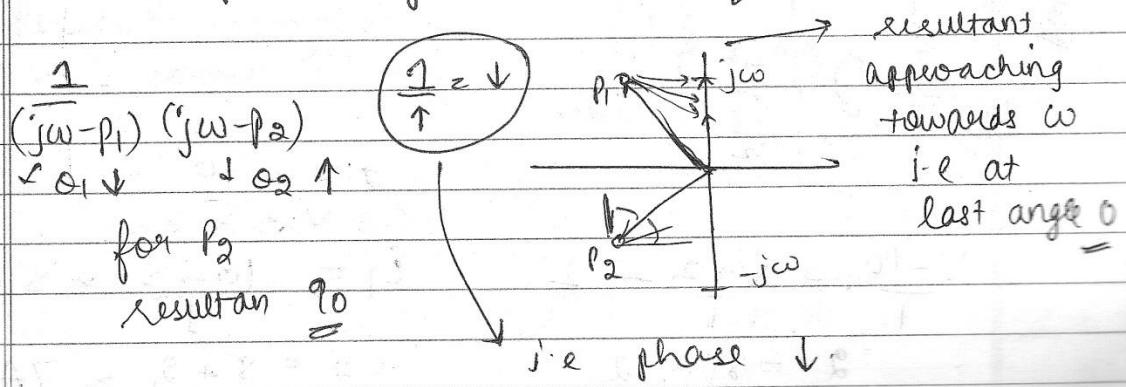Pole location exactly on j\omega axis, means max. magnitude, most selectivity, least B.W.
This is practically not realizable.



20/4/2014


30/8/2014

MBDWRITEWELL
Date ..
Page ..

steady state analysis of dc circuit


Single Tuned Circuit

Q

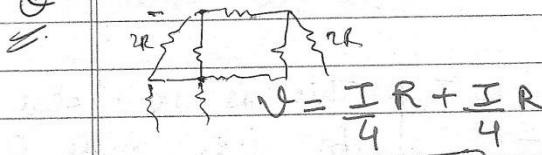


$$I_4 \approx 3\pi +$$

$$V = \frac{R}{2} I$$

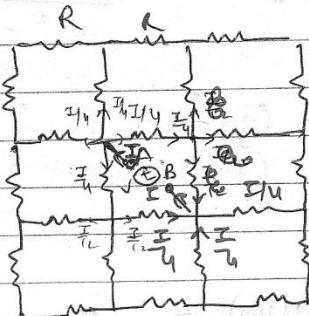

Identical nodes.

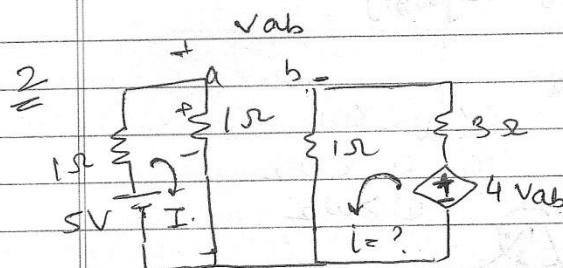

$$\textcircled{1} 5 = (1+1)I$$

$$\textcircled{2} \sum I = I$$


$$\textcircled{3} 1 \times 5 - 1 \times i - v_{ab} = 0$$

$$\textcircled{4} 5 - i - v_{ab} = 0$$

$$\textcircled{5} 4v_{ab} + 4i = 0$$

$$\frac{5}{2} = 2i$$

$$\frac{\sum}{4} = i$$

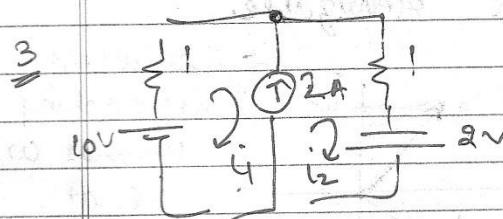

$$2V = 10$$


$$V = 5$$

$$\frac{V-10}{1} + \frac{V+2}{1} = 2$$

$$i_1 = \frac{10-5}{1} = 5A$$


$$2V - 8 = 2$$

$$i_2 = \frac{5+2}{1} = 7A$$

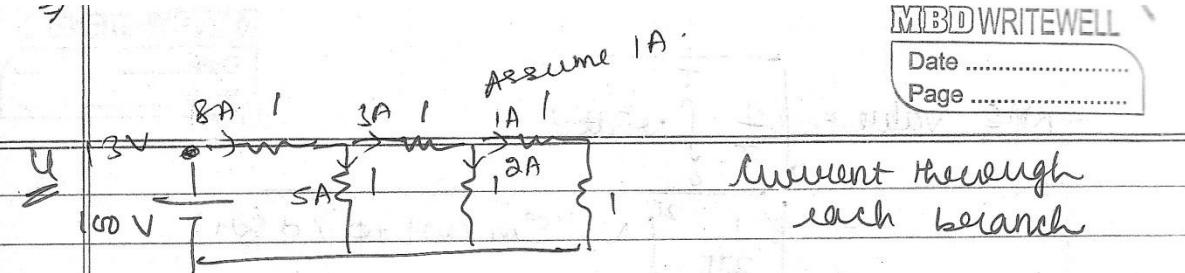

$$13V - 1A \quad \text{Principle of homogeneity.}$$

$$100V - 1 \times 100 = 100V \quad A$$

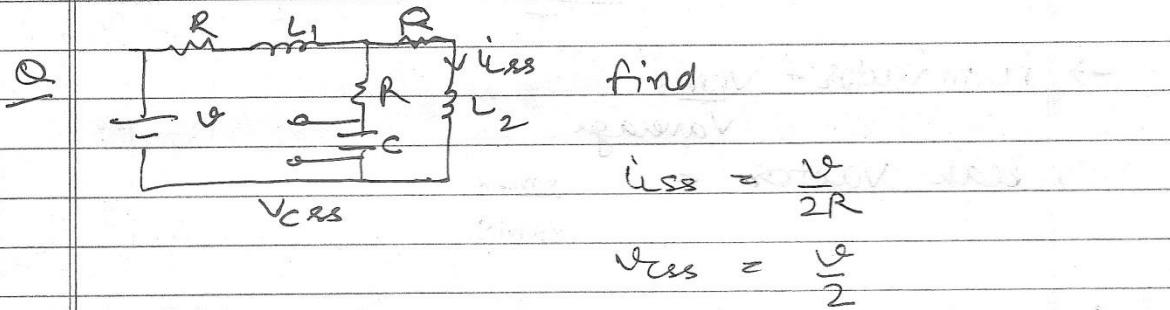


Steady state analysis of AC circuit

$$v(t) = V_m \sin \omega t$$

rotating with speed ω .


$$v_i(t) = V_m \sin(\omega t + \phi)$$
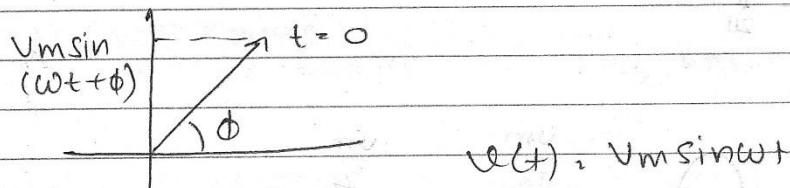
$$\begin{aligned} & V_m \sin \omega t \\ & \text{at } t=0 \\ & V_m \cos \omega t \end{aligned}$$



Phasor notation
i.e. in terms of \underline{RMS}

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

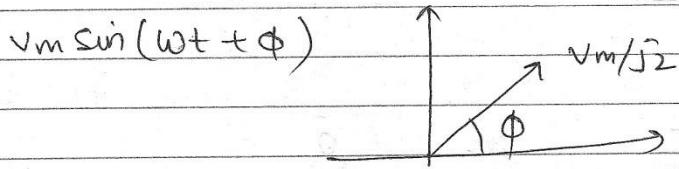


$$\rightarrow \text{RMS value} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_m^2 \sin(\omega t + \phi) d(\omega t)}$$

$$\rightarrow \text{Average value} = \frac{\int_0^T v dt}{T}$$

$$\rightarrow \text{Form vector} = \frac{V_{\text{RMS}}}{V_{\text{average}}}$$
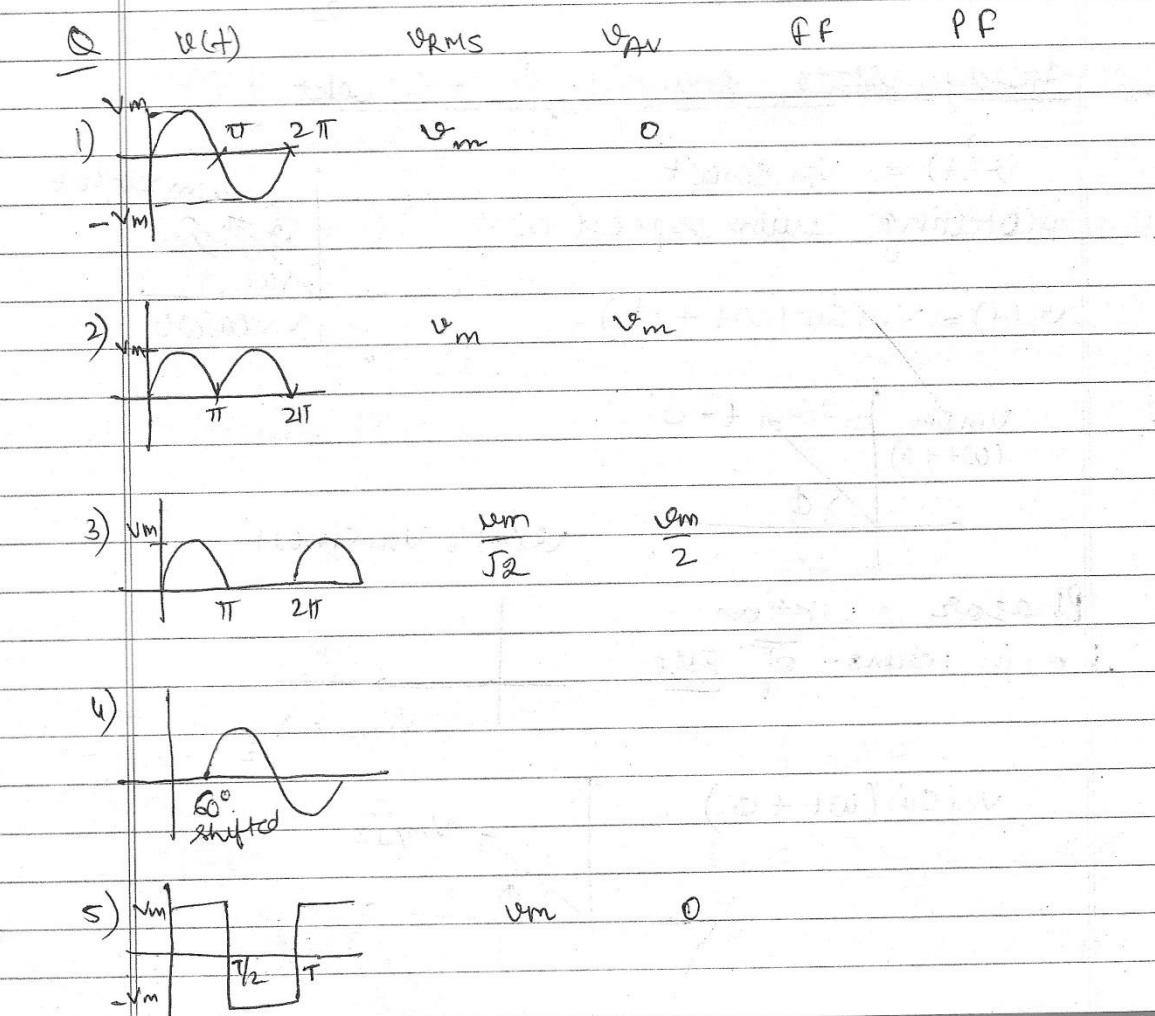
$$\rightarrow \text{Peak Vector} = \frac{V_{\text{max}}}{V_{\text{RMS}}}$$




$v(t)$

v_{RMS}

v_{AV}


6)

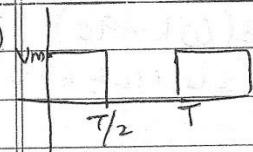


$$\frac{V_m}{\sqrt{2}}$$

$$\frac{V_m}{2}$$

7)

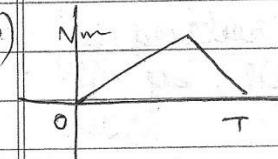

8)

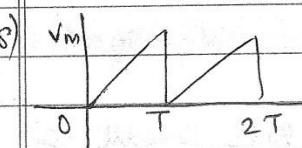


$$y = \frac{V_m}{T} t$$

$$\int_0^T \left(\frac{V_m t}{T} \right)^2 dt$$


$$= \int_0^T \frac{1}{T} \frac{V_m^2}{3} t^3 dt$$

$$= \frac{1}{T^3} \frac{V_m^2 T^3}{3} = \frac{V_m^2}{3}$$

9)

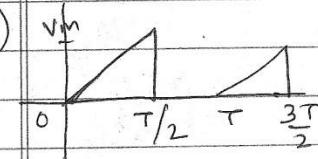

10)

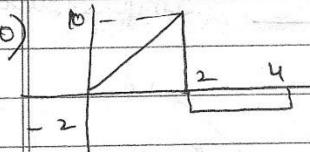

→ always expressed as RMS value.

$$\# v_i(t) = V_m \sin \omega t \quad v_a(t) = V_m \cos \omega t$$

$$v_i(t) = -j v_a(t)$$

$$v_a(t) = +j v_i(t)$$

$$v_i'(t) = V_m \omega \cos \omega t$$

$$= +\omega j v_i(t) = +j \omega V_m \sin \omega t$$

$$\sin \omega t = \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$$

$$\textcircled{*} \quad j \sin \omega t = j \left(\frac{e^{j\omega t} - e^{-j\omega t}}{2j} \right) = \frac{e^{j(\omega t + 90^\circ)} - e^{-j(\omega t + 90^\circ)}}{2j}$$


$$\cos(\omega t + 90^\circ) + i \sin(\omega t + 90^\circ) = \frac{\cos(\omega t + 90^\circ)}{2i} - \frac{i \sin(\omega t + 90^\circ)}{2i}$$

$$\rightarrow V_1' = j\omega v_1$$


$$\rightarrow V_2' = j\omega v_2$$

$$\rightarrow \int_{0}^{t} V_1(t') dt' = \frac{1}{j\omega} V_1(t)$$

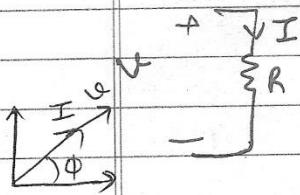j.e under steady stat
derivative replaced by $j\omega$
and integral by $\frac{1}{j\omega}$




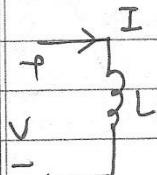$V = IR$. V = RMS value of
sineoidal source
No phase change
 $b/w V \& I$




$$V = L \frac{di}{dt} \quad j\omega I \cdot jX_L$$

$$i = \frac{v}{j\omega L}$$

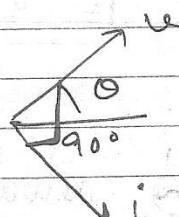


lagging type of n/w

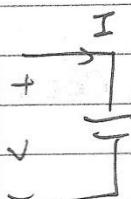


$$I = C \frac{dv_c}{dt}$$

$$i = j\omega C v_c$$

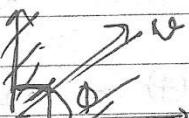


leading type of n/w

$$jX_C = \frac{1}{j\omega C} = -jX_C$$

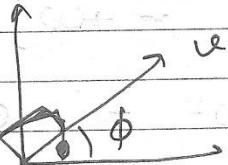

Take I as reference

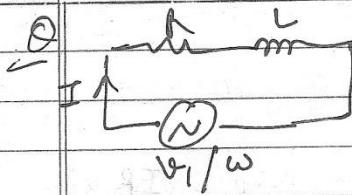

calculate voltage across R & L.

$$V_R = IR$$

$$V_L = j\omega L I$$

$$V_L = j\omega L I$$


$$V = V_R + V_L$$

$$V_R = IR \quad \phi = \tan^{-1} \frac{\omega L}{R}$$

Angle b/w V and I

$\cos \phi$ = power factor $0 < \cos \phi < 1$

$$Z = \frac{V}{I} = R + j\omega L$$

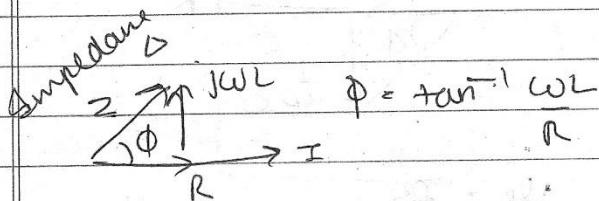

Total power


$$VI = V_R I + V_L I$$

$$P_s = I^2 R + j\omega L I^2$$

complex power = $P_{act.}$ + $j P_{react.}$ reactive power of inductor

$$S = P + j Q$$

Active power due to resistor

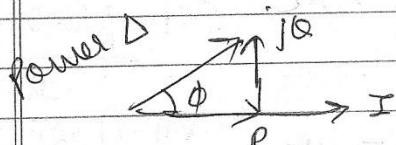


$$\phi = \tan^{-1} \frac{\omega L}{R}$$

$$\rightarrow P = |S| \cos \phi$$

$$\rightarrow Q = |S| \sin \phi$$

Only S = Magnitude


Current
Reference voltage

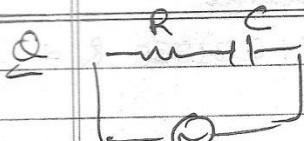

$$V = (R + j\omega C) I$$

$$V_C = -j \frac{I}{\omega C}$$



$$V_R = IR$$

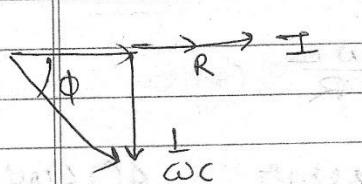

$$\tan^{-1} \frac{1}{\omega C} = \tan^{-1} \frac{1}{\omega CR}$$

+ heading NW.


$$Z = R - j \frac{1}{\omega C}$$

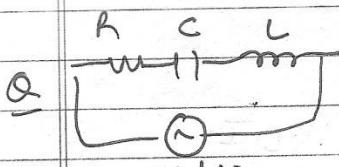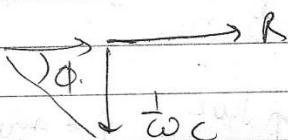

$$V_R = IR$$


$$V_L = j\omega L I$$

$$V_C = -j \frac{I}{\omega C}$$

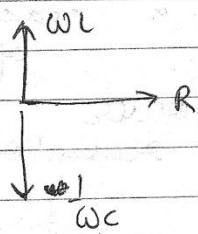

$$\tan^{-1} \left[\frac{\omega L - \frac{1}{\omega C}}{R} \right]$$

Assume $X_L > X_C$

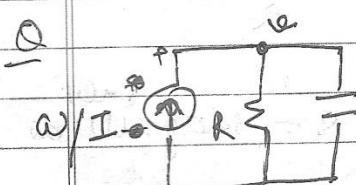


$$V_R = V_C = V$$

$$I = I_R + I_C$$

$$I = \frac{V}{R} + \frac{V \omega C}{j}$$

$$j\omega C V$$

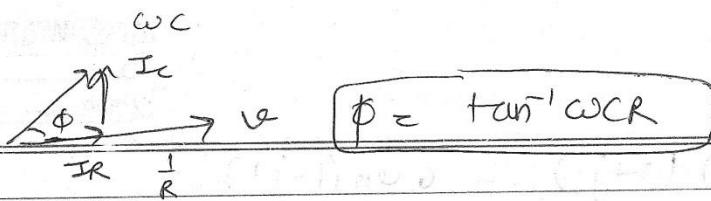Current Δ

In parallel ~~across~~ Z cannot be added directly so
Y.

$$Y = G + jB \quad G = \frac{1}{R} \quad B = \omega C$$


Angle b/w conductance & $\gamma \rightarrow jB$ Admittance ϕ

Admittance

$$\gamma \text{ and } G = \phi$$

$$S = VI \quad P = V \cdot I_R \quad Q = V I_C$$

$$S = P + jQ$$

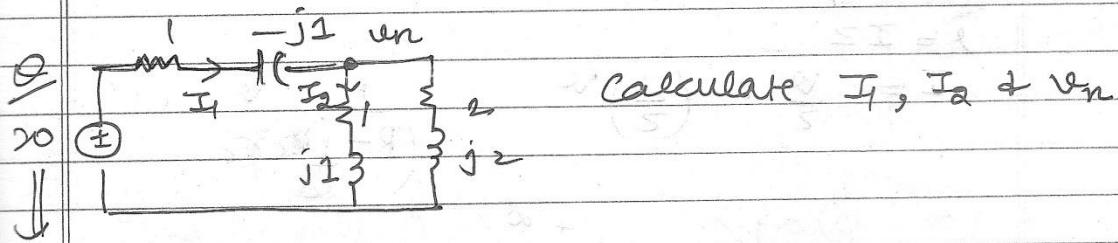

$$20\sqrt{2} \sin \omega t \quad \frac{V_n - 20}{1-j1} + \frac{V_n}{1+j1} + \frac{V_n}{2+j2} = 0$$

$$(V_n - 20)(1-j1)$$

$$+ \frac{V_n(1-j1)}{2}$$

$$+ \frac{V_n(2+j2)}{8}$$

$$\frac{(1-j1)(1+j1)(2+j2)}{4-(1+j1)} = \frac{-2\sqrt{2}(1+j1)}{4-(1+j1)}$$

$$4(V_n - 20)(1+j1) + 4V_n(1-j1) + 2V_n(1-j1)$$

$$2V_n(-j1) \quad \{ \quad 6V_n(1-j1)$$


$$4(v_n - 20)(1+j) + 6v_n(1-j) \\ 4(v_n + jv_n - 20 - 20j) + 6v_n - 6v_nj$$

$$10v_n - 2v_nj - 80 - 80j = 0$$

$$v_n(10 - 2j) = 80(1 + j)$$

$$v_n = \frac{80(1+j)}{(10-2j)} = \frac{80(1+j)}{2(5-j)}$$


$$v_n = 40 \frac{(1+j)}{(5-j)}$$

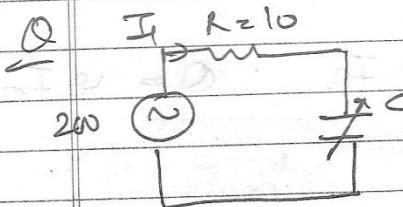


Plot locus of I_1

$$I = IZ$$
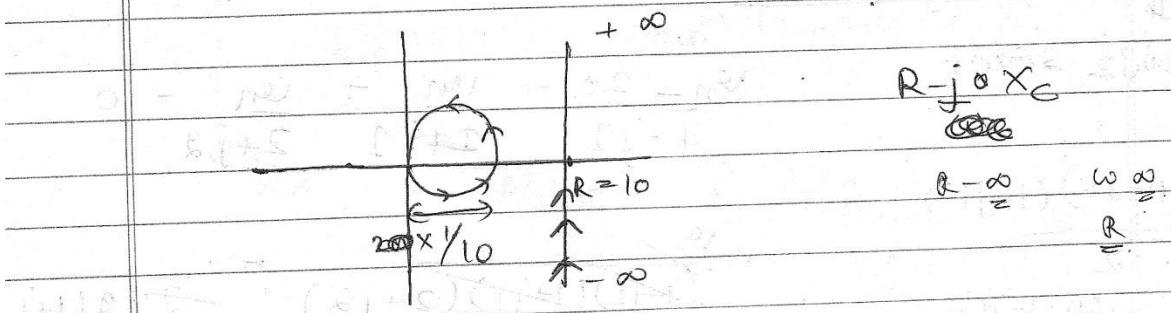
$$I = \frac{V}{Z} \cdot \left(\frac{1}{Z}\right)^V \cdot \frac{1}{(R-jX_C)}$$




$0 \rightarrow \infty$


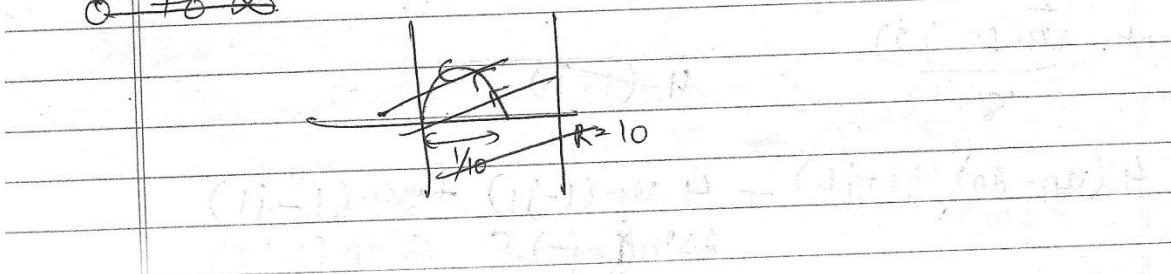


$$R - jX_C \rightarrow 0 \rightarrow \infty$$

movement from lower value to higher value

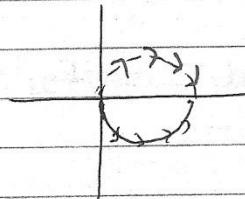

Ans 2

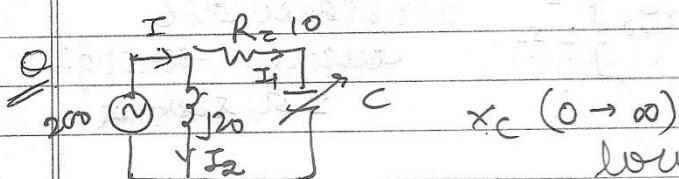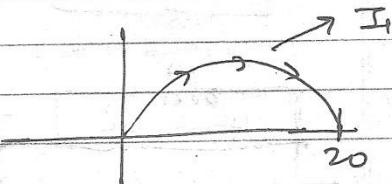



$$X_C (0 \rightarrow \infty)$$

Locus of I_2

Locus of I

$$I_2 = \frac{200}{j20} = -j10$$
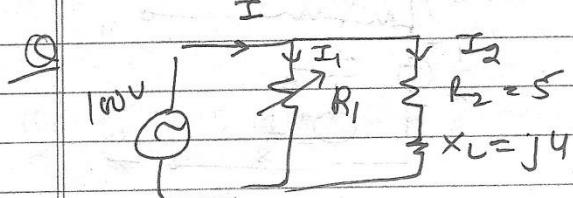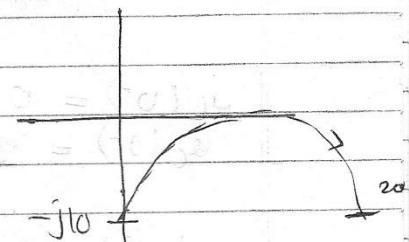
$$\begin{aligned} I &= I_1 + I_2 \\ &= -j10 + \frac{200}{10 + jX_C} \end{aligned}$$



$$R_1 \rightarrow (0 - \infty)$$

find locus of $I_1 + I$

$$I = I_1 + I_2$$


$$I_2 = \frac{100}{5 + j4}$$





$$I_1 = \frac{100}{R_1}$$

$$I = \left(\frac{1}{R_1}\right) 100$$

$$R_1 \rightarrow 0 \rightarrow \infty$$
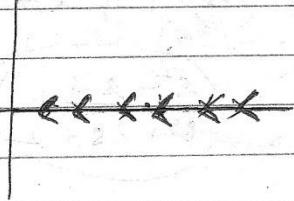
$$\frac{1}{R_1} \rightarrow \infty \rightarrow 0$$



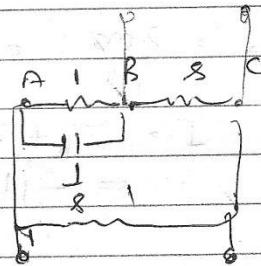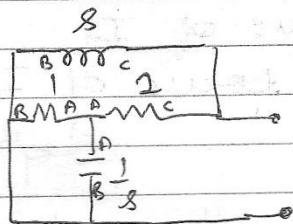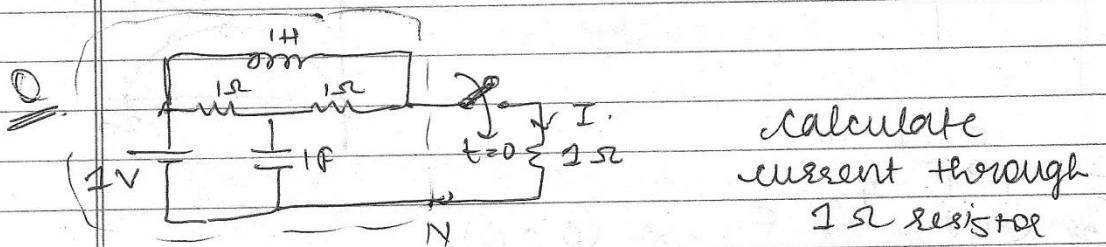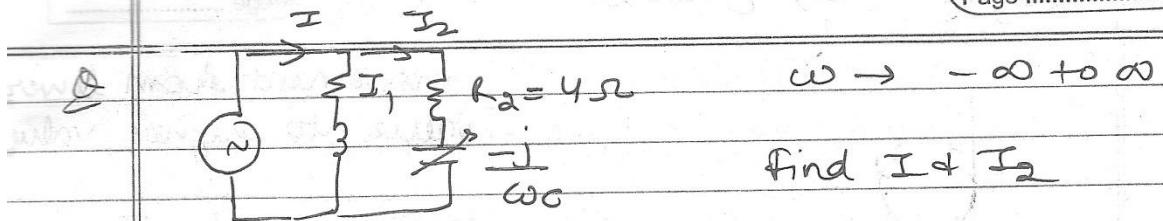


$$j_L(0^-) = 0$$

$$v_C(0^-) = 1$$

$$\frac{\frac{1}{8} \times 1}{\frac{1}{8} + 1} = \frac{\frac{1}{8}}{\frac{1}{8} + 1}$$

$$= \frac{1}{1+8}$$

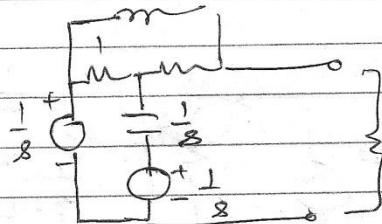

$$\frac{1 + 8(1+8)}{(1+8)} = \frac{1+8+8^2}{1+8}$$


$$\frac{(8^2 + 8 + 1)}{(8+1)} = \frac{8^2 + 8 + 1}{8^2 + 8 + 1 + 8 + 1}$$

$$\frac{8^2 + 8 + 1}{(8+1)} = \frac{8^2 + 8 + 1}{8^2 + 2 \cdot 8 + 2}$$

$$\frac{8^2 + 8 + 1}{8^2 + 2 \cdot 8 + 2} = \frac{8(8+2)}{8^2 + 2 \cdot 8 + 2}$$

$$V_{TH} = \frac{1}{2}$$


This N/W equivalent to

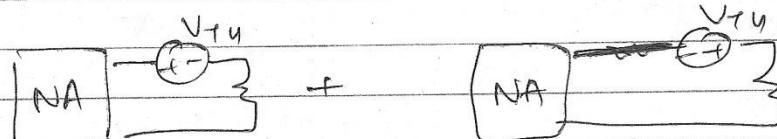

i.e. total voltage across switch = 0
when switch open

$$V_{SW} = V_{OC} = V_{TH}$$

Q Find $\underline{I}(s)$.

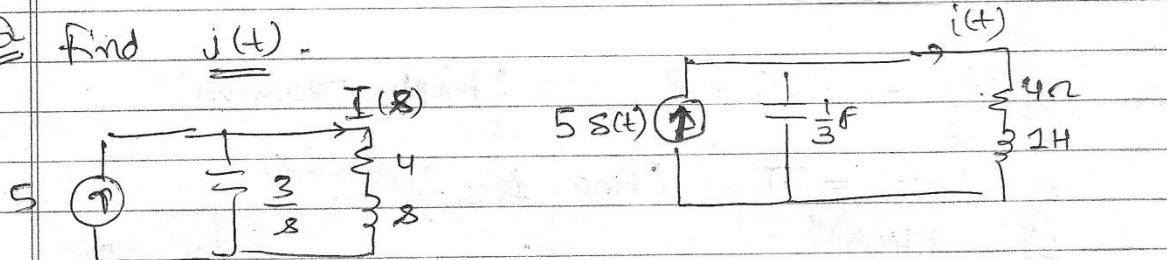




$$\underline{I}(s) = \frac{\frac{3}{s}}{4 + \frac{3}{s} + \frac{3}{8}} \times 5$$


Q $I(0^-) \neq 0$

$I_{L2}(0^-) \neq 0$

$V_L(0^-) \neq 0$

find V_{TH}, Z_{TH} .

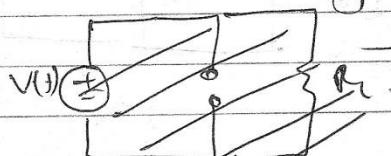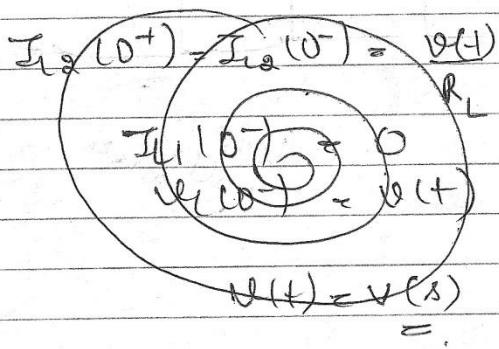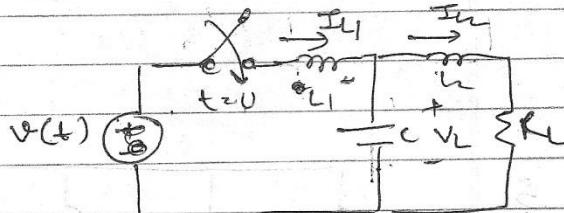


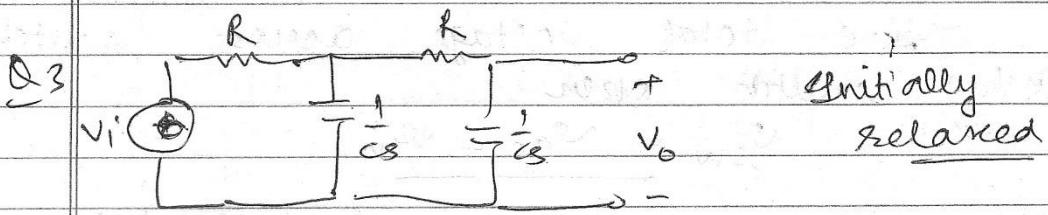


1) $\frac{V_0}{V_i} = H(s) = ?$ (Apply Thevenin)

2) $|H(s)| = \pi$ (find freq.)


3) $|H(j\omega)|$

4. Superposition Thm.

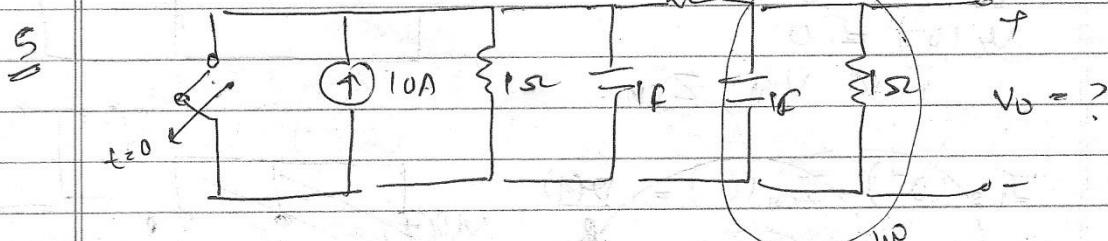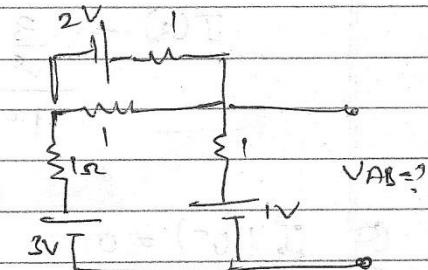


Solve Initial cond. = 0

load N/W
voltage source


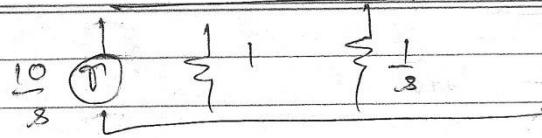


$$Z_{TH} = \frac{1}{8} + \frac{1}{8+1} = \frac{1+8+1}{8+1} = \frac{8+2}{8+1}$$
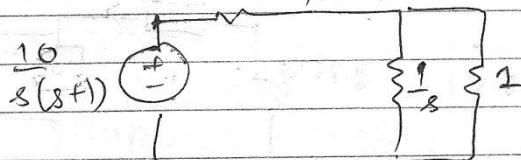
$$\begin{aligned} V_{TH} &= \frac{1}{8} \left(\frac{1}{1+\frac{1}{8}} \times \frac{10}{8} \right) \\ &= \frac{1}{8} \left(\frac{8}{8+1} \times \frac{10}{8} \right) \\ &= \frac{1 \times 10}{8 (8+1)} \\ &= \frac{(8+2)}{(8+1)} \end{aligned}$$





Using Thevenin

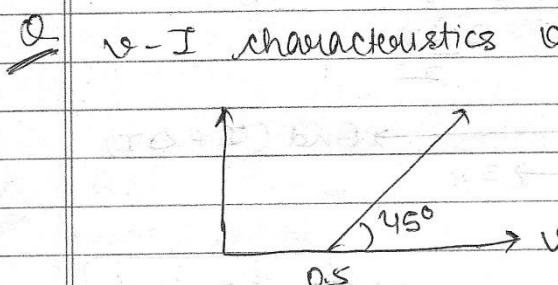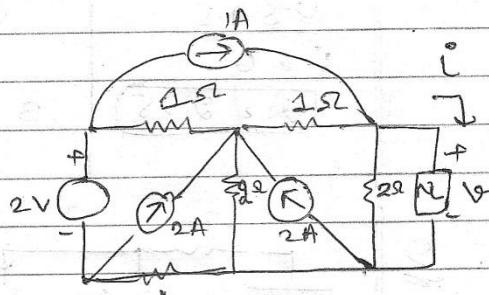

$$R_{TH} = \frac{10}{8} \approx 1 \quad \text{and} \quad Z_{TH} \approx 1$$
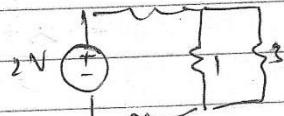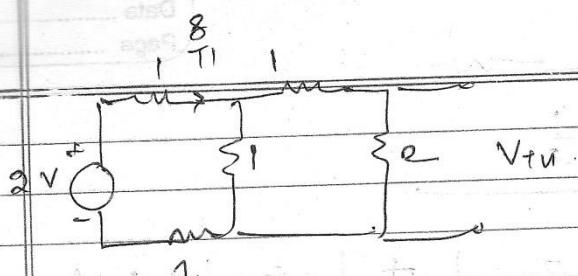
$$\begin{aligned} \frac{10}{8} \times \frac{1}{8+1} &= \frac{3+2}{3} = \frac{5}{3} \\ \frac{3 \times 2}{3+2} &= \frac{6}{7} \end{aligned}$$



$$\left\{ \begin{array}{l} \frac{3 \times 1}{3+1} = \frac{3}{4} + 2 \\ \frac{2 \times 4}{11} = \frac{8}{11} \end{array} \right.$$

Current (2) = $\frac{1}{3} \frac{8}{11}$
 $= \frac{8}{33}$

$$V_{tu} = 2.75 \text{ V}$$

$$2.75 - i - v = 0$$




$$v \leq 0.5$$

$$i = 0$$

$$v = 2.75$$

$$3.25 - 2v = 0$$

$$v = \frac{3.25}{2}$$

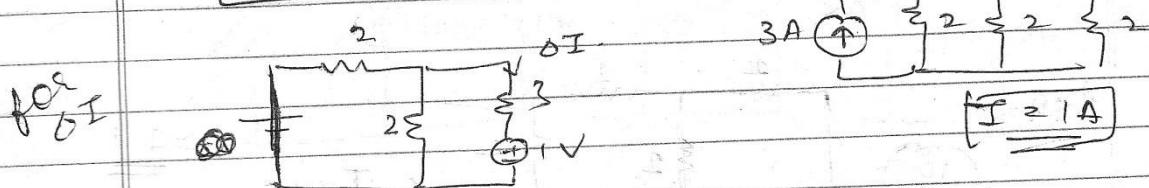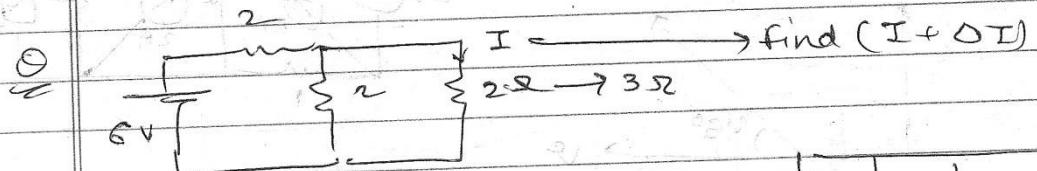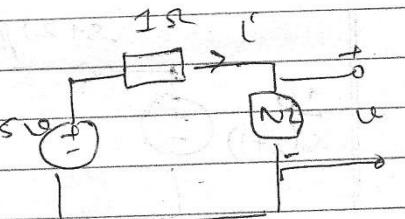

~~$$6 = 2I_1 + 2(I_1 - I_2)$$~~

~~$$3I_2 + 1 + 2(I_2 - I_1) = 0$$~~

~~$$6I_2 - I_1 + 1 = 6$$~~


$$1 \left\{ \begin{array}{l} \\ \end{array} \right\} 3 - \frac{1}{4} A = \Delta I$$

$$I + \Delta I = 1 - \frac{1}{4} = \frac{3}{4}$$


Q find value of R_L for which power transfer max

$$P = V_R I_R$$

differentiate the equation to 0

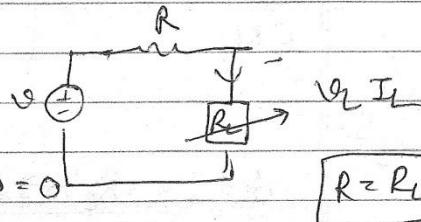

$$R = R_L$$

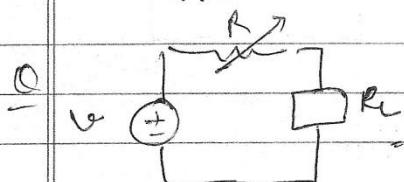

$$\frac{R_L}{R+R_L} V = \frac{V}{R+R_L}$$


$$P = \frac{V^2 R_L}{(R+R_L)^2} = \frac{(R+R_L)^{-1}}{(R+R_L)^2}$$

$$\frac{dP}{dR} = -R_L V^2 (R+R_L)^{-3}$$


$$\frac{dP}{dR} = -R_L V^2 \frac{1}{(R+R_L)^3} = 0 \quad (1) + (-1)$$

$$R \rightarrow 0$$

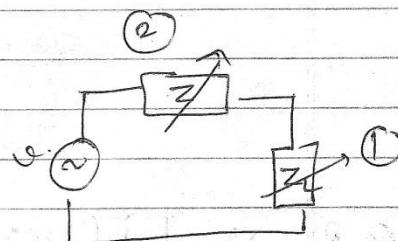Q find value of Z for which max transfer at Z_L





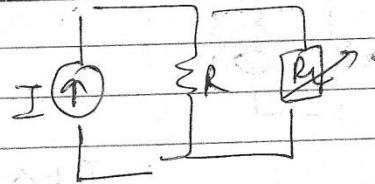
$$S = \left[\frac{R}{(R+R_L)} I \right]^2 R_L$$



$$\frac{dP}{dR_L} = \frac{R^2 R_L I^2}{(R+R_L)^2}$$

$$\frac{dP}{dR_L} = R^2 I^2 \frac{[(R+R_L)^2 - R_L^2]}{(R+R_L)^4}$$

6

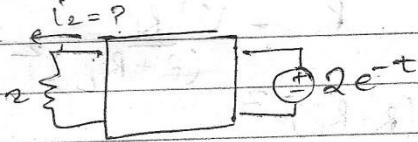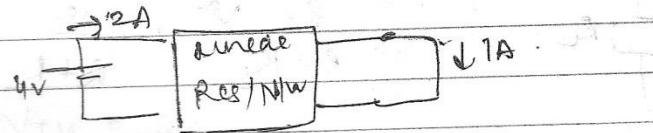
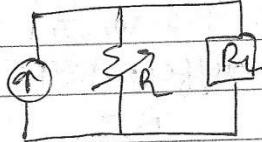
thus $R_L \rightarrow \infty$ 

$$4(-i_2) + (0) = 2i_2(2) + 2e^{-t}(1).$$

$$-4i_2 - 4i_2 = 2e^{-t}$$

$$-8i_2 = 2e^{-t}$$

$$i_2 = -\frac{e^{-t}}{4}$$

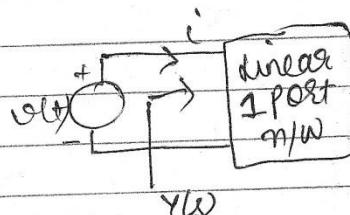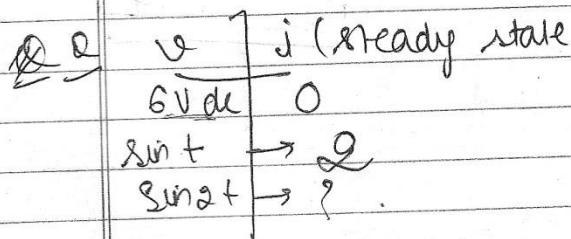

$$Y(s) \rightarrow S = -1 \pm j1 \text{ and } 2 \text{ zeroes.}$$

$$\frac{Y(s)}{V(s)} = \frac{I(s)}{V(s)} = \frac{(s-z_1)(s-z_2)}{(s+1+j)(s+1-j)}$$

$$\frac{Y(s)}{V(s)} = \frac{(s-z_1)(s-z_2)}{(s+1)^2 + 1}$$

$$Y(s) = \frac{(s-z_1)(s-z_2)}{s^2 + 2s + 1} = \frac{(s-z_1)(s-z_2)}{s^2 + 2s + 1}$$

$$\frac{I(s)}{V(s)} = \frac{(s-z_1)(s-z_2)}{s^2 + 2s + 2}$$

$$6V \cdot \frac{z_1 z_2}{2} = 0 \\ z_1 z_2 = 0$$


$$s = j \\ \left| \frac{(j-z_1)(j-z_2)}{1-2j} \right| \sin \theta = 2$$

$$\text{Also } \phi = 0$$

$$H(s) = \frac{4s}{s^2 + 2s + 2} = \frac{4j\omega}{s \cdot (j\omega + 1 - j\phi) (j\omega + 1 + j\phi)}$$

$$-2 \pm \sqrt{4 - 4 \times 1 \times 2} \\ s = -1 \pm j$$
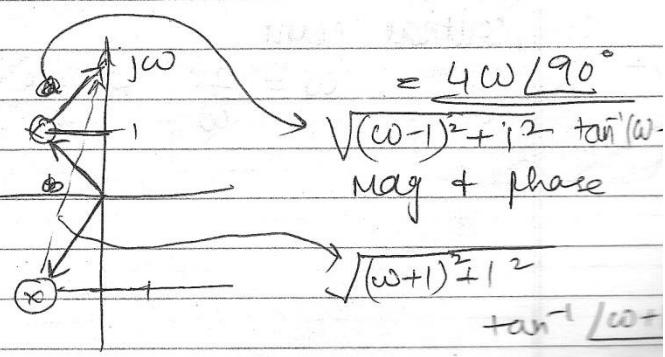
$$\frac{4j\omega}{[j\omega - (-1+j)] [j\omega - (-1-j)]}$$



$$At \ j^2 = -3 \quad \underline{4(2)/90} \\ \sqrt{1^2+1^2} = \underline{\tan^{-1}(1)} \quad \sqrt{3^2+1^2} = \tan^{-1}(3)$$

$$\frac{8}{\sqrt{2}\sqrt{10}} = \frac{190-45}{190} - \tan^{-1} 3 \\ = 1.78 \quad \underline{-26.5}$$


j^2+1

$$j(\infty) \quad \frac{190}{190} = \underline{(-90)}$$

Neg $\rightarrow \infty$
of the vectors

$$\frac{\infty}{\infty^2}$$

$$10 \rightarrow \underline{0}$$

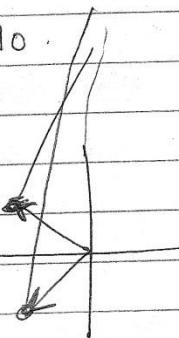

$$H(s) = \frac{4}{(s+2)^2 + 2}$$

$$H(j\omega) = \frac{4}{(j\omega+2)^2 + 2}$$

$$|H(j\omega)| = \frac{4}{\cancel{(j\omega+2)^2 + 4}} \quad \frac{4}{\cancel{2^2 + (\omega-\frac{2}{\omega})^2}}$$

$$\tan^{-1} \left(\frac{\omega - \frac{2}{\omega}}{2} \right)$$

Critical point

$$\omega = \frac{2}{\omega} \Rightarrow \omega^2 = 2$$

$$\Rightarrow \omega = \sqrt{2}$$

$$V_o(s) = \frac{1}{C s}$$

$$\frac{1+R}{C s}$$

$$= \frac{1}{1+R C s} = \frac{1/R C}{s + 1/R C}$$

$$= \frac{1}{R C} \left[\frac{1}{j\omega + \frac{1}{R C}} \right]$$

$$|H(s)| = \frac{1}{R C} \sqrt{\omega^2 + \left(\frac{1}{R C}\right)^2} \quad \text{tan}^{-1}(C R C)$$

$$\omega \rightarrow 0$$

$$|H(s)| = 1$$


$$\omega \rightarrow \infty = 0$$

$$-\tan^{-1}(0) = 0$$

$$-\tan^{-1}(\infty) = -90^\circ$$

\equiv

$$|H(s)|$$

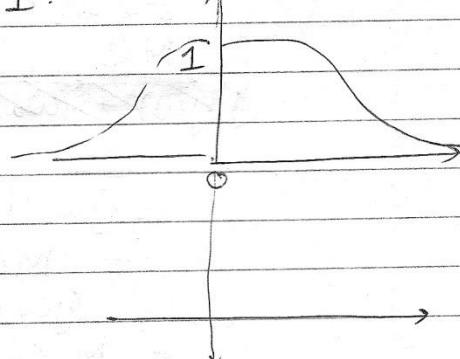

$$\frac{1}{R C} = \frac{1}{\sqrt{2}}$$

$$\frac{1}{R C} \sqrt{2} = \sqrt{\omega_c^2 + \left(\frac{1}{R C}\right)^2}$$

$$\frac{2}{(R C)^2} = \omega_c^2 + \frac{1}{(R C)^2}$$

$$\frac{1}{(R C)^2} = \omega_c^2$$

$$\omega_c = \frac{1}{R C}$$

~~$$\omega = \frac{1}{R C}$$~~

$$\frac{(w)^2 + w_0^2}{-w + w_0}$$

Q $H(s) = (s^2 + w_0^2) H_1(s)$ $\rightarrow M \angle \phi$

$$(s + j\omega_0)(s - j\omega_0) \cancel{(s-j\omega_0)(s+j\omega_0)}$$

$$(j\omega + w_0)(j\omega - j\omega_0)$$

$$[j(\omega + w_0)][j(\omega - w_0)] \quad \cancel{100} \cancel{200} \cancel{300} \cancel{400}$$

$$\tan^{-1} \frac{\omega + w_0}{\omega - w_0} \text{ Mag } \sqrt{(\omega^2 + w_0^2)^2 + (\omega^2)^2}$$

$$= 90^\circ - 90^\circ \quad \omega < \omega_0 \quad |H| = M (w_0^2 - \omega^2)$$

$$= 90^\circ + 90^\circ \quad \omega > \omega_0$$

$$= 180^\circ$$

Q $H(s) = \frac{H(s)}{s^2 + w_0^2}$

$$\cancel{M \angle \phi} \quad \cancel{|H(s)|} = \cancel{M} \quad \cancel{(w^2)^2 -}$$

$$\cancel{j(j\omega)^2 + (w_0)^2} \cancel{+ H_1(s)}$$

$$(s + j\omega_0)(s - j\omega_0)$$

$$= M \angle \phi$$

$$(j\omega + j\omega_0) - (j\omega - j\omega_0)$$

$$= M \angle \phi$$

$$j(\omega + \omega_0) j(\omega - \omega_0)$$

$$\omega < \omega_0$$

$$\cancel{\angle \phi} = \angle \phi$$


$$180^\circ - 90^\circ$$

$$\frac{\cancel{\angle \phi}}{180^\circ - 90^\circ} = \angle \phi - 180^\circ \quad \omega > \omega_0$$

Q $H(s) = \frac{(j\omega)^2 + \omega_1^2 + H_1(s)}{(j\omega)^2 + \omega_2^2} \quad \omega_1 < \omega_2$

$$-\frac{\omega^2 + \omega_1^2 + H_1(s)}{-\omega + \omega_2} = M \angle \phi$$


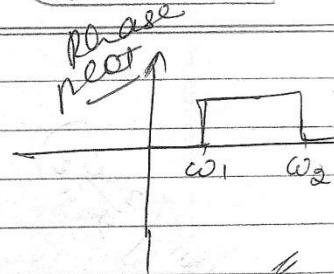
$$\frac{(s+j\omega_1)(s-j\omega_1)}{(s+j\omega_2)(s-j\omega_2)}$$



$$\begin{aligned} & (j\omega + j\omega_1)(j\omega - j\omega_1) \\ & (j\omega + j\omega_2)(j\omega - j\omega_2) \\ & j(\omega + \omega_1) j(\omega - \omega_1) \\ & j(\omega + \omega_2) j(\omega - \omega_2) \end{aligned}$$

phase 0 $\omega < \omega_1$
phase 180 $\omega > \omega_1$

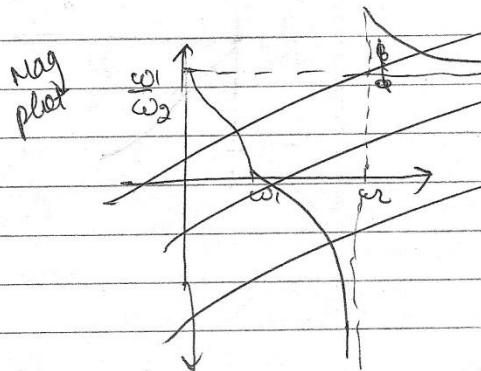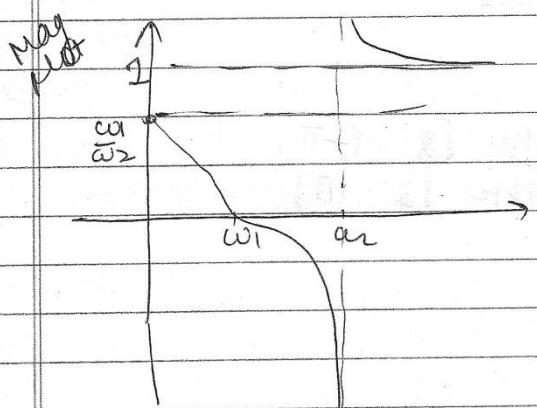0 $\omega < \omega_2$
-180 $\omega > \omega_2$




$$H(s) = \frac{(s-1)^2 + 1}{(s+1)^2 + 1} = \frac{s^2 + 1 - 2s + 1}{s^2 + 2s + 1 + 1} = \frac{s^2 - 2s + 2}{s^2 + 2s + 2}$$

$$Z_{12} = 1 \pm j$$

$$P_{12} = -1 \pm j$$

$$\text{Mag (Zeroses)} = 1$$

$$\text{Mag (Poles)}$$

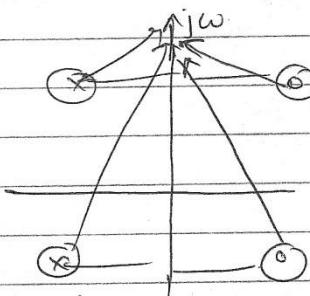

$|H| = k = \text{All pass fn.}$

$$\frac{(j\omega)^2 - j\omega + 2}{(j\omega)^2 + 2j\omega + 2}$$

$$\begin{aligned} & -\omega^2 - 2j\omega + 2 \\ & -\omega^2 + 2j\omega + 2 \end{aligned}$$

$$\frac{(2-w) - 2j\omega}{(2-w) + 2j\omega} = \tan^{-1}\left(\frac{-2\omega}{2-w}\right)$$


$$\tan^{-1} = \frac{(2-w)}{2\omega}$$

$$\frac{2\omega}{2-w}$$

$$\tan^{-1}\left(\frac{-2\omega}{2-w}\right)$$

$$\frac{2\omega}{2-w}$$
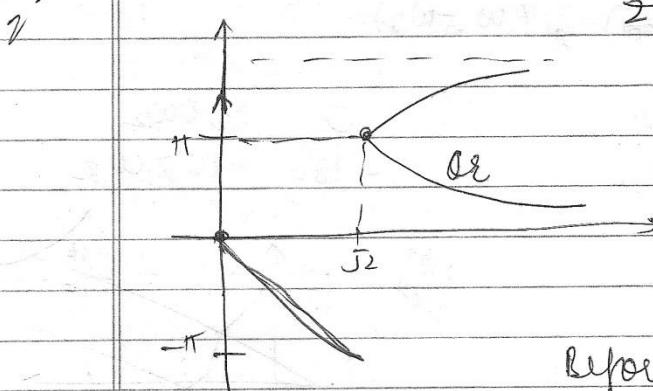
$$2 \times \tan^{-1}\left(\frac{\omega}{2}\right)$$



$$\omega = \sqrt{2}$$

$$\tan^{-1}\left(\frac{\infty}{\infty}\right)$$

Before $\sqrt{2}$ ($-\pi$)
After $\sqrt{2}$ (π)

20/9/2014

Date
Page


$$\tan^{-1} \left(\frac{2\omega}{2-\omega^2} \right)$$

State VARIABLE

Info at any point of time that need to be known to find out the response under the influence of excitation at that particular instant of time.

State variable here

is $I_L(t_1)$ and $v_C(t_1)$

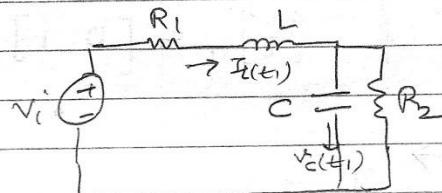


Q

$$S.V = v_C$$

$$O/P V = v_C, v_R$$

$$I/P V = v_i$$

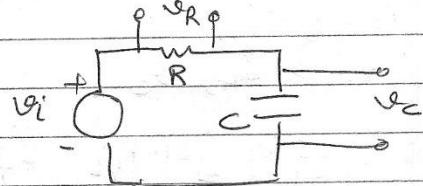

$$i_C = C \frac{dv_C}{dt}$$

$$v_C = \frac{i_C}{C}$$

$$v_i = v_R + v_C$$

$$= i_C R + v_C$$

$$v_i = R C v_C + v_C$$

$$v_C = \frac{v_i}{R_C} - \frac{v_C}{A_C}$$

$$v_C = [1] v_C + [0] v_i$$

$$v_R = v_i - v_C$$


$$= [-1] v_C + [1] v_i$$

$$\rightarrow y \rightarrow v_c (0|P)$$

$$u \rightarrow v_i (I|P)$$

x (state variable is)

i_L and v_c

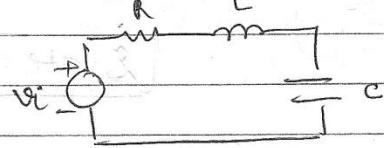

for state variable find dynamic elements

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_c \end{bmatrix} = \begin{bmatrix} -R_L & -1/L \\ 1/C & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} 1/L \\ 0 \end{bmatrix} v_i$$


$$v_c = [0 \ 1] \begin{bmatrix} i_L \\ v_c \end{bmatrix} + [0] v_i$$

\rightarrow

$$y \rightarrow v_c$$

$$u \rightarrow v_i$$

$x \rightarrow i_L, v_c$

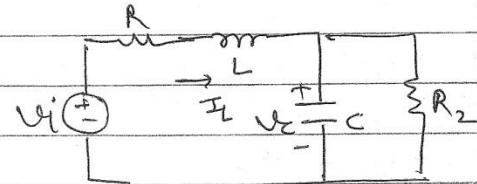

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_c \end{bmatrix} = \begin{bmatrix} -R_1/L & -1/L \\ 1/C & -1/R_2 C \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} 1/L \\ 0 \end{bmatrix} v_i$$


$$v_c = [0 \ 1] \begin{bmatrix} i_L \\ v_c \end{bmatrix} + [0] v_i$$

\rightarrow

$$I|P \quad e$$

$$0|P \quad i$$
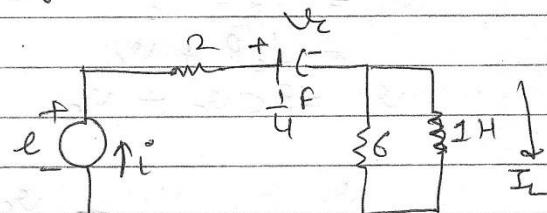
$$A = \begin{bmatrix} -1/2 & 3 \\ -3/4 & -3/2 \end{bmatrix}$$




$$B = \begin{bmatrix} 1/2 \\ 3/4 \end{bmatrix}$$

$$C = \begin{bmatrix} -1/8 & 3/4 \end{bmatrix}$$

$$D = \begin{bmatrix} 1/8 \end{bmatrix}$$

$\rightarrow I/P = e_1, e_2, i_s$
 $O/P = i_1, i_2$
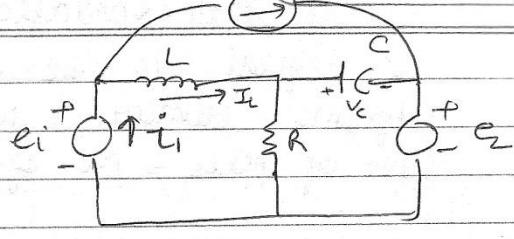
$$U = \begin{bmatrix} e_1 \\ e_2 \\ i_s \end{bmatrix}$$



$$O/P \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \rightarrow \begin{bmatrix} v_C \\ i_L \end{bmatrix}$$

$$A = \begin{bmatrix} -\frac{1}{RC} & \frac{1}{C} \\ -\frac{1}{L} & 0 \end{bmatrix}$$


$$B = \begin{bmatrix} 0 & -\frac{1}{RC} & 0 \\ \frac{1}{L} & -\frac{1}{L} & 0 \end{bmatrix}$$

$$C \rightarrow \begin{bmatrix} 0 & 1 \\ \frac{1}{R} & -1 \end{bmatrix}$$


$$D \rightarrow \begin{bmatrix} 0 & 0 & 1 \\ 0 & \frac{1}{R} & -1 \end{bmatrix}$$

$\rightarrow 2$ state variables


Current through L same v_i

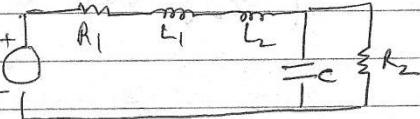

\rightarrow similarly 2 state variables

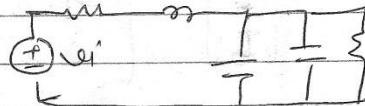


$\rightarrow 2$ state variables

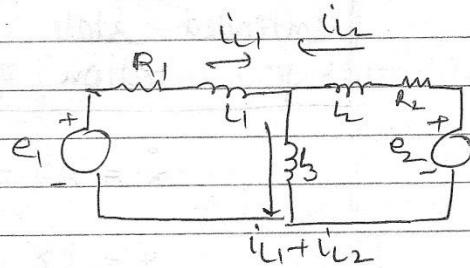

$\rightarrow 2$ state variable

loop including C 's.

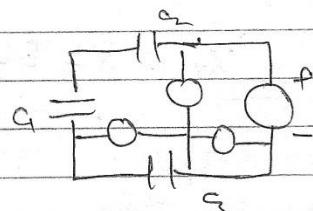Voltage of one can be represented in terms of other 2.



→ No. of state variables for a given system
 is equal to no. of dynamically independent dynamic element = No. of eigen values =
 No. of poles = No. of zeroes = No. of natural v.


Q

$$C_1 = C_2 = C_3 = 1F$$

$$R_1 = R_2 = R_3 = 1\Omega$$

$$Y = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \quad U = \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}$$

state variables = 2

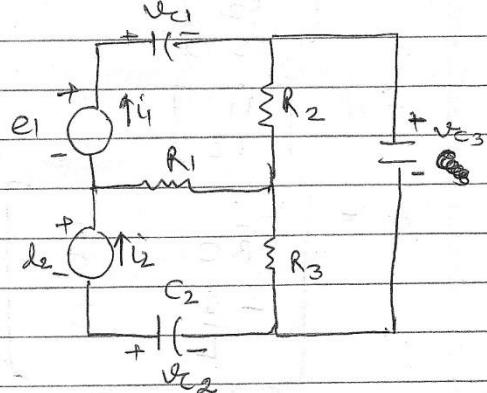

$$i_1 + i_2 = ve_1 - ve_2 + ve_3$$

$$\begin{bmatrix} \dot{v}_{e_1} \\ \dot{v}_{e_2} \end{bmatrix} = \begin{bmatrix} -1/3 & 0 \\ 0 & -1/3 \end{bmatrix} \begin{bmatrix} ve_1 \\ ve_2 \end{bmatrix} + \begin{bmatrix} 1/3 & 0 \\ 0 & 1/3 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} + \begin{bmatrix} 1/3 & 1/3 \\ -1/3 & -1/3 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}$$

$$\begin{bmatrix} \dot{i}_1 \\ \dot{i}_2 \end{bmatrix} = \begin{bmatrix} -1/3 & 0 \\ 0 & 1/3 \end{bmatrix} \begin{bmatrix} ve_1 \\ ve_2 \end{bmatrix} + \begin{bmatrix} 1/3 & 0 \\ 0 & 1/3 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}$$

intended state space representation of system

$$\dot{x} = Ax + Bu + Eu$$

$$y = cx + du + fu$$

$$x_n = x - Eu \rightarrow \dot{x}_n = \dot{x} - Eu$$

$$x = x_n + Eu$$

$$\dot{x}_n + E\dot{u} = Ax_n + AEu + Bu + E\dot{u}$$

$$\dot{x}_n = Ax_n + (AE + B)u$$

$$y = Cx_n + (CE + D)u + F\dot{u}$$

$$s x(s) - x(0^+) = Ax(s) + Bu(s)$$

0^+ (because above equation valid for $t = 0^+$)

$$x(s) = (SI - A)^{-1}x(0^+) + (SI - A)^{-1}Bu(s)$$

$$y(s) = Cx(s) + Du(s)$$

$$= C(SI - A)^{-1}x(0^+) + [C(SI - A)^{-1}B + D]u(s)$$

zero IIP solⁿ

Poles λ_i

zero state solⁿ

Poles of λ_i and

poles of $U(s)$

$$= \sum a_i e^{\lambda_i t} \Big|_{\lambda_i} + \sum b_i e^{\lambda_i t} + \sum c_k e^{p_k t}$$


steady state Respon

Transient response.

Q Ans

$$\begin{bmatrix} \dot{v}_c \\ \dot{i}_c \end{bmatrix} = \begin{bmatrix} -3/2 & 1/2 \\ -1/2 & -1/3 \end{bmatrix} \begin{bmatrix} v_c \\ i_c \end{bmatrix}$$
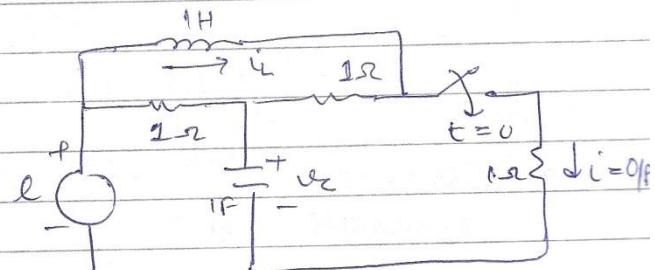
$$+ \begin{bmatrix} 1/2 \\ 1 \end{bmatrix} [e]$$



$$i = \begin{bmatrix} 1/2 & 1/2 \end{bmatrix} \begin{bmatrix} v_c \\ i_c \end{bmatrix}$$

O/P independent of I/P
unforced system.

$$x(0^+) = \begin{bmatrix} e \\ 0 \end{bmatrix}$$

$$\boxed{i(t) = 1 - 0.5e^{-t} + 0.5te^{-t}, \quad t > 0.}$$

$$\begin{aligned} y(s) &= C(SI - A)^{-1}B + D && [\text{keeping initial}] \\ u(s) & && [\text{cond} = 0] \end{aligned}$$

State Transition Matrix

$$\phi(t) = e^{At} = I + \frac{At}{1!} + \frac{A^2t^2}{2!} + \dots$$

A = Matrix.

$$\boxed{\dot{\phi}(t) = A\phi(t)}$$

↓
All terms of $n \times n$

$$\phi(t) = []_{n \times n}$$

i) $\phi(t) = [I]_{n \times n}$

ii) $\phi(t_2 - t_1) = \phi(t_2 - t_3) \cdot \phi(t_3 - t_2)$

iii) $\phi^{-1}(t) = \phi(-t)$

$$\begin{aligned} x(t) &= x(0)e^{At} \\ x(t-t_0) &= x(t_0)e^{A(t-t_0)} \end{aligned}$$

→ Laplace Transform

$$\begin{aligned} \dot{x} &= Ax \\ x(s) &= (S I - A)^{-1} x(0) \end{aligned}$$

$$L^{-1}((S I - A)^{-1}) = e^{At}$$

→ Convert e^{At} into ∞ sum series then
summate it

→ Diagonilization of Matrix

$$|SI - A| = 0$$

$$(\lambda_1, \lambda_2, \dots, \lambda_n) \quad T^{-1}AT = \begin{bmatrix} \lambda_1 & & & \\ & \ddots & & 0 \\ & & \lambda_2 & \\ & & & \ddots & \lambda_n \end{bmatrix}$$

T = Transformation Matrix or Similarity transformation Matrix.

$$e^{At} = T \begin{bmatrix} e^{\lambda_1 t} & & & \\ & e^{\lambda_2 t} & & \\ & & \ddots & \\ & & & e^{\lambda_n t} \end{bmatrix} T^{-1}$$

→ Cayley Hamilton Thm.

$$|SI - A| = 0$$

↪ Roots $\lambda_1, \lambda_2, \dots, \lambda_n$

$$e^{At} = C_0(t) + C_1(t) \cdot A + C_2(t) A^2 + \dots + C_{n-1} A^{n-1}$$

$$\left\{ \begin{array}{l} e^{\lambda_1 t} = C_0(t) + C_1(t) \lambda_1 + C_2(t) \lambda_1^2 + \dots + C_{n-1} \lambda_1^{n-1} \\ e^{\lambda_2 t} = \dots \\ \vdots \\ e^{\lambda_n t} = \dots \end{array} \right.$$

Q $A = \begin{bmatrix} -1 & 0 \\ 1 & -2 \end{bmatrix}$

Solv $n=2$

$$e^{At} = C_0 + C_1 A$$

$$\begin{bmatrix} s+1 & 0 \\ 1 & s+2 \end{bmatrix}$$

$$(s+1)(s+2) - 0 = 0$$

$$\begin{aligned} s &= -1 \\ s &= -2 \end{aligned}$$

$$\begin{aligned} e^{-1t} &= C_0 + G A \\ e^{-2t} &= C_0 + G A \end{aligned}$$

$$\Phi(t) = \begin{bmatrix} e^{-t} & 0 \\ e^{-t} - e^{(3)t} & e^{-2t} \end{bmatrix}$$

$$e^{-t} = C_0 - G$$

$$e^{-2t} = C_0 - 2G$$

$$e^{-t} - e^{-2t} = G$$

$$e^{-t} + e^{-t} - e^{-2t} = C_0$$

$$2e^{-t} - e^{-2t} = G$$

$$e^{-t} = 0 \cdot (2e^{-t} - e^{-2t}) + [e^{-t} - e^{-2t}] \begin{bmatrix} -1 & 0 \\ 1 & -2 \end{bmatrix}$$

$$\underline{\Phi} \quad A = \begin{bmatrix} 0 & -1 & -3 \\ -6 & 0 & -2 \\ 5 & -2 & -4 \end{bmatrix}$$

$$\lambda_1 = -1 = \lambda_2$$

$$\lambda_3 = -2$$

$$e^{At} = C_0 + G A + G A^2$$

$$\rightarrow X = AX + BU$$

$$X(t) = \int_0^t e^{t-(t-\tau)} B U(\tau) d\tau + e^{At} X(0)$$

$$= e^{At} * B U(t) + e^{At} X(0)$$

$$X(t) = \Phi(t) * B U(t) + \Phi(t) X(0)$$

$$\rightarrow y(t) = C_0(t) \cdot x(0) + C_0(t) * Bu(t) + Du(t)$$

Q

$$\dot{x} = f(x, u, t)$$

$$y = h(x, u, t)$$

$$\begin{aligned} \dot{x} &= f(x, u) && \text{autonomous} \\ y &= h(x, u) && \text{system.} \end{aligned}$$

$$\rightarrow \begin{bmatrix} e^{-t} - e^{-2t} & 0 \\ 0 & 2e^{-t} - e^{-2t} \end{bmatrix} + \begin{bmatrix} -e^{-t} + e^{-2t} & 0 \\ e^{-t} - e^{-2t} & -2e^{-t} + 2e^{-2t} \end{bmatrix}$$

$$= \begin{bmatrix} e^{-t} & 0 \\ e^{-t} - e^{-2t} & e^{-2t} \end{bmatrix}$$

$$\dot{x} = f(x) + g(x)u$$

↑
Affine System

If $\dot{x} = f(x)$ unforced system.

In case of NL system, harmonic components may be present corresponding to constant freq. Input NL system can exhibit multiple mode of behaviour

$$\dot{x} = f(x) \quad \dot{x} = f(\cancel{x}, u)$$

$$x \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_m \end{bmatrix} \quad u \begin{bmatrix} u_1 \\ u_2 \\ \vdots \\ u_m \end{bmatrix}$$

↑ point

$$\begin{aligned} x_1 &= f_1(x, u) = 0 \\ x_2 &= f_2(x, u) = 0 \\ &\vdots \\ x_n &= f_n(x, u) = 0 \end{aligned} \quad \left. \begin{array}{l} (\cancel{x}_1, u_1, e) \\ (\cancel{x}_2, u_2, e) \end{array} \right\}$$

At \hat{x}_e point $f(x_e, u_e) = 0$

To find out linear model around $\equiv m$ point for a NL system will disturb the system from \equiv point with very small deviation.

$$(x_c + \Delta x, u_c + \Delta u)$$

Now linearize the system around x_c & u_c

$$\left. \frac{dx}{dt} \right|_{x_c, u_c} = f(x_c, u_c) + \frac{\partial f}{\partial x} \Big|_{x_c, u_c} \Delta x + \frac{\partial f}{\partial u} \Big|_{x_c, u_c} \Delta u + \dots$$

$$AT \equiv_m f(x_c, u_e) = 0$$

$$\frac{d(x + \Delta x)}{dt} \Big|_{x_e + u_e} \quad \underbrace{\frac{du}{dt}}_{\text{impulse}} \Big|_{x_e + u_e} = 0$$

$$\delta x^i = \left[\frac{\partial f}{\partial x} \right]_{\text{new}} \delta x + \left[\frac{\partial f}{\partial u} \right]_{\text{new}} \delta u$$

↓
↓
 A B

$$A = \begin{bmatrix} \frac{\partial f_1}{\partial x_1} & \frac{\partial f_1}{\partial x_2} & \dots & \frac{\partial f_1}{\partial x_n} \\ \frac{\partial f_2}{\partial x_1} & \frac{\partial f_2}{\partial x_2} & \dots & \frac{\partial f_2}{\partial x_n} \\ \vdots & \vdots & \ddots & \vdots \\ \frac{\partial f_m}{\partial x_1} & \frac{\partial f_m}{\partial x_2} & \dots & \frac{\partial f_m}{\partial x_n} \end{bmatrix} \quad B = \begin{bmatrix} \frac{\partial f_1}{\partial u_1} & \dots & \frac{\partial f_1}{\partial u_m} \\ \frac{\partial f_2}{\partial u_1} & \dots & \frac{\partial f_2}{\partial u_m} \\ \vdots & \vdots & \vdots \\ \frac{\partial f_m}{\partial u_1} & \dots & \frac{\partial f_m}{\partial u_m} \end{bmatrix}$$

$$\left. \begin{array}{l} \dot{x} = A \Delta x + B \Delta u \\ \dot{y} = [C] \Delta x + D \Delta u \end{array} \right\} \rightarrow \begin{array}{l} \text{applicable} \\ \text{at } \approx m \text{ point} \end{array}$$

One dimensional


$$\dot{x} = a x$$


$$x(t) = x(0) e^{at}$$

2 dimensional

$$\begin{aligned} \dot{x} &= f_1(x, y) & f_1, f_2 &\text{N.L.} \\ \dot{y} &= f_2(x, y) & f_2 &\text{N.L.} \\ &&& \text{of } (x, y) \end{aligned}$$

Then starting from any initial cond.
 $(\Delta x^2 + \dots + \Delta u^2)$ system will follow a particular
 Neglect path in (x, y) plane. That path is
 called as vector field.
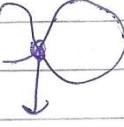
$$\frac{d\vec{x}}{dt}$$

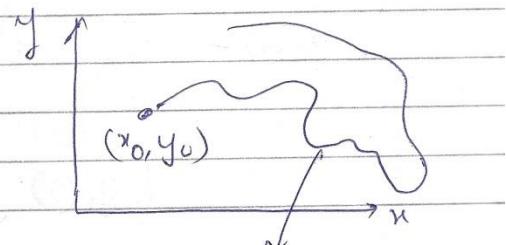


vector field
(will never intersect)

vector field cannot intersect other than $\approx m$
 because that will need 2 directions of vector
 field at intersection point.

$$\begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} \frac{\partial f_1}{\partial x} & \frac{\partial f_1}{\partial y} \\ \frac{\partial f_2}{\partial x} & \frac{\partial f_2}{\partial y} \end{bmatrix} \begin{bmatrix} \Delta x \\ \Delta y \end{bmatrix}$$

$$\begin{bmatrix} \dot{x} \\ \dot{y} \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} \text{ impnt}$$

$$x = Ax$$

\rightarrow If $x_1(t) = \begin{bmatrix} x_1(t) \\ y_1(t) \end{bmatrix}$ and $x_2(t) = \begin{bmatrix} x_2(t) \\ y_2(t) \end{bmatrix}$
 are 2 linearly independent ^{on} for given system.

$$x(t) = c_1[x_1(t)] + c_2[x_2(t)]$$

To find out $x_1(t)$ and $x_2(t)$ we have to
 find out a direction for which system
 behaviour is one-D. That direction
 is called eigen direction.

$$(\lambda I - A) = 0 \quad \text{initial cond. Matrix}$$

$$\lambda = \lambda_1, \lambda_2$$

$$|A - \lambda_1 I| x = 0 \quad \begin{bmatrix} x_1(0) \\ y_1(0) \end{bmatrix}$$

$$x_1(t) = \vec{v}_{\lambda_1} \cdot e^{\lambda_1 t}$$

$$= \begin{bmatrix} x_1(0) \\ y_1(0) \end{bmatrix} e^{\lambda_1 t}$$

$$\begin{aligned} x_2(t) &= v_{\lambda_2}(t) e^{\lambda_2 t} \\ &= \begin{bmatrix} x_2(0) \\ y_2(0) \end{bmatrix} e^{\lambda_2 t} \end{aligned}$$

$$\begin{bmatrix} x(t) \\ y(t) \end{bmatrix} = c_1 \begin{bmatrix} x_1(0) \\ y_1(0) \end{bmatrix} e^{\lambda_1 t} + c_2 \begin{bmatrix} x_2(0) \\ y_2(0) \end{bmatrix} e^{\lambda_2 t}$$

Q $\dot{x} = \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} -4 & -3 \\ 2 & 3 \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix}$

$$\begin{bmatrix} x(0) \\ y(0) \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix} \quad \text{find out complete sol'n.}$$

$$\begin{bmatrix} \lambda+4 & -3 \\ -2 & \lambda-3 \end{bmatrix}$$

$$(\lambda+4)(\lambda-3) - (-6) = 0$$

$$\lambda^2 - 3\lambda + 4\lambda - 12 + 6 = 0$$

$$\lambda^2 + \lambda - 6 = 0$$

$$\lambda = 2, -3$$

$$\lambda = 2$$

$$\lambda = -3$$

$$(A - 2I)x = 0$$

$$\begin{bmatrix} -6 & -3 \\ 2 & 1 \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} = 0$$

$$-6x - 3y = 0$$

$$2x + y = 0$$

$$\text{If } x = 1$$

$$y = -6 - 3y = 0$$

$$-2y = 6 \Rightarrow$$

$$(y = -3)$$

$$v_2 = \begin{bmatrix} 3 \\ -1 \end{bmatrix} \quad (\text{can be any})$$

\therefore no. of eigen vectors possible.

$$\begin{bmatrix} x(t) \\ y(t) \end{bmatrix} = C_1 e^{2t} \begin{bmatrix} 1 \\ -2 \end{bmatrix} + C_2 e^{-3t} \begin{bmatrix} 3 \\ -1 \end{bmatrix}$$

$$x(t) = C_1 e^{2t} + 3C_2 e^{-3t}$$

$$y(t) = -2C_1 e^{2t} - C_2 e^{-3t}$$

By using initial cond.

~~$x(t)$~~ $1 = C_1 + 3C_2 \quad \text{--- (1)}$

$1 = -2C_1 - C_2 \quad \text{--- (2)}$

$2 = 2C_1 + 6C_2$

$1 = -2C_1 - C_2$


$\underline{3 = 5C_2}$

$1 = -2C_1 - \frac{3}{5}$

$C_2 = \frac{3}{5}$

$1 + \underline{3} = -2C_1$

$\frac{5}{5} \cdot \frac{4}{5} = C_1$

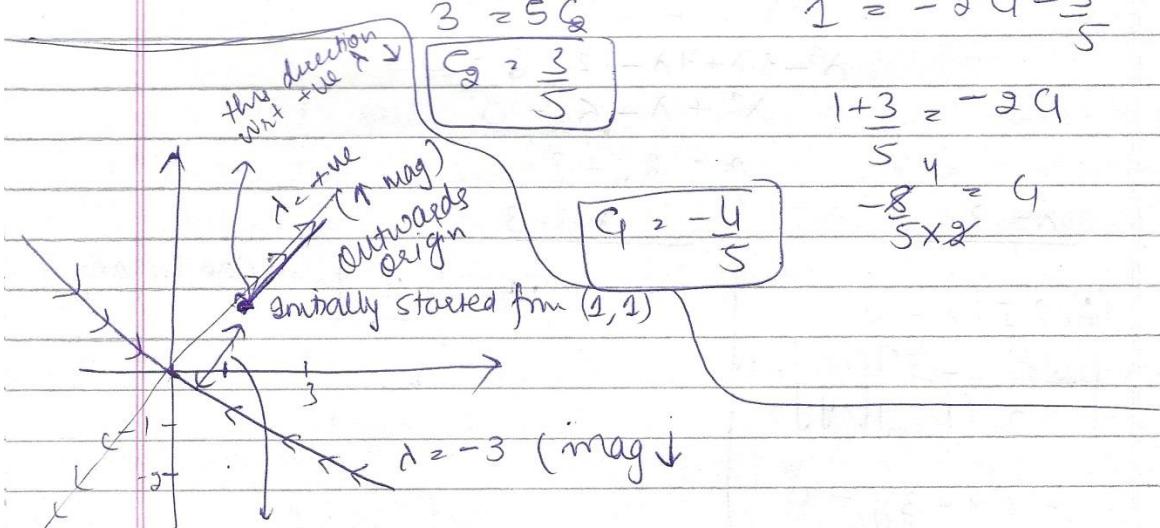

this distance w.r.t. +ve λ ↑

1) $\lambda_1 = +ve$

$\lambda_2 = -ve$

(3 cases) [Saddle pt. $\cong m$ pnt]
(attractor) towards origin

2) $\lambda_1 = -ve$

$\lambda_2 = -ve$

(point is called
repeller) → Unstable

3) $\lambda_1 = +ve$

$\lambda_2 = +ve$


more
away from
origin

If $\lambda = \sigma \pm j\omega$


$\sigma = +\text{ve}$

$\sigma = -\text{ve}$


$\sigma = 0$

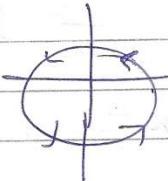


$\sigma = +\text{ve}$

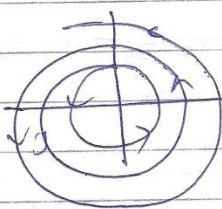

$\sigma = -\text{ve}$

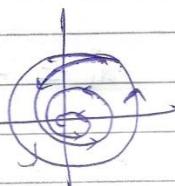

limit cycle

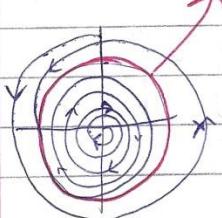

Q. $\ddot{x} + 3\dot{x} + x^3 = 0$ find \equiv pnt.

linearize system around \equiv pnt & find matrix A. Then find eigen values of linearized system.

$y = x_1$

$\dot{x}_1 = x_2$

stable

$\dot{x}_2 = -x_1^3 - 3x_2$

$f_1(f_1)$

$f_2(f_2)$

To find \equiv pnt

$x_2 = 0$

$-x_1^3 - 3x_2 = 0$

$x_1 = 0$

$x_2 = 0$

$$\begin{bmatrix} \frac{\partial f_1}{\partial x_1} & \frac{\partial f_1}{\partial x_2} \\ \frac{\partial f_2}{\partial x_1} & \frac{\partial f_2}{\partial x_2} \end{bmatrix}$$

$$X = AX$$

$$\text{Now } |A| - A = 0$$

Q $\dot{x}_1 = -x_1^2 + x_1 x_2$

$$\dot{x}_2 = -2x_2^2 + x_2 - x_1 x_2 + 2$$

(find x_e , $[A]$, λ)

Q $\dot{x}_1 = -x_1 + x_2 + x_1 (x_1^2 + x_2^2)$

$$\dot{x}_2 = -x_1 + x_2 + x_2 (x_1^2 + x_2^2)$$

find $\equiv m$ pt.

Q $\dot{x} = 3x + 4y$

$$\dot{y} = x - y$$

find solution.

$$\begin{bmatrix} x(0) \\ y(0) \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$\begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} 3 & 4 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix}$$

$$\begin{bmatrix} \lambda-3 & 4 \\ -1 & \lambda+1 \end{bmatrix}$$

$$(\lambda-3)(\lambda+1) + 4 = 0$$

$$\lambda^2 + \lambda - 3\lambda - 3 + 4 = 0$$

$$\lambda^2 - 2\lambda + 1 = 0$$

$$\lambda = 1, 1$$

$$\text{Soln} = [C_1 + S_1 t] e^{\lambda t}$$

Selectivity & Q factor same in notes

Selectivity cut.


$$f(t) = c\omega_0 \sin(\omega_0 t + \phi)$$

$$y(t) = n\omega_0 \sin(\omega_0 t + \phi) \quad n > 1$$


$$\int f(t)g(t) dt = 0$$

Reciprocity Theorem:

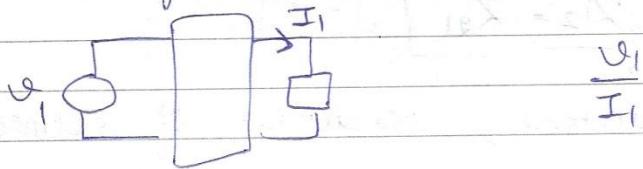A linear n/w containing bilateral 2 terminal elements and reciprocal 2 terminal elements, then the ratio of transform of response & excitation remains unchanged if the location of response and excitation are interchanged.




$$\frac{V_1}{I_1}$$

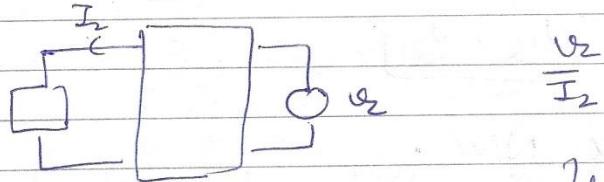

$$\frac{V_2}{I_2}$$

$$\frac{V_1}{I_1} = \frac{V_2}{I_2} \text{ for Reciprocity}$$

Symmetric n/w

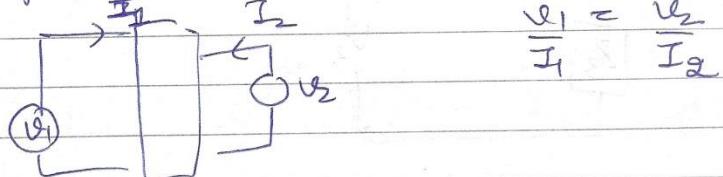

$$\frac{V_1}{I_1} = \frac{V_2}{I_2}$$

Z- Parameters



$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

\rightarrow Z_{11} is not similar to that as in Cramer's
 & it is cofactor of Z_{11} .

MBD WRITEWELL

Date

Page

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{12} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

for reciprocal n/w

$$\boxed{Z_{12} = Z_{21}}$$


for γ -parameters, condition of reciprocity is

$$\boxed{Y_{12} = Y_{21}}$$

for symmetric N/W

$$\boxed{Z_{11} = Z_{22}}$$

$$\boxed{Y_{11} = Y_{22}}$$

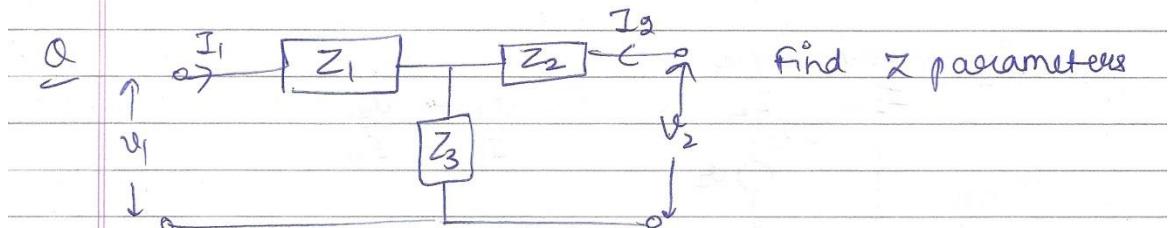

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{11} = Z_1 + Z_3$$

$$Z_{21} = Z_3$$

$$Z_{12} = Z_3$$

$$Z_{22} = Z_2 + Z_3$$

rule.

$y_{ii} \rightarrow$ self admittance
of i th node


y_{ij} - relative admittance
b/w i and j

MBDWRITER

Date

Page
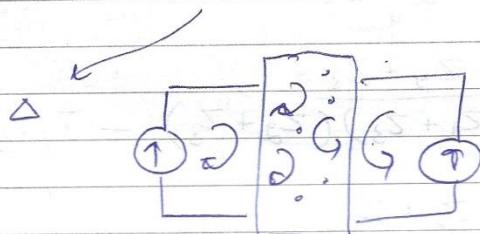
$$\begin{bmatrix} I_1 \\ I_2 \\ 0 \\ 0 \\ \vdots \\ 0 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} & \dots & y_{1K} \\ y_{21} & y_{22} & \dots & \\ \vdots & \vdots & & \\ & y_{K1} & \dots & y_{KK} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_K \end{bmatrix}$$



If there are only two
current sources

$$V_{10} = \frac{\Delta_{11} \cdot I_1 + \Delta_{21} \cdot I_2}{\Delta} + 0 + 0 + \dots$$

We know

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$\therefore Z_{11} = \frac{\Delta_{11}}{\Delta} \quad Z_{21} = \frac{\Delta_{21}}{\Delta}$$

$$\text{Similarly } Z_{12} = \frac{\Delta_{12}}{\Delta} \quad Z_{22} = \frac{\Delta_{22}}{\Delta}$$

for Z
parameters

mesh basis sys. determinant


$$\begin{bmatrix} V_1 \\ V_2 \\ 0 \\ 0 \\ \vdots \\ 0 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \dots & Z_{1K} \\ 1 & & & \\ | & & & \\ Z_{K1} & \dots & Z_{KK} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_K \end{bmatrix}$$

Z_{ii} = self impedance of i th mesh.

Z_{ij} = mutual b/w loop $i \& j$

$$I_1 = \frac{\Delta_{11}}{\Delta} V_1 + \frac{\Delta_{21}}{\Delta} V_2$$

y_{11} y_{12}

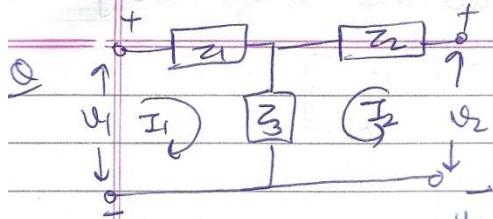

find Y parameters
by step by step
procedure.

$$\begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

next


$$Y_{11} = \frac{\Delta_{11}}{\Delta} = \frac{Z_2 + Z_3}{(Z_1 + Z_3)(Z_2 + Z_3) - Z_3 Z_3}$$

$$= \frac{Z_2 + Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}$$

$$Y_{12} = \frac{\Delta_{21}}{\Delta} = \frac{Z_3}{Z_1}$$

$$Y_{21} = \frac{\Delta_{12}}{\Delta} = \frac{Z_3}{Z_1}$$
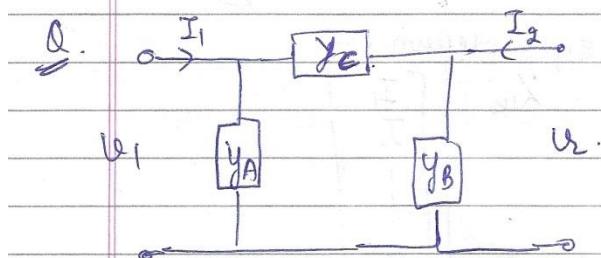
$$Y_{22} = \frac{\Delta_{22}}{\Delta} = \frac{Z_1 + Z_3}{Z_1}$$



find Y parameters

$$Y_{11} = \frac{I_1}{U_1} \quad U_2 = 0$$


$$I_2 = Y_A \cdot I_1$$

$$Y_A + Y_C$$

$$I_2 = Y_A \cdot I_1$$

$$v_1 = I_1 \begin{bmatrix} y_A y_C \\ y_A + y_C \end{bmatrix}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

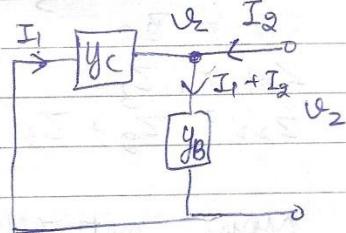

$$I_1 = -V_2 y_C$$

$$\frac{I_1}{V_2} = -\frac{y_C}{y_A + y_C} = Y_{12}$$

$$\begin{bmatrix} Y_{21} = -y_C \\ Y_{22} = y_B + y_C \end{bmatrix}$$

$$Y_{11} = y_A + y_C$$

$$Y = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} y_A + y_C & -y_C \\ -y_C & y_B + y_C \end{bmatrix}$$

$$Z_{11} = \frac{y_B + y_C}{\Delta m}$$

$$Z_{12} = \frac{+y_C}{\Delta m}$$

$$Z_{21} = \frac{+y_C}{\Delta m}$$

$$Z_{22} = \frac{y_A + y_C}{\Delta m}$$

$$V_1 = (Z_{11} + Z_{12})I_1 + Z_{12}(I_2 - I_1)$$

$$V_2 = Z_{12}(I_1 - I_2) + (Z_{22} + Z_{12})I_2$$

* for T m/w Z parameters easy

for T = Y " "

Use Z or Y for one and then use conversion for other

→ Condition taken is n/w is reciprocal

Page

If a black box is given with 2 port n/w s.


$$Z_{11} = Z_1 + Z_3$$

$$Z_{12} = Z_3$$

$$Z_{21} = Z_3$$

$$Z_{22} = Z_2 + Z_3$$

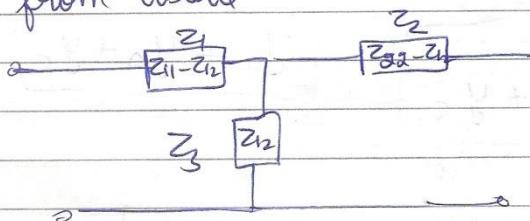Now network synthesis, i.e. construction of T- n/w from above



Similarly π net can be designed using Y-param etc.

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{12} = Y_{21}$$

Similarly
for Y

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{12}V_1 + Y_{22}V_2$$

$$I_1 = (Y_{11} + Y_{12})V_1 + Y_{12}(V_2 - V_1)$$


$$I_2 =$$

h parameters hybrid parameters


$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}I_2$$


$$h_{11} = \left. \frac{v_1}{I_1} \right|_{v_2=0}$$

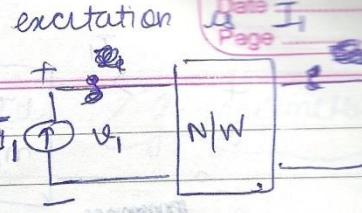


$I_1 \rightarrow 0$ represents poles

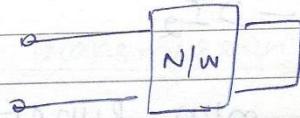

$$\therefore h_{12} = \left. \frac{v_1}{v_2} \right|_{I_1=0}$$

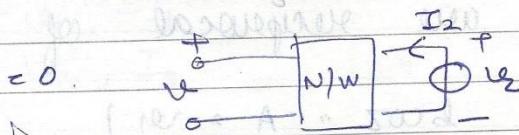

$v_2 \rightarrow 0$

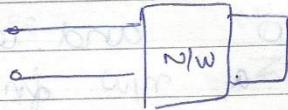

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{v_2=0}$$

$$h_{22} = \left. \frac{I_2}{v_2} \right|_{I_1=0}$$

poles of h parameters represents natural λ & under the conditions first port open and second is short.

t -parameters transmission line parameters


excitation is v_1, I_1

response is $v_2, -I_2$

because these parameters are used to calculate power

If power = $v_1 I_1$

O/P u $\leftarrow -v_2 I_2$

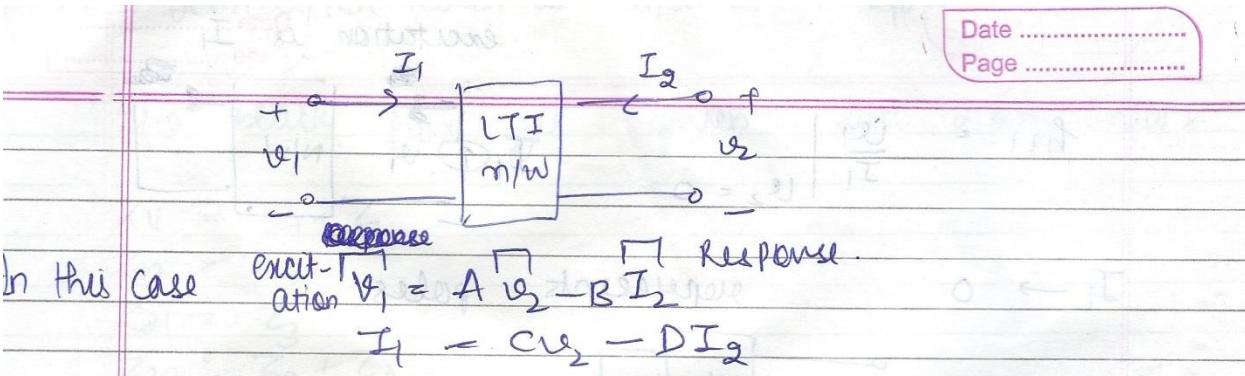

~~A~~ A, B, C, D are not m/w functions. Instead they are reciprocal of m/w fns.

$$\text{bcoz } A = \frac{v_1}{v_2} \mid_{I_2=0}$$

Now $I_2 = 0$ and $v_2 = 0$ not possible
 \therefore not a m/w fn.

both short


$$B = -\frac{v_1}{I_2} \mid_{v_2=0}$$

$$C = \frac{I_1}{v_2} \mid_{I_2=0}$$

both open

$$D = -\frac{I_1}{I_2} \mid_{v_2=0}$$

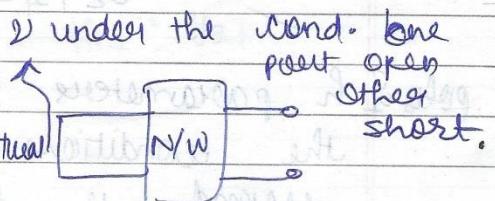zeros of A represent natural because A is



reciprocal

$$\frac{v_2}{v_1}$$

$$v_2 = 0$$

$$\text{and } I_2 = 0$$

zeros of B \rightarrow

Inverse hybrid parameters \rightarrow g -parameters

Excitation \rightarrow I_1, V_2
 Response \rightarrow V_1, I_2

Inverse transmission line parameters

Excitation \rightarrow $V_1, -I_1$
 Response \rightarrow V_2, I_2

Excitation	Response	N/W parameters
I_1, I_2	V_1, V_2	Z -parameters
V_1, V_2	I_1, I_2	γ parameters
I_1, V_2	I_2, V_1	H parameters
V_1, I_2	I_1, V_2	g -parameters
V_1, I_1	$V_2, -I_2$	$ABCD$ parameters
V_2, I_2	$V_1, -I_1$	$A'B'C'D'$ "

Note
★

In $ABCD$ & $A'B'C'D'$ relationship is written
 as excitation in terms of response.
 In all four other, response in terms
 of excitation

$$V_1 = A V_2 - B I_2$$

$$I_1 = C V_2 - D I_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$B = \left. -\frac{V_1}{I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$D = \left. -\frac{I_1}{I_2} \right|_{V_2=0}$$

(really hot weather)
MBD **WRITER**
Date 9/6/2013
Page

for reciprocity $\frac{V_1}{I_2} = \frac{V_2}{I_1}$

$$\frac{V_1}{I_2} = \frac{V_2}{I_1}$$

$\therefore I_1 = 0, I_2 = 0$

$$A/B = -\frac{I_2}{V_2}$$

$$\frac{C}{D} = -\frac{I_2}{V_2}$$

$$\Rightarrow \frac{A}{B} = \frac{C}{D}$$

$$\boxed{AD - BC = 0}$$

$$\begin{vmatrix} A & B \\ C & D \end{vmatrix} = 1$$

from def.

$$D = CV_2 - DI_2$$

$$\frac{V_2}{I_2} = D/C$$

$$V_1 = AV_2 - BI_2$$

$$V_1 = AV_2$$

$$\frac{V_1}{V_2} = A$$

$$\frac{V_1}{V_2} \times \frac{V_2}{I_2} = \frac{AC}{D}$$

$$\frac{V_1}{I_2} = \frac{AD}{BC}$$

for symmetry

$$\frac{V_1}{I_1} = \frac{V_2}{I_2}$$

$I_1 = 0, I_2 = 0$

$$V_1 = h_{11} \frac{V_2}{I_2} + h_{12} \frac{I_2}{V_2}$$

$$I_2 = h_{21} \frac{V_2}{I_1} + h_{22} \frac{I_1}{V_1}$$

$$\frac{V_1}{I_2} \Big|_{I_1=0} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$h_{11} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

$$h_{12} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{21} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

$$h_{22} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

$$\left. \begin{array}{l} 0 = h_{11}v_2 + h_{22}i_1 \\ -h_{11}v_2 = h_{22}i_1 \\ \frac{v_2}{I_1} = -\frac{h_{22}}{h_{11}} \end{array} \right\}$$

X.

$$\left. \begin{array}{l} v_1 = h_{11}v_2 \\ v_1 = h_{11} \\ \frac{v_1}{v_2} = h_{11} \end{array} \right\} \quad \left. \begin{array}{l} h_{11} = \frac{v_1}{I_2} \\ h_{21} = \frac{v_1}{I_1} \end{array} \right\} \quad I_1 = 0$$

$$\left. \begin{array}{l} h_{11} = -\frac{h_{22}}{h_{21}} \\ h_{21} \end{array} \right\}$$

for reciprocity of h parameters

$$h_{12} = -h_{21}$$

For symmetry

$$\left. \begin{array}{l} \frac{v_1}{I_1} \\ I_2 = 0 \end{array} \right\} = \left. \begin{array}{l} \frac{v_2}{I_2} \\ I_1 = 0 \end{array} \right\}$$

$$\left. \begin{array}{l} \frac{I_2}{v_2} \\ v_1 = 0 \end{array} \right\} = \left. \begin{array}{l} \frac{I_1}{v_1} \\ v_2 = 0 \end{array} \right\}$$

$$-\frac{h_{12}h_{21} + h_{11}h_{22}}{h_{22}} = \frac{1}{h_{22}}$$

$$h_{11}h_{22} - h_{12}h_{21} = 1$$

$$\begin{vmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{vmatrix} = 1$$

Q. y parameter to h parameter conversion

$$\begin{aligned} I_1 &= y_{11} v_1 + y_{12} v_2 \\ I_2 &= y_{21} v_1 + y_{22} v_2 \end{aligned} \quad -\textcircled{1}$$

h parameters $v_1 = h_{11} I_1 + h_{12} I_2$

$$I_2 = h_{21} I_1 + h_{22} I_2 \quad -\textcircled{2}$$

$$I_2 = y_{21} \left(I_1 - \frac{y_{12} v_2}{y_{11}} \right) + y_{22} v_2$$

Compare

$$I_2 = \left(\frac{y_{21}}{y_{11}} I_1 \right) + \left(y_{22} - \frac{y_{21} \cdot y_{12}}{y_{11}} \right) v_2$$

$\downarrow h_{21}$ $\downarrow h_{22}$

$$v_1 = (I_1) y_{11} - \left(\frac{y_{12}}{y_{11}} \right) v_2$$

$\downarrow h_{11}$ $\downarrow h_{12}$

Q y parameter to ABCD parameters

$$\begin{aligned} I_1 &= g_{11} v_1 + g_{12} I_2 \\ v_2 &= g_{21} v_1 + g_{22} I_2 \end{aligned} \quad -\textcircled{1}$$

$$v_1 = \frac{I_2 - g_{22} I_2}{g_{21}}$$

$$\begin{aligned} v_1 &= A v_2 - B I_2 \\ I_1 &= C v_2 - D I_2 \end{aligned}$$

$$I_1 = g_{11} \left(\frac{I_2 - g_{22} I_2}{g_{21}} \right) + g_{12} I_2$$

(1) - (9)

$$I_1 = \frac{g_{11} V_2}{g_{21}} - \frac{g_{11} g_{22}}{g_{21}} I_2 + g_{12} I_2$$

$$I_1 = \frac{g_{11} V_2}{g_{21}} - \left(g_{11} \frac{g_{22}}{g_{21}} - g_{12} \right) I_2$$

$$C = \cancel{g_{11}} \frac{g_{11}}{g_{21}}$$

$$D = g_{11} \frac{g_{22}}{g_{21}} - g_{12}$$

$$V_1 = \frac{V_2}{g_{21}} - \frac{g_{22}}{g_{21}} I_2$$

$$A = \frac{1}{g_{21}}$$

$$B = \frac{g_{22}}{g_{21}}$$

Q 2 parameter to ABCD.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_1 = A V_2 - B I_2$$

$$I_1 = C V_2 - D I_2$$

$$I_1 = V_2 - \frac{Z_{22}}{Z_{21}} I_2$$

$$C = \frac{1}{Z_{21}}$$

$$D = \frac{Z_{22}}{Z_{21}}$$

$$V_1 = \frac{Z_{11} V_2}{Z_{21}} - \left[\frac{Z_{22}}{Z_{21}} - Z_{12} \right] I_2$$


$$A = \frac{Z_{11}}{Z_{21}}$$

$$B = \frac{Z_{22} - Z_{12}}{Z_{21}}$$

2-port N/W under LOAD


External relationship
we get in this
case is

$$V_2 = -I_2 Z_L$$

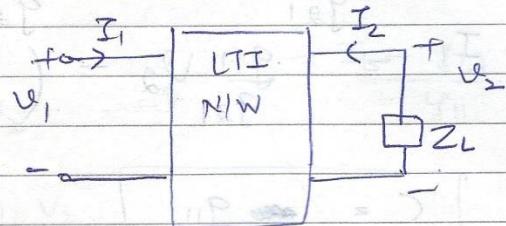

2. calculate Z, Y, h, t parameters

$$Z_{11} = \left| \frac{V_1}{I_1} \right| \quad I_2 = 0$$

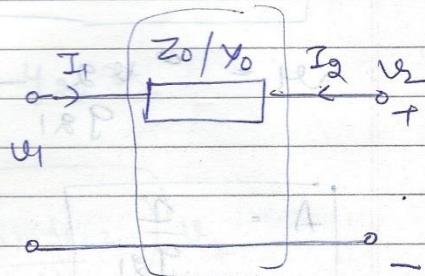

$$Z_{11} = \infty$$

$$Z_{12} = \left| \frac{V_1}{I_2} \right| \quad I_1 = 0 = -Z_0$$

$$\left| \frac{V_2}{I_1} \right| = Z_{21} = -Z_0 \quad Z_{22} = \infty$$

$$Y_{11} = Y_0$$

$$h_{11} = Y_{11} = Y_0$$

$$Y_{12} = -Y_0$$

$$h_{12} = -Y_{12} = -(-Y_0)$$

$$Y_{21} = -Y_0$$

$$Y_{22} = Y_0$$


$$= 1$$

$$T = \begin{bmatrix} 1 & Z_0 \\ 0 & 1 \end{bmatrix}$$


$$h_{21} = Y_{21} = -Y_0 = -1$$

$$h_{22} = Y_{22} - \frac{Y_{21}Y_{12}}{Y_{11}}$$

$$= Y_0 - \frac{(-Y_0)(-Y_0)}{Y_0} = 0$$

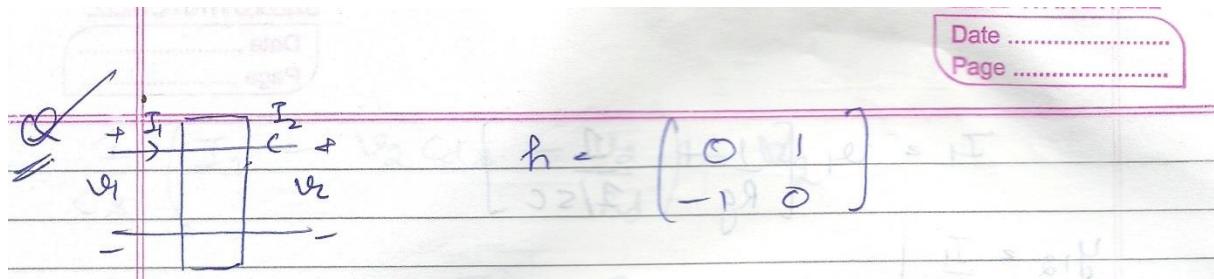
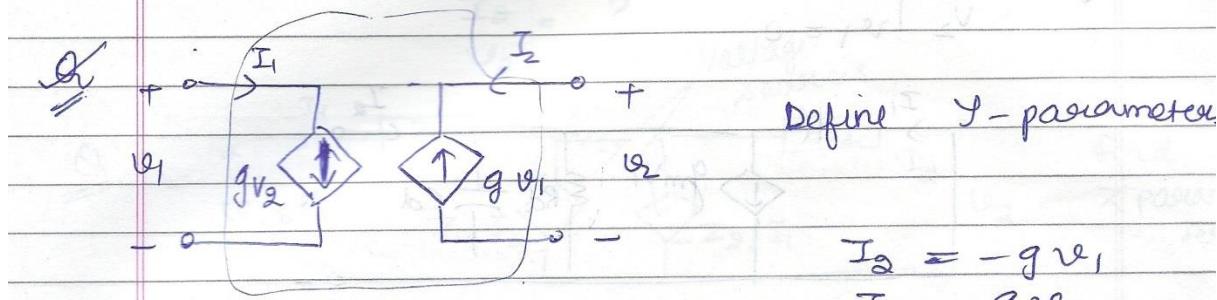
$$h = \begin{pmatrix} 0 & 1 \\ -1 & 0 \end{pmatrix} = \begin{pmatrix} 0 & 1 \\ 0 & -1 \end{pmatrix}$$





$$\begin{aligned} I_2 &= -g v_1 \\ I_1 &= g v_2 \end{aligned}$$

$$Y_{11} = \frac{I_1}{v_1} \Big|_{v_2=0} = \frac{g v_2}{v_1} \Big|_{v_2=0} = 0$$

$$Y_{12} = \frac{I_1}{v_2} \Big|_{v_1=0} = \frac{g v_1}{v_2} \Big|_{v_1=0} = g$$


$$Y_{21} = \frac{I_2}{v_1} \Big|_{v_2=0} = -\frac{g v_1}{v_1} \Big|_{v_2=0} = -g$$

$$Y_{22} = \frac{I_2}{v_2} \Big|_{v_1=0} = -\frac{g v_1}{v_2} \Big|_{v_1=0} = 0$$

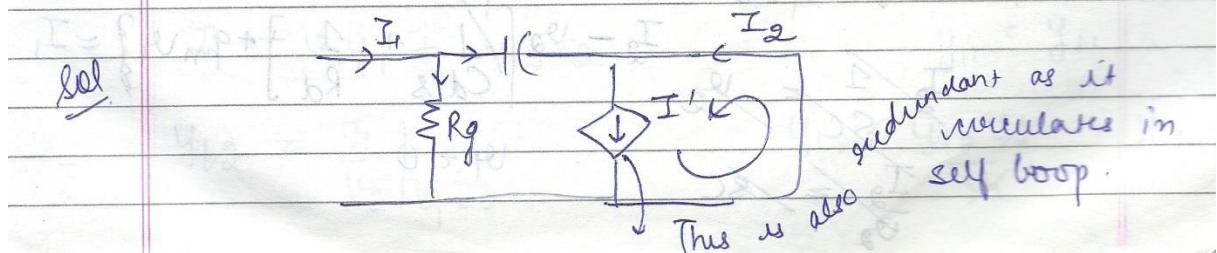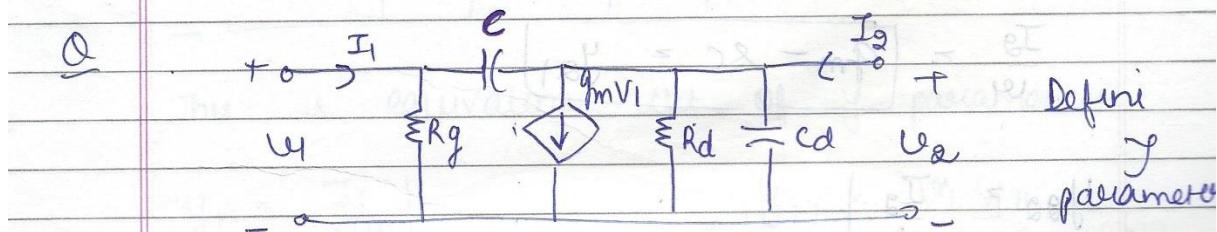

$$I_1 = v_1 \left[\frac{1}{Rg} + \frac{1}{SC} \right]$$


$$Y_{12} = \frac{I_1}{v_2} \Big|_{v_1=0}$$

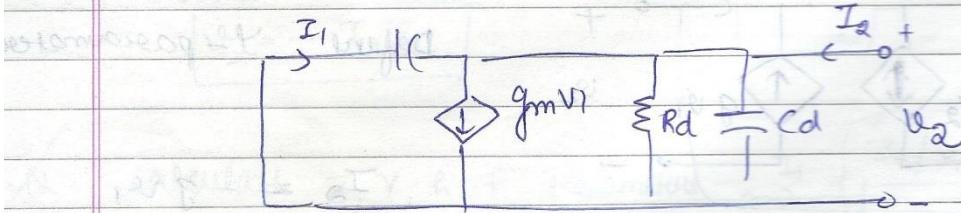

$$-I_1 \frac{1}{SC} = v_2$$

$$\frac{I_1}{v_2} = -SC$$

$$Y_{21} = \frac{I_2}{v_1} \Big|_{v_2=0}$$

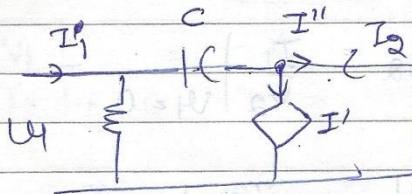

$$-I'' + I' = I_2$$

$$v_1 = \frac{1}{SC} I''$$

$$I_2 = g_m v_1 - SC v_1$$

$$I'' = SC v_1$$

$$I_2 = (g_m - SC) v_1$$

$$\frac{I_2}{v_1} = \boxed{g_m - SC = Y_{21}}$$

$$Y_{22} = \frac{I_2}{v_2} \Big|_{v_1=0}$$

$$I_2 - v_2 \left[\frac{1}{CdS} + \frac{1}{Rd} \right] + g_m v_1 = I_1$$


$$\frac{I_2}{v_2} = \frac{1}{SC}$$

$$v_1 = 0$$

$$\frac{I_2}{v_2} = \frac{1}{SC}$$

$$\frac{1}{C_8} \left(I_2 - v_2 C_{ds} - \frac{v_2}{R_d} \right) = V_2$$

$$\frac{I_2}{V_2} = ?$$

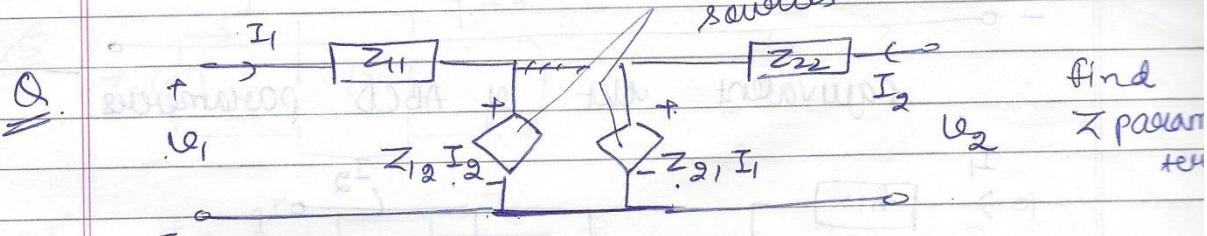


$$Z_{11} = \frac{V_1}{I_1} \quad | \quad I_2 = 0$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$Z_{11} = \frac{Z_{11} I_1}{I_1}$$

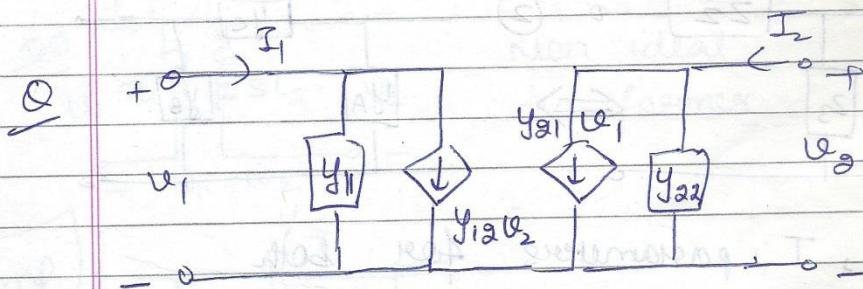This is equivalent net of \$Z\$-parameters.



This is equivalent net of \$Y\$-parameters.

$$Y_{11} = \frac{I_1}{V_1} \quad | \quad V_2 = 0$$


$$Y_{11} = \frac{Y_1 Y_{11}}{Y_1}$$

$$I_1 = V_1 Y_1 + Y_{12} V_2$$


$$Y_{11} = Y_{11}$$

$$Y_{12} = \frac{I_1}{V_2} \quad | \quad V_1 = 0$$

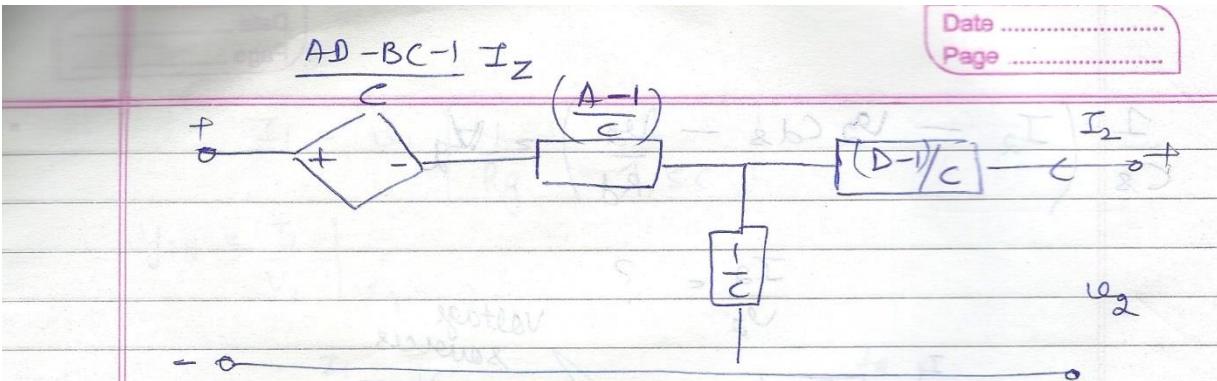
$$Y_{12} = \frac{Y_{12} Y_2}{Y_2} = Y_{12}$$



equivalent circuit of ABCD parameters

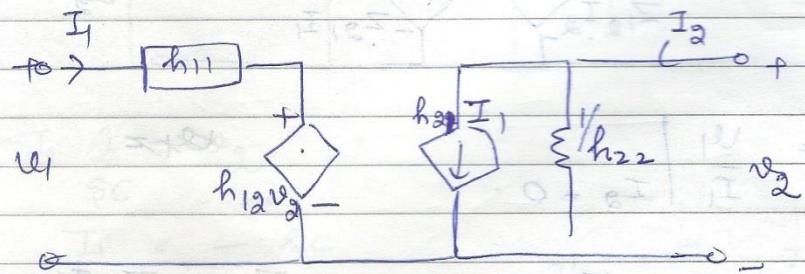

* Problems related to T and Π m/w

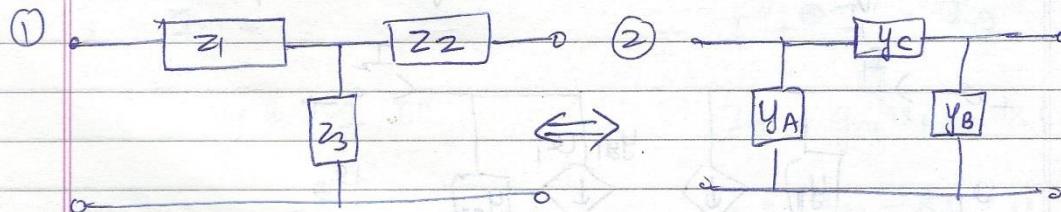

Q1 Find z , y , T parameters for both


After calculating ^{on}, equate the parameters of both T & Π .






Q2 Also check cond. of reciprocity for both

Q3 Calculate Y_{in}

i.e.
$$\frac{I_1}{V_1} \Big|_{Z_L}$$

in terms of Y or Z parameters

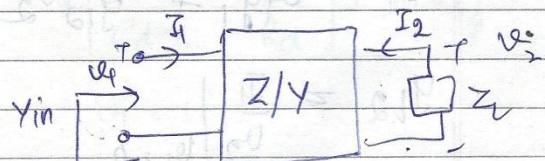

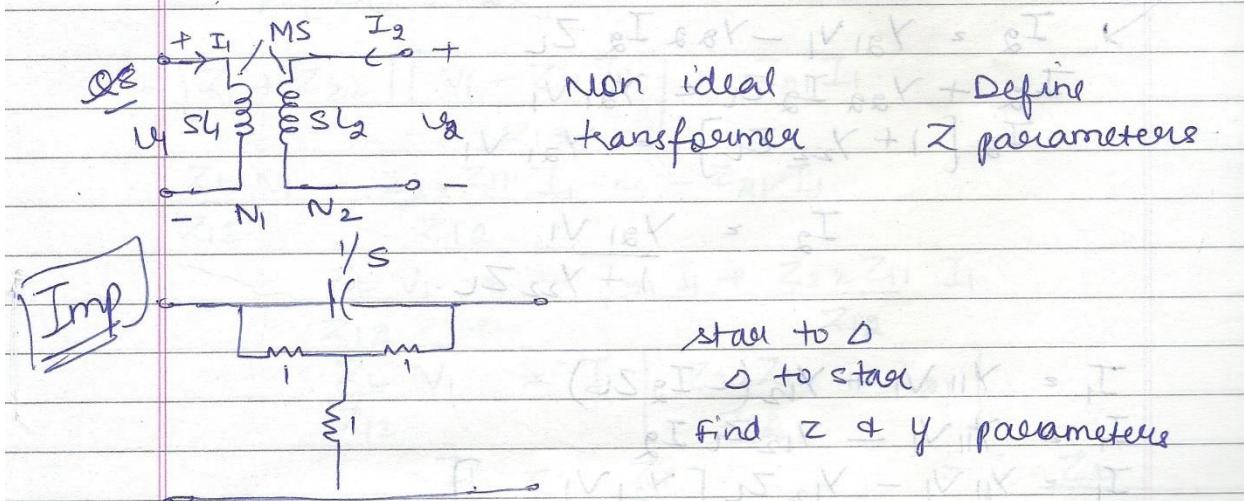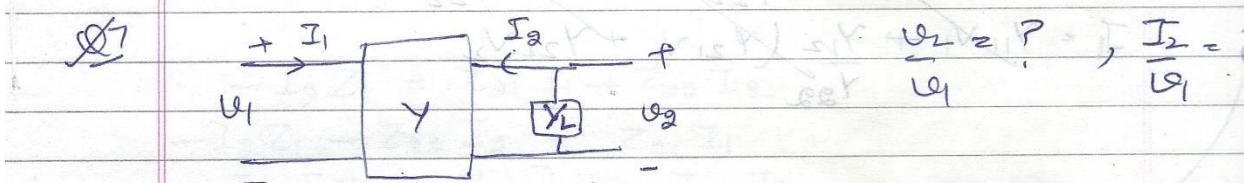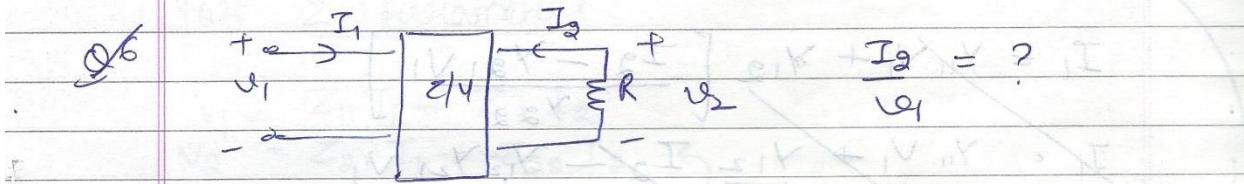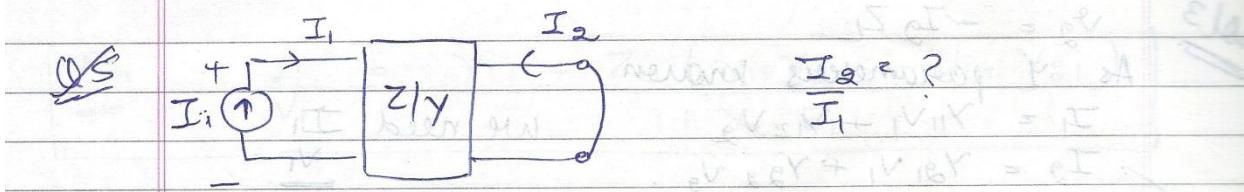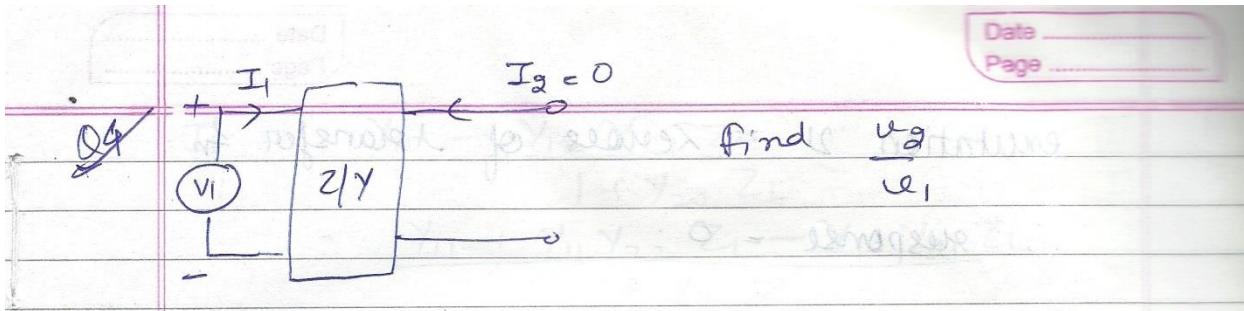

If $Z_{11} = \frac{3s+2}{2s+1}$

If excitation is $5e^{-2/3t}$

for steady state

NOW here V of excitation $-2/3$
Zeros of transfer fn $= -2/3$

excitation $V_1 = \text{Zeroes of transfer fn}$

$\therefore \text{response} = 0$

~~sol3~~ $V_2 = -I_2 Z_L$

As y parameters known

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{we need } \underline{\frac{I_1}{V_1}}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$I_1 = Y_{11} V_1 + Y_{12} \left[\frac{I_2 - Y_{21} V_1}{Y_{22}} \right]$$

$$I_1 = Y_{11} V_1 + \frac{Y_{12}}{Y_{22}} I_2 - \frac{Y_{12} Y_{21}}{Y_{22}} V_1$$

$$I_1 = Y_{11} V_1 + \frac{Y_{12}}{Y_{22}} (Y_{21} V_1 + Y_{22} V_2)$$

$$\rightarrow I_2 = Y_{21} V_1 - Y_{22} I_2 Z_L$$

$$I_2 + Y_{22} I_2 Z_L = Y_{21} V_1$$

$$I_2 [1 + Y_{22} Z_L] = Y_{21} V_1$$

$$I_2 = \frac{Y_{21} V_1}{1 + Y_{22} Z_L}$$

$$I_1 = Y_{11} V_1 + Y_{12} (-I_2 Z_L)$$

$$I_1 = Y_{11} V_1 - Y_{12} Z_L I_2$$

$$I_1 = Y_{11} V_1 - Y_{12} Z_L \left[\frac{Y_{21} V_1}{1 + Y_{22} Z_L} \right]$$

$$I_1 = Y_{11} V_1 - \frac{Y_{12} Y_{21} Z_L V_1}{1 + Y_{22} Z_L}$$

$$I_1 = V_1 \left[Y_{11} - \frac{Y_{12} Y_{21} Z_L}{1 + Y_{22} Z_L} \right]$$

$$\frac{I_1}{V_1} = \frac{Y_{11} - Y_{12}Y_{21}Z_L}{1 + Y_{22}Z_L}$$

$$= \frac{Y_{11} + Y_{11}Y_{22}Z_L - Y_{12}Y_{21}Z_L}{1 + Y_{22}Z_L}$$

$$\left[\frac{y_{in}^o}{=} = \frac{I_1}{V_1} = \frac{Y_{11} + Z_L(Y_{11}Y_{22} - Y_{12}Y_{21})}{1 + Y_{22}Z_L} \right]$$

for Z -parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \hookrightarrow$$

$$V_2 = -I_2Z_L$$

$$-I_2Z_L = Z_{21}I_1 + Z_{22}I_2$$

$$-I_2Z_L - Z_{22}I_2 = Z_{21}I_1$$

$$-I_2[Z_L + Z_{22}] = Z_{21}I_1$$

$$+ [Z_L + Z_{22}] \left[\frac{V_1 - Z_{11}I_1}{Z_{12}} \right] = -Z_{21}I_1$$

$$\frac{Z_L V_1 - Z_{22}Z_{11}}{Z_{12}} I_1 = -Z_{21}I_1$$

$$\frac{Z_L V_1}{Z_{12}} = -Z_{21}I_1 + \frac{Z_{22}Z_{11}}{Z_{12}} I_1$$

$$\frac{Z_L V_1}{Z_{12}} = I_1 \left[\frac{Z_{22}Z_{11}}{Z_{12}} + Z_{21} \right]$$

$$\frac{I_1}{V_1} = \frac{\frac{Z_L}{Z_{12}}}{\frac{Z_{22}Z_{11}}{Z_{12}} + Z_{21}}$$

4. $I_1 = Y_{11}V_1 + Y_{12}V_2$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$I_2 = 0$$

$$Y_{21}V_1 = -Y_{22}V_2$$


$$\left[\begin{array}{l} V_2 = -\frac{Y_{21}}{Y_{22}}V_1 \\ V_1 \end{array} \right] \quad I_1 = \frac{V_1}{Y_{11}} = \frac{V}{Y}$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$V_1 = Z_{11}I_1$$
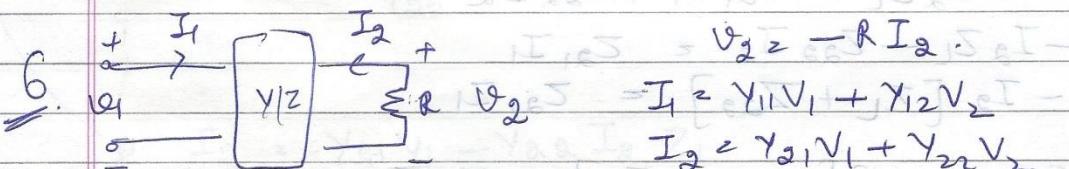
$$\left[\begin{array}{l} V_2 = \frac{Z_{21}}{Z_{11}}I_1 \\ V_1 \end{array} \right]$$



$$I_2 = Y_{21}V_1 + Y_{22}(-RI_2)$$

$$I_2 [1 + Y_{22}R] = Y_{21}V_1$$

$$I_2 = \frac{Y_{21}V_1}{1 + Y_{22}R}$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$


$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$V_1 = Z_{11} \left[\frac{V_2 - Z_{22}I_2}{Z_{21}} \right] + Z_{12}I_2$$

$$V_1 = -\frac{Z_{11}}{Z_{21}} [R + Z_{22}] I_2 + Z_{12}I_2$$

$$V_1 = I_2 \left[Z_{12} - \frac{Z_{11}}{Z_{21}} (R + Z_{22}) \right]$$
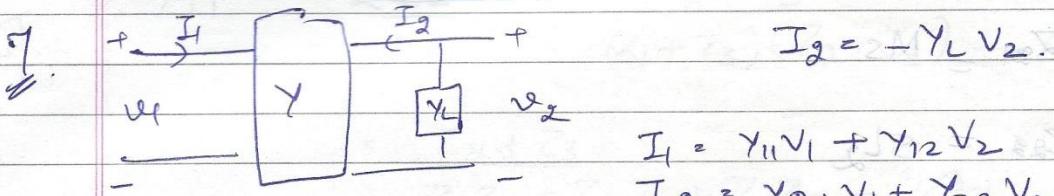
$$\boxed{\frac{I_2}{V_1} = \frac{Z_{21}}{Z_{12} Z_{21} - Z_{11} R - Z_{11} Z_{22}}}$$



$$I_2 = -Y_L V_2$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$\boxed{\frac{V_2}{V_1} = \frac{-Y_L V_2}{Y_{21} V_1 + Y_{22} V_2} = \frac{-Y_{21}}{Y_{21} + Y_{22}}}$$

$$I_2 = Y_{21} V_1 + Y_{22} \left(\frac{-I_2}{Y_L} \right) \left[-\frac{I_2}{Y_L} \right]$$

$$I_2 + \frac{I_2}{Y_L} Y_{22} = Y_{21} V_1$$

$$I_2 \left[1 + \frac{Y_{22}}{Y_L} \right] = Y_{21} V_1$$

$$\frac{I_2}{V_1} = \frac{Y_{21}}{1 + \frac{Y_{22}}{Y_L}}$$

$$\boxed{\frac{I_2}{V_1} = \frac{Y_{21} Y_L}{1 + Y_{22}}}$$

8

$$V_1 = S_L I_1 + S_M I_2$$

$$V_2 = S_M I_1 + S_L I_2$$

$$Z_{11} = \boxed{\frac{V_1}{I_1} \Big|_{I_2=0} = S_L}$$

$$Z_{12} = \frac{V_1}{I_2} \quad I_1 = 0$$

$$= M_S$$

$$\frac{V_1}{I_2} = \frac{N_1}{N_2}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$Z_{21} = M_S$$

$$Z_{22} = S L_2$$

S $I_1 = Y_{11} V_1 + Y_{12} V_2$

L $I_2 = Y_{21} V_1 + Y_{22} V_2$

$$V_2 = 0 \Rightarrow I_1 = Y_{11} V_1$$

$$I_2 = Y_{21} V_1$$

$$\frac{I_2}{I_1} = \frac{Y_{21}}{Y_{11}}$$

$$\textcircled{D} \quad V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$Z_{21} I_1 = -Z_{22} I_2$$

$$\frac{I_2}{I_1} = -\frac{Z_{21}}{Z_{22}}$$

1 $Z_{11} = Z_1 + Z_3$

$$Z_{22} = Z_2 + Z_3$$

$$Z_{12} = Z_3$$

$$Z_{21} = Z_3$$

$$\Delta Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

$$\begin{bmatrix} Z_1 + Z_3 & Z_3 \\ Z_3 & Z_2 + Z_3 \end{bmatrix}$$

II

$$\begin{aligned} Y_{12} &= Y_{21} = -Y_3 \\ Y_{11} &= Y_1 + Y_3 \\ Y_{22} &= Y_2 + Y_3 \end{aligned}$$

Y

I

$$Y_{11} = \frac{Z_{22}}{\Delta Z} = \frac{Z_2 + Z_3}{(Z_1 + Z_3)(Z_2 + Z_3) - Z_3(Z_3)}$$

$$= \frac{Z_2 + Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_3 Z_2 - Z_3^2 + Z_3^2}$$

$$Y_{12} = -\frac{Z_{11}}{\Delta Z} = -\frac{Z_1 + Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_3 Z_2 - Z_3^2}$$

$$Y_{21} = -\frac{Z_{21}}{\Delta Z} = -\frac{Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_3 Z_2 - Z_3^2}$$

$$Y_{22} = \frac{Z_{11}}{\Delta Z} = \frac{Z_1 + Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_3 Z_2 - Z_3^2}$$

II m/w

$$Z_{11} = \frac{Y_{22}}{\Delta Y} = \begin{bmatrix} Y_1 + Y_3 & -Y_3 \\ -Y_3 & Y_2 + Y_3 \end{bmatrix}$$

$$\begin{aligned} \Delta Y &= (Y_1 + Y_3)(Y_2 + Y_3) - Y_3^2 \\ &= Y_1 Y_2 + Y_1 Y_3 + Y_3^2 - Y_3^2 + Y_3 Y_2 \end{aligned}$$

$$Z_{11} = \frac{Y_1 + Y_3}{Y_1 Y_2 + Y_1 Y_3 + Y_3 Y_2}$$

$$Z_{12} = -\frac{Y_{12}}{\Delta Y} = \frac{Y_3}{Y_1 Y_2 + Y_1 Y_3 + Y_3 Y_2}$$


$$Z_{21} = -\frac{Y_{21}}{\partial Y} = \frac{Y_3}{\partial Y}$$

$$Z_{22} = \frac{Y_{11}}{\partial Y} = \frac{Y_1 + Y_3}{\partial Y}$$

Now

$$Z_1 + Z_3 = \frac{Y_1 + Y_3}{Y_1 Y_2 + Y_1 Y_3 + Y_2 Y_3}$$

Similarly equate other

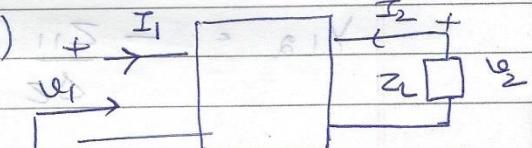Q $Z_{in} = \frac{V_1}{I_1} = -Z_L$ (given) \rightarrow 

find h parameters.

Sol

$$V_2 = -I_2 Z_L$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$\boxed{\frac{V_1}{I_1} = \frac{V_2}{I_2} = k = -Z_L}$$

$$V_1 = k I_1$$

$$V_2 = k I_2$$

$$I_{21} = \frac{V_1}{I_1}$$

$$k I_1 = h_{11} I_1 + h_{12} k I_2$$

$$I_2 = h_{21} I_1 + h_{22} k I_2$$

Ans.

$$\begin{bmatrix} 0 & k \\ 1/k & 0 \end{bmatrix}$$

$$(k - h_{11}) I_1 = h_{12} k I_2 \quad (1) \quad \frac{V_1}{I_1} = h_{21}$$

$$(1 - h_{22} k) I_2 = h_{21} I_1 \quad \frac{V_2}{I_2} = \frac{I_1}{I_2}$$


~~$$(k - h_{11}) I_1 = h_{12} k I_2$$~~

~~$$h_{21} I_1 = (1 - h_{22} k) I_2$$~~

~~$$\frac{I_1}{I_2} = \frac{(1 - h_{22} k)}{h_{21}}$$~~


From
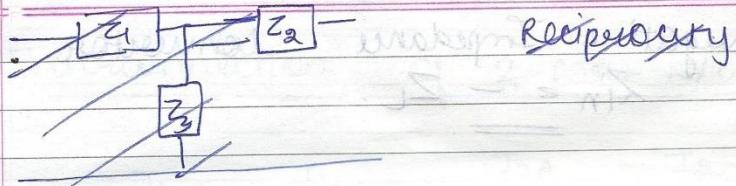
$$\begin{aligned} &\checkmark \text{ find } \frac{I_1}{I_2} \\ &\text{then } \frac{I_1}{I_2} = \frac{V_1}{V_2} \end{aligned}$$



INTERCONNECTION OF TWO PORT N/W

Parallel Inter Connection.

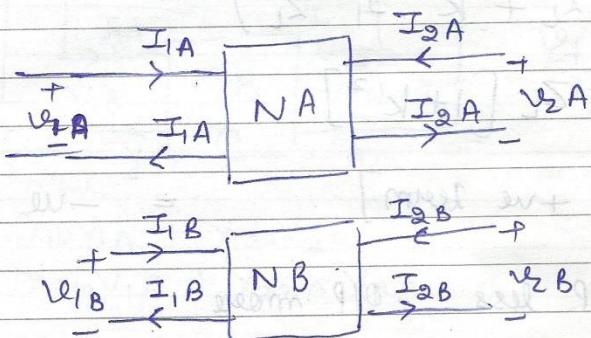

Voltage at port 1 of m/w A = Voltage at port 1 of m/w B.

$$\frac{V_1}{I_1} = \frac{V_2}{I_2} = k = -Z_L$$

$$V_1 = k' V_2 \quad I_1 = k' I_2$$

$$\text{Now } \frac{V_1}{I_1} = k = h_{11}$$

$$h_{21} = 1/k$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$V_1 = k I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + \frac{1}{k} V_2$$

$$V_1 = V_2 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + \frac{1}{k} V_2$$

This is Negative Impedance Converter

where $\underline{Z_{in}} = -Z_L$.

$$\begin{aligned} \text{Power} &= V_1 I_1 + V_2 I_2 \\ &- (I_1^2 Z_L + I_2^2 Z_L) \\ &- (I_1^2 Z_L + k'^2 I_1^2 Z_L) \\ &- I_1^2 Z_L [1 + k'^2] \\ &- [\text{+ve term}] = -\text{ve power} \end{aligned}$$

means I_{PP} less, O/P more

means this is active n/w like transistors, diodes etc are used inside the n/w.

for active n/w

$$\begin{aligned} P &= V_1 I_1 + V_2 I_2 + \dots + V_n I_n < 0 \\ \text{or } P &= V_1 I_1 + V_2 I_2 + \dots + V_n I_n \geq 0 \quad [\text{RLC n/w}] \\ \text{assume } & \end{aligned}$$

$$V_1 I_1 + V_2 I_2 + \dots + V_n I_n = 0$$


$$V_1 I_1 + I_{180^\circ} = 0 \quad V_{180^\circ} + I_{180^\circ} = 0$$

$$V_1 I_1 + I_{180^\circ} = 0 \quad V_{180^\circ} + I_{180^\circ} = 0$$

$$V_1 I_1 + I_{180^\circ} = 0 \quad V_{180^\circ} + I_{180^\circ} = 0$$

Interconnection of 2 port N/W

Parallel

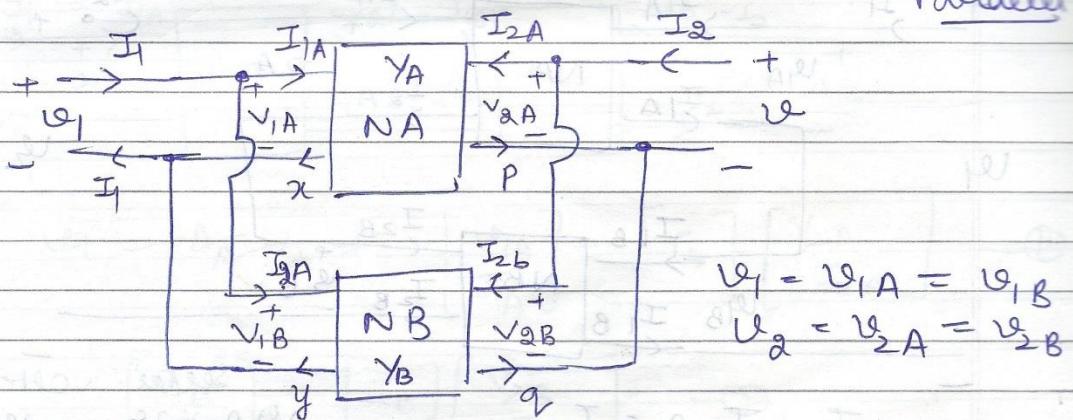

$$v_1 = v_{1A} = v_{1B}$$

$$v_2 = v_{2A} = v_{2B}$$

$$I_{1A} = Y_{11A}V_{1A} + Y_{12A}V_{2A}$$

$$I_{2A} = Y_{21A}V_{1A} + Y_{22A}V_{2A}$$

$$I_{1A} = Y_{11A}v_1 + Y_{12A}v_2$$

$$I_{2A} = Y_{21A}v_1 + Y_{22A}v_2$$

$$I_{1B} = Y_{11B}v_1 + Y_{12B}v_2$$

$$I_{2B} = Y_{21B}v_1 + Y_{22B}v_2$$

$$I_1 = Y_{11}v_1 + Y_{12}v_2$$

$$I_2 = Y_{21}v_1 + Y_{22}v_2$$

$$I_1 = I_{1A} + I_{1B}$$


$$I_2 = I_{2A} + I_{2B}$$

$$I_1 = (Y_{11A} + Y_{11B})v_1 + (Y_{12A} + Y_{12B})v_2$$

$$I_2 = (Y_{21A} + Y_{21B})v_1 + (Y_{22A} + Y_{22B})v_2$$

$$\left[\frac{I_1}{I_2} \right] = [Y] \left[\begin{array}{c} v_1 \\ v_2 \end{array} \right]$$

$$\boxed{[Y] = [Y_A] + [Y_B]}$$

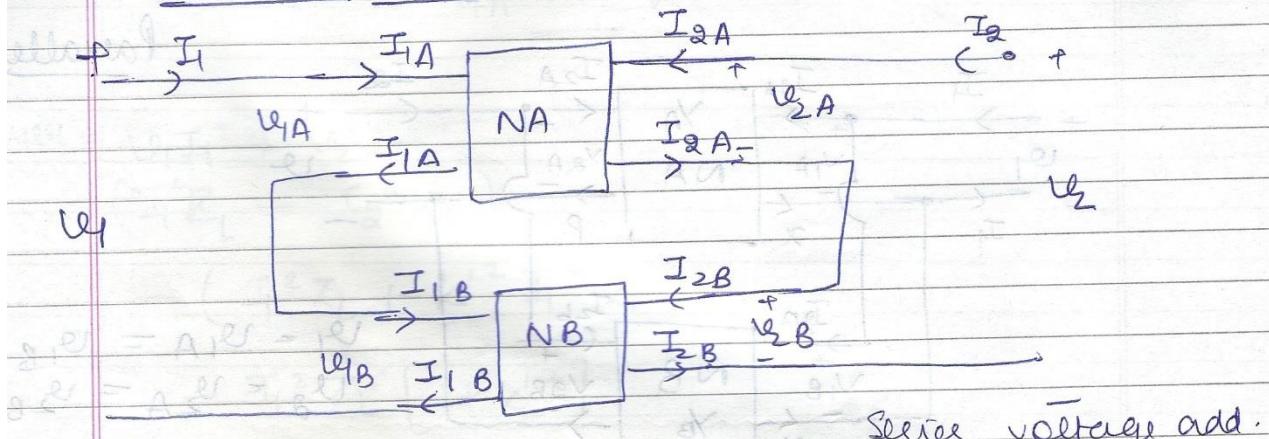Series Connection

$$I = I_{1A} = I_{1B}$$

$$I_2 = I_{2A} = I_{2B}$$

Series voltage add.

$$V_{1A} + V_{1B} = V_1$$

$$V_{2A} + V_{2B} = V_2$$

$$\begin{bmatrix} V_{1A} \\ V_{2A} \end{bmatrix} = [Z_A] \begin{bmatrix} I_{1A} \\ I_{2A} \end{bmatrix}$$

$$\begin{bmatrix} V \\ V \end{bmatrix} = [V_a] + [V_b]$$

$$[Z][I] = [Z_A][I_A]$$

$$+ [Z_B][I_B]$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

all equal

$$\therefore [Z] = [Z_A] + [Z_B]$$

combined of
whole nkt

$$\begin{bmatrix} V_{1B} \\ V_{2B} \end{bmatrix} = [Z_B] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \left(\begin{bmatrix} V_{1A} \\ V_{2A} \end{bmatrix} + \begin{bmatrix} V_{1B} \\ V_{2B} \end{bmatrix} \right) \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


$$= [Z_A + Z_B] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\therefore Z = [Z_A] + [Z_B]$$

$$[Z_A] + [Z_B] = [Z]$$

Cascade Connection

$$-I_2 = -I_{2B}$$

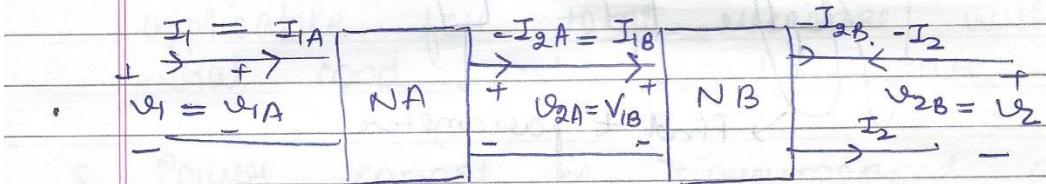

$$\begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = [T_A] \begin{bmatrix} v_{2A} \\ -I_{2A} \end{bmatrix} \quad \textcircled{1}$$

$$\begin{bmatrix} v_{1B} \\ I_{1B} \end{bmatrix} = [T_B] \begin{bmatrix} v_{2B} \\ -I_{2B} \end{bmatrix} \quad \textcircled{2}$$

$$\begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = [T] \begin{bmatrix} v_2 \\ -I_2 \end{bmatrix} \quad \textcircled{3}$$

$$\textcircled{1} = \begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = [T_A] \begin{bmatrix} v_{2A} \\ -I_{2A} \end{bmatrix}$$

↓

$$\begin{bmatrix} v_{1B} \\ I_{1B} \end{bmatrix}$$

From \textcircled{2}


$$\begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = [T_A] [T_B] \begin{bmatrix} v_{2B} \\ -I_{2B} \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = [T_A] [T_B] \begin{bmatrix} v_2 \\ -I_2 \end{bmatrix}$$

$$\boxed{[T] = [T_A][T_B]}$$

find T parameter
individually.

eg

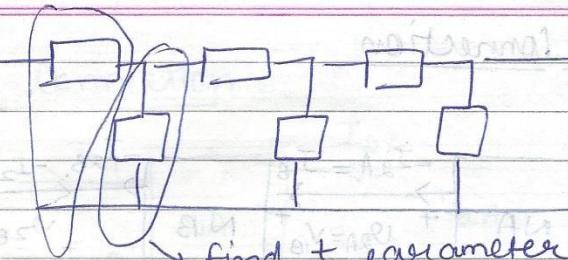

→ find t parameter

Now multiplication of matrices repetitively

NETWORK THEOREMS

- * In AC circuits or sinusoidal replace $s = j\omega$.


Superposition Theorem

In a linear n/w acted upon by several independent sources, response in any element of the n/w is the sum of responses obtained with one source acting at a time and the other sources being deactivated.


- * If dependant sources are present in the n/w then the dependant source will be untouched while calculating the response to one of the independent source.

- * Deactivation of source means short circuit for voltage source and open " " current "

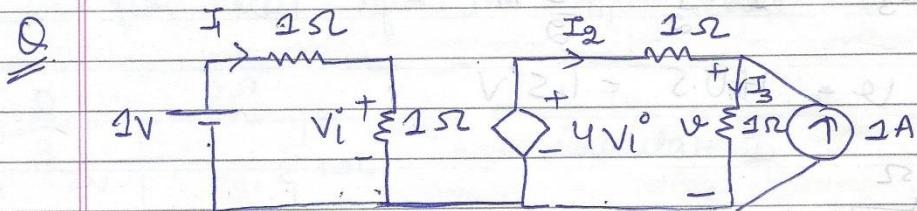- * During transient analysis or while calculating total response, superposition theorem is applicable for total response with zero initial cond and steady state response.
- * Power cannot be superimposed as it is non linearly related to V & I .



Calculate V , I_1 , I_2 , I_3 .

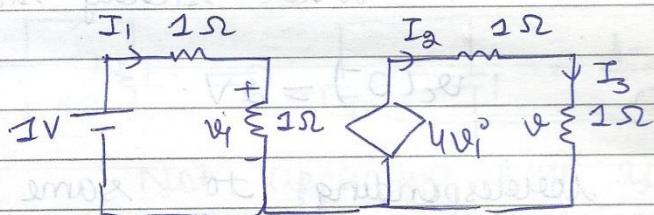

$$I = I_1 + \frac{V}{1} \quad 1 = I_1$$

$$2I_1 = 1$$

$$I_1 = \frac{1}{2}$$

$$V_i = \frac{1}{2} \times 1$$

$$= \frac{1}{2} V$$


$$4V_i = 2V$$

$$2V = I_2(1+1)$$

$$\boxed{I_2 = 1A = I_3}$$

$$V = \frac{1}{2} \times 1$$

$$\boxed{V = 1V}$$

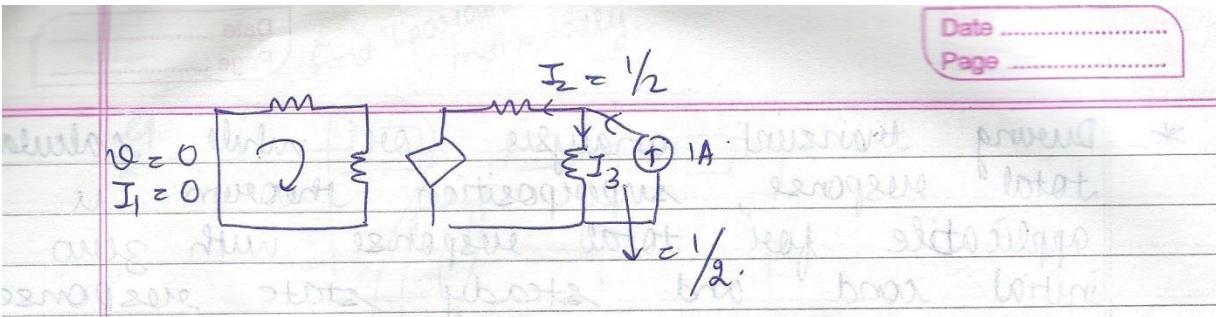


$$\therefore I_1 = \frac{1}{2} + 0 = \frac{1}{2} A$$

$$I_2 = 1 - \frac{1}{2} = \frac{1}{2} A$$

$$I_3 = 1 + \frac{1}{2} = \frac{3}{2} A$$

$$v = 1 + 0.5 = 1.5 V$$

Q

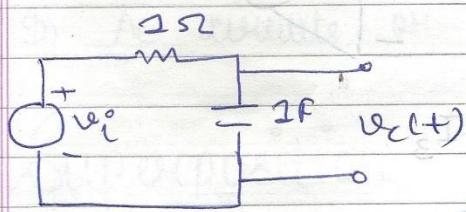

i) find voltage across capacitor under steady state


$$v_i = 4 + \cos t$$

$$v_c(0^-) = 2 V$$

- a) Total response corresponding to same excitation.

Soln
(i)


$$\text{find } \frac{v_c(s)}{v_i(s)}$$

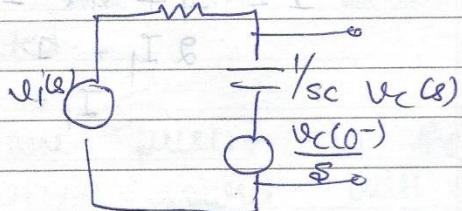

- (ii) for total find response corresponding to 4, cos t and $v_c(0^-)$ individually then add

2) Substitution Theorem

If an element (linear or non linear) in a m/w is replaced by a voltage source whose voltage at any instant of time is equal to the voltage existing across the element in the original element then the condition for rest of the m/w are unaltered.

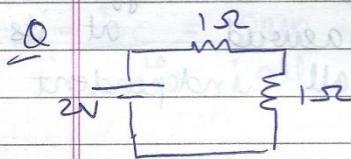

Calculate I

$$I = 1A$$

$$I = \frac{2V}{2\Omega} = 1A$$



Now I = 1A
same

$$\frac{1}{1A} = \frac{1}{1} = \frac{1-1}{0} = \text{no defined current}$$


which was actually 1

Not applicable here as this is not solvable

Alternatively

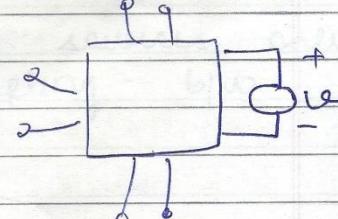
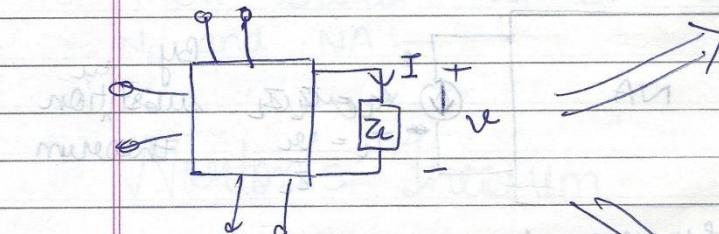


both substitutions
are possible

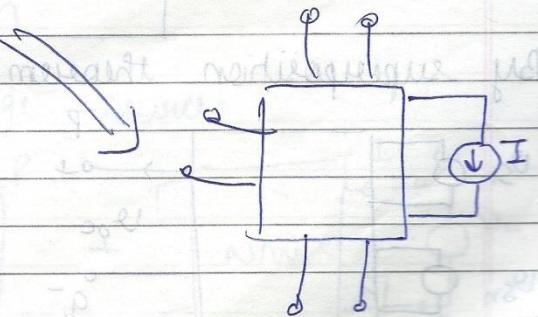


Thevenin's Theorem

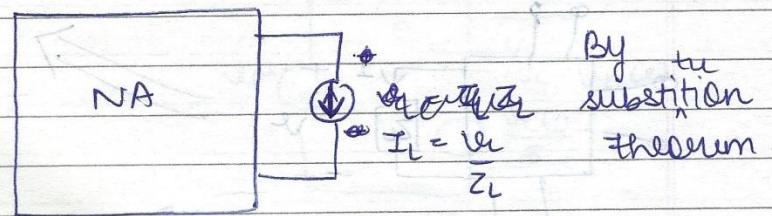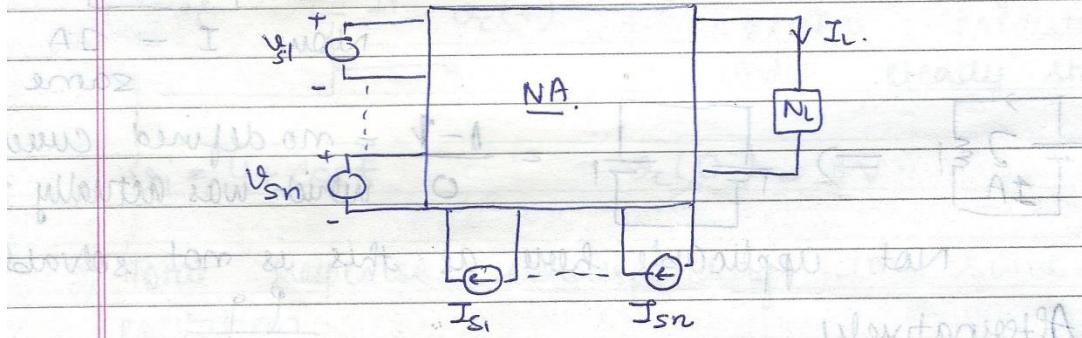An 2 terminal n/w NA containing linear elements & independent source is equivalent to a simpler n/w containing an independent voltage source in series with a 2-terminal n/w having impedance $Z_0(s)$. in series The source voltage is open circuit voltage of NA. The impedance $Z_0(s)$ is effective opp. impedance of N/W A measured at its terminals. after deactivating all independent sources in NA.




By superposition theorem

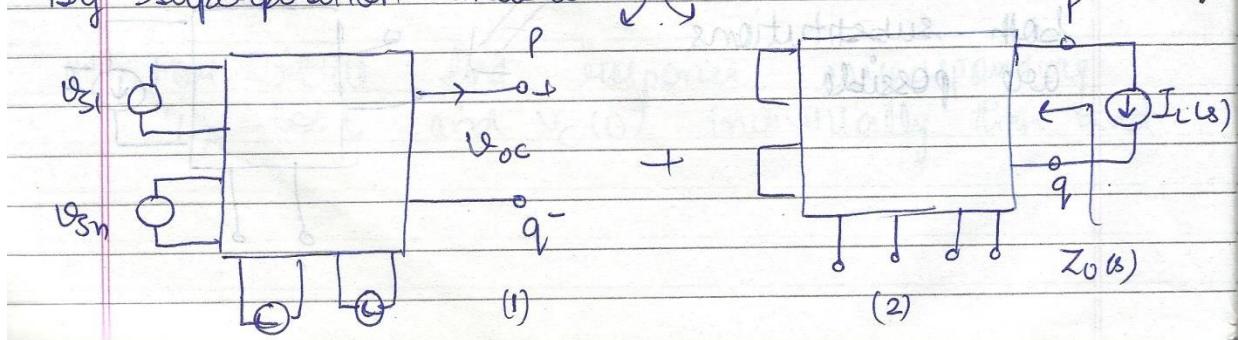

An (2)

$$P_{pq} = -I_L(s) Z_0(s)$$
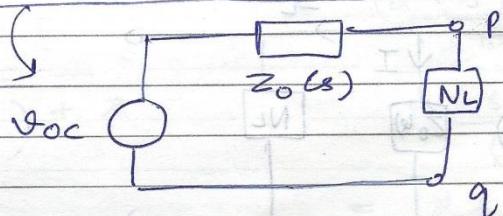
$$V_{pq} = V_L = V_{oc} - I_L(s) Z_0(s)$$




$V_{TH} = \underline{V_{oc}} =$ open circuit voltage b/w terminal p & q with all independent sources present in NA activated

$Z_{TH} = \underline{Z_0(s)}$ = Impedance of NA seen from terminal p & q with all independent sources present in that n/w deactivated

- 1) NA must be linear but N_L may be linear or non-linear.
- 2) Deactivation of independent sources only.
- 3) There should not be coupling b/w N_L and NA.


Noelton's Theorem

Substitution by voltage source

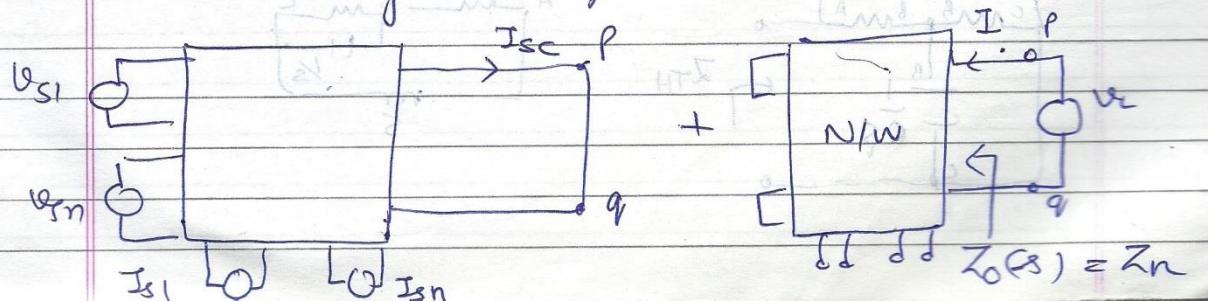

$$I_L = I_{SC} - I$$

$$I = \frac{V_L}{Z_0(s)}$$

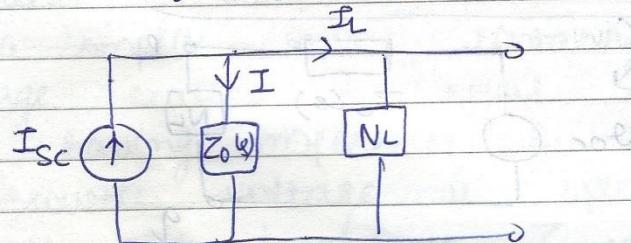

Now if pq is open circuit then $I_L = 0$

$$I_{SC} = I$$




$$I_{SC} = \frac{V_{OC}}{Z_0}$$

Norton's current

$$V_L = \left[\frac{V_{OC}}{Z_0} \right] \frac{Z_0(s)}{Z_0(s) + Z_L}$$

* All conditions of Thévenin are also applicable here in as NORTON

Q find $i(s)$
by Thévenin

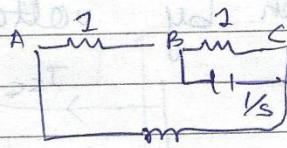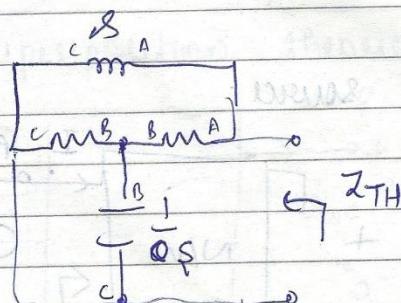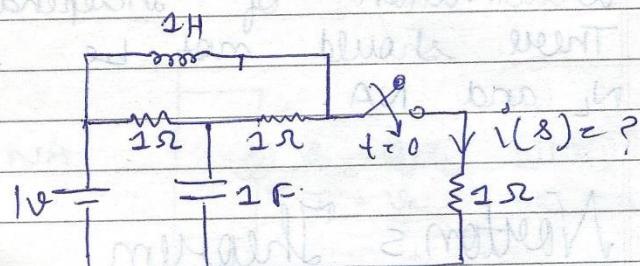


$$\frac{1 \times 1}{s} \quad \frac{1}{s} \quad \frac{1+1}{s+1} \quad \frac{1+s+1}{s+1} = \frac{2+s}{s+1}$$

$$\frac{1+s}{s} \quad \frac{s+1}{s}$$


$$\left(\frac{2+s}{s+1} \right) (s) = \frac{(2+s)s}{s+1}$$

$$\frac{(2+s)}{(s+1)} + s = \frac{2+s+s^2+s}{(s+1)}$$


$$= \frac{2s+s^2}{s^2+2s+2}$$

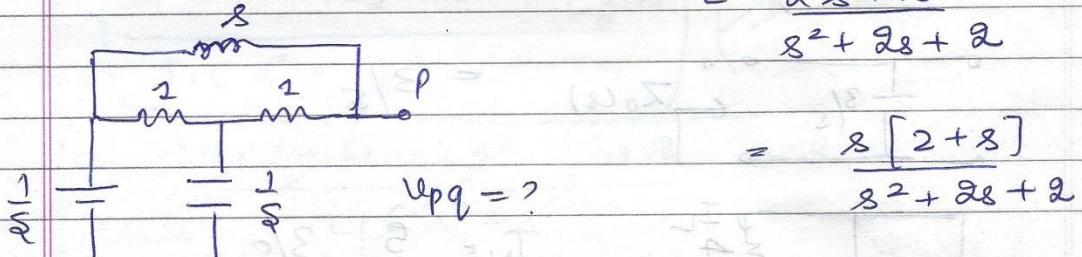


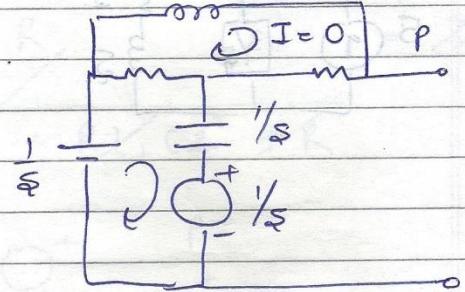
$$I = \frac{\frac{1}{s}}{\frac{s(2+s)}{s^2+2s+2}}$$



$$V_{TH} = V_{pq} = \frac{1}{s}$$

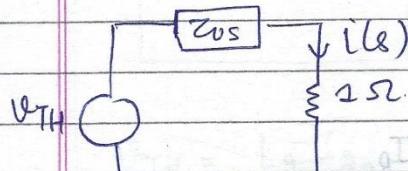

$$i(s) = \frac{V_{TH}}{Z_0(s) + 1}$$

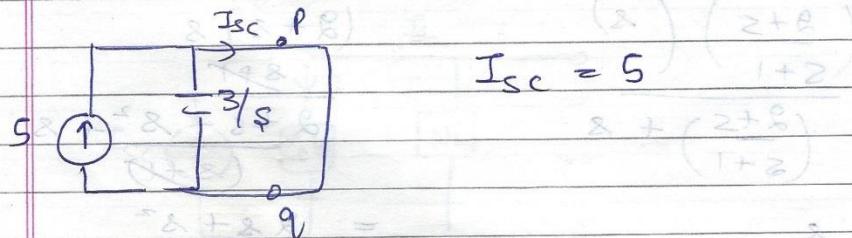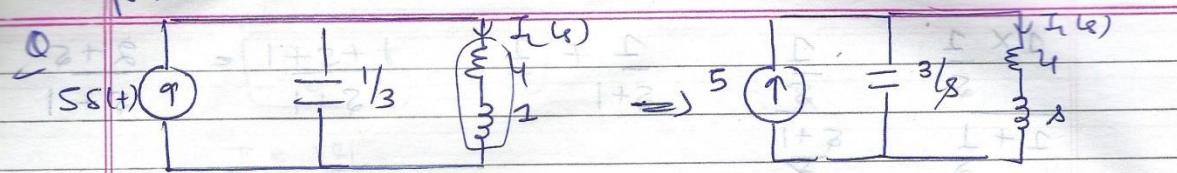

$$\frac{1}{Z_0(s)} = \frac{1}{\frac{3}{8}} = \frac{8}{3}$$


$$I_{L(s)} = \frac{5 \cdot \frac{3}{8}}{\frac{3}{8} + 4 + \frac{1}{4}}$$

$$= \frac{15}{81}$$

$$= \frac{15}{3 + 4 \cdot 8 + 8^2}$$

$$I_{L(s)} = \frac{15}{3 + 4 \cdot 8 + 8^2}$$

Now calculate $I_L(t)$

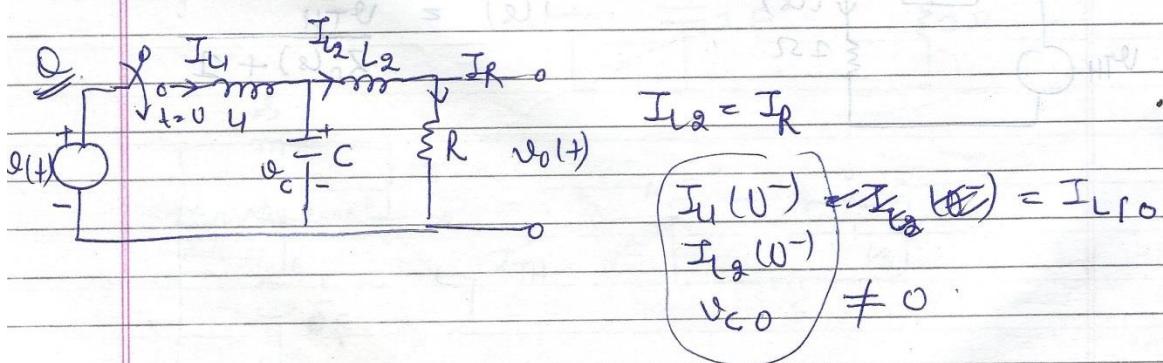

Calculate $V_C(t)$

Date
Page

$\frac{V_s}{Z_0 \text{ TH}} = \frac{1}{\frac{1}{C\omega} + \frac{1}{L_1\omega^2} + R}$

$\frac{1}{C\omega} = \frac{1}{L_1\omega^2 + 1}$

$\frac{1}{L_1\omega^2 + 1} = \frac{1}{L_1 C \omega^2 + 1}$

$\frac{1}{L_1 C \omega^2 + 1} = \frac{1}{\omega^2 + \frac{1}{L_1 C}}$



$\frac{1}{\omega^2 + \frac{1}{L_1 C}} = \frac{1}{\omega^2 + \frac{1}{L_1 C} + \frac{L_2}{L_1 L_2 C \omega^3} + \frac{L_2}{L_1 L_2 C \omega^3}}$

$\frac{1}{\omega^2 + \frac{1}{L_1 C} + \frac{L_2}{L_1 L_2 C \omega^3} + \frac{L_2}{L_1 L_2 C \omega^3}} = \frac{1}{\omega^2 + \frac{1}{L_1 C} + \frac{L_2}{L_1 L_2 C \omega^3} + \frac{L_2}{L_1 L_2 C \omega^3} + \frac{R}{L_1 C \omega^2}}$

$V_{TH} = \frac{V_s}{\omega^2 + \frac{1}{L_1 C} + \frac{L_2}{L_1 L_2 C \omega^3} + \frac{L_2}{L_1 L_2 C \omega^3} + \frac{R}{L_1 C \omega^2}}$


$V_{TH} = \frac{V_s + L_2 I_{20} - \frac{V_{CO}}{\omega}}{S L_1 + \frac{1}{C \omega}}$

voltage across capacitor

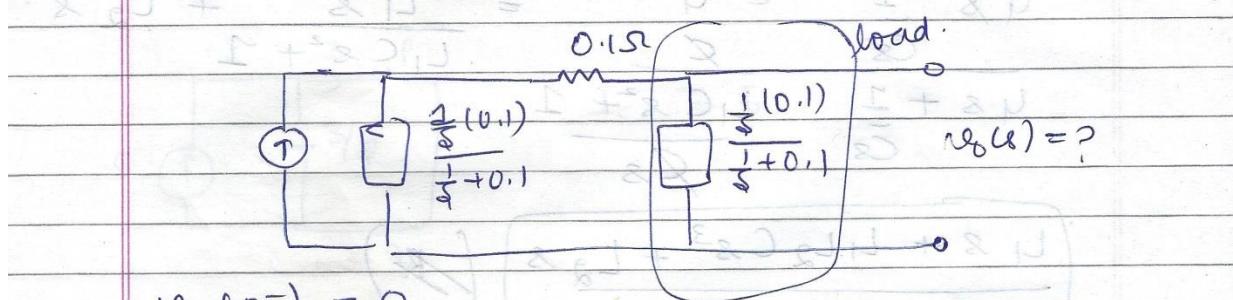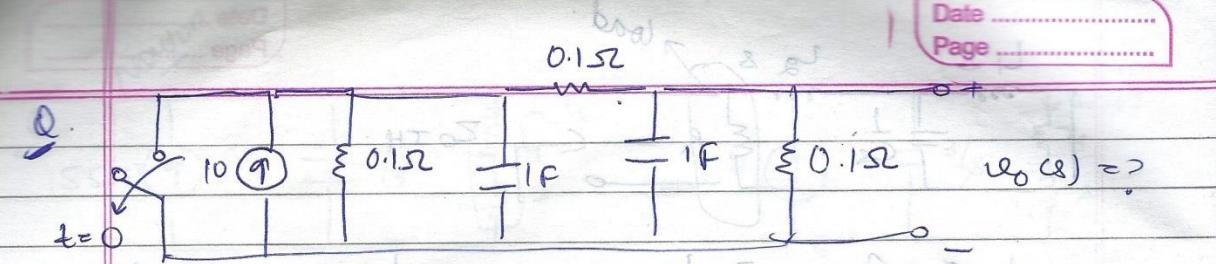

$$v_c(0^-) = 0$$


As initially current will be flowing
in

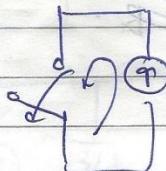

$I_{sc} \text{ } 0.1 \Omega$

$$I_{sc} = \frac{z}{z+0.1} + \frac{10}{s}$$

$$Z_0 = z + 0.1$$

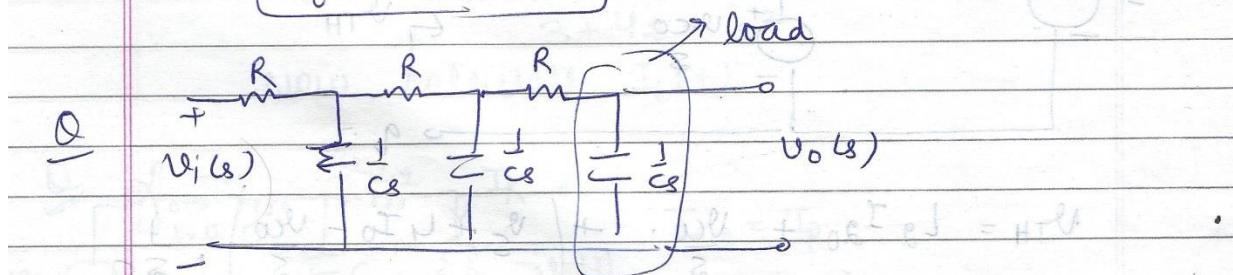


Calculate $\left| \frac{v_o(s)}{v_i(s)} \right|$

(ii) $\left| \frac{v_o(j\omega)}{v_i(j\omega)} \right| = \pi$ find ω_0

(iii) $\left| \frac{v_o}{v_i} \right| = ?$ if $\omega = \omega_0$

Millman's Theorem

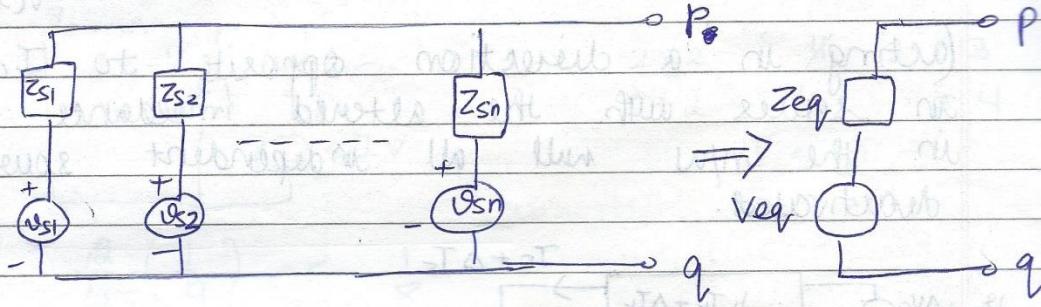

Acc. to NORTON theorem

$$Y_{sc} = \sum_{k=1}^n Y_{sk}$$

I_{sc} = Voltage across
Admittance

$$V_{eq} = \frac{\sum_{k=1}^n V_{sk} \cdot Y_{sk}}{\sum_{k=1}^n Y_{sk}}$$

$$Z_{eq} = \frac{1}{\sum_{k=1}^n Y_{sk}}$$


Compensation Theorem

In a linear n/w acted upon by independent sources and impedance $Z(s)$ carrying current is changed to $Z(s) + \Delta Z(s)$ then the


\Rightarrow if I_s has initial condition then the equivalent initial condition source remains the same
 \Rightarrow if ΔZ has some initial condition then the equivalent initial condition sources must be included.

incremental change produced in the whole n/w will be identical to those produced by a voltage source $\Delta Z(s) \cdot I(s)$
 $V(s)$

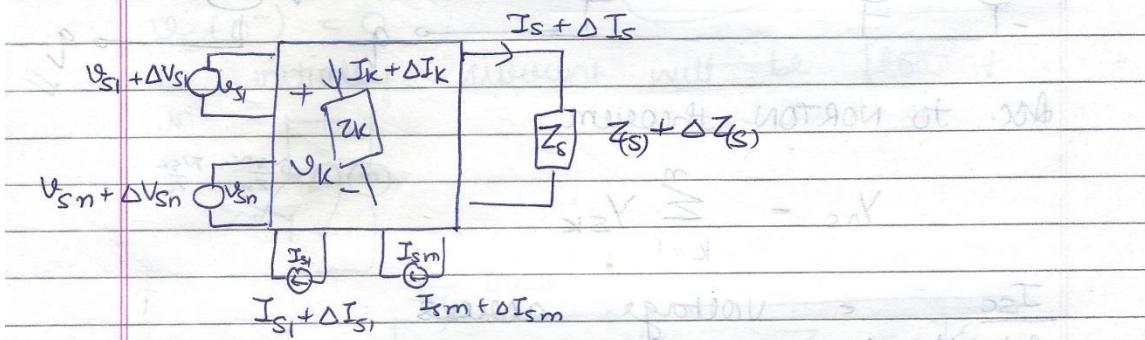
(acting in a direction opposite to $I(s)$)
 in series with the altered impedance in the n/w will all independent sources deactivated.


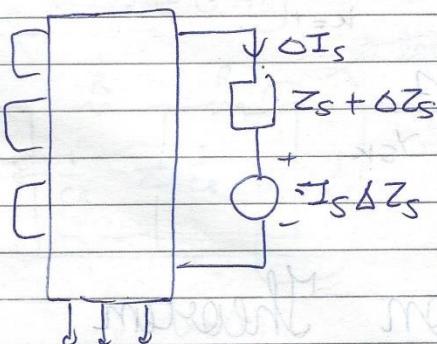
$$\begin{aligned}
 &= (I_s + \Delta I_s)(Z_s + \Delta Z_s) \\
 &= I_s Z_s + \Delta I_s (Z_s + \Delta Z_s) + I_s + \Delta Z_s
 \end{aligned}$$



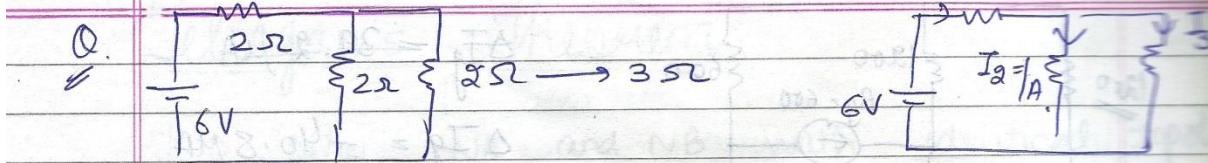- \Rightarrow ΔZ need not to be small.
- \Rightarrow it can be used to compute the incremental change in entire n/w.
- \Rightarrow There should not be any coupling b/w ΔZ and any other elements in the n/w.



$$\Delta I_1 = \frac{1}{8} \text{ A}$$

$$\Delta I_2 = \frac{1}{8} \text{ A}$$

$$I_3 = -\frac{1}{4} \text{ A}$$

$$\frac{2 \times 2}{2+2} = \frac{4}{4} = 1 + 3 = 4$$

$$I = \frac{1}{4} \text{ A}$$

$$\frac{2}{4} \left(\frac{1}{R_2} \right) = \frac{1}{8}$$

$$I_1' = 2 - \frac{1}{8}$$



$$I_2' = 1 + \frac{1}{8}$$

$$I_3' = 1 - \frac{1}{4}$$

Q. Nominal value of $R_x = 600 \Omega$

with tolerance value $\pm 5\%$.

Calculate I_g

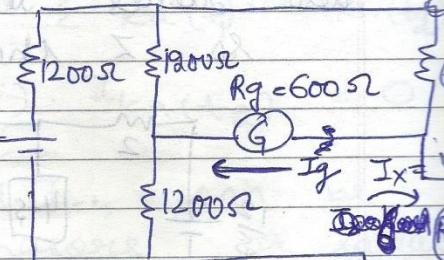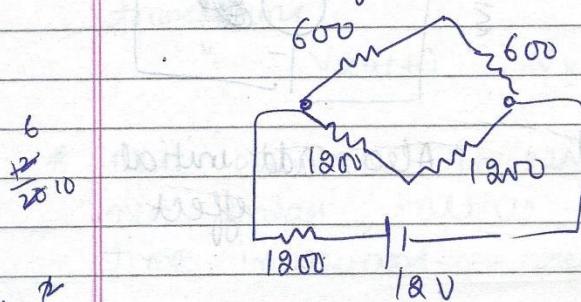

$$\frac{400}{1200 \times 2499} \approx 4.2 \text{ mA}$$

$$36.44 \text{ mA}$$

$$28.63 \text{ mA}$$

$$= 800 + 1200$$


$$= 2000$$

$$I = \frac{12}{2000} = 6 \text{ mA}$$

$$1000$$


$$30 \times 1200$$

$$570 < R_x < 630$$

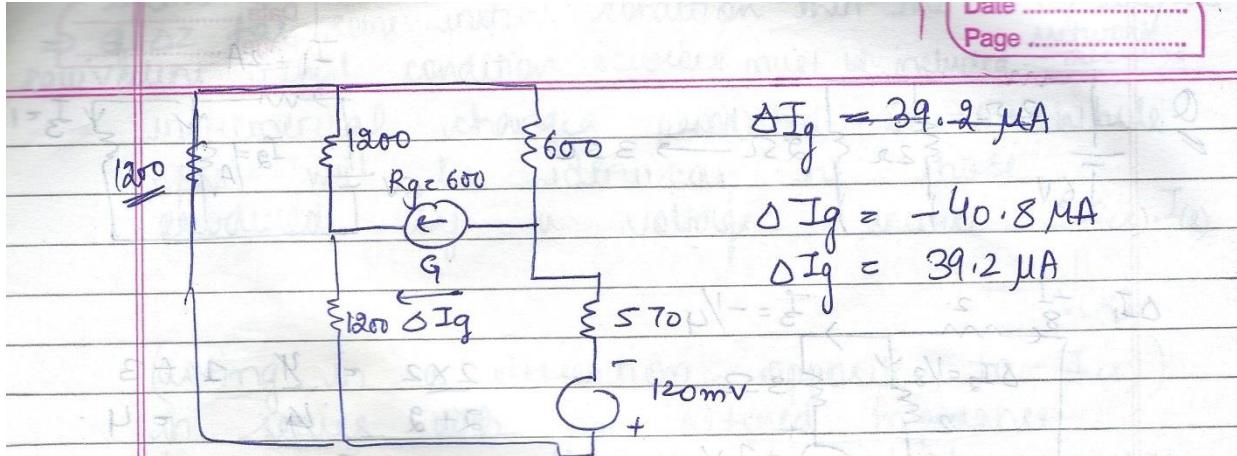


Q. Previously L acts as short circuit

$$I_s(0^-) = 2A$$

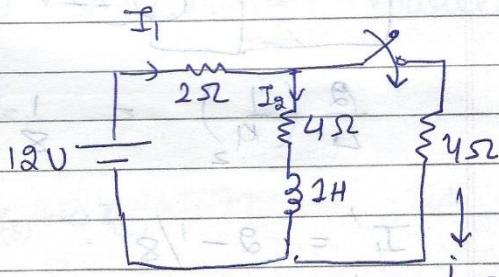

Now after closing switch impedance of L also comes in existence


so Z changes from Y to $Y + S$.

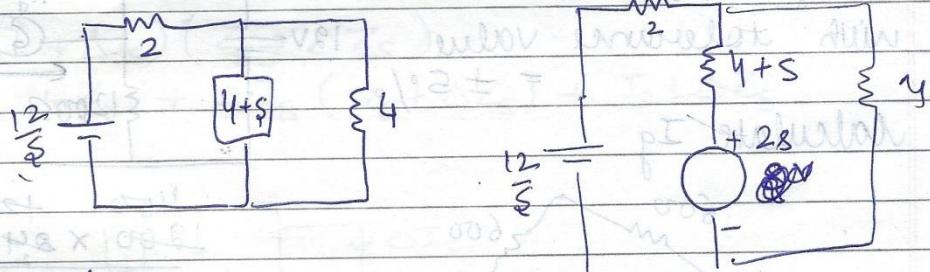

~~2(Y+Z) = 8~~


$$\underline{\underline{Q}} \quad 2(Y + S - X) \\ 2S$$

Also add initial effect

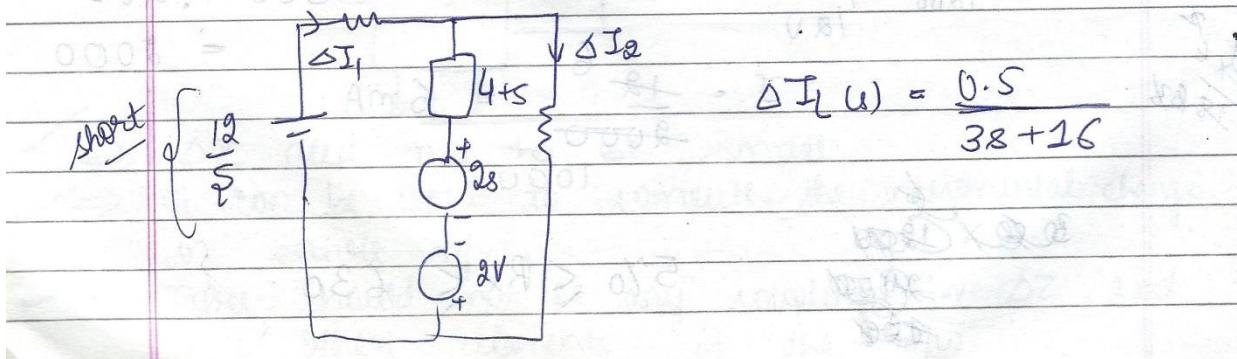

Tellegen's Theorem

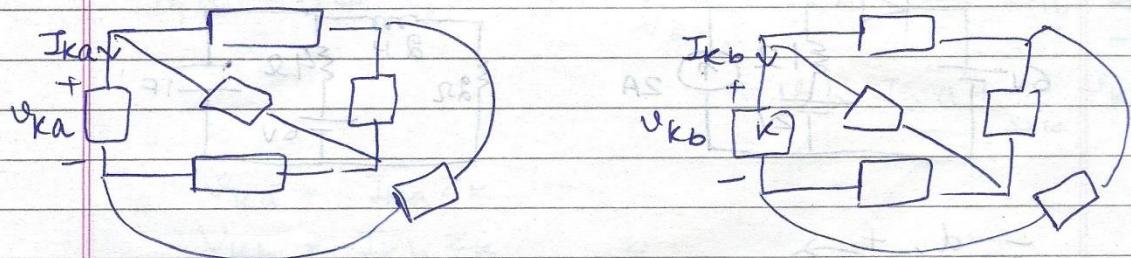Two N/W NA and NB with identical topology



Acc. to Tellegen's theorem

$$\sum v_{ka} I_{kb} = \sum v_{kb} I_{ka} \quad (\text{for all } k) = 0$$

* If A & B are different N/W but with identical topology then $\sum v_{ka}(+) \cdot I_{kb}(t_2) = \sum v_{kb}(+i) \cdot I_{ka}(t_2) = 0$



* v_{ka} and I_{ka} , v_{kb} and I_{kb} can be instantaneous values, phases or laplace transforms.

$$v_{ka(t)} \quad v_{ka(j\omega)} \quad v_{ka(s)}$$

* N/W elements in NA and NB may be linear, non linear, active, passive, time variant, time invariant, reciprocal, non reciprocal

* NA & NB both n/w's may be same and v_k , I_k measured at same instant or diff. instants of time, then also Tellegen's theorem applicable.

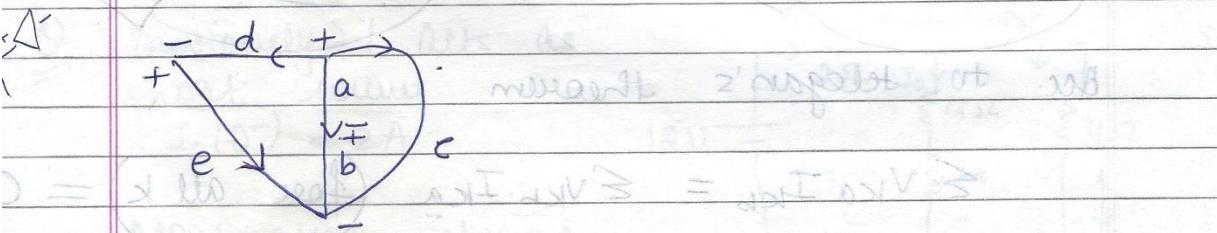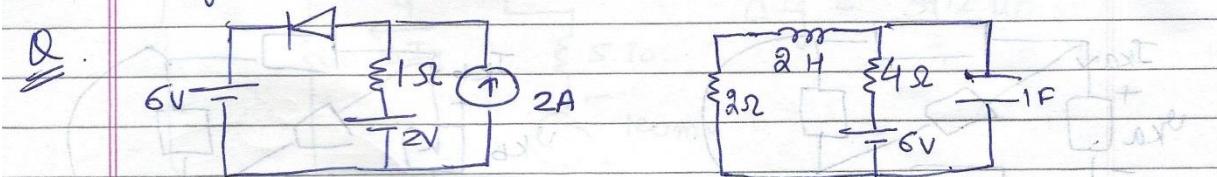
* If KCL / KVL not applicable for eg:- may be in case of non linear elements, then Tellegen's theorem not applicable.




	V_A	I_A	V_B	I_B
a	2V	2A		-1
b	2V	2A		-1
c	4V	-2A		0
d	-2V	0		1
e	6V	0		*

$$\sum V_A I_A = 0$$

Application of Tellegen's Theorem

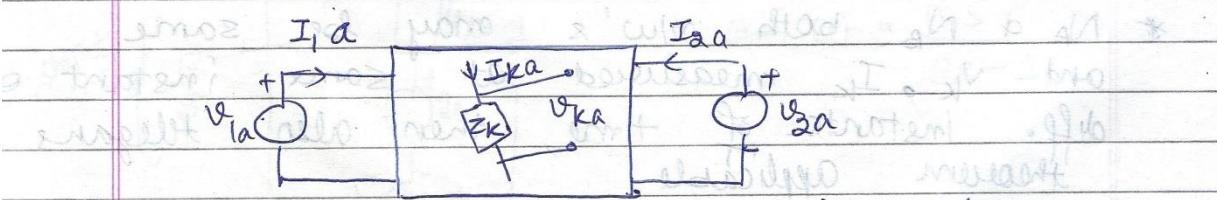

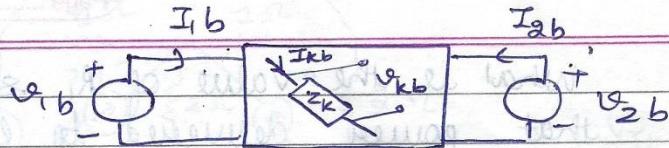N/w is reciprocal (means consists of $R(C(n))$)



$$v_{1a} \cdot I_{1b} + v_{2a} \cdot I_{2b} + \sum_k v_{ka} I_{kb} = v_{1b} \cdot I_{1a} \\ + v_{2b} \cdot I_{2a} + \sum_k v_{kb}$$

$$v_{ka} = I_{ka} Z_k$$

$$v_{kb} = I_{kb} Z_k$$

Put above : Then both side cancel.

$$v_{1a} \cdot I_{1b} + v_{2a} \cdot I_{2b} = v_{1b} \cdot I_{1a} + v_{2b} \cdot I_{2a}$$

for Z parameter reciprocity cond.

$$\text{or } I_{2a} = I_{1b} = 0$$

$$\text{or } I_{1a} = I_{2b} = 0$$

$$\text{i.e. } \frac{v_{2a}}{I_{1a}} = \frac{v_{1b}}{I_{2b}}$$


$$\text{or } z_{21} \Big|_{I_1=0} = z_{12} \Big|_{I_2=0}$$

Maximum Power Transfer Theorem

A n/w delivers max. power to a load R_L when $R_L =$ Thvenin's eq. resistance of n/w


In AC circuit for power to be max.

$$Z_L = Z_{TH}^*$$


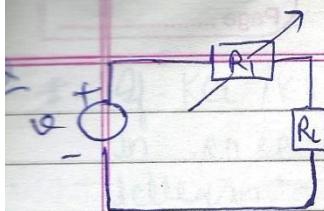


What is the value of R_L such that power delivered to load is max.

Soln $R_L = 0$

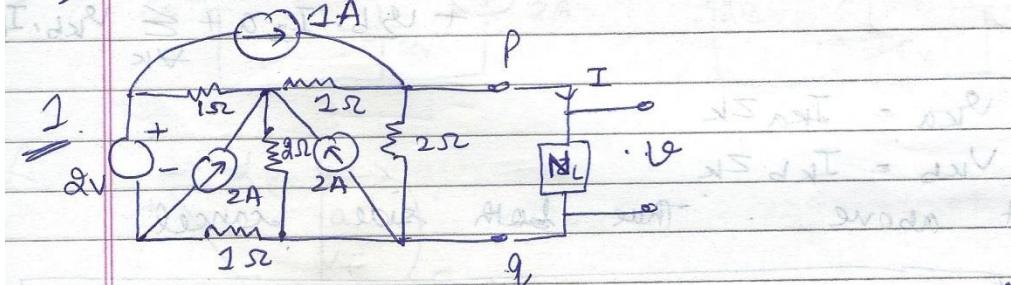

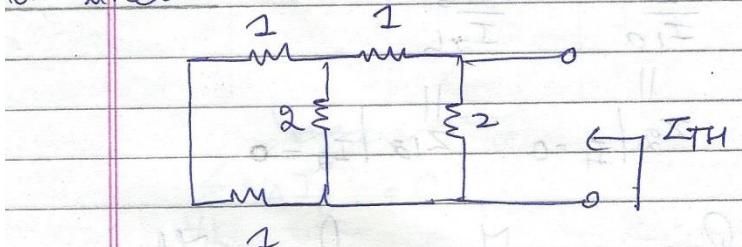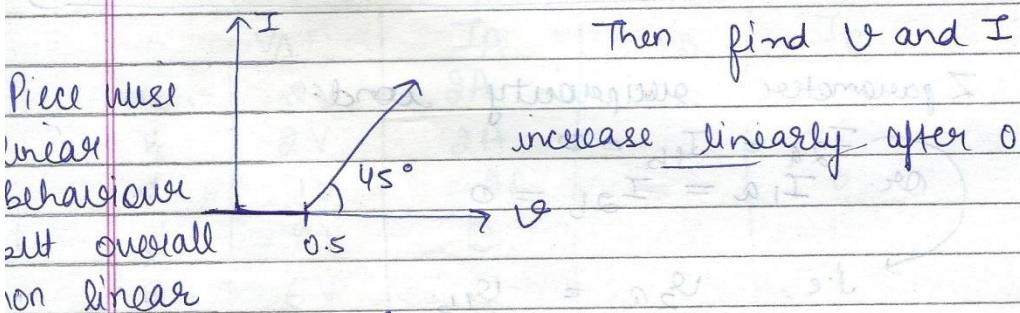
V-I characteristic represented graphically.



$$\frac{2+2}{2} = \frac{4}{2} = 2 + 1 = 2$$

$$\frac{2 \cdot 2}{2+2} = \frac{4}{4} = 1 \quad 1 + 1 = 2$$

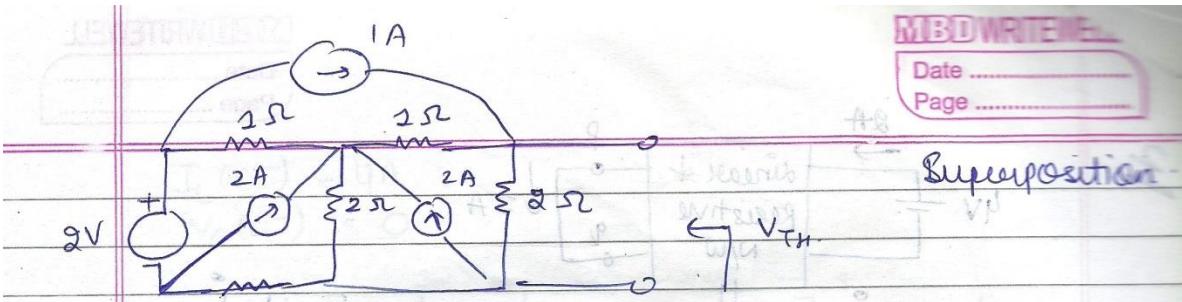
$$\frac{2 \cdot 2}{2+2} = \frac{4}{4} = 1 \Omega$$




MBDWRITER

Date
Page

Superposition

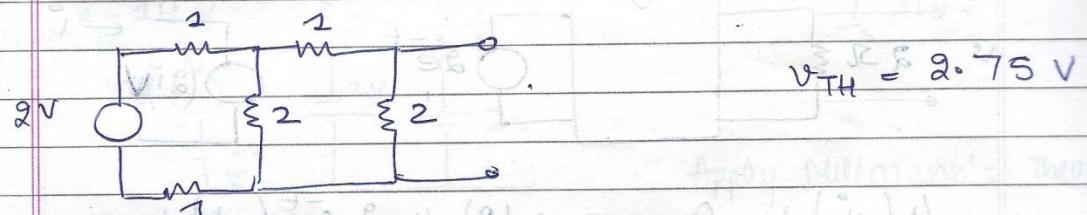

$$V_{TH} = 2.75 \text{ V}$$

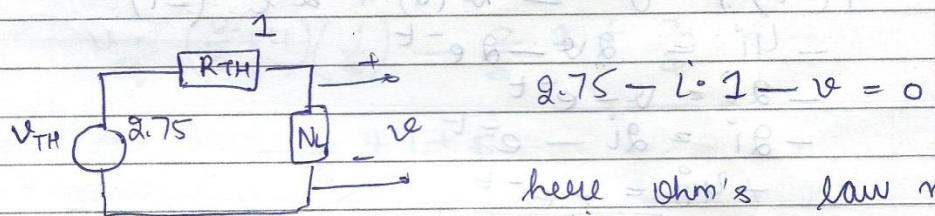

here Ohm's law not
valid as it is non linear

$$i = \begin{cases} 0 & v \leq 0.5 \\ v - 0.5 & v > 0.5 \end{cases}$$

Now two solutions possible as there are 2 regions

$$v \leq 0.5$$

$$i = 0$$

$$2.75 - i - v = 0$$

$$v = 2.75$$

↓

This itself is contradiction
as $v \leq 0.5$

$$v > 0.5$$

$$i = v - 0.5$$

$$2.75 - (v - 0.5) - v = 0$$


$$2.75 + 0.5 = 2v$$

$$3.25 = 2v$$

$$v = \frac{3.25}{2}$$

$$v = 1.625$$

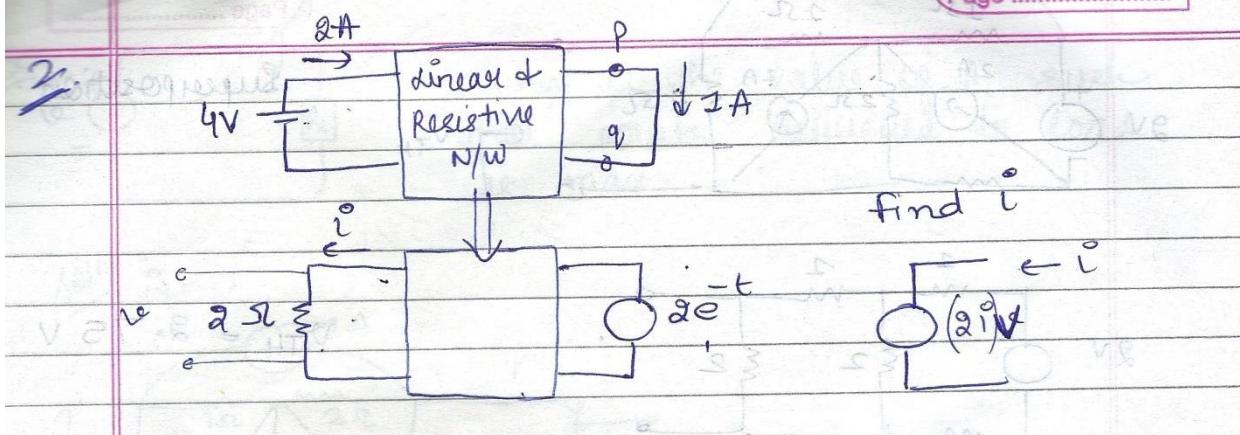There is no operating pt for m/w N_L under the application of given m/w N lies in the region of $v \leq 0.5$



$$4(-i) + 0 = v(8) + 2e^{-t}(-1)$$



$$-4i = 2v - 2e^{-t}$$

$$-2i = v - e^{-t}$$

$$-2i = 2i - e^{-t}$$

$$+4i = +e^{-t}$$


$$i = \frac{e^{-t}}{4}$$

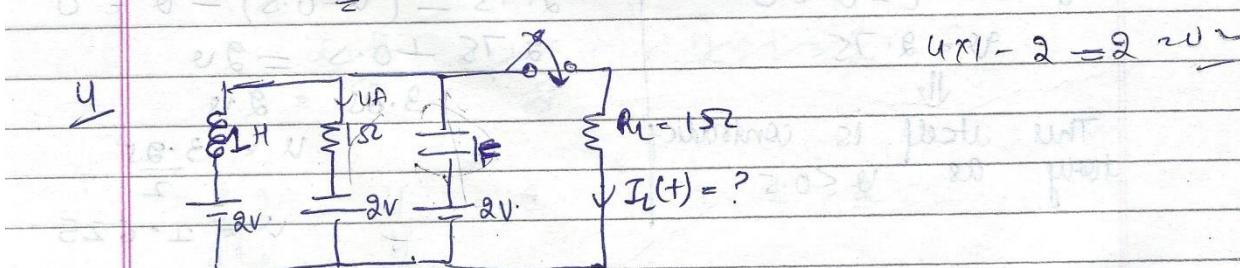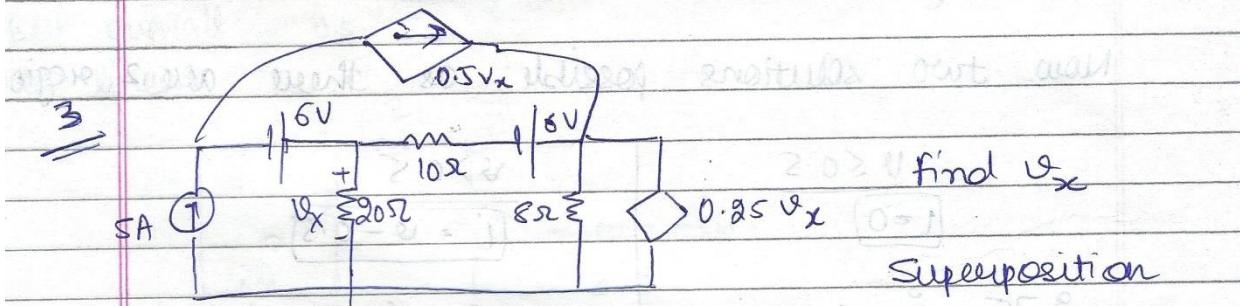

8. To find initial conditions

$$I_L(0^-) = 4A$$

$$V_C(0^-) = 0$$

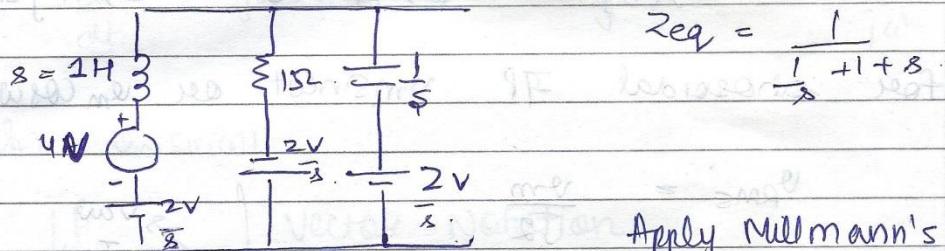


$$V_{eq} = \left(\frac{2}{s} + 4\right)\left(\frac{1}{s}\right) - \frac{2}{s} \cdot 2 + \frac{2}{s} \cdot \frac{1}{s}$$

Apply Nullmann's Theorem

$$\frac{1}{s} + 1 + \frac{1}{s}$$

AC Circuit Analysis

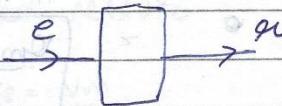In this analysis we calc. steady state response.



$$R(s) = H(s) E(s) \rightarrow \text{freq. at } e(t) = \omega$$

$$R_t = H(j\omega) \cdot E_t$$

$$R(t) = \frac{a_1 + jb_1}{a_2 + jb_2} V_m \sin \omega t$$

$$= \frac{|A_1|}{|A_2|} \angle (\phi_1 - \phi_2) V_m \sin \omega t$$

$$|A_2| = \downarrow$$

$$\frac{|A_1|}{|A_2|} e^{j\theta} V_m \left(e^{\frac{j\omega t}{2i}} - e^{-\frac{j\omega t}{2i}} \right)$$

$$\frac{|A_1|}{|A_2|} V_m \left(\frac{e^{j\theta} e^{j\omega t}}{2i} - \frac{e^{j\theta} e^{-j\omega t}}{2i} \right)$$

$$e^{\frac{j(\omega t + \theta)}{2i}} - e^{\frac{-j(\omega t - \theta)}{2i}}$$


$$\cos(\omega t + \theta) + j \sin(\omega t + \theta) - \cos(\omega t - \theta) + j \sin(\omega t - \theta)$$

for sinusoidal IP $v_m \sin \omega t$ or $i_m \cos \omega t$

$$V_{\text{RMS}} = \frac{v_m}{\sqrt{2}}$$


$$V_{\text{av}} = 0$$

$$I_{\text{av}} = 0$$

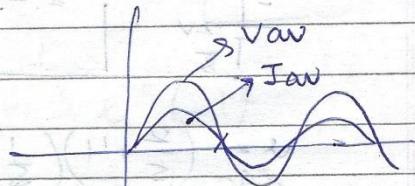

$$P_{\text{av}} \neq 0$$
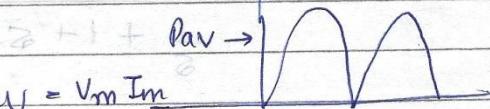
$$\text{Max value of } P_{\text{av}} = v_m i_m$$



$$\text{Average value for half cycle} = \frac{2v_m}{\pi}$$

$$\text{Max. value of } P_{\text{av}} \text{ for half cycle} = \frac{2(v_m i_m)}{\pi}$$

$$\cancel{V_{\text{RMS}}} \quad \therefore \quad = \boxed{\frac{v_m i_m}{2}} \text{ RMS value of power.}$$

$$\Rightarrow \text{Form factor} = \frac{\text{Peak value}}{\text{RMS value}}$$

$$= \frac{v_m}{\frac{v_m}{\sqrt{2}}} = \sqrt{2} = 1.414$$

$$\Rightarrow \text{Misp factor or peak factor} = \frac{\text{Peak value}}{\text{Average value}}$$

$$= \frac{v_m}{\frac{2v_m}{\pi}} = \frac{\pi}{2} = 1.57$$

Confirm from book

RMS value is effective value of signal

MBDWRITEWELL

Date
Page NETWORKS


$$\Rightarrow \frac{d}{dt} \rightarrow s X(s) \quad \int() dt \rightarrow \frac{1}{s} X(s)$$

$$\Rightarrow \frac{d}{dt} \rightarrow j\omega X(j\omega) \quad \int() dt \rightarrow \frac{1}{j\omega} X(j\omega)$$

$$v(t) = V_m \sin(\omega t)$$

B

Vector Notation



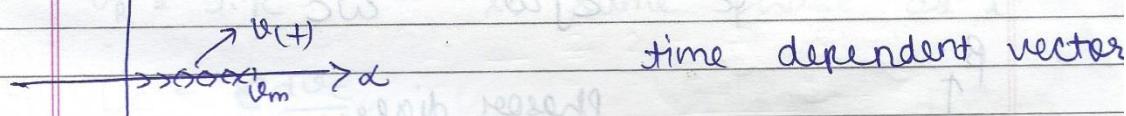



time dependent vector

oscillatory type of behaviour
vector notation at instantaneous value

Phase Notation

$$If v_m \sin(\omega t + \theta)$$

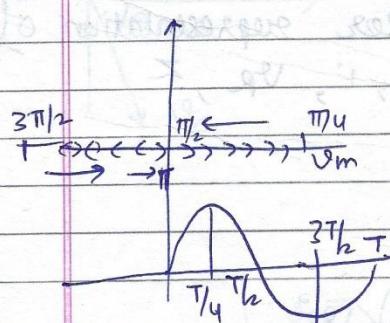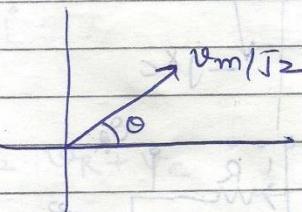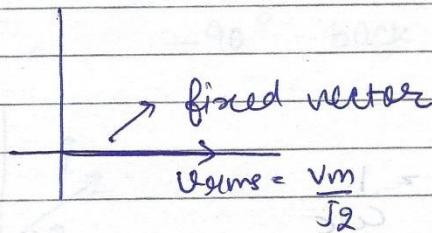

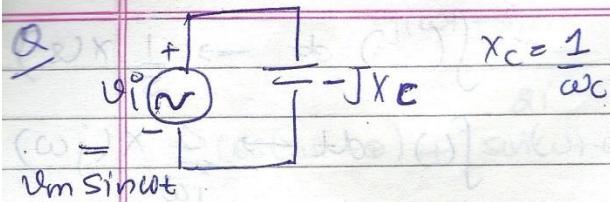

$$X_C = \frac{1}{\omega C}$$

$$i_C = j\omega C \cdot V_i^o$$

$$i_C = C \frac{dV_C}{dt}$$


$$i_C = C \cdot j\omega \cdot V_C$$

$$\frac{V_C}{i_C} = \frac{1}{C j \omega} = \frac{-j}{\omega C}$$

series parallel circuit

$$I_C(\text{rms}) = \text{Phasor diag.}$$
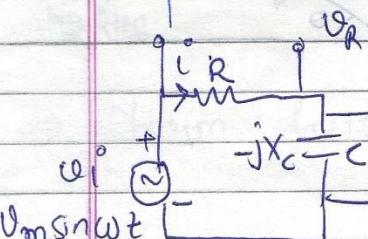
$$V_{\text{rms}} = V_C = \frac{V_m}{\sqrt{2}}$$



$$X_C = \frac{1}{\omega C}$$

Plot phasor representation of
 V_i, V_C, i, V_R, Z

$$i_C = C \frac{dV_C}{dt}$$

$$i_C = C \cdot j\omega \cdot V_C$$

$$i_C = C \cdot j\omega \left(\frac{-jX_C}{R - jX_C} \right) V_i^o$$

$$i_C = \frac{C \omega X_C}{R - jX_C} V_i$$

Diagram illustrating phasors:

Current i is at angle $\theta = \tan^{-1}\left(\frac{X_C}{R}\right)$

Voltage $v_m = v_i$ is at angle α

Relationships:

$$j = \frac{v_i}{|z|} \angle \tan^{-1}\left(-\frac{X_C}{R}\right)$$

$$= \frac{v_i}{|z|} \angle -\tan^{-1}\left(-\frac{X_C}{R}\right)$$

$$= \left|\frac{v_i}{z}\right| \angle \tan^{-1}\left(\frac{X_C}{R}\right)$$


$$v_R = i \cdot R \quad \text{so same phase as } i$$

$$i_C = C j \omega v_c$$



$$i_C = C j \omega \cdot v_c$$




$$v_c = \frac{i}{C j \omega} = \frac{i \times C}{j} = -j X_C i$$

-90° back from i

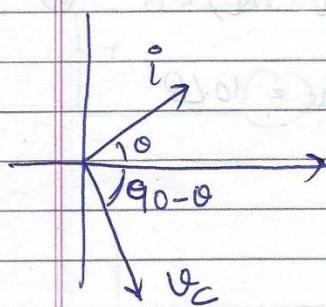

$$v_i = v_R + v_c$$

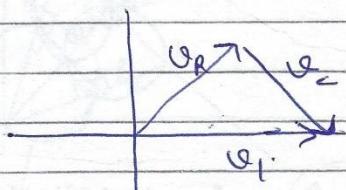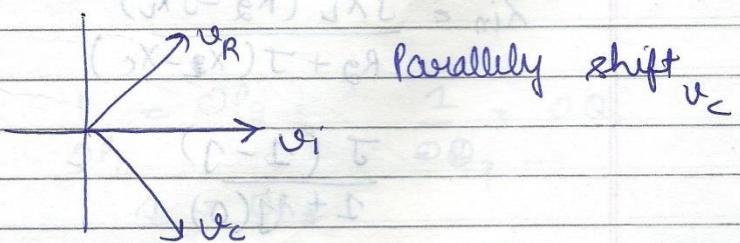

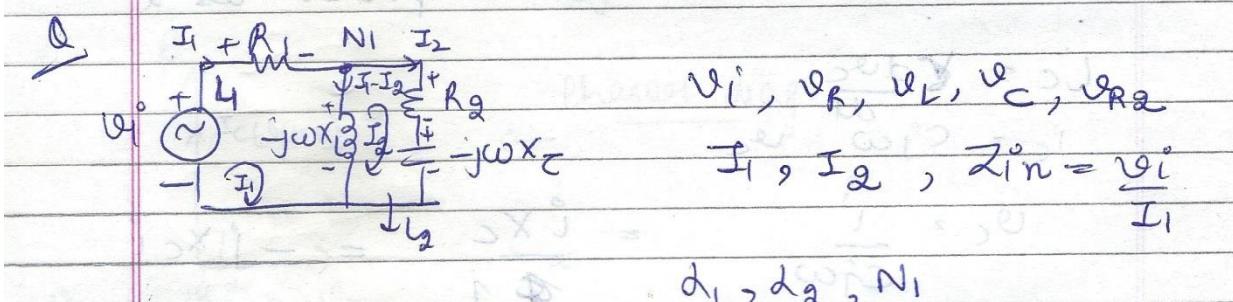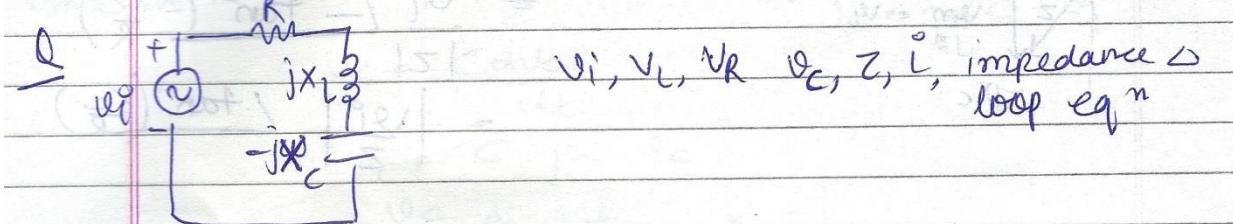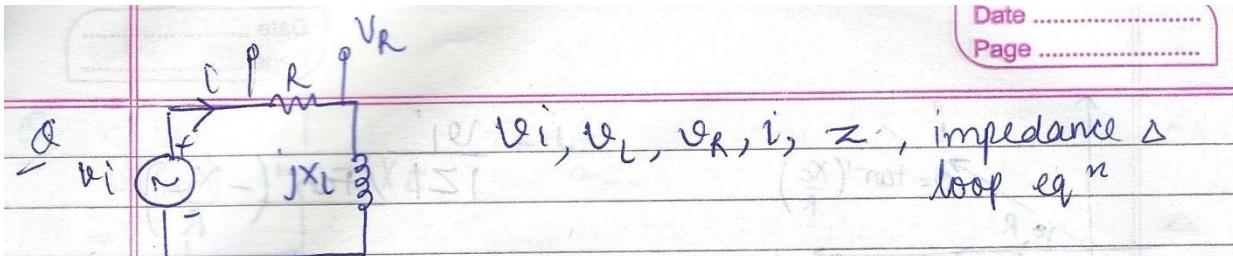

Solⁿ

~~1~~ $I_1 = V_i - I_1 R_1 - (I_1 - I_2) j X_L = 0 \quad \text{--- (1)}$

$j X_L (I_1 - I_2) - I_2 R_2 + I_2 (j X_C) = 0 \quad \text{--- (2)}$

$R_1 = R_2 = X_L = X_C = 1 \quad V_{RMS} = 10 \text{ V}$

$$Z_{in} = \frac{j X_L (R_2 - j X_L)}{R_2 + j(X_L - X_C)}$$

$$= \frac{j(1-j)}{1+j(0)} = \frac{j(-1)}{2} = -1$$

$$Z_{in} = -1 + j$$


Focus Diagram

R values from $-\infty$ to ∞


As it can't be

-ve so


$R \rightarrow 0 - \infty$

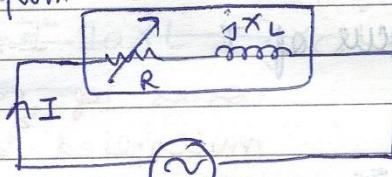

$$Z = R + jXL$$

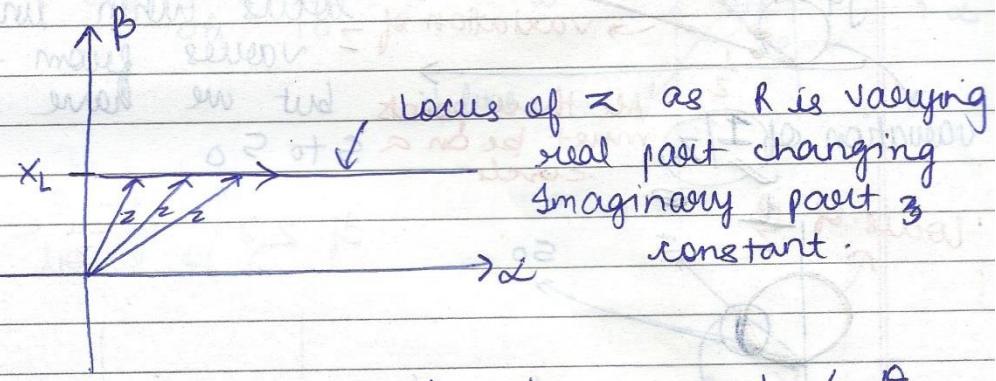

$$V = IZ \quad I = VY \quad Y = \frac{1}{IZ} = \frac{1}{|Z|} \angle -\theta$$

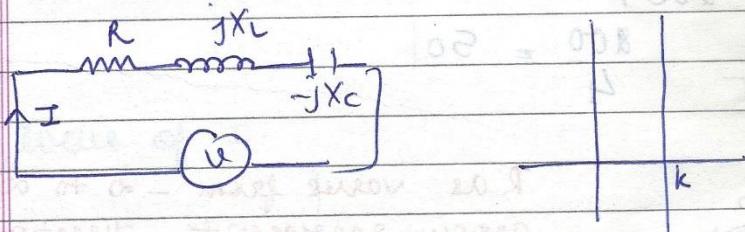

$$\frac{1}{OP_1} = OR_2 \quad \frac{1}{OP_2} = OR_1$$


$$\frac{1}{OR_1} = OR_2$$

$$OP_1, OP_2 \approx 1$$

$$OR_1, OR_2 \approx 1$$

$$OQ_1, OQ_2 \approx 1$$

$$\left(\frac{1}{Z}\right) \approx$$

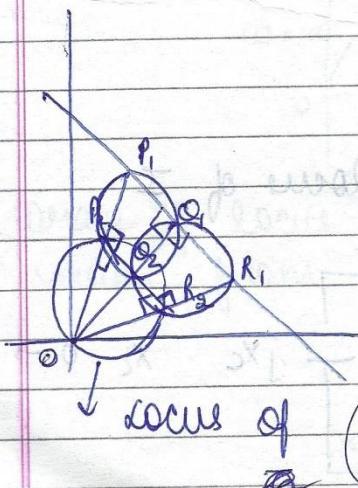

Q Ob variation of $R = 5 - 50 \angle z$. $X_L = 4$ $V = IZ$
 Say $V = 200 \angle 0^\circ$

Represent the locus of I $I = \left(\frac{1}{z}\right) V$.


Locus of $\frac{1}{z}$ is locus of I multiplied by v .

NOW this is the

Locus when line

values from $-\infty$ to ∞

All these points must be on a circle.

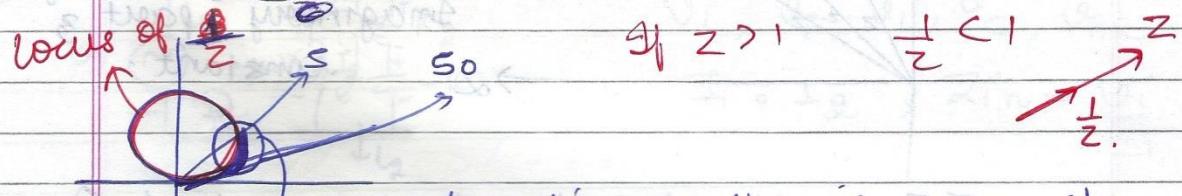


So only this portion is locus of y .

$$I = 200Y$$

$$\text{diameter } \frac{200}{4} = 50$$

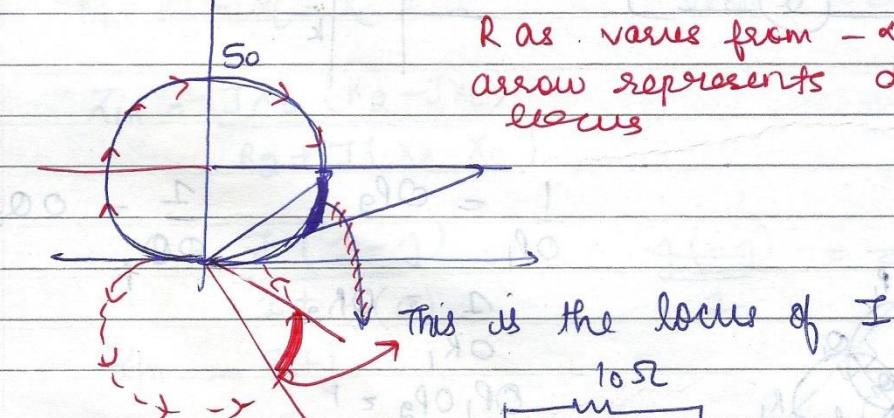
R as values from $-\infty$ to ∞
 arrow represents direction of locus



Q $R = 10 \angle z$

$$V = 200 V$$

$$X_C = 0 \text{ to } \infty$$

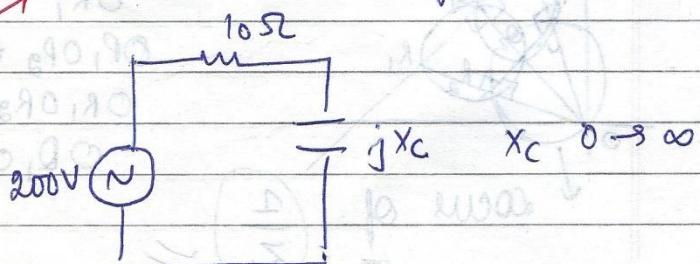

HBD WRITEWELL
Date _____

locus of Inverse of points lying on straight line
 is a circle passing through origin whose diameter = ∞
 except one line that passes through origin $y=x$.
 Then its locus will be a hyperbola

↓ find locus of I .

This case

can occur when both R
 and $L = 0$

i.e. when

$$\text{both are varied. } \frac{1}{OP_2} = \frac{1}{OP_1} = \frac{1}{10}$$


$$Z = 10 + jx_c$$

$\frac{1}{r}$
 I distn
 from
 origi

$$\frac{1}{r} = 0 \quad \text{at } B \quad P_1 \quad 10 = w$$

1 line

for $0 \rightarrow \infty$.
 locus of X

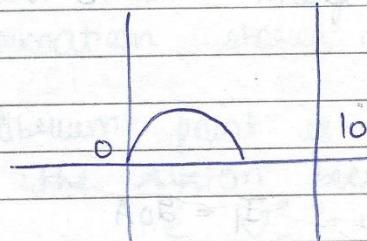


$$I = 200Y$$

when $X = 0$


$$I = \frac{200P}{10} = 20$$

$$I = 200 \times 0 \\ = 0$$

locus of I .

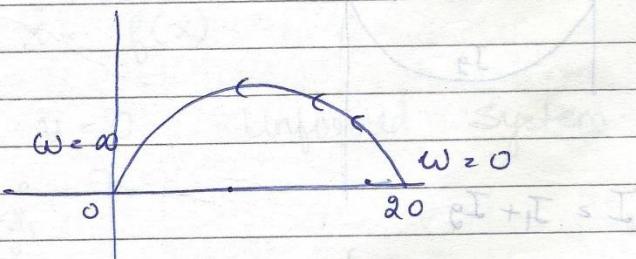

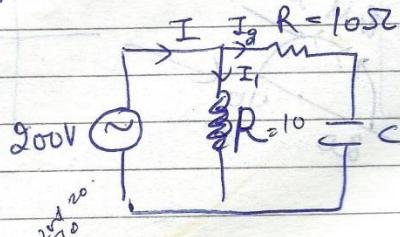
Q) Draw of locus of I if freq. of supply voltage varies from 0 to ∞



satisfy w vanishes

$Z_{in} =$
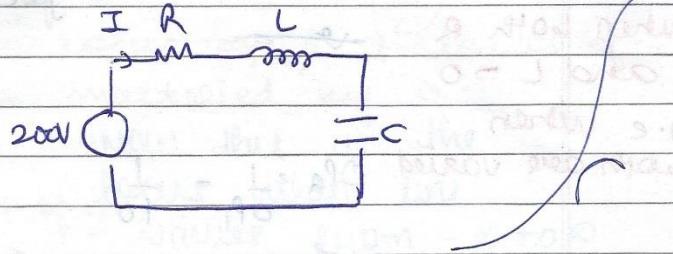
$$\frac{Q^2}{Z_{in}} = R + j\omega L - j \frac{1}{\omega C}$$




$$\omega = 0$$

$$Z_{in} = R - j\infty$$

$$\omega = \infty$$


$$Z_{in} = R + j\infty$$

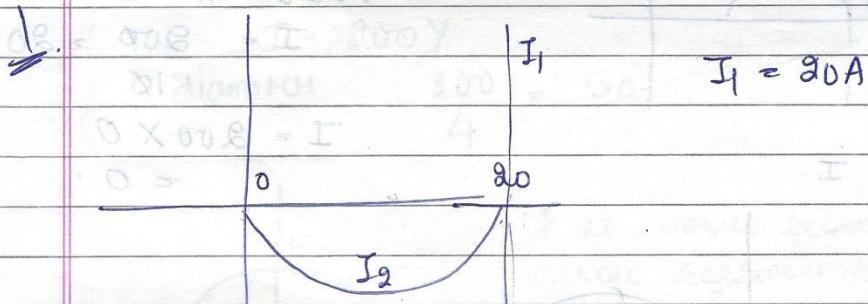
Imag. part vanishes from $-\infty$ to ∞ .



$$I_1 = 20A$$

$$I = I_1 + I_2$$

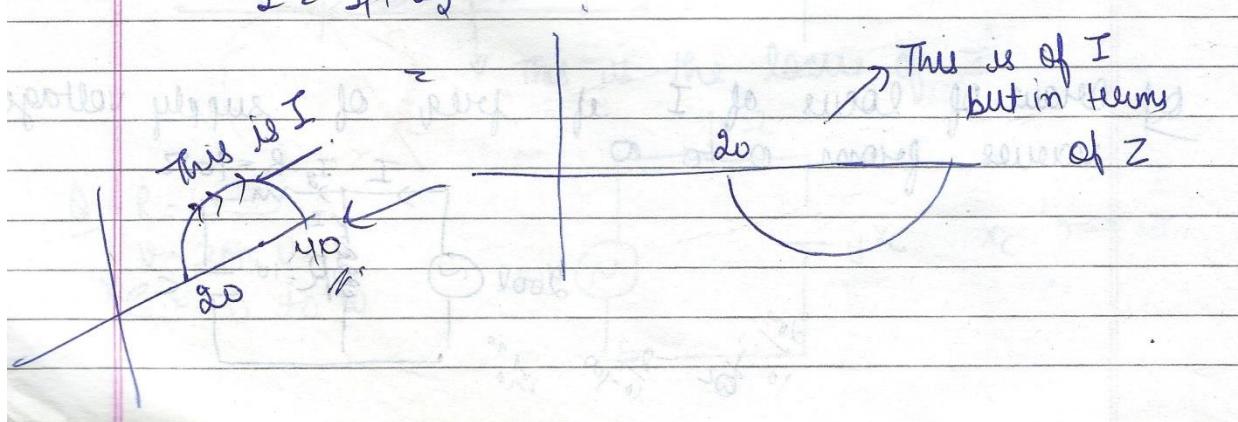

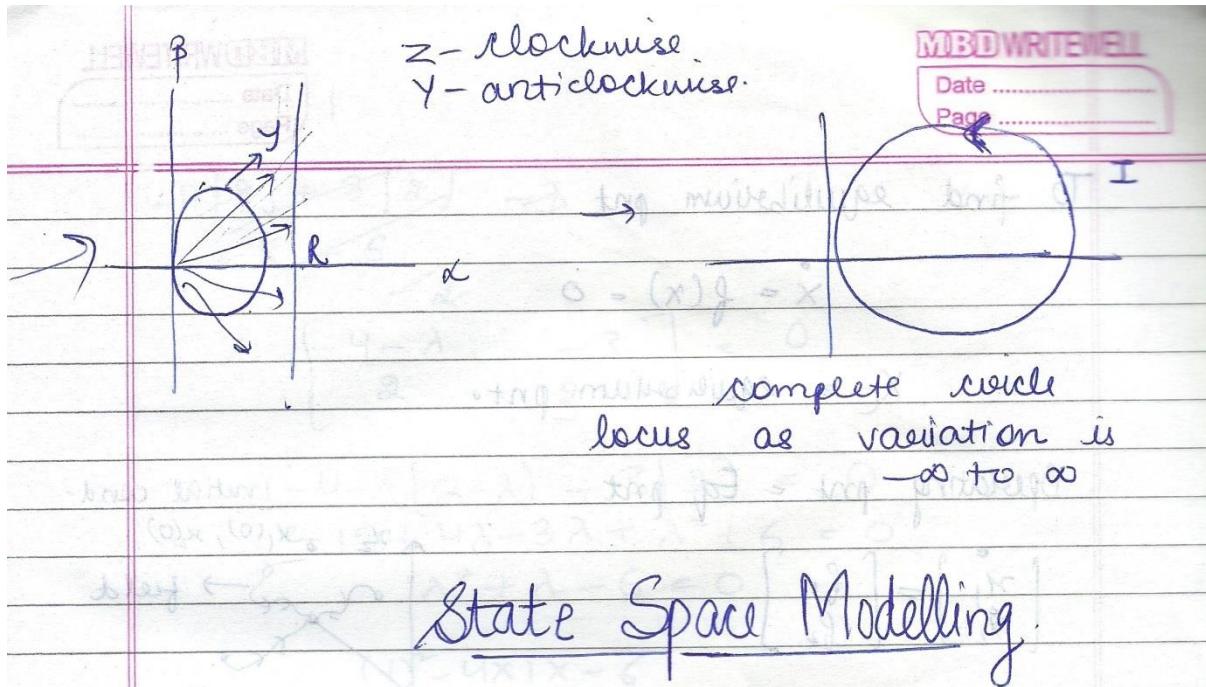

State Space Modelling.

Applied to non linear system.
state variable defines the state of a system i.e information stored at particular instant

Equilibrium point is the point where dynamic of the system becomes zero.

$$\text{i.e } \dot{x}_1^* = 0 \quad \dot{x}_2^* = 0 \quad \dots \quad \dot{x}_n^* = 0 \quad \begin{matrix} \dot{x} = f(x, u, t) \\ \text{state variable} \end{matrix} \quad \begin{matrix} \downarrow \\ \text{I/P variable} \end{matrix}$$

autonomous system $\dot{x} = f(x)$
 $u = 0$ Unforced System

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \vdots \\ \dot{x}_n \end{bmatrix} = f(x_1, x_2, x_3, \dots, x_n) = \begin{bmatrix} f_1(x) \\ f_2(x) \\ \vdots \\ f_n(x) \end{bmatrix}$$


To find equilibrium pt

$$\dot{x} = f(x) = 0$$

x_c = equilibrium pt.

Operating pt = Eq. pt
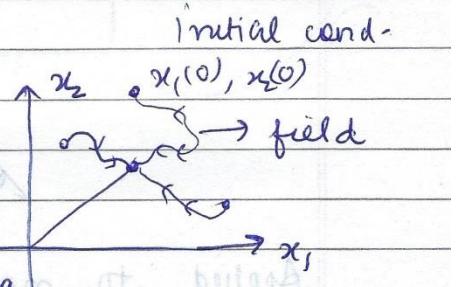
$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} f_1 \\ f_2 \end{bmatrix}$$



Now as 2 variables are changing
so if we find a direction
in which if initial condition is present
then both move in that direction forever

$$\begin{aligned} \dot{x} &= kx \leftarrow \text{eigenvalue} \quad \lambda = \text{constant matrix} \\ \dot{x} &= \lambda x \quad \text{direction} \end{aligned}$$

Now it gets converted to single variable
slope represents rate of change of
 x_1 & x_2 .

$$\frac{dx}{dt} = \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} -4 & -3 \\ 2 & 3 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

$$\begin{aligned} \dot{x} &= Ax = \lambda x \\ (A - \lambda I)x &= 0 \quad \text{characteristic eqn} \\ A - \lambda I &= 0 \end{aligned}$$

$$\begin{bmatrix} -4 & -3 \\ 2 & 3 \end{bmatrix} - \lambda \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} = 0$$

$$\begin{matrix} -4[8] + 3[2] \\ -8 + 6 \end{matrix} \rightarrow$$

$$\cancel{-2}$$

$$\begin{bmatrix} -4-\lambda & -3 \\ 2 & 2-\lambda \end{bmatrix} = 0$$

$$-4-\lambda[3-\lambda] + 3[2] = 0$$

$$-12 + 4\lambda - 3\lambda + \lambda^2 + 6 = 0$$

$$\lambda^2 + \lambda - 6 = 0$$

$$(1)^2 - 4 \times 1 \times -6$$

$$1 + 24 = 25$$

$$\frac{-1+5}{2} = \frac{-1+5}{2} = \frac{4}{2} = 2$$

$$= \frac{-1-5}{2} = -3$$

means 2 eigen directions possible.

$$[A - \lambda I][x] = 0 \quad \cancel{\lambda - 2 = 0}$$

$$\begin{bmatrix} -4 & -3 \\ 2 & 3 \end{bmatrix} - 2 \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - 6 = 3y_1$$

$$\begin{bmatrix} -6 & -3 \\ 2 & 2 \end{bmatrix} \begin{bmatrix} x_1 \\ y_1 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \quad -2 = y_1$$

$$-6x_1 - 3y_1 = 0 \quad \text{multiple soln's poss}$$

$$2x_1 + y_1 = 0 \quad \cancel{2x_1}$$

$$\begin{matrix} 6x_1 + 3y_1 = 0 \\ -6x_1 - 3y_1 = 0 \end{matrix}$$

1, -2 is one of
the solns

$$v_1 = \begin{bmatrix} 1 \\ -2 \end{bmatrix}$$

$$(A+3I)(X)$$

$$\begin{bmatrix} -4 & -3 \\ 2 & 3 \end{bmatrix} + 3[I]$$

$$\begin{bmatrix} -4+3 & -3 \\ 2 & 3+3 \end{bmatrix}$$

$$\begin{bmatrix} -1 & -3 \\ 2 & 6 \end{bmatrix} \begin{bmatrix} x_2 \\ y_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\begin{aligned} -x_2 - 3y_2 &= 0 \\ 2x_2 + 6y_2 &= 0 \end{aligned}$$


$$-1 = 3y_2 \quad y_2 = -\frac{1}{3}$$

~~$$\frac{x}{3} + 6y_2 = 0 \quad 6y_2 = \frac{2}{3}$$~~

$$2(1) + 6\left(-\frac{1}{3}\right) = 0$$

$$2 - 2 = 0$$
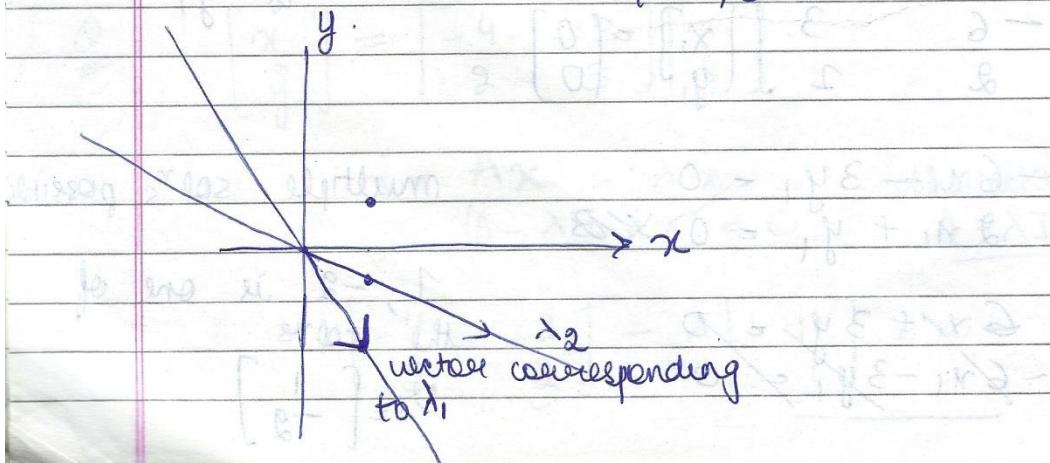
$$= \begin{pmatrix} 1, -\frac{1}{3} \end{pmatrix} \quad v_2 = \begin{bmatrix} 1 \\ -1/3 \end{bmatrix}$$



$$\dot{x} = \lambda_1 x$$

$$x_1(t) = [1] e^{-\lambda_1 t} C_1$$

$$y_1(t) = [-2] e^{-\lambda_1 t} C_2$$

This is not general soln

$$X(t) = \begin{bmatrix} x_1(t) \\ y_1(t) \end{bmatrix} = C_1 \begin{bmatrix} 1 \\ -2 \end{bmatrix} e^{-\lambda_1 t}$$

so C_1, C_2 cannot be found by putting initial conditions as this is not general soln.

$$x_2(t) = C_2 \begin{bmatrix} 1 \\ -1/3 \end{bmatrix} e^{-\lambda_2 t}$$

Both are linear independent
 $\Rightarrow x_1(t) \neq k x_2(t)$

so general soln $x(t) = C_1 x_1(t) + C_2 x_2(t)$

form of multi-dimensional system $x(t) = C_1 \begin{bmatrix} 1 \\ -2 \end{bmatrix} e^{-\lambda_1 t} + C_2 \begin{bmatrix} 1 \\ -1/3 \end{bmatrix} e^{-\lambda_2 t}$

(Q) $A = \begin{bmatrix} -2 & 1 \\ 1 & -2 \end{bmatrix}$ proceed similarly

$$\Rightarrow \begin{bmatrix} x(t) \\ y(t) \end{bmatrix} = C_1 \begin{bmatrix} e^{-\lambda_1 t} \\ -2e^{-\lambda_1 t} \end{bmatrix} + C_2 \begin{bmatrix} e^{-\lambda_2 t} \\ -\frac{1}{3}e^{-\lambda_2 t} \end{bmatrix}$$

Take initial cond. x_0, y_0

$$Ax_0 + A = (x_0)b$$

$$Ax_0 = b$$

$$(s+4)(s+3) - 3(-2) = s^2 + 8 + 12 + 6$$


$$s^2 + 8 - 6$$

Inverse \Rightarrow

$$\begin{bmatrix} \frac{s-3}{s^2+s-6} & \frac{2}{s^2+s-6} \\ -\frac{3}{s^2+s-6} & \frac{s+4}{s^2+s-6} \end{bmatrix}$$

Network Function

$$H(s) = \frac{R(s)}{E(s)}$$

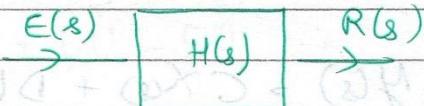

Assumption Linear, lumped, finite, passive, bilateral n/w

Actual size negligible as compared to
wavelength of excitation

Wavelength of excitation in India = 6000 km.

$$R(s) = \frac{E(s)}{H(s)}$$

H(s) will be real and rational

Rational = ratio of 2 polynomials.

or real & rational fn. of s, z
or $j\omega$ (Sineoidal)

But value of s = $-1, j\omega, \infty$

(discrete)

$s^2 + 2s + 1 \rightarrow$ Polynomial, real

$s^2 + s^{3/2} + 1 \rightarrow$ Not poly, not real

$s^3 + s^2 + \sqrt{s} \rightarrow$ Not poly, not real

$e^s + 1 \rightarrow$ Not poly, length of series be finite

finite
series

real - if we put real value of s , quantity should also be real.

MBD WRITE WELL

Date

Page

$s + s^{-1}$ - NOT polynomial, rational fn
 $s^2 + s + 1$ - Polynomial, NOT real

✓ Polynomial is a finite series with +ve integral power

✓ A poly. is said to be real if we put real value of variable, then value of poly. is real

$$R(s) = H(s) \cdot E(s)$$

$$= \sum_i \frac{A_i}{(s - p_i)} + \sum_j \frac{A_j}{(s - p_j)}$$

for stable system

BIBO system p_i = Poles corresponding to $H(s)$

i.e $R < 0$ p_j = Poles corresponding to $E(s)$

i.e bounded

$$\text{signal} = \underbrace{\sum_i A_i e^{-p_i t}}_{\text{Natural response}} + \underbrace{\sum_j A_j e^{-p_j t}}_{\text{Forced response}}$$

$$H(s) = \frac{I(s)}{V(s)}$$

$$\frac{I(s)}{V(s)} = \frac{1}{R + SC}$$

$$= \frac{1}{R \left[1 + \frac{SC}{R} \right]}$$

$$= \frac{1}{C \left[\frac{R}{C} + S \right]}$$



find $i(t)$


$$\frac{I(s)}{V(s)} = \frac{1/C}{(s + R/C)} = H(s)$$

$$E(s) = \frac{1}{s + 1}$$

$$I(s) = A e^{-R/C t} + B e^{-t}$$


should

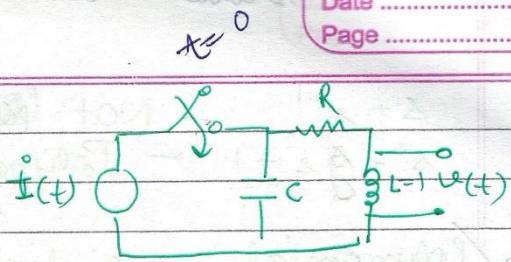Q $v(t) = \text{response}$
find \Rightarrow transfer fn.



i.e. find $H(s) = \frac{V(s)}{I(s)}$
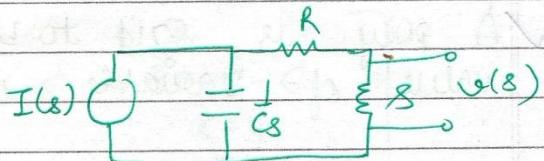
$$V(s) = \begin{bmatrix} \frac{1}{Cs} & I(s) \\ (1 + R + s) \\ Cs \end{bmatrix}$$



$$\frac{Vs}{I(s)} = \frac{\frac{1}{Cs}}{\frac{1 + R + s}{Cs}} = \frac{1/Cs}{1 + CR + s^2}$$

$$= \frac{s}{s^2 + sCR + 1}$$

$$= \frac{s}{C \left[s^2 + sR + \frac{1}{C} \right]}$$

$$= \frac{s/C}{s^2 + sR + \frac{1}{C}}$$

Q If poles of \Rightarrow transform fn are $-2, -1$ find
 R and C

$$(s+2)(s+1)$$

$$(R)^2 - 4 \times 1 \times 1 \\ C$$

$$\frac{R^2 - 4}{C}$$


$$s^2 + 3s + 2 = s^2 + sR + \frac{1}{C}$$

$$\frac{1}{C} = 2$$

$$R = 3$$

$$H(s) = \frac{2s}{s^2 + 3s + 2}$$

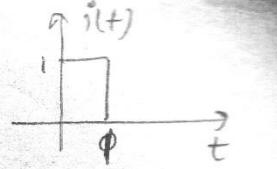Q. If $i(t)$ excitation is given
then find $v(t)$ for same
N/W



$$H(s) = \frac{2s}{s^2 + 3s + 2}$$

$$v(s) = \left(\frac{2s}{s^2 + 3s + 2} \right) I(s).$$

~~$v(t) = Ae^{-2t} + Be^{-t}$~~

$$v(t) = \left(\frac{2s}{s^2 + 3s + 2} \right) \left(t - \frac{e^{-s}}{s} \right)$$

$$\frac{2s}{s^2 + 3s + 2} \left(\frac{1}{s} \right) - \frac{2s}{s^2 + 3s + 2} \left(\frac{e^{-s}}{s} \right)$$

$$\begin{aligned} i(t) &= u(t) - u(t-1) \\ I(s) &= \frac{1}{s} - \frac{1}{s} e^{-s} \\ &= \frac{(1 - e^{-s})}{s} \end{aligned}$$

$$= \boxed{Ae^{-2t} + Be^{-t} - C[e^{-2(t-1)} + e^{-(t-1)}]u(t-1)}$$

✓ 3 cases in N/W function

$$H(s) = \frac{N(s)}{D(s)}$$

both are real polynomial
 $N(s) + D(s)$. Thus it is
rational function.

a) If degree of $N(s) < D(s)$

$$H(s) = \sum_i \frac{A_i}{s - p_i}$$

b) If degree of $N(s) = D(s)$

$$H(s) = K + \frac{N_1(s)}{D(s)}$$

$N_1(s) \leq D(s)$

then partial fraction of $\frac{N_1(s)}{D(s)}$ is again

$$\sum_i \frac{A_i}{s - p_i}$$

c) If deg. of $N(s) > D(s)$

$$\boxed{D \{ N(s) \} Y = Q + D \{ D(s) \} Y}$$

$$H(s) = A_2 s^2 + A_1 s + A_0 + \frac{N_2 s}{D(s)}$$

where $D \{ N_2(s) \} < D \{ D(s) \}$

$$d(s'(t)) = S$$

$$\underline{d^{-1}(s)} = \underline{s'(+)}$$

$$H(j\omega) = \frac{N(j\omega)}{M(j\omega)}$$

$$\Rightarrow |H(j\omega)| e^{j\phi(j\omega)} \quad \text{Euler representation}$$

$$\checkmark \quad \text{Re}[H(j\omega)] + j \text{Im}[H(j\omega)]$$

$$|H(j\omega)| \cos \phi(j\omega) + |H(j\omega)| \sin \phi(j\omega) \quad \text{Cartesian representation}$$

How to convert $\frac{H(s)}{N(s)}$ to above representations

$$H(s) = \frac{N(s)}{M(s)}$$

$$H(s) = \frac{s^2 + 2s + 1}{s^2 + 2s + s^0}$$

$$= [s^2 + s^0] + 2s$$

$$(m_1) \underbrace{[s^2 + s^0]}_{\text{even part}} + \underbrace{2s}_{\text{odd part } (m_2)}$$

$$H(s) = \frac{m_1(s) + m_2(s)}{m_1(s) + m_2(s)}$$

$$= \frac{m_1(s) + m_2(s)}{m_1(s) + m_2(s)} \frac{(m_1(s) - m_2(s))}{(m_1(s) - m_2(s))}$$

$$= \frac{n_1 m_1 - n_1 m_2 + n_2 m_1 - n_2 m_2}{m_1^2 - m_2^2}$$

even fn of s means when we put s or $-s$
ans. is $f(s)$.

MBD WRITEWELL

Date

Page

$$\begin{aligned}
 H(s) &= \frac{E - O + O - E}{E + O - O - E} \\
 &\text{even fn of } s \\
 &= \underbrace{(n_1 m_1 - n_2 m_2) + (n_2 m_1 - n_1 m_2)}_{m_1^2 - m_2^2} \rightarrow \text{real term} \\
 &+ \underbrace{\text{even + odd fn of } s}_{\text{fn of } s} \\
 &\text{Put } s = j\omega
 \end{aligned}$$

$$H(j\omega) = \operatorname{Re}[H(j\omega)] + j \cdot \operatorname{Im}[H(j\omega)]$$

$$|H(j\omega)| = \sqrt{[\operatorname{Re}(H)]^2 + [\operatorname{Im}(H)]^2} \rightarrow |H(j\omega)|^2$$

even fn
of ω

$$\phi(j\omega) = \tan^{-1} \frac{\operatorname{Im}(H(j\omega))}{\operatorname{Re}(H(j\omega))} \rightarrow \text{odd fn}$$

of ω

$$H(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_0 s^0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_0 s^0}$$

$$m = \text{No. of finite zeros} = \left(\frac{a_m}{b_n} \right) k \left(\frac{s^m + a_{m-1} s^{m-1} + \dots + a'_0 s^0}{s^n + a'_{n-1} s^{n-1} + \dots + a''_0 s^0} \right)$$

$$n = \text{No. of finite poles} \quad \frac{a_m}{b_n} = k = \text{gain of the fn.}$$

1) • In general if $m < n$ then system fn is said to be proper rational fn.

2) • If $m = n$ then $H(s)$ can be written as

$$H(s) = (\text{C}) + \text{proper rational fn}$$

j.e. one impulse present in response \downarrow constant

Inverse Laplace of constant = Impulse fn

- 3) • If $n < m$ (Improper fn) (Non realizable)

$$H(s) = (a_k s^k + a_{k-1} s^{k-1} + \dots + a_0 s^0)$$

+ Proper rational fn.

In this case not only impulse present in response but also its derivative.

Above two cases are not physically realisable as impulse practically not available. Single impulse could be tolerated but derivative can never be tolerated.

LFBP - linear, dumped, finite, passive, bilateral

This is physically realisable sys.

Frequency DOMAIN ANALYSIS

$$\text{Now if } H(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_0 s^0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_0 s^0}$$

$$= k \left\{ \frac{s^m + a_{m-1} s^{m-1} + \dots + a'_0 s^0}{s^n + b'_{n-1} s^{n-1} + \dots + b'_0 s^0} \right\}$$


$$= k \left| \begin{array}{c} \prod_{i=1}^m (s - z_i) \\ \hline \prod_{j=1}^n (s - p_j) \end{array} \right| \quad |s = jw|$$

$$= k \frac{\pi (j\omega - z_i)}{\pi (j\omega - p_i)}$$

$$|H(j\omega)| e^{\phi(j\omega)} = \text{Re}(H(j\omega)) + j \text{Im}(H(j\omega))$$

GOOD WRITING

Date
Page

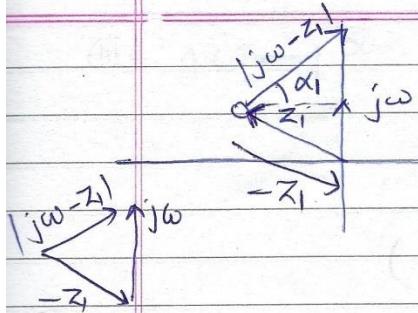

$$N_1 = |j\omega - z_1| \quad M_1 = |j\omega - p_1| = M_1$$

$$\frac{|j\omega - z_1|}{|j\omega - z_1|} = \alpha_1 \quad \frac{|j\omega - p_1|}{|j\omega - p_1|} = \theta_1$$

$$\frac{k N_1 \alpha_1 \cdot N_2 \alpha_2 \cdot N_3 \alpha_3 \cdots N_m \alpha_m}{M_1 \theta_1 + M_2 \theta_2 + \cdots + M_n \theta_n}$$


n, m = No. of poles & zeroes

N, M = Mag. of poles & zeroes

$$= k \frac{N_1 N_2 N_3 \cdots N_m}{M_1 M_2 M_3 \cdots M_n} \frac{1/\alpha_1 + 1/\alpha_2 + \cdots + 1/\alpha_m}{1/\theta_1 + 1/\theta_2 + \cdots + 1/\theta_n}$$

$$= \left[\frac{k N_1 \cdot N_2 \cdots N_m}{M_1 \cdot M_2 \cdots M_n} \right] \sqrt{\sum_{i=1}^m \frac{1}{\alpha_i^2} - \sum_{j=1}^n \frac{1}{\theta_j^2}}$$

magnitude of $(j\omega)$

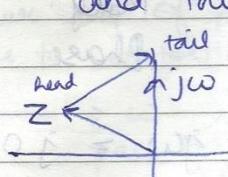

In case of proper rational fn

m = Total no. of finite zeroes

$n-m$ = N. o. of zeroes lying at ∞ .

$$f(s) = \frac{4s+2}{s^2+8s+2} \quad j\omega = ja \quad \text{find the mag. of } f(j\omega) \quad \text{And Phase of } f(j\omega)$$

$$-2 \pm 2i$$

$$(2)^2 - 4 \times 1 \times 2$$

$$4 - 8 = -4 = 2i$$

$$-1 \pm 1i$$

$$M = \frac{1}{(8-wi)} \frac{48}{(8+1-i)(8+1+i)} =$$

$$f(j_2) = \frac{4j_2}{(j_2+1-j)(j_2+1+j)}$$

$$\frac{1}{0} \quad \infty$$

$\approx 8j$

$(j+1) \quad (3j+1)$

$$Mag = \frac{8}{\sqrt{1+1}} = \frac{8}{\sqrt{2}} = \frac{8}{\sqrt{2} \cdot \sqrt{2}} = \frac{2\sqrt{2}}{\sqrt{2} \cdot \sqrt{2}} = \frac{2}{2} = 2$$

$$\text{Phase} = \tan^{-1} \frac{s}{o} - \tan^{-1} \frac{l}{l} - \tan^{-1} \frac{3}{1}$$

$$= q_0 - \tan^{-1} 1 - \tan^{-1} 3$$

$$M(j\omega) = \text{Re } \hat{a}^2 [H(j\omega)] + \text{Im } \hat{a}^2 [H(j\omega)]$$

Mag. plot is even fn. \Rightarrow based
Phase plot is odd fn.

$$(ii) \quad j\omega = j0$$

$$\frac{8(j_0)}{(j_0 + l - j)(j_0 + l + j)}$$

$$= \underbrace{0j}_{(1-j)(1+j)} \rightarrow \text{null vector} \quad \begin{matrix} \text{mag. } 0 \\ \text{but direction } 90^\circ \end{matrix}$$

$$= \frac{0}{\sqrt{2}} = 0$$

$$\tan^{-1} \frac{0}{0} + \tan^{-1} 1 - \tan^{-1} 1$$


not defined ~~also~~ $\angle \text{bus} = 90^\circ$

(ii) $j\omega = j\infty$

$$\frac{4j\infty}{(\infty + 1 - j)(\infty + 1 + j)} = \frac{\infty}{\infty \cdot \infty} = 0.$$

$$\begin{aligned}\text{Phase} &= \tan^{-1} \frac{\infty}{0} - \tan^{-1} \frac{0}{\infty} - \tan^{-1} \frac{\infty}{1} \\ &= 90^\circ - 0^\circ - 90^\circ \\ &= -90^\circ\end{aligned}$$

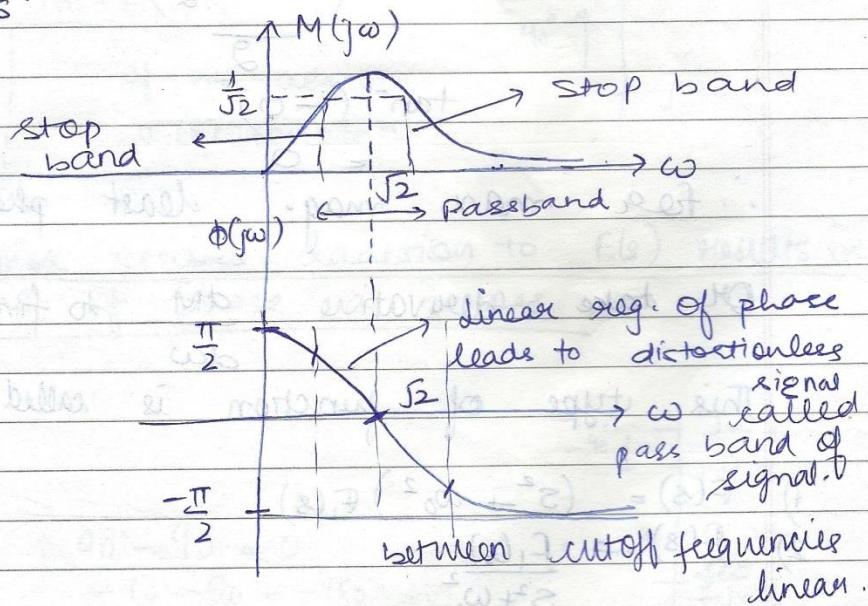Now behaviour of $F(s)$ can be plotted on these basis.



Freq. at which phase zero.

$$\begin{aligned}\frac{4(j\omega)}{(j\omega)^2 + 2j\omega + 2} &= \frac{4j\omega}{2j\omega - \omega^2 + 2} \\ &= \frac{4}{2 + j\left(\omega - \frac{2}{\omega}\right)}\end{aligned}$$

$$-\frac{4}{\sqrt{\omega^2 + (\omega - \frac{\omega_2}{2})^2}} \tan^{-1} \left(-\frac{\omega - \frac{\omega_2}{2}}{\frac{\omega_2}{2}} \right)$$

for mag. max den. least

$$\omega - \frac{\omega_2}{2} = 0$$

$$\omega = \frac{\omega_2}{2}$$

$$\boxed{\omega = \sqrt{\omega_2}}$$

Putting $\omega = \sqrt{\omega_2}$ in phase

$$\omega_0 \text{ bottom } \tan^{-1} \left(\frac{\sqrt{\omega_2} - \frac{\omega_2}{2}}{\frac{\omega_2}{2}} \right) = 0$$

$$\tan^{-1}(-0) = 0$$

∴ for max. mag. least phase.

Or take derivative $\frac{dM}{d\omega}$ to find max. value -

This type of function is called BAND PASS.

$$1) F(s) = (s^2 + \omega_0^2) F_1(s)$$

$$s^2 = -\omega_0^2$$

$$2) F(s) = \frac{F_1(s)}{s^2 + \omega_0^2}$$

$$s = \pm j\omega_0$$

$$3) F(s) = \frac{s^2 + \omega_1^2}{s^2 + \omega_2^2} \quad \omega_1 < \omega_2$$


$F(s) \Rightarrow |F_1(j\omega)| = M_1$ Mag. phase of
 $\angle F_1(j\omega) \phi_1$ $f_1(j\omega)$ known

$(j\omega - z_1)$ form

$$(j\omega - j\omega_0)(j\omega + j\omega_0) \\ (j\omega - (-j\omega_0))$$


if $\omega < \omega_0$

$$-90^\circ + 90^\circ = 0$$

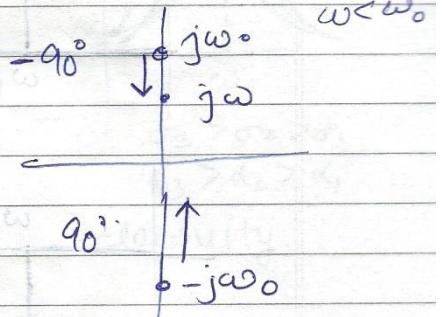

There is a jump in phase

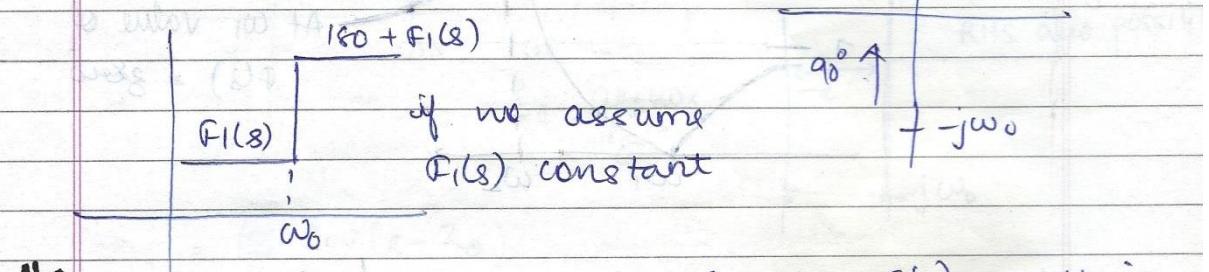of $F(s)$ by 180° at $\omega = \omega_0$ i.e. location of zeroes




∵ complex zeroes addition to $F(s)$ results in jump of phase at zeroes

2) $F_1(s)$

$$(s^2 + \omega_0^2)$$

$$90^\circ - 90^\circ = 0$$

$$-90^\circ - 90^\circ = -180^\circ$$

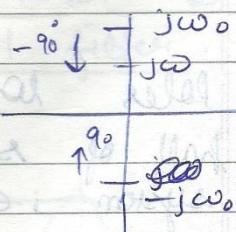


$$0 + \phi_1 \quad \text{if } \omega < \omega_0 \\ -180 + \phi_1 \quad \text{if } \omega > \omega_0$$



Introduction of -180° phase

$$j\omega + j\omega_0 \quad \text{at } \omega = \omega_0 \\ j\omega - (-j\omega_0)$$

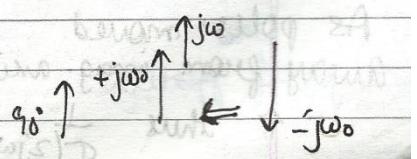
$$\text{Mag} = \frac{k}{(\omega^2 - \omega_0^2)}$$



3

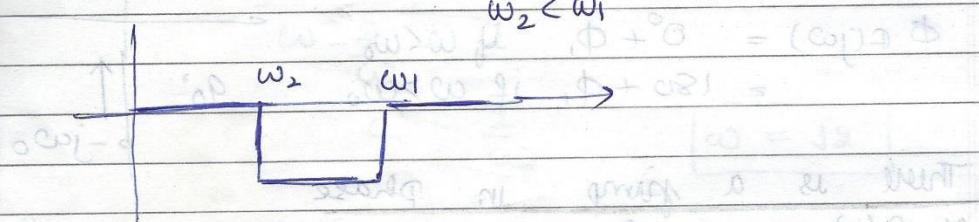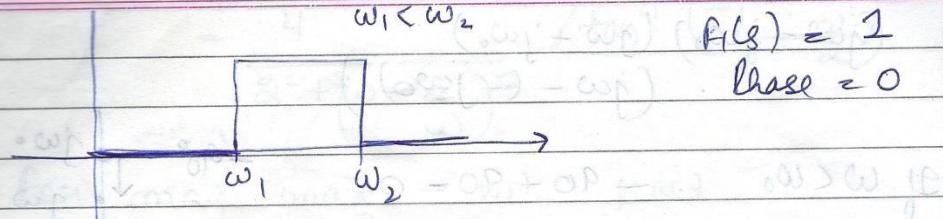

- Mag. of $F(s)$ at zeroes is zero

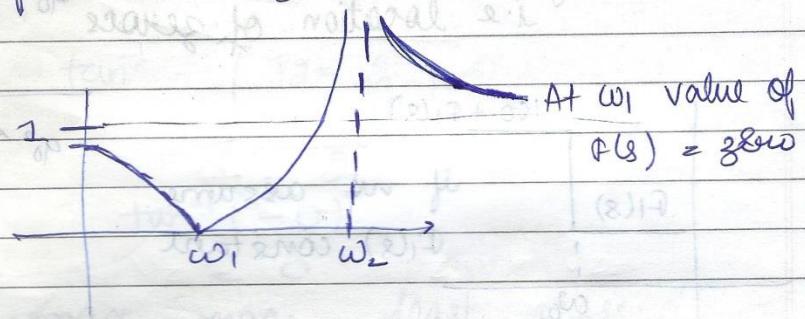

Now (at +ve infinity form ∞/∞ spiral)

$$\lim_{s \rightarrow 0} \frac{s^2 + \omega_1^2}{s^2 + \omega_2^2} = \frac{2s}{\omega_2 s} = 1$$

means including $j\omega \rightarrow$ axis


Poles location will always be in closed half of s plane for a physically realisable system i.e. (ZIFPB)

whatever be the phase earlier to ω_2 , it will \downarrow rapidly $\otimes -j\omega$ poles jump at zeros in finite duration.


As poles moved away from imag. axis now value not ∞

$\sigma \uparrow$ thus $\frac{1}{\sigma(2j\omega + \alpha)} \downarrow \otimes -j\omega$ but very large

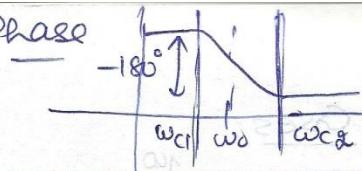σ value τ transition
smooth
 σ value less, transition
abrupt.



MBD RITEWELL

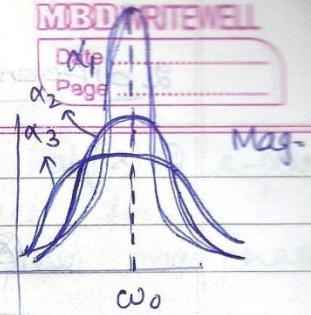

$(S-P_1) (S-P_2)$

low pass special case of

→ Band pass when $\omega_0 = 0$

→ High pass when $\omega_0 = \infty$

- Mag. large - better range of selectivity
- small mag - poor range of selectivity.

$$\sigma_3 > \sigma_2 > \sigma_1$$

$$\alpha_3 > \alpha_2 > \alpha_1$$

- when zeroes loc. α is slightly away from jω axis

phase will

↑ rapidly

at ω_0

by approx

$$180^\circ$$


shifting on

RHS also possib



$$Z_{f2} = (S - Z_1)(S - Z_2)$$

Now mag. not zero but tending to zero.

called BAND STOP or
BAND NOTCH filter.

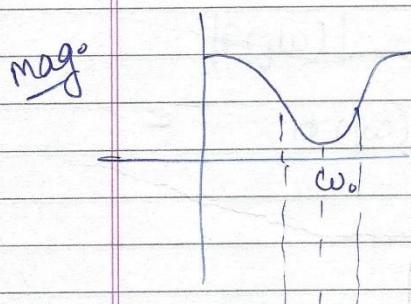

$$0.707 H_{\max} = 3 \text{ db}$$

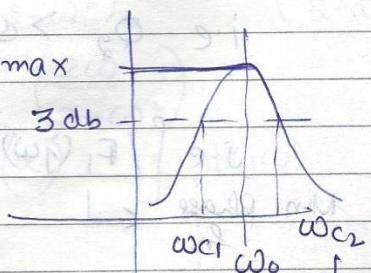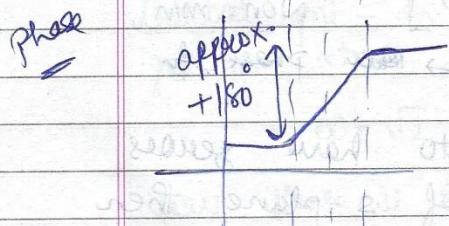


Man.
cutoff freq.


2 different Cases

Date
Page

$F_1(s)$

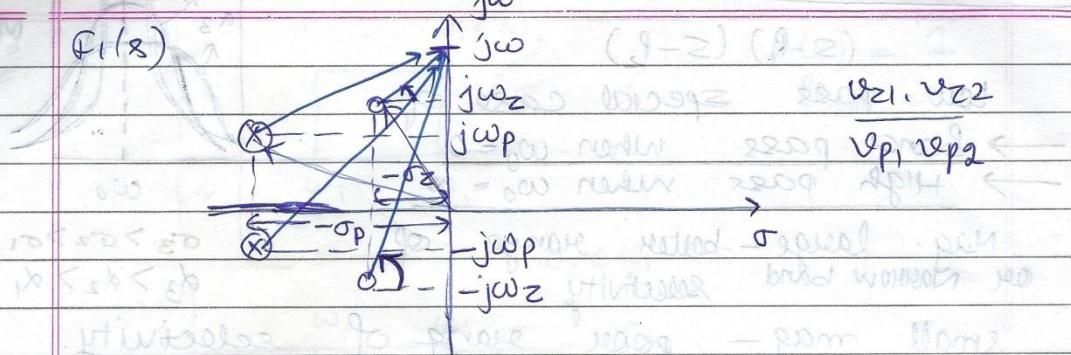

$F_2(s)$

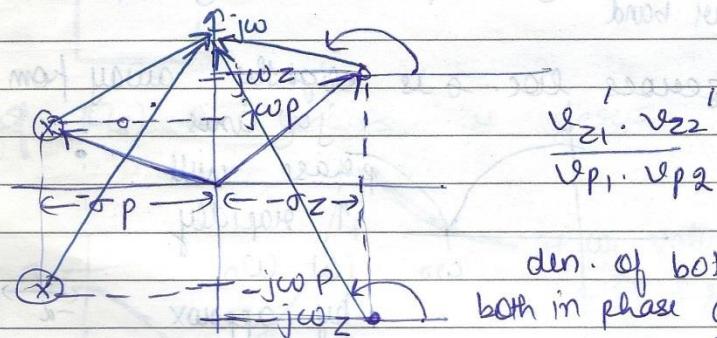

den. of both same
both in phase as well
as mag.

$$|v_{z1}| = |v_{z2}|$$

$$|v_{z2}'| = |v_{z2}|$$

i.e. overall mag. of $F_1(j\omega) = F_2(j\omega)$

Zeros Poles

$$(\alpha_2 > \alpha_1) \quad (\theta_1 = \theta_2)$$

$$\alpha_2 - \theta_2 > \alpha_1 - \theta_1$$

$$\text{i.e. } \phi_2 > \phi_1$$

$$\text{i.e. } [F_1(j\omega) < F_2(j\omega)] \quad \text{Non. min.}$$

Min. phase fn.

phase fn.

including ω axis If system fn is restated to have zeros only on open left half of s -plane then it is called min phase fn. If system fn.

Having zeros on closed right half of s -plane
then it is called non-min. phase fn.

- If no $j\omega$ axis not included then max phase fn


Q $F(s) \Rightarrow F(j\omega)$

Mag. $|F(j\omega)| = 1$.
 always

Non min. phase fn.

Mag. function

All pass

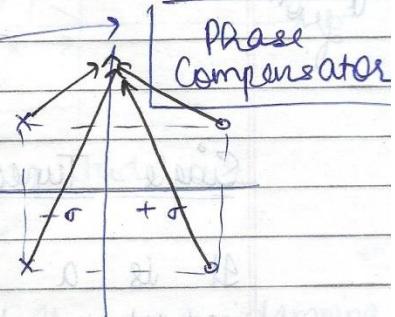

Application [Phase equaliser or Delay Equaliser].

Phase = non-zero.

$$\text{Q. } F(s) = \frac{k((s-1)^2 + 1)}{(s+1)^2 + 1} = k \frac{(s-1+i)(s-1-i)}{(s+1+i)(s+1-i)}$$

Solⁿ $\therefore F(j\omega) = \frac{k(2-\omega^2) - 2j\omega}{2-\omega^2 + 2j\omega}$

All pass

$$|F(j\omega)| = K$$

$$\begin{aligned} \phi(j\omega) &= -\tan^{-1}\left(-\frac{2\omega}{2-\omega^2}\right) - \tan^{-1}\left(\frac{2\omega}{2-\omega^2}\right) \\ &= -2 \tan^{-1}\left(\frac{2\omega}{2-\omega^2}\right) \end{aligned}$$


Critical pt - fn where $\tan^{-1}(x) = \phi(j\omega)$


goes to ∞

$$\omega = \sqrt{2}$$

NOW this is break solⁿ

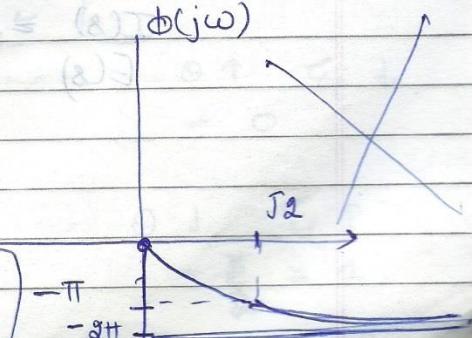After $\sqrt{2}$ are -ve. One more
-ve sign outside so $\phi = +ve.$



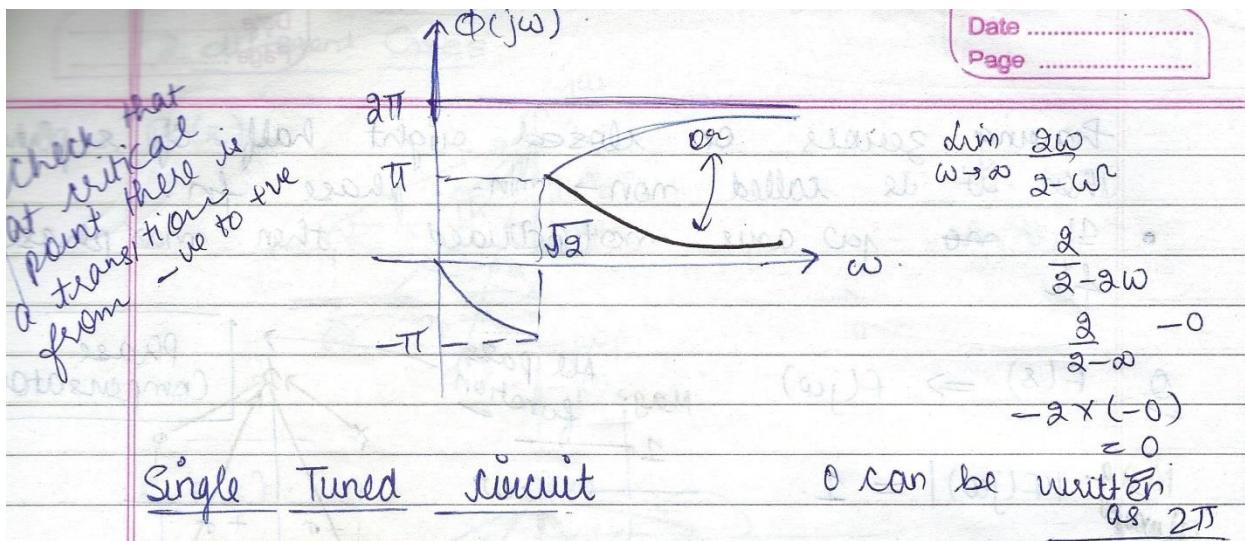

Single Tuned Circuit

θ can be written as 2π

It is a circuit in which there is one inductor & one capacitor connected in such a way that they resonate i.e. the reactance of the inductor & reactance of capacitor together will show no reactance outside at a particular freq. This is called phenomenon of resonance or tuning.

Single tuned circuit has resonance only at one freq.


Q

$$\frac{I(s)}{E(s)} = ? \quad \text{Driving pt}$$

for when

excitation &

response connected to
same port.

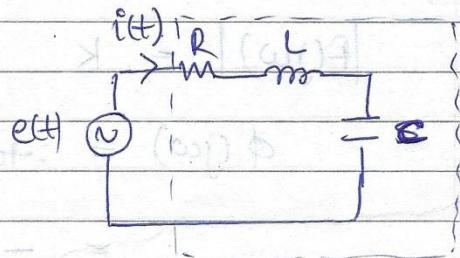

$$I(s) =$$


$$\frac{E(s)}{L(s^2 + \frac{R}{L}s + \frac{1}{LC})}$$

$$= \frac{s}{L(s-p_1)(s-p_2)}$$

$$P_{1,2} = -\alpha \pm j\beta$$

ω_n represents undamped natural frequency.

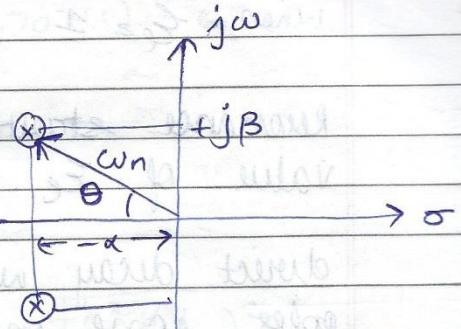because if there is no damping then ω_n is the freq. at which the circuit will show ∞ magnitude or i.e. ∞ amount of selectivity.



Damping decided by real part. If $\tau = 0$ damping zero.

$$\alpha = \omega_n \cos \theta$$

$$\beta = \omega_n \sin \theta$$

$$\xi_p = \frac{\cos \theta}{\omega_n} = \frac{\alpha}{|\omega_n|} = \text{Damping factor.}$$

(quality of decay)

$$\underline{\xi_p \uparrow, \tau \uparrow} = \frac{\alpha}{\sqrt{\alpha^2 + \beta^2}}$$

$$\alpha = \omega_n \cdot \xi_p$$

$$\beta = \omega_n \sqrt{1 - \xi_p^2} = \beta = \omega_n \sin \theta = \omega_n \sqrt{1 - \cos^2 \theta}$$

\therefore Any ^{2nd order transfer} fn can be represented as $= \omega_n \sqrt{1 - \xi_p^2}$

$$\frac{I(s)}{V(s)} = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

$$\underline{\Omega} \quad \text{If } \theta \rightarrow \frac{\pi}{2}, \quad \xi_p \rightarrow ? \quad \theta \uparrow \quad \xi_p \downarrow \quad = 0$$


$$\underline{\Omega \rightarrow 0} \quad \xi_p \rightarrow ? \quad \theta \downarrow \quad \xi_p \uparrow \quad = \frac{1}{2} = 1$$

when $\xi_e = 1$ damping max.


resonance starts at a finite value of ξ_e

direct decay when $\theta = 0$

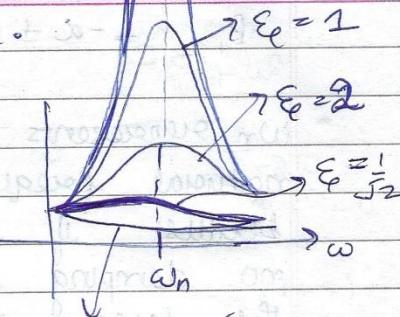pole some on real axis
so graph either of two




At a pt direct decay will start

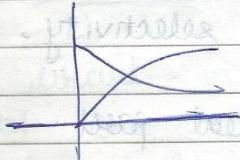

Amplitude of peak represents amount of selectivity. Higher amount of mag., good selectivity, lower " " " bad selectivity.

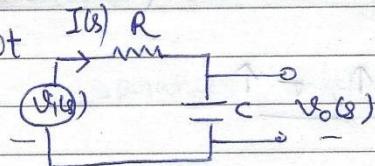Q. Draw mag. and phase plot for the transfer fn.




$$V_o(s) = \frac{1}{C} \int I(s) dt$$


$$V_o(s) = \frac{I(s)}{C s}$$

$$V_o(s) = R I(s) + \frac{I(s)}{C s}$$

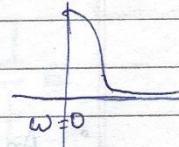
$$\frac{V_o(s)}{V_i(s)} = \frac{1}{R + \frac{1}{C s}} = \frac{1}{R s + 1}$$



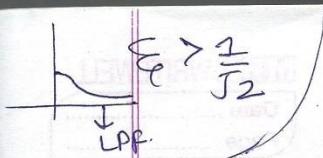At $B = 0$ i.e. imaginary part = 0 we are getting max. peak. Thus low pass filter.



Mag plot

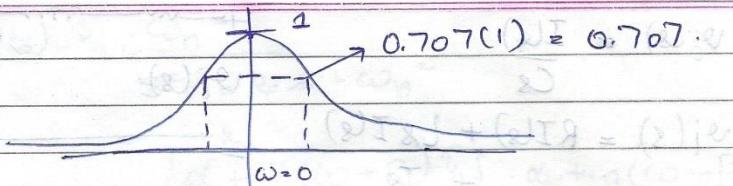(case of max flatness)
(poorest PPF)

$$\frac{1}{RC} \left[\frac{1}{j\omega + \frac{1}{RC}} \right] = \frac{1}{RC} \sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}$$


At $\omega = 0$

$$\text{Max value} = \underline{\underline{1}}$$

* Cut off freq. also called Half Power freq.

- Q which of the foll. statements is / are true
- 1) All pass fn cannot be a deviating pt fn.
 - 2) Non min. phase fn cannot be a " " "
 - 3) Min phase fn cannot be a " " "
 - 4) All of these are correct.

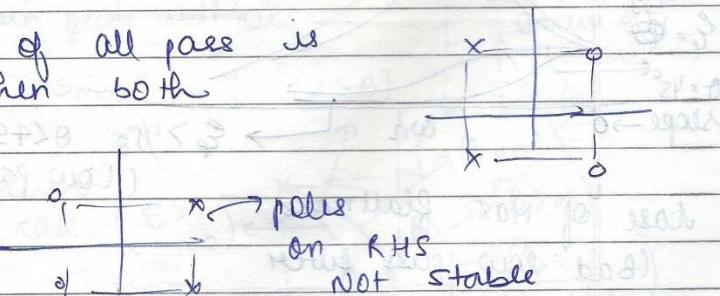As plot of Z of all pass is
when of Y then both
interchange



* Transfer fn may be a ratio fn so in that case it is not necessarily that poles & zeroes interchange.

$$V_o(s) = \frac{I(s)}{Cs}$$

R L

$$\frac{1}{L} s + V_o(s)$$


$$V_i(s) = R I(s) + L s I(s) + \frac{I(s)}{Cs}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{Cs}}{\frac{R + Ls + \frac{1}{Cs}}{Cs}} = \frac{1}{RCs + LCs^2 + 1}$$

$$= \frac{1}{LC} \left[s^2 + \frac{R}{L}s + \frac{1}{LC} \right].$$

$$\rho_{1,2} = -\frac{R}{2L} \pm j \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

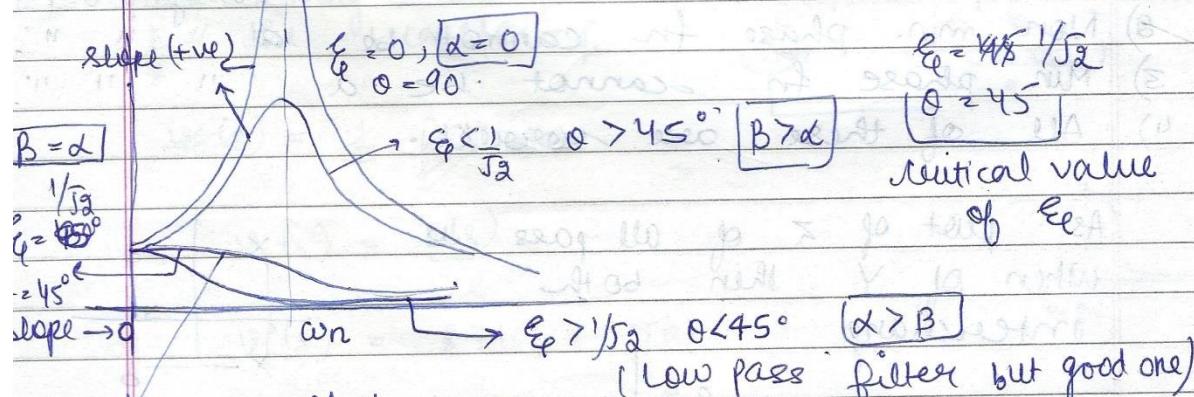$\downarrow \alpha \quad \pm \quad \downarrow \beta$



case of Max. flatness

(Bad low pass filter
in this case)

$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta_p s + \omega_n^2}$$

$$= \frac{k}{(\alpha + j(\omega + \beta))^2 \cdot (\alpha + j(\omega - \beta))^2}$$

$$|H(j\omega)| = \frac{k}{\sqrt{\alpha^2 + (\omega + \beta)^2} \cdot \sqrt{\alpha^2 + (\omega - \beta)^2}}$$

$$M(j\omega)^2 = \frac{k^2}{(\alpha^2 + (\omega + \beta)^2)(\alpha^2 + (\omega - \beta)^2)}$$

for $M(j\omega)$ to be max. $M^2(j\omega)$ must be max.

$$\frac{d[M(j\omega)^2]}{d\omega} = 0$$

$$\boxed{\omega_{max} = \beta^2 - \alpha^2}$$

$$\begin{aligned}\omega_{max} &= \omega_n \sqrt{1 - \zeta_p^2} - \omega_n \zeta_p \\ &= \omega_n \cdot \sqrt{1 - \zeta_p^2} - \omega_n \zeta_p\end{aligned}$$


$$\boxed{\omega_{max}^2 = \omega_n^2 (1 - 2\zeta_p^2)}$$

freq. at which peak will occur.

and peak will occur at
 $\omega = 0$

* To easily find ω_{max}

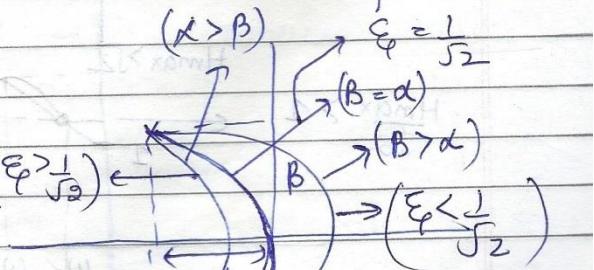Peaking will occur
only in $\beta > \alpha$ case ($\zeta_p > \frac{1}{\sqrt{2}}$)



Point ① and ② represent
the intersection of
two circles.

ω_{max}
where they
intersect y-axis.

Thus this intersection gives ω_{max}
This curve is called peaking circle.

$$|H(j\omega)| \rightarrow \text{Peak} \quad \text{when } \beta > \alpha \Rightarrow Q > 45^\circ \\ \Rightarrow \xi_p < \frac{1}{\sqrt{2}}$$

Q factor

$$Q \text{ factor} = \frac{1}{2\xi_p}$$


Half Power frequency / cut off frequency

If voltage signal is considered


Then at this

point $\frac{V_{max}}{\sqrt{2}}$

$$\text{and Power} = \frac{P_{max}}{2}$$

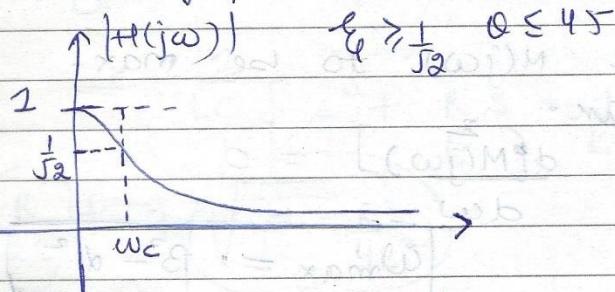
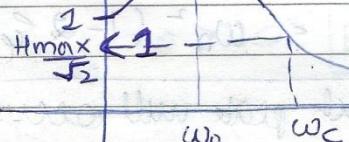
$$H_{max} < \frac{1}{\sqrt{2}} \quad \xi_p < \frac{1}{\sqrt{2}}$$



Half Power Points

$$\frac{H_{max}}{\sqrt{2}} > 1$$



Power

$$\frac{P}{2}$$

NETWORKS (Resonance)

$$\omega_0^2 = \omega_{c1} \cdot \omega_{c2}$$

GRAPH THEORY